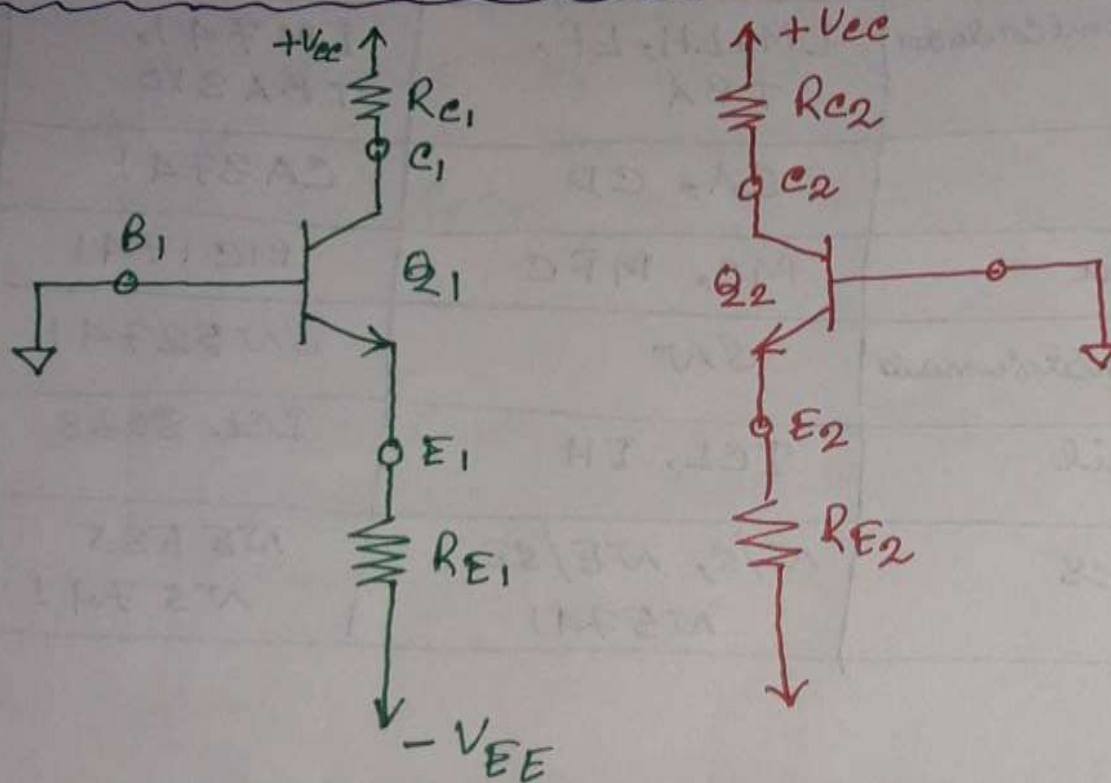


Operational Amplifier


OP AMP

Differential Amplifier



Two identical emitter biased circuit.

OP AMP

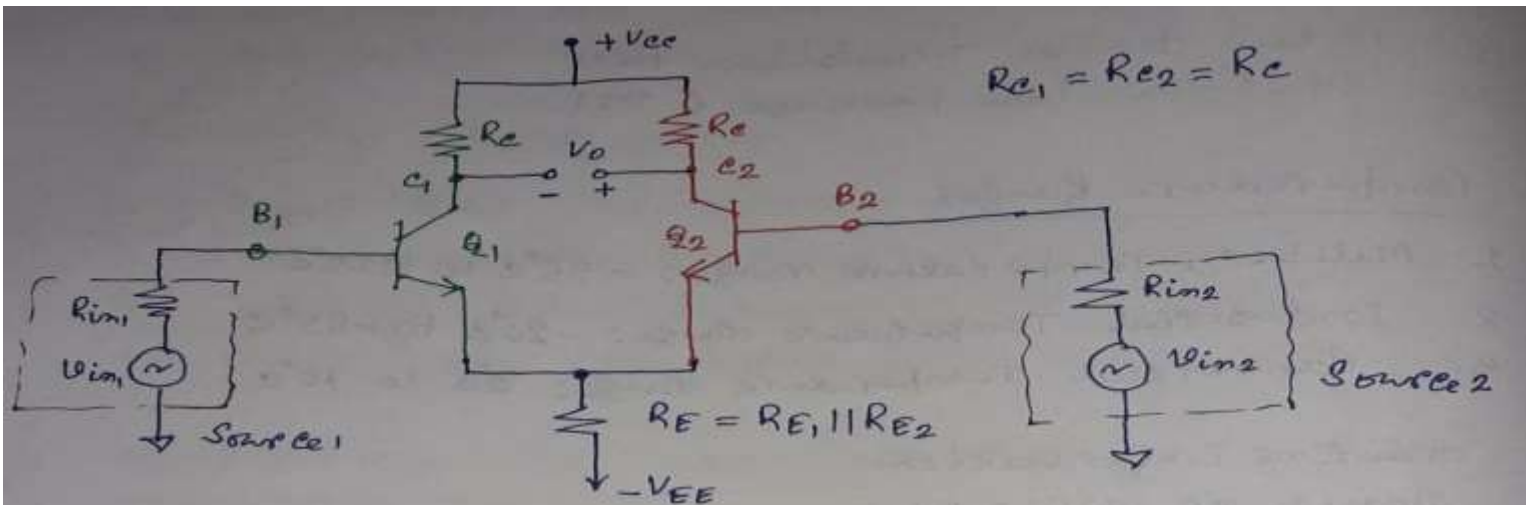

Differential Amplifier

or

Difference Amplifier

OP AMP

Four Differential Amplifier Configurations

- <1> Dual-input, balanced-output differential amplifier
- <2> Dual-input, unbalanced-output ^{differential} ~~differential~~ amplifier
- <3> Single-input, balanced output differential amplifier
- <4> Single-input unbalanced output differential amplifier

Balanced o/p : o/p between two collectors


Unbalanced o/p : o/p between one of the collector and ground.

OP AMP

Dual Input, Balanced Output Differential Amplifier

DC Analysis

(Deactivate
AC Sources)

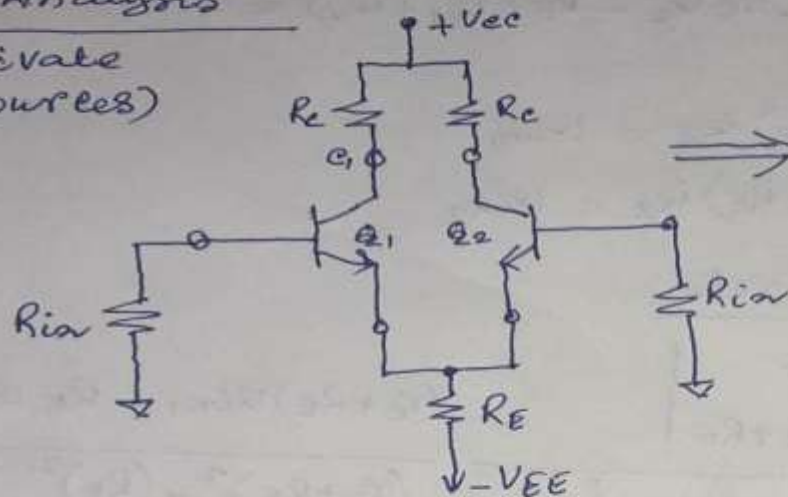

⇒ Placement
of Q point.
↓
middle of load
line.



$$|+V_{CC}| = |-V_{EE}|$$

OP AMP

Ac Analysis

> Deactivate DC sources

> T equivalent r_e model is used.

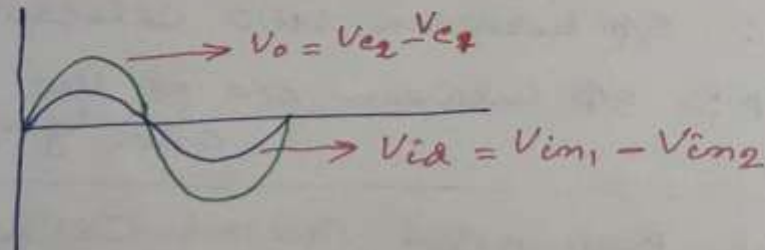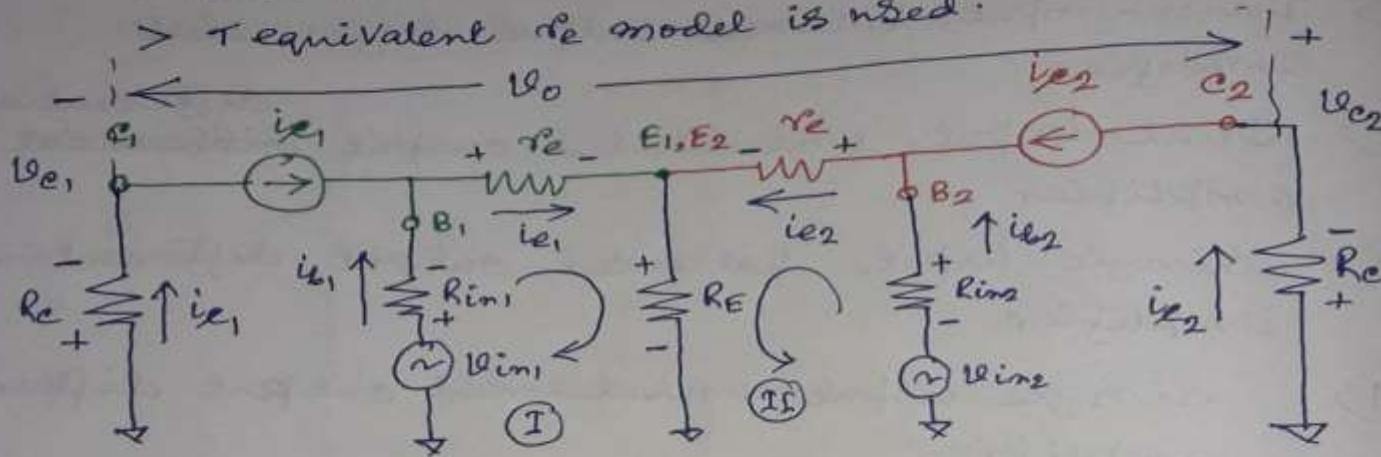

OP AMP

$$\begin{aligned} V_{in1} - \overset{\text{Small}}{\underbrace{R_{in1} i_{b1}}} - r_e i_{e1} - R_E (i_{e1} + i_{e2}) &= 0 \\ V_{in2} - \overset{\text{Small}}{\underbrace{R_{in2} i_{b2}}} - r_e i_{e2} - R_E (i_{e1} + i_{e2}) &= 0 \end{aligned}$$

$$\begin{aligned} (r_e + R_E) i_{e1} + (R_E) i_{e2} &= V_{in1} \\ (R_E) i_{e1} + (r_e + R_E) i_{e2} &= V_{in2} \end{aligned}$$

Using Cramer's rule

$$i_{e1} = \frac{\begin{vmatrix} V_{in1} & R_E \\ V_{in2} & r_e + R_E \end{vmatrix}}{\begin{vmatrix} r_e + R_E & R_E \\ R_E & r_e + R_E \end{vmatrix}} = \frac{(r_e + R_E) V_{in1} - R_E V_{in2}}{(r_e + R_E)^2 - (R_E)^2}$$

OP AMP

$$i_{e2} = \frac{\begin{vmatrix} r_e + R_E & v_{in1} \\ R_E & v_{in2} \end{vmatrix}}{\begin{vmatrix} r_e + R_E & R_E \\ R_E & r_e + R_E \end{vmatrix}} \cdot \frac{(r_e + R_E)^2 - (R_E)^2}{(r_e + R_E)^2 - (R_E)^2}$$

$$= \frac{(r_e + R_E) v_{in2} - (R_E) v_{in1}}{(r_e + R_E)^2 - (R_E)^2}$$

$$\begin{aligned} V_o &= V_{c2} - V_{c1} \\ &= -R_c i_{e2} - (-R_c i_{e1}) \\ &= R_c i_{e1} - R_c i_{e2} \\ &= R_c (i_{e1} - i_{e2}) \quad \text{since } i_c \approx i_e \end{aligned}$$

OP AMP

$$V_o = R_c \left[\frac{(r_e + R_E) V_{in1} - (R_E) V_{in2}}{(r_e + R_E)^2 - (R_E)^2} - \frac{(r_e + R_E) V_{in2} - (R_E) V_{in1}}{(r_e + R_E)^2 - (R_E)^2} \right]$$

$$= R_c \frac{(r_e + R_E)(V_{in1} - V_{in2}) + (R_E)(V_{in1} - V_{in2})}{(r_e + R_E)^2 - (R_E)^2}$$

$$= R_c \frac{(r_e + 2R_E)(V_{in1} - V_{in2})}{r_e(r_e + 2R_E)}$$

$$\therefore \boxed{V_o = \frac{R_c}{r_e} (V_{in1} - V_{in2})}$$

$$A_d = \text{Differential Gain} = \frac{V_o}{V_{id}} = \frac{R_c}{r_e}$$

OP AMP

Differential input resistance.

$$R_{i1} = \left. \frac{v_{in1}}{i_{i1}} \right|_{v_{in2}=0} = \left. \frac{v_{in1}}{i_{e1}/\beta_{ac}} \right|_{v_{in2}=0}$$

$$= \frac{\beta_{ac} v_{in1}}{\frac{(r_e + R_E) v_{in1} - (R_E)(0)}{(r_e + R_E)^2 - R_E^2}}$$

$$= \frac{\beta_{ac} \cdot r_e (r_e + 2R_E)}{(r_e + R_E)}$$

$$r_e + 2R_E \approx 2R_E, \quad r_e + R_E \approx R_E$$

$$\boxed{R_{i1} = 2 \beta_{ac} r_e}$$

OP AMP

$$\begin{aligned} R_{i2} &= \left. \frac{v_{in2}}{i_{b2}} \right|_{v_{in1}=0} = \left. \frac{v_{in2}}{i_{e2}/\beta_{ac}} \right|_{v_{in1}=0} \\ &= \frac{\beta_{ac} v_{in2}}{\frac{(r_e + R_E) v_{in2} - (R_E)(0)}{(r_e + R_E)^2 - (R_E)^2}} \\ &= \frac{\beta_{ac} r_e (r_e + 2R_E)}{(r_e + R_E)} \end{aligned}$$

$$\boxed{R_{i2} = 2 \beta_{ac} r_e}$$

OP AMP

Output Resistance

$$R_{o1} = R_{o2} = R_c.$$

Inverting & noninverting terminal.

$$V_o = \frac{R_c}{R_e} (V_{in1} - V_{in2})$$

if $V_{in1} = V_{in}$, $V_{in2} = 0$

$$\therefore V_o = \frac{R_c}{R_e} V_{in}$$


(noninverting terminal)

if $V_{in1} = 0$, $V_{in2} = V_{in}$

$$V_o = - \frac{R_c}{R_e} V_{in}$$


(inverting terminal)

OP AMP

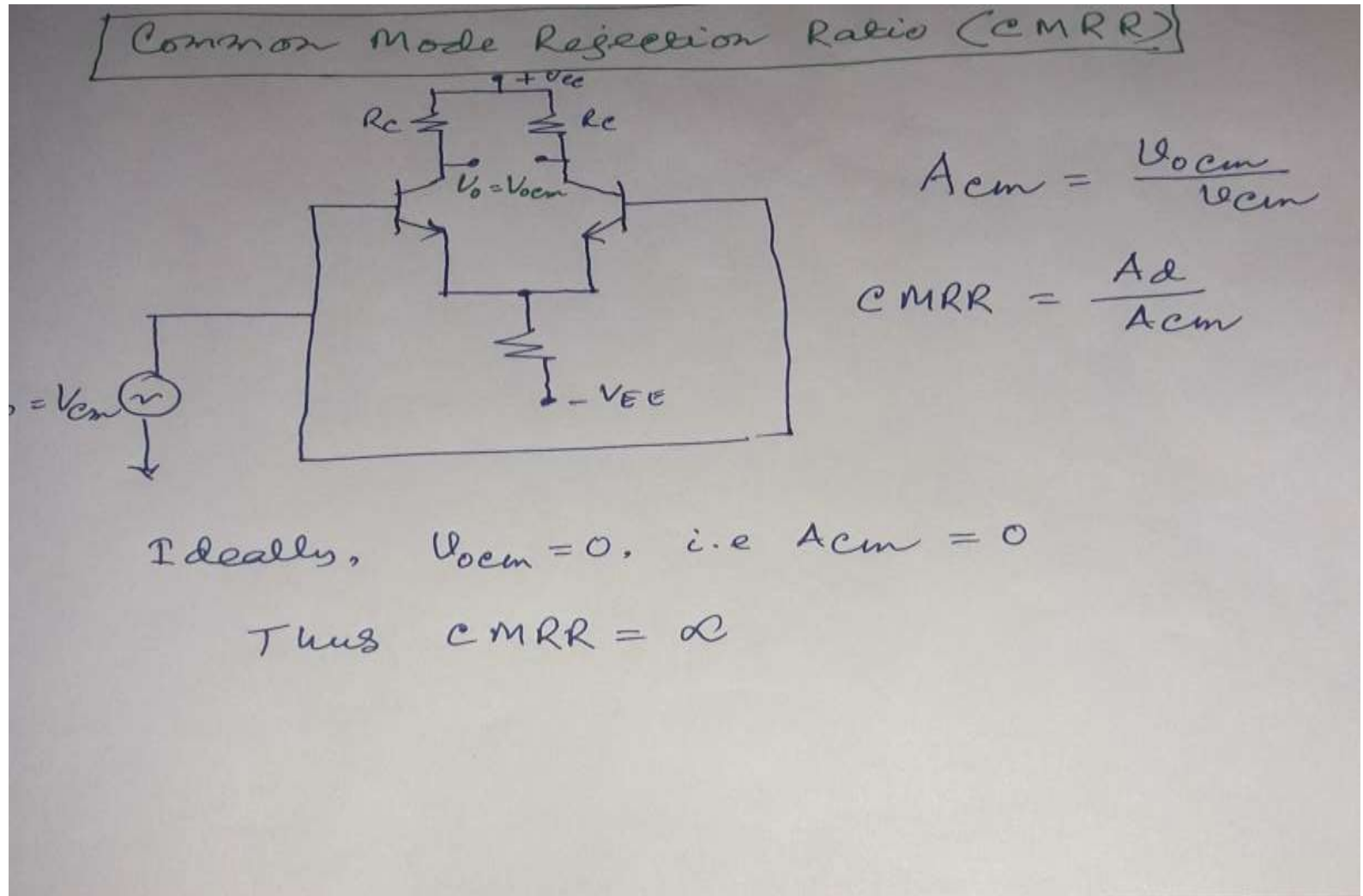


OP AMP

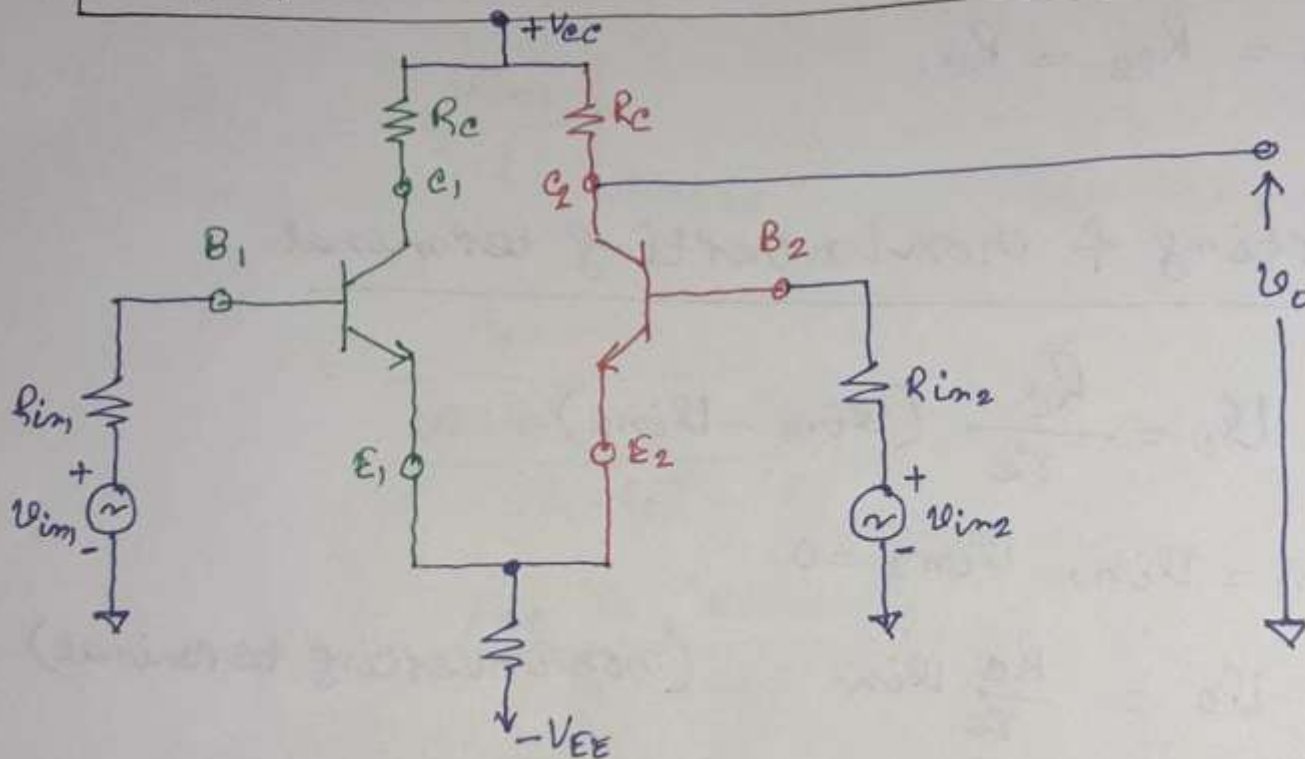Dual input, Unbalanced o/p Differential Amplifier



OP AMP

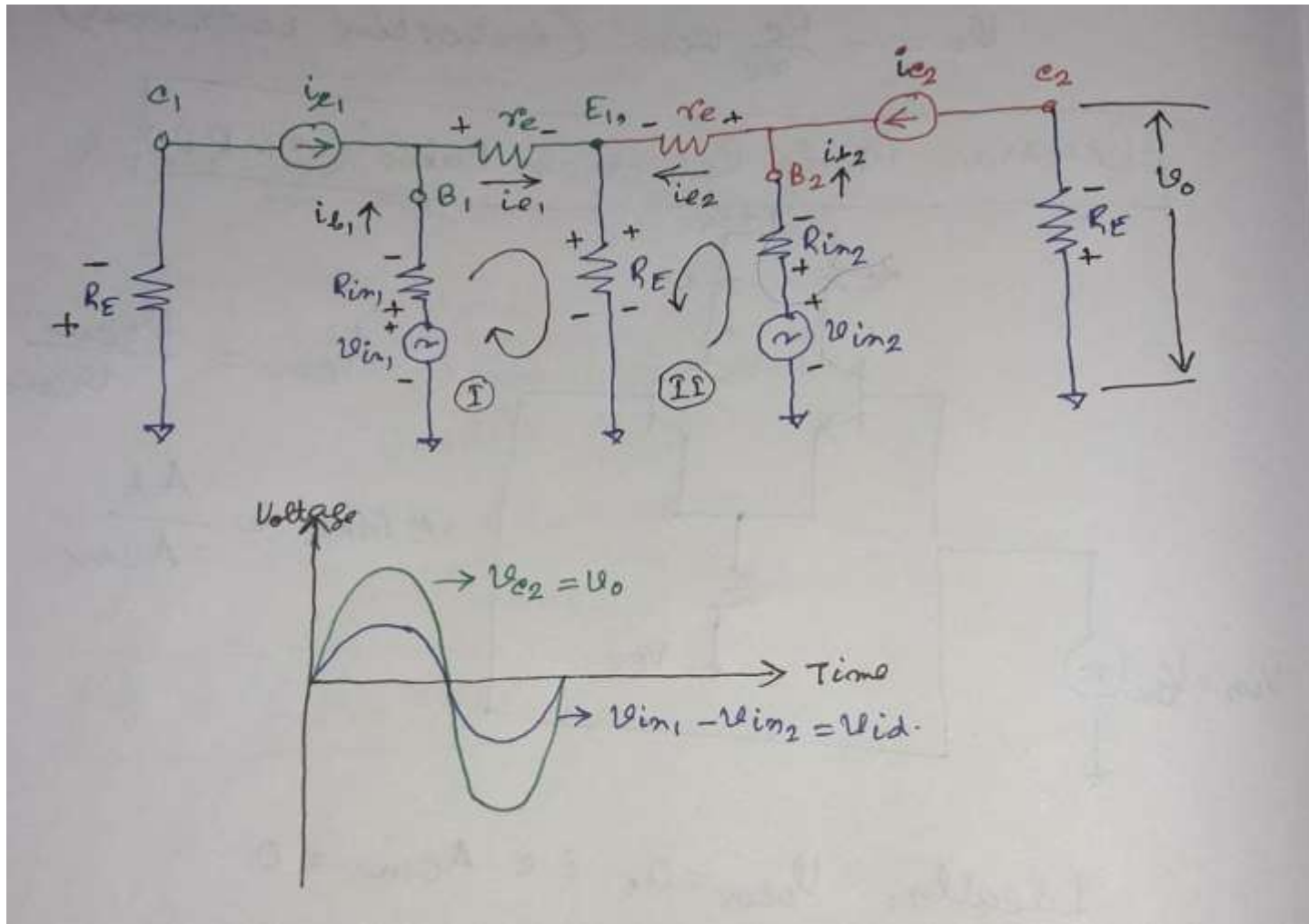

OP AMP

The output voltage is

$$V_o = V_{e2} = -R_E i_{e2} = -R_E i_{e2} \quad \text{Since } i_e = i_e$$

$$= -R_E \cdot \frac{(r_e + R_E) V_{in2} - (R_E) V_{in1}}{(r_e + R_E)^2 - (R_E)^2}$$

$$= R_E \cdot \frac{(R_E) V_{in1} - (r_e + R_E) V_{in2}}{r_e (r_e + 2R_E)}$$

Generally,

$$R_E \gg r_e, \text{ Hence, } r_e + R_E \approx R_E \text{ \& } r_e + 2R_E \approx 2R_E$$

$$V_o = R_E \cdot \frac{(R_E) V_{in1} - (R_E) V_{in2}}{r_e (2R_E)}$$

$$= \frac{R_E \cdot R_E (V_{in1} - V_{in2})}{2r_e R_E}$$

$$= \frac{R_E}{2r_e} (V_{in1} - V_{in2})$$

$$\boxed{A_d = \frac{V_o}{V_{id}} = \frac{R_E}{2r_e}} \quad \text{Voltage Gain.}$$

OP AMP

Differential input resistance

$$R_{i1} = R_{i2} = 2\beta_{ac} r_e$$

Output resistance

$$R_o = R_c$$

OP AMP

Single input Balanced op Differential Amplifier

$$V_o = \frac{R_c}{r_e} V_{in}$$

$$A_d = \frac{V_o}{V_{in}} = \frac{R_c}{r_e} \quad \text{Voltage Gain}$$

Differential input resistance

$$R_i = 2 \beta a c r_e$$

Output resistance

$$R_{o1} = R_{o2} = R_c$$

OP AMP

Single input Unbalanced o/p Differential Amplifier

$$V_o = \frac{R_c}{2r_e} V_{in}$$

$$A_d = \frac{V_o}{V_{in}} = \frac{R_c}{2r_e} \quad \text{Voltage Gain}$$

Differential input resistance


$$R_i = 2\beta a_e r_e$$

Output Resistance

$$R_o = R_c$$

OP AMP

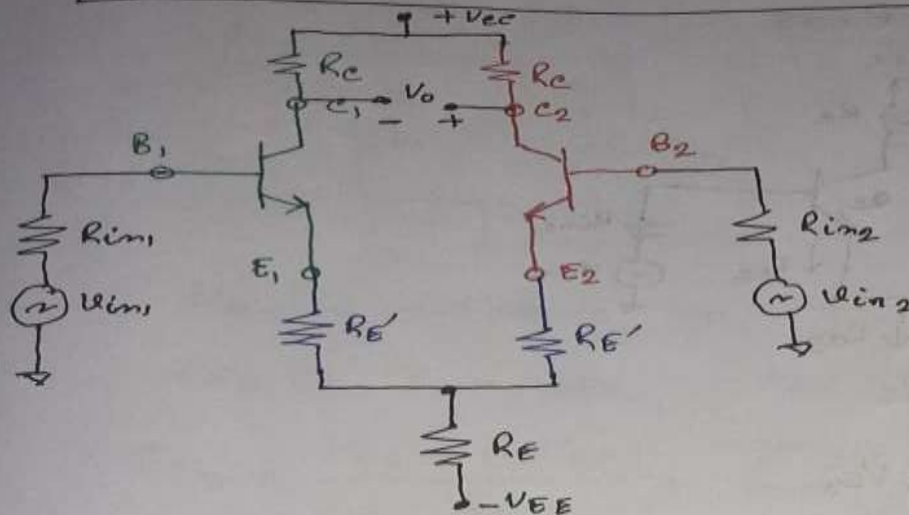Differential Amplifier with Swamping Resistance



By using external resistance RE' , the dependence on r_e' can be reduced. Generally,
 $RE' \gg r_e$

$$A_d = \frac{V_o}{V_{id}} = \frac{R_c}{r_e + RE'} \approx \frac{R_c}{RE'}$$

$$R_{i1} = R_{i2} = 2\beta_{ac}(r_e + RE') \approx 2\beta_{ac}RE'$$

$$R_{o1} = R_{o2} = R_c$$


OP AMP

To get desired performance of the differential amplifier it is very important to keep emitter current I_E constant.

OP AMP

Attempts to make Constant Emitter Current

Constant Current Bias

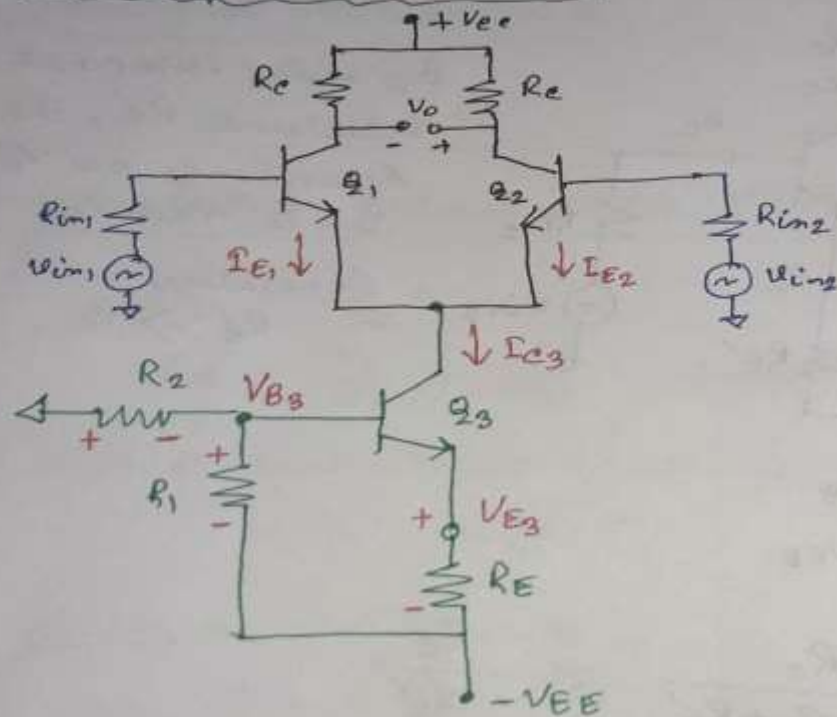

OP AMP

$$V_{B3} = - \frac{R_2 V_{EE}}{R_1 + R_2}$$


$$V_{E3} = V_{B3} - V_{BE3} = - \frac{R_2 V_{EE}}{R_1 + R_2} - V_{BE3}$$

$$I_{E3} \approx I_{C3} = \frac{V_{E3} - (-V_{EE})}{R_E}$$

$$I_{C3} = \frac{V_{EE} - \left[\frac{R_2 V_{EE}}{R_1 + R_2} \right] - V_{BE3}}{R_E}$$

$$I_{E1} = I_{E2} = \frac{I_{C3}}{2} = \frac{V_{EE} - \left[\frac{R_2 V_{EE}}{R_1 + R_2} \right] - V_{BE3}}{2 R_E}$$

OP AMP

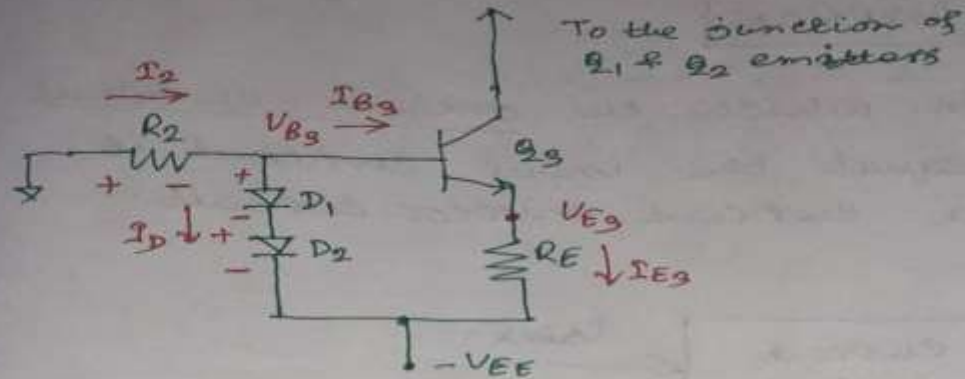

$$V_{B3} = -V_{EE} + 2V_D$$


$$V_{E3} = V_{B3} - V_{BE3} = -V_{EE} + 2V_D - V_{BE3}$$

$$I_{E3} = \frac{V_{E3} - (-V_{EE})}{R_E} = \frac{2V_D - V_{BE3}}{R_E}$$

if $V_D = V_{BE3}$

$$I_{E3} = \frac{V_D}{R_E}$$

OP AMP

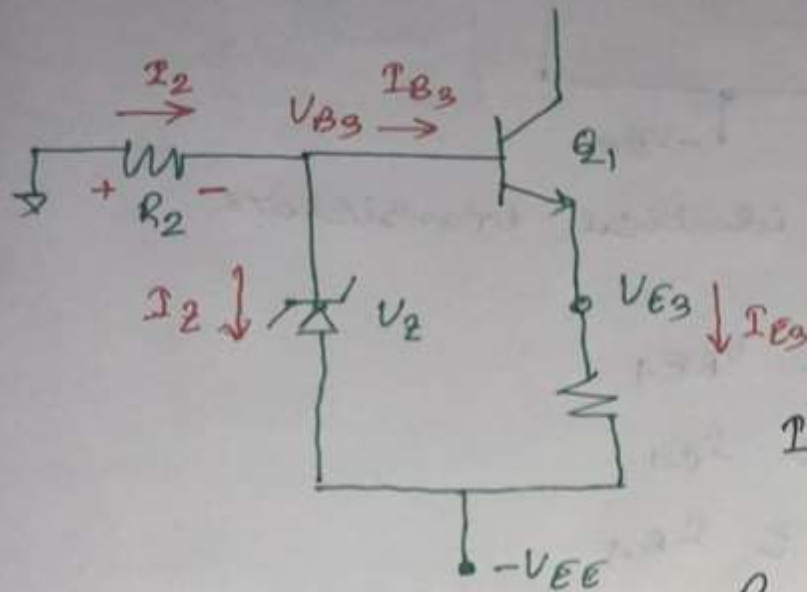

$$V_{B3} = -V_{EE} + V_2$$

$$V_{E3} = -V_{EE} + V_2 - V_{BE3}$$

$$I_{E3} = \frac{V_{E3} - (-V_{EE})}{R_E}$$


$$I_{E3} = \frac{V_2 - V_{BE3}}{R_E}$$

$$R_2 = \frac{V_{EE} - V_2}{I_2}$$


OP AMP

CURRENT MIRROR

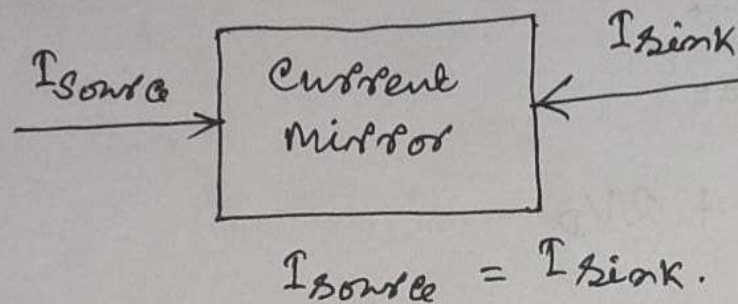The circuit in which the output current is forced to equal the input current is said to be a current mirror circuit.



OP AMP

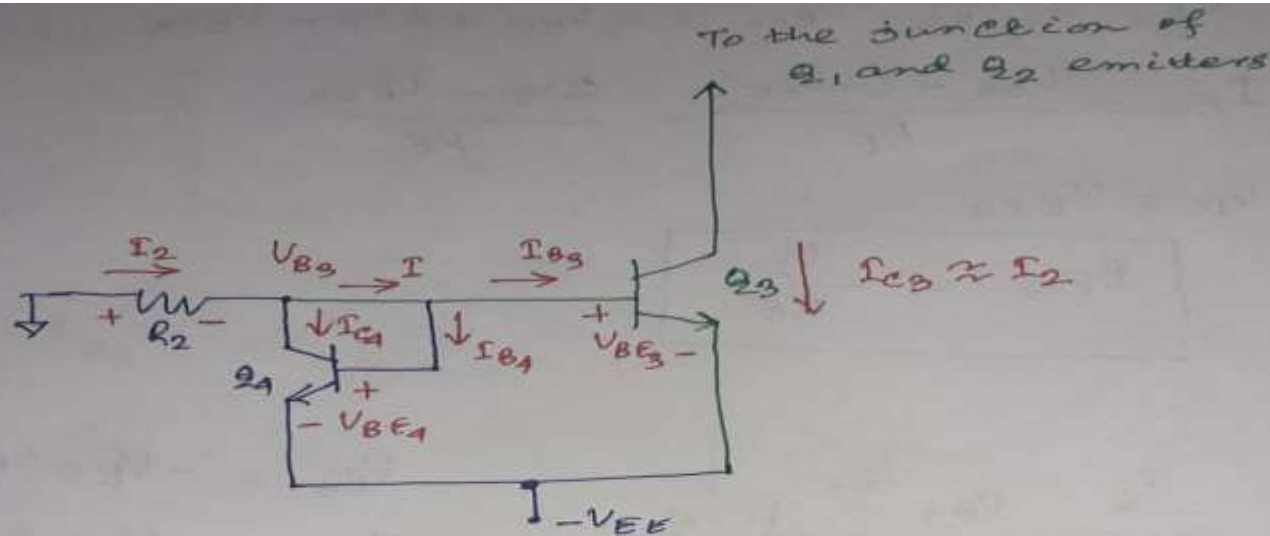

Q_3 & Q_4 are identical transistors.

$$V_{BE3} \approx V_{BE4}$$

$$I_{C3} \approx I_{C4}$$

$$I_{B3} \approx I_{B4}$$

OP AMP

$$\begin{aligned} I_2 &= I_{C4} + I \\ &= I_{C4} + 2I_{B4} = I_{C3} + 2I_{B3} \\ &= I_{C3} + 2\left(\frac{I_{C3}}{\beta_{dc}}\right) \\ &= I_{C3} \left(1 + \frac{2}{\beta_{dc}}\right) \end{aligned}$$


$$\therefore \boxed{I_2 \approx I_{C3}}$$

$$-R_2 I_2 - V_{BE3} + V_{EE} = 0$$


$$\therefore \boxed{I_2 = \frac{V_{EE} - V_{BE3}}{R_2}}$$

OP AMP

CASCADED DIFFERENTIAL AMPLIFIER STAGES.

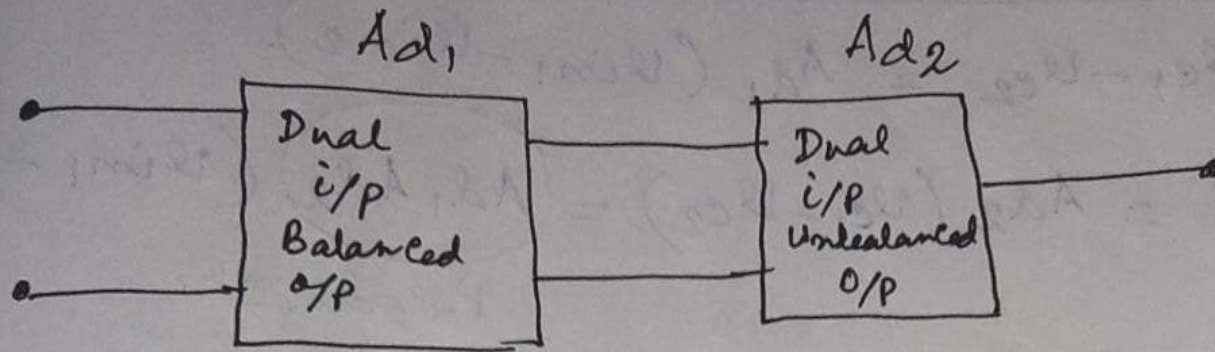

OP AMP

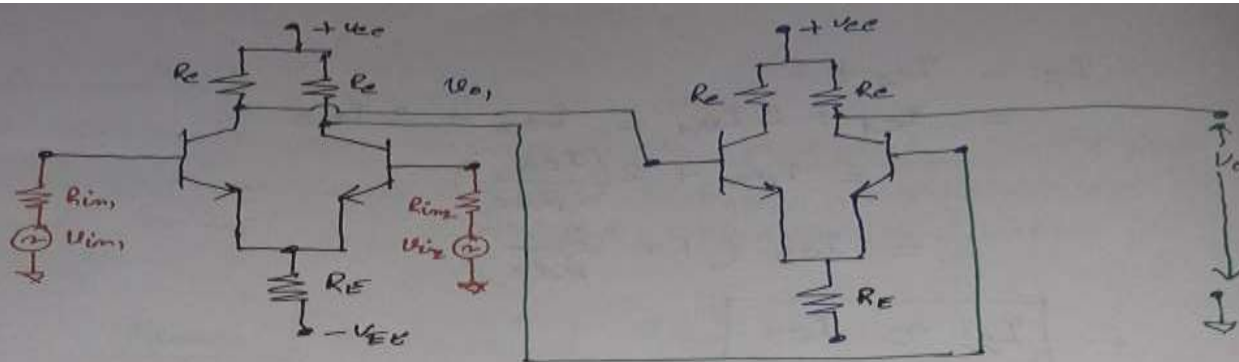

$$V_{O1} = A_{d1} (V_{in1} - V_{in2})$$

~~$$V_{O2} = A_{d2} (V_{in2} - V_{in1})$$~~

$$V_{c1} = A_{d1} V_{in1}$$

$$V_{c2} = A_{d2} V_{in2}$$

$$V_{c1} - V_{c2} = A_{d1} (V_{in1} - V_{in2})$$


$$\therefore V_O = A_{d2} (V_{c1} - V_{c2}) = \underbrace{A_{d1} A_{d2}}_{\text{Product}} (V_{in1} - V_{in2})$$

OP AMP


Level Translator

Because of the direct coupling dc level ~~at the~~ ~~input~~ of the OP rises up. Increase in dc level ~~at the input~~ tends to shift the operating point, which may cause distortion. So with the help of Level translator attempts are made to fix this problem.


OP AMP

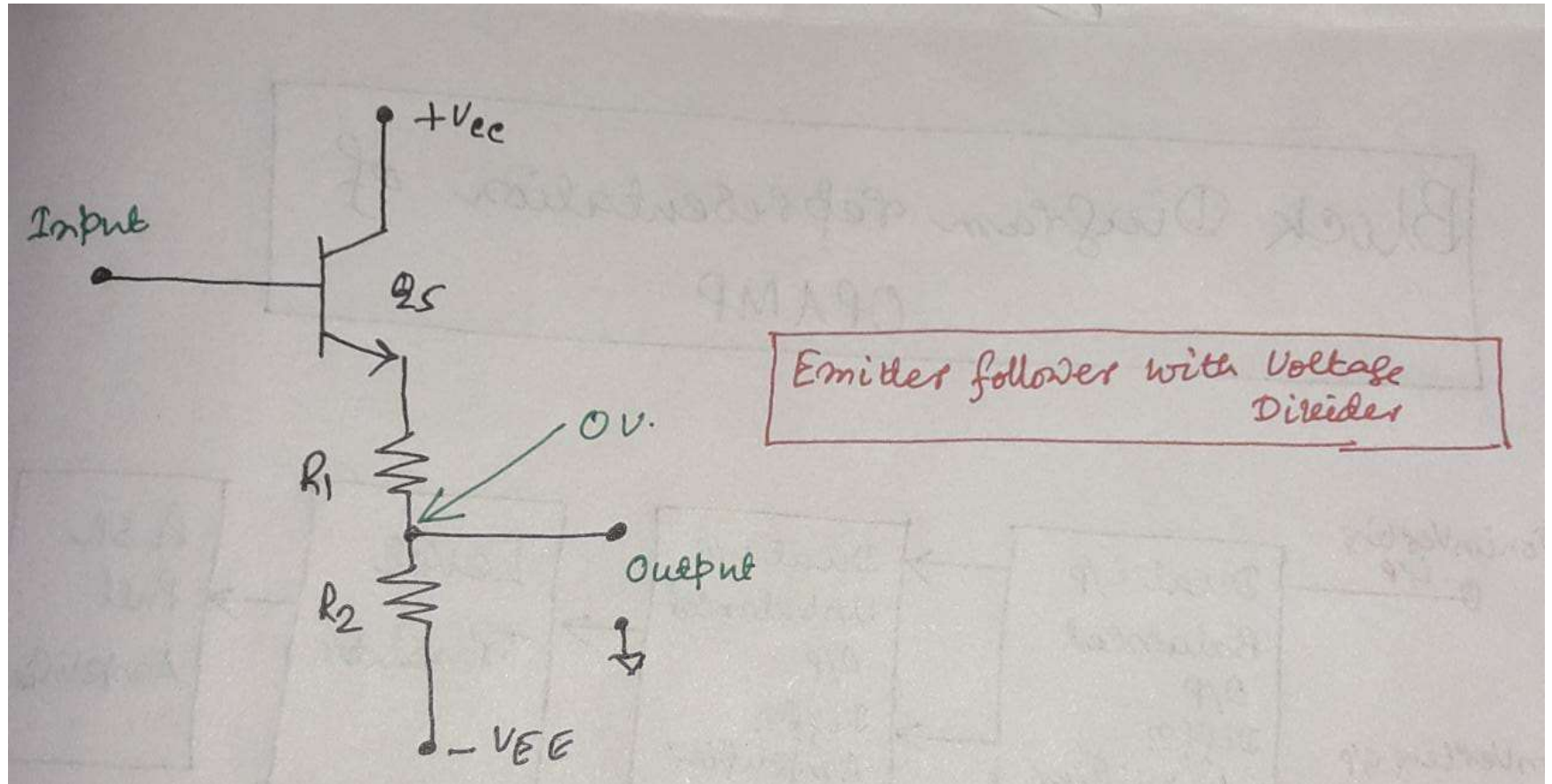

OP AMP

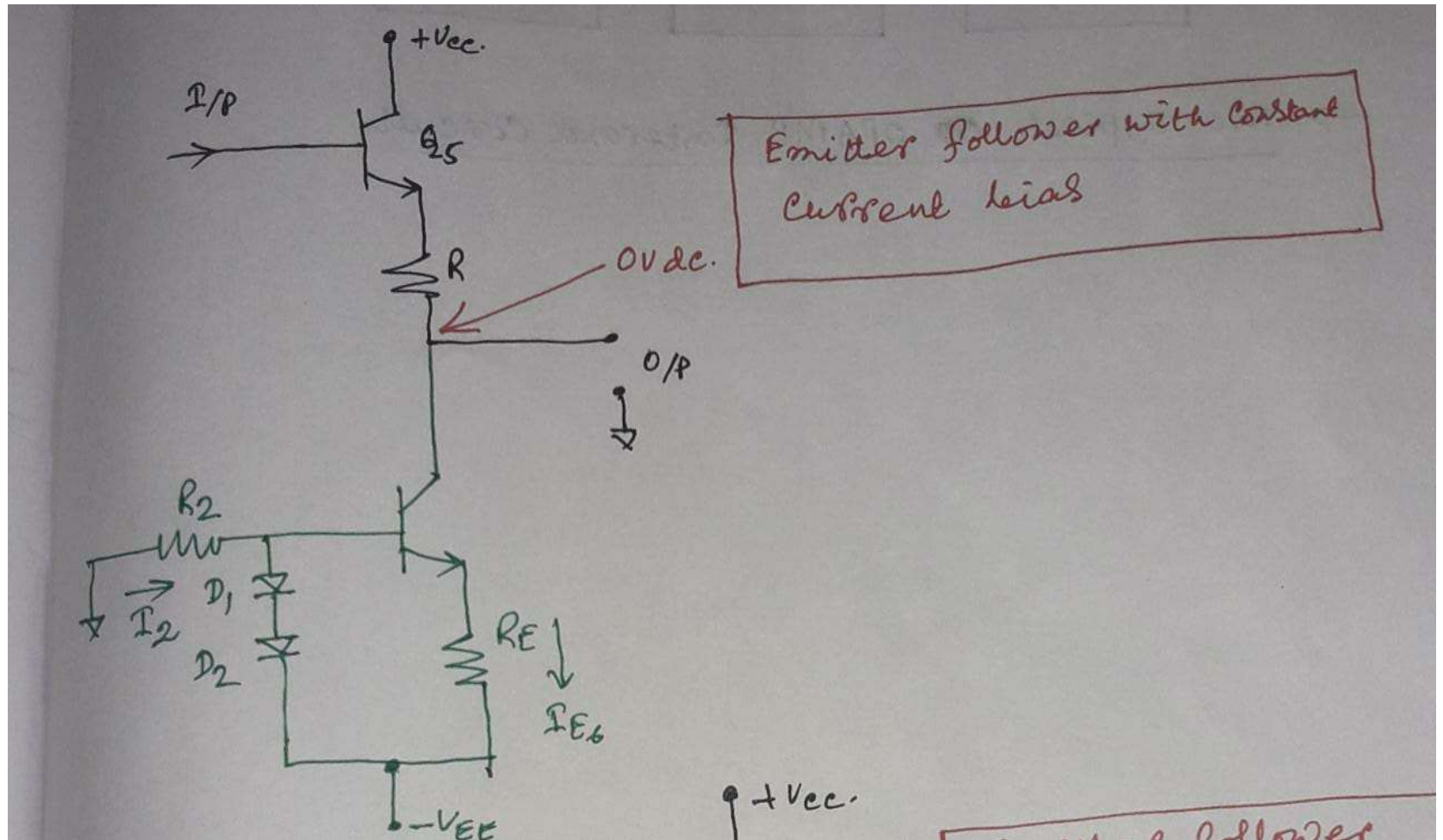


OP AMP

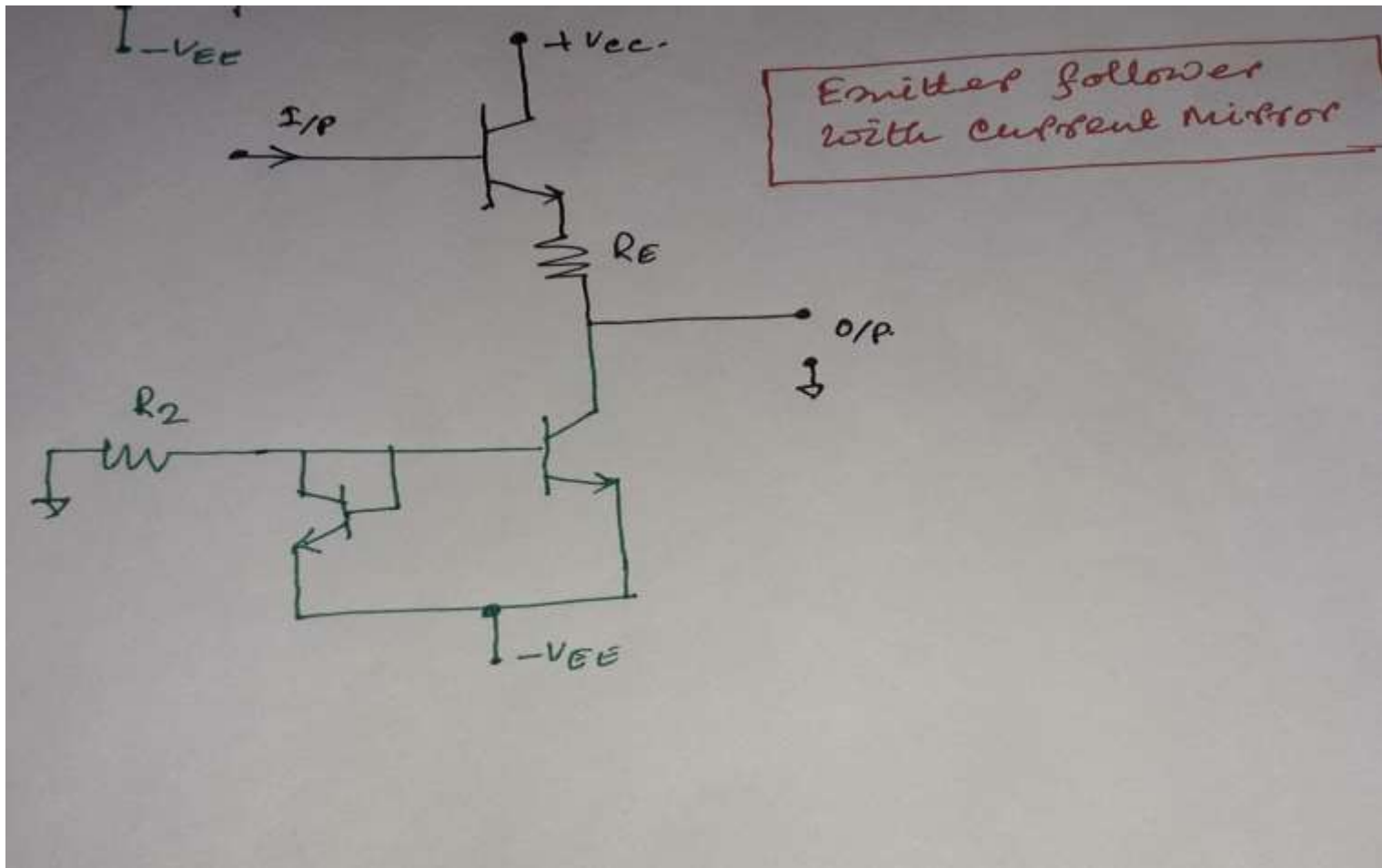


OP AMP

Block Diagram representation of
OPAMP

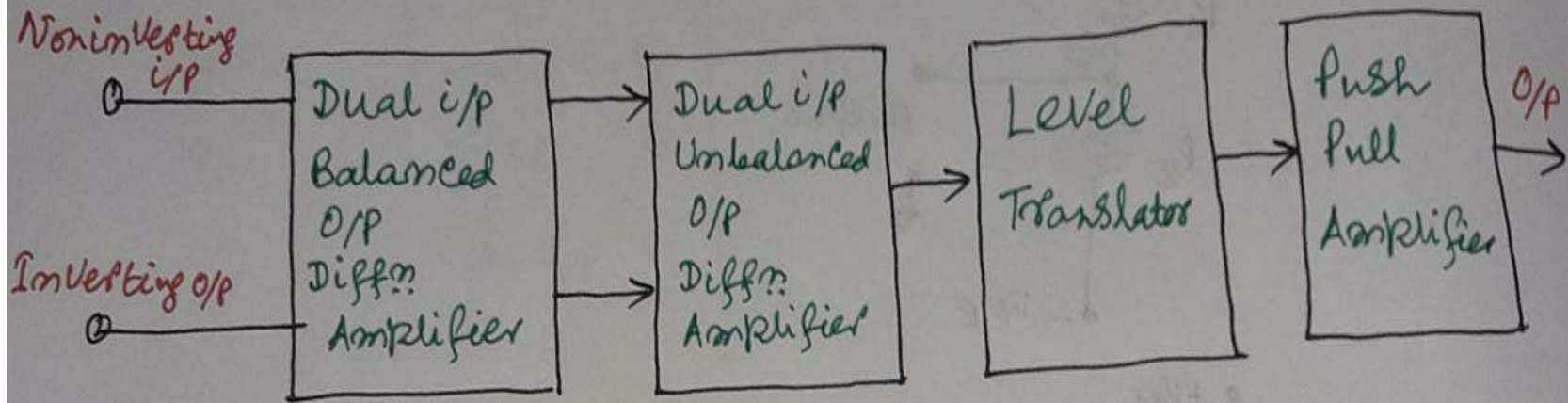


OP AMP

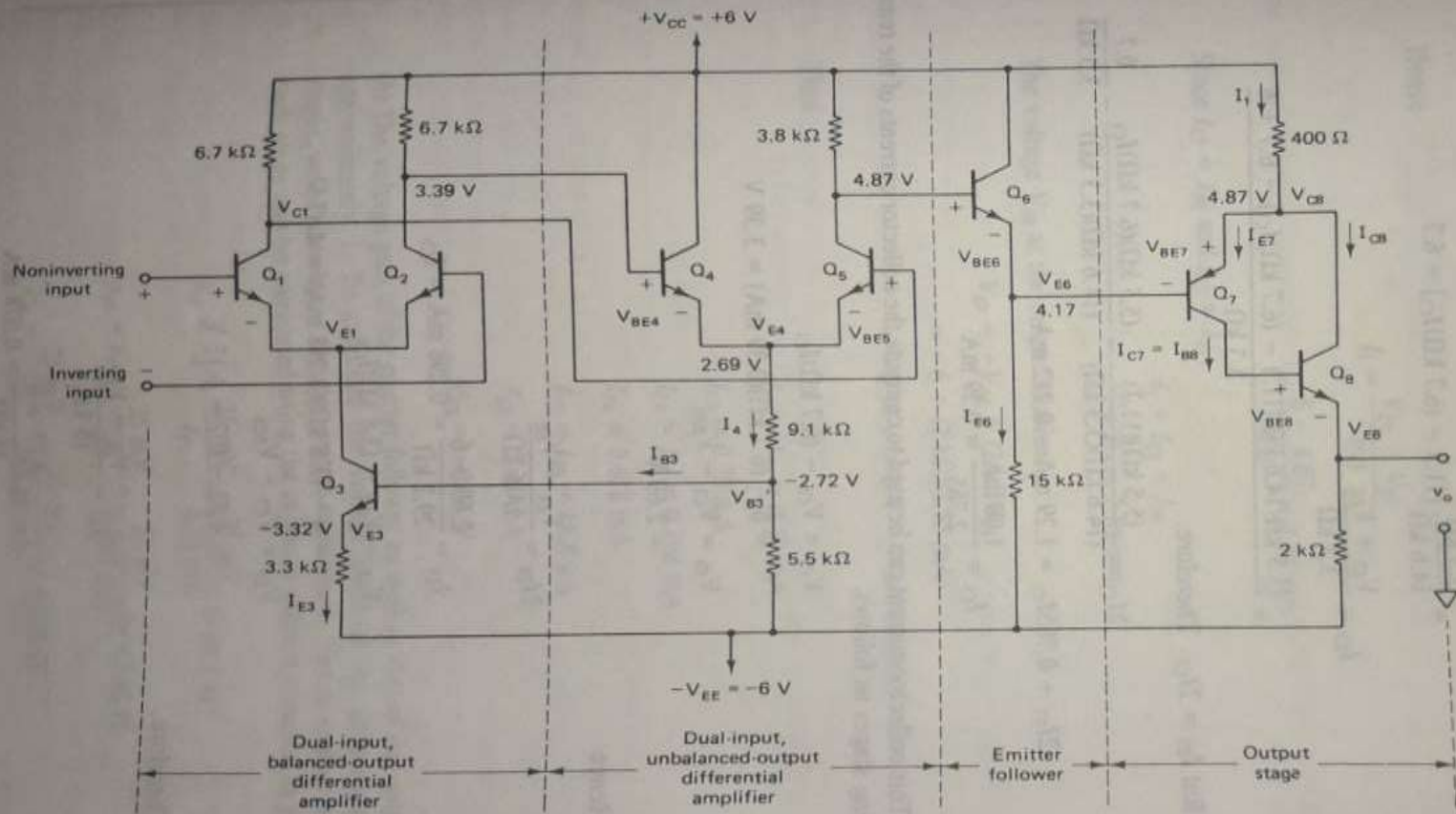

Equivalent circuit of the MC1435 op-amp. (Courtesy of Motorola Semiconductor, Inc.)


OP AMP

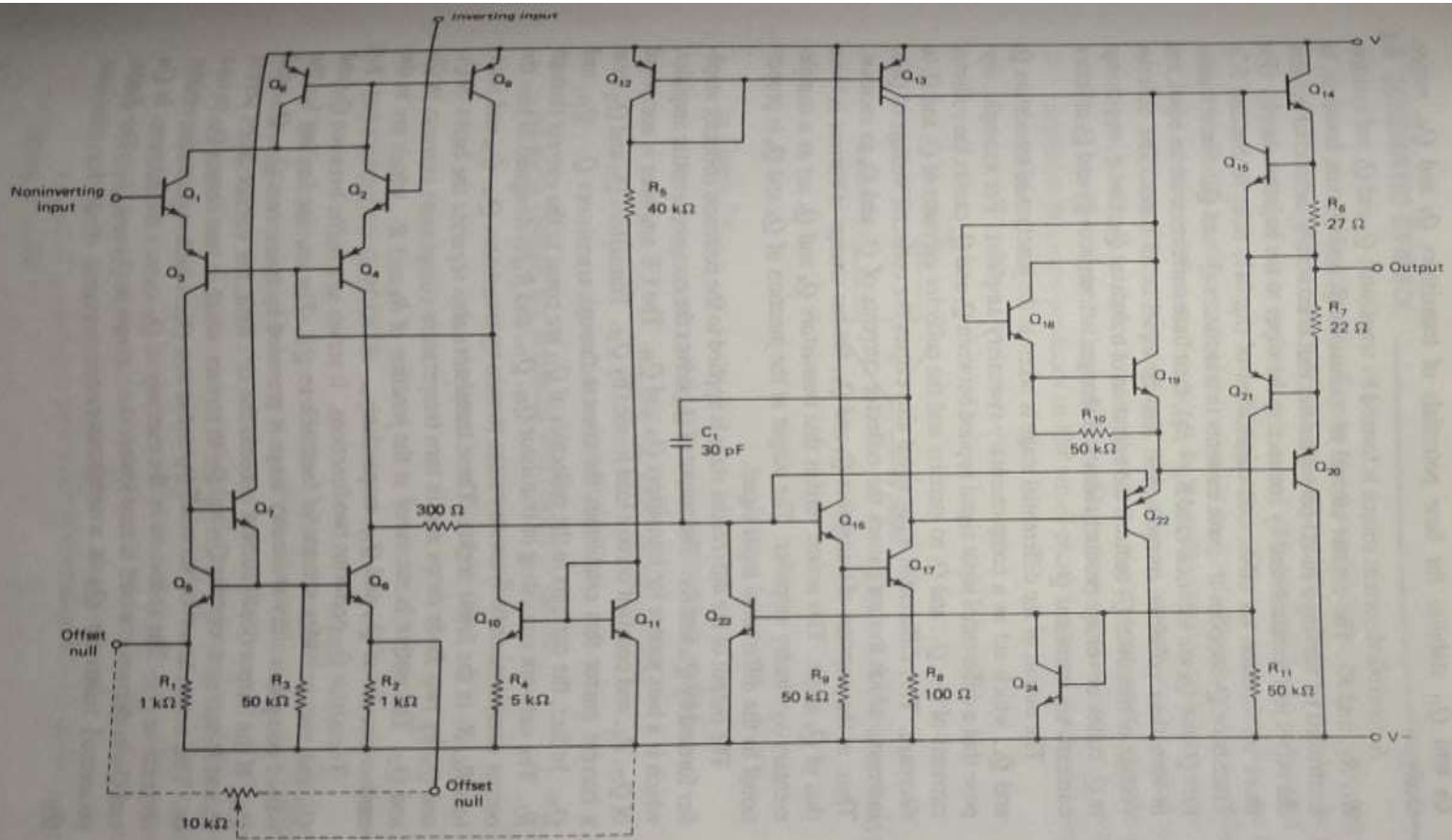

Equivalent circuit of the 741 op-amp. (Courtesy of Fairchild Semiconductor Corporation.)

OP AMP

SCHEMATIC SYMBOL

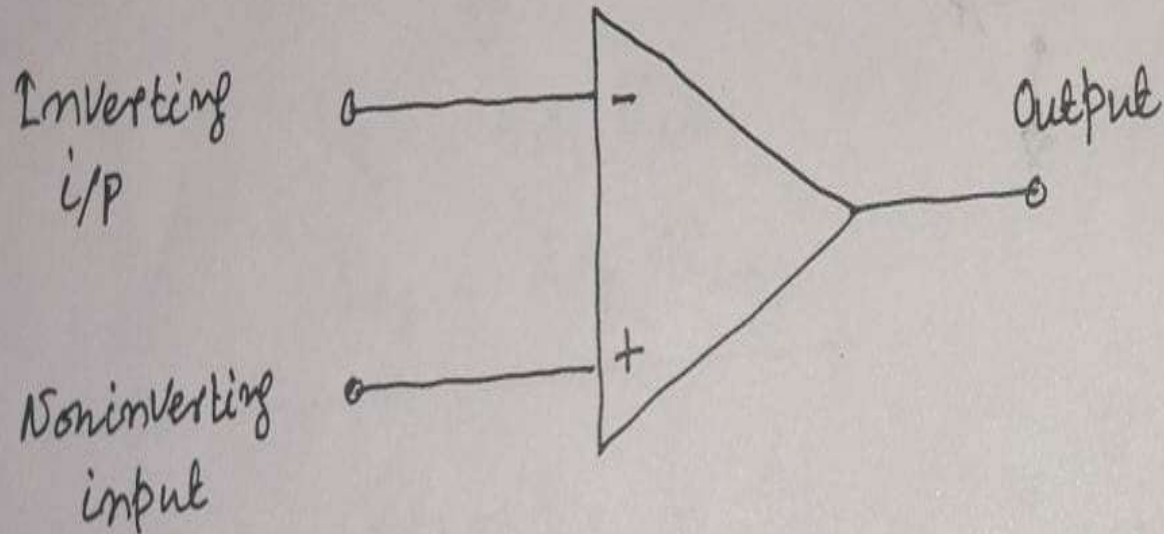


OP AMP

THE IDEAL OPAMP

Characteristics

- <1> Infinite Voltage Gain
- <2> Infinite Input Impedance
- <3> Zero Output Impedance
- <4> Zero Output Voltage when input voltage is zero.
- <5> Infinite Bandwidth.
- <6> Infinite Common Mode Rejection Ratio.
- <7> Infinite Slew rate.


OP AMP

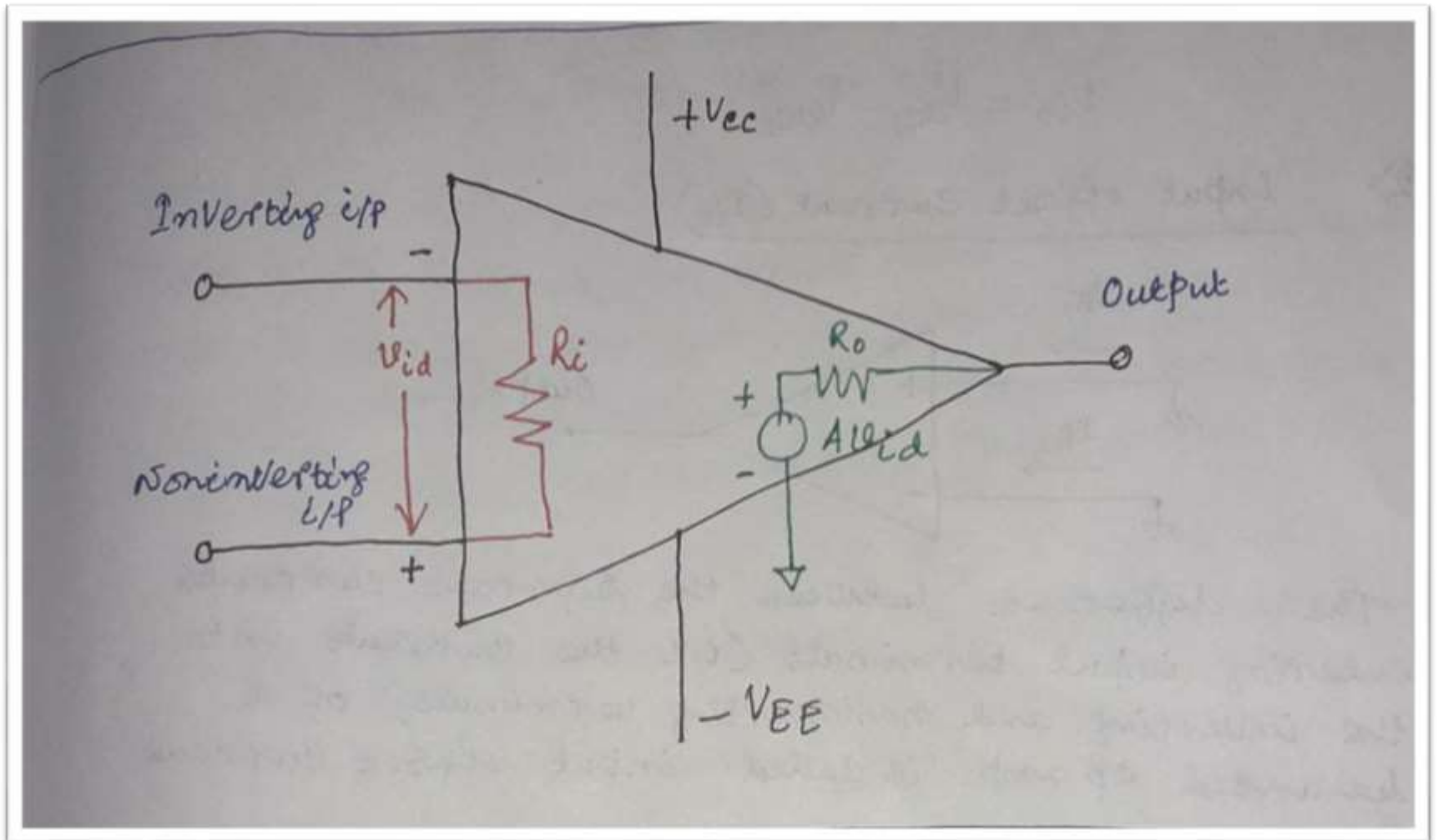

OP AMP

Parameters of Operational Amplifier

① Input offset voltage (V_{io})

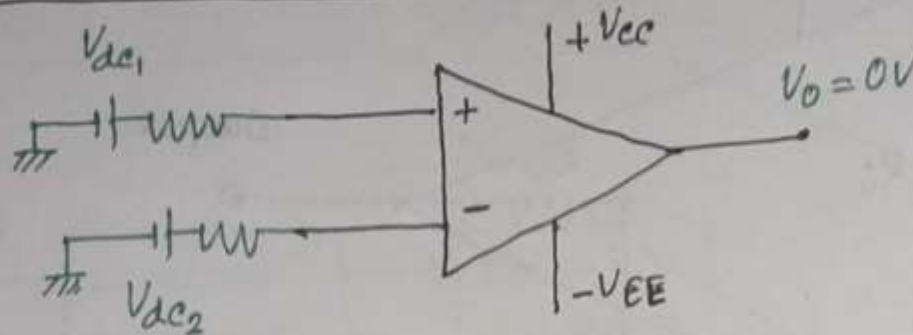


Input offset voltage is the voltage that must be applied between two input terminals to balance the op-amp i.e. to null (making zero) the output.

$$V_{io} = V_{dc1} - V_{dc2}$$

OP AMP

<2> Input offset current (I_{io})

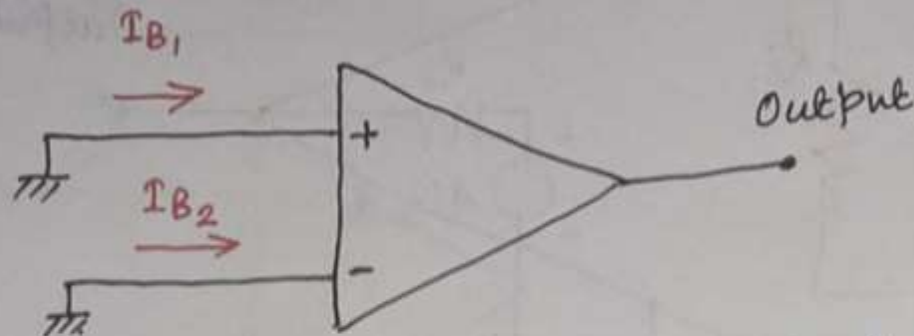

The difference between the separate currents entering input terminals (i.e. the currents into the inverting and noninverting terminals) of a balanced op amp is called input offset current I_{io} .

$$I_{io} = |I_{B1} - I_{B2}| \text{ when } V_o = 0$$


OP AMP

<3> Input Bias Current (I_B)

Input bias current I_B is one half of the sum of the separate currents entering the two input terminals of a balanced OPamp.

$$I_B = \frac{I_{B1} + I_{B2}}{2} \text{ when } V_o = 0.$$


<4> Differential Gain (A_d)

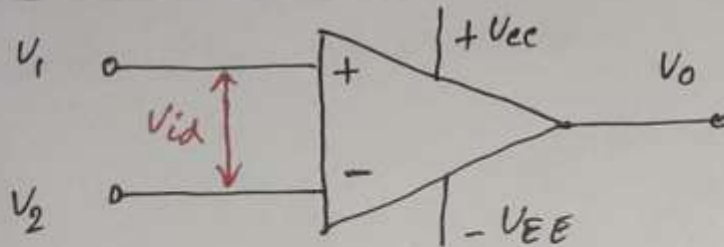

$$A_d = \frac{V_o}{V_{id}}$$

OP AMP

(5) Common Mode Voltage Gain. (A_{cm})

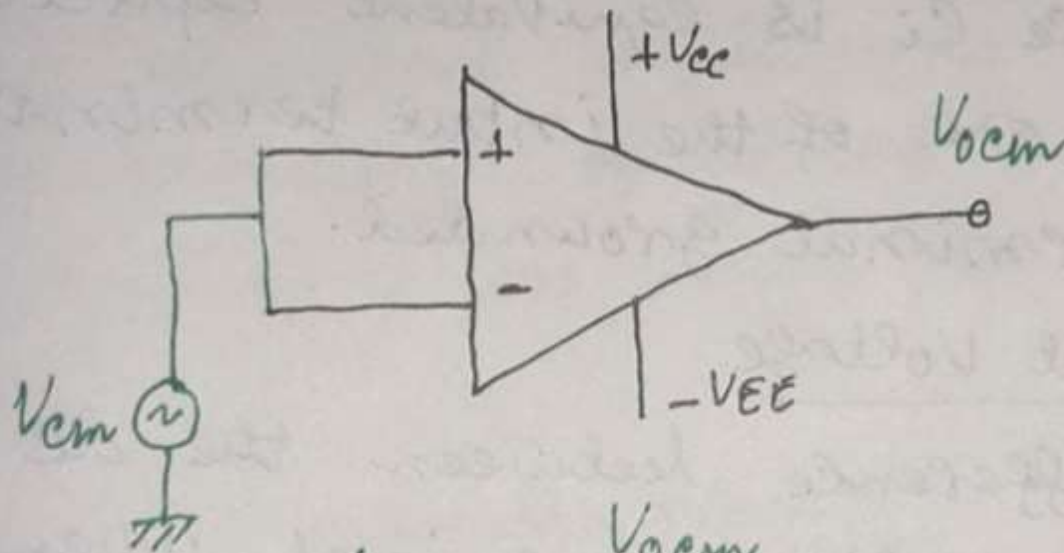

$$A_{cm} = \frac{V_{ocm}}{V_{cm}}$$

OP AMP

6) Common Mode Rejection Ratio (CMRR)

It is the ratio of the differential voltage gain (A_d) to the common mode voltage gain (A_{cm})

$$CMRR = \left| \frac{A_d}{A_{cm}} \right|$$

Generally A_{cm} is very small and A_d nearly equal to A' (large signal gain) is very large.

Hence CMRR is very large. Therefore CMRR is often expressed in decibel (dB) units.

$CMRR \uparrow$, $A_{cm} \downarrow$ This offers effective rejection of common mode signals like noise etc.

OP AMP

<7> Input offset Current Drift.

$$\parallel \frac{\Delta I_{io}}{\Delta T}$$

<8> Input offset Voltage Drift.

$$\parallel \frac{\Delta V_{io}}{\Delta T}$$

<9> Differential Input Resistance (R_i)

It is defined as the equivalent resistance that can be measured at one of the input terminals with other terminal grounded.

Value of R_i is generally very large. This prevents loading of OP Amp.

OP AMP

<10> Input Capacitance (C_i)

Input capacitance C_i is equivalent capacitance measured at one of the input terminals with other terminal grounded.

<11> Output Offset Voltage

It is the difference between the DC voltage present at the output terminal when two input terminals are grounded. V_{oo} denotes Output Offset Voltage.

OP AMP

<12> Slew Rate (SR)

It is defined as the maximum rate of change of Output Voltage with respect to time.

It can also be defined as the time rate of change of Output Voltage of closed loop amplifier under large-signal condition.

$$SR = \left. \frac{dV_o}{dt} \right|_{\max} \dots (V/\mu s)$$

SR gives us the information about how fast the output of OPAMP can change with the change in input.

If requirement of Output Signal is greater than Slew rate, distortion occurs. Thus, in ac applications Slew rate is very important parameter.

OP AMP

(13) Supply Voltage Rejection Ratio (SVRR)

It is defined as the ratio of change in V_{io} to the variation in supply voltage.

It is also termed as PSRR, expressed in $\mu V/Volt$ or decibel.

OP AMP

(14) Output Resistance (R_o)


It is equivalent resistance measured between output terminal of OP AMP and ground. Generally R_o is less so as to avoid loading effect.

(15) Gain - Bandwidth Product.

Gain-bandwidth product is the bandwidth of the op-amp when the voltage gain is 1.


OP AMP

Inverting Amplifier

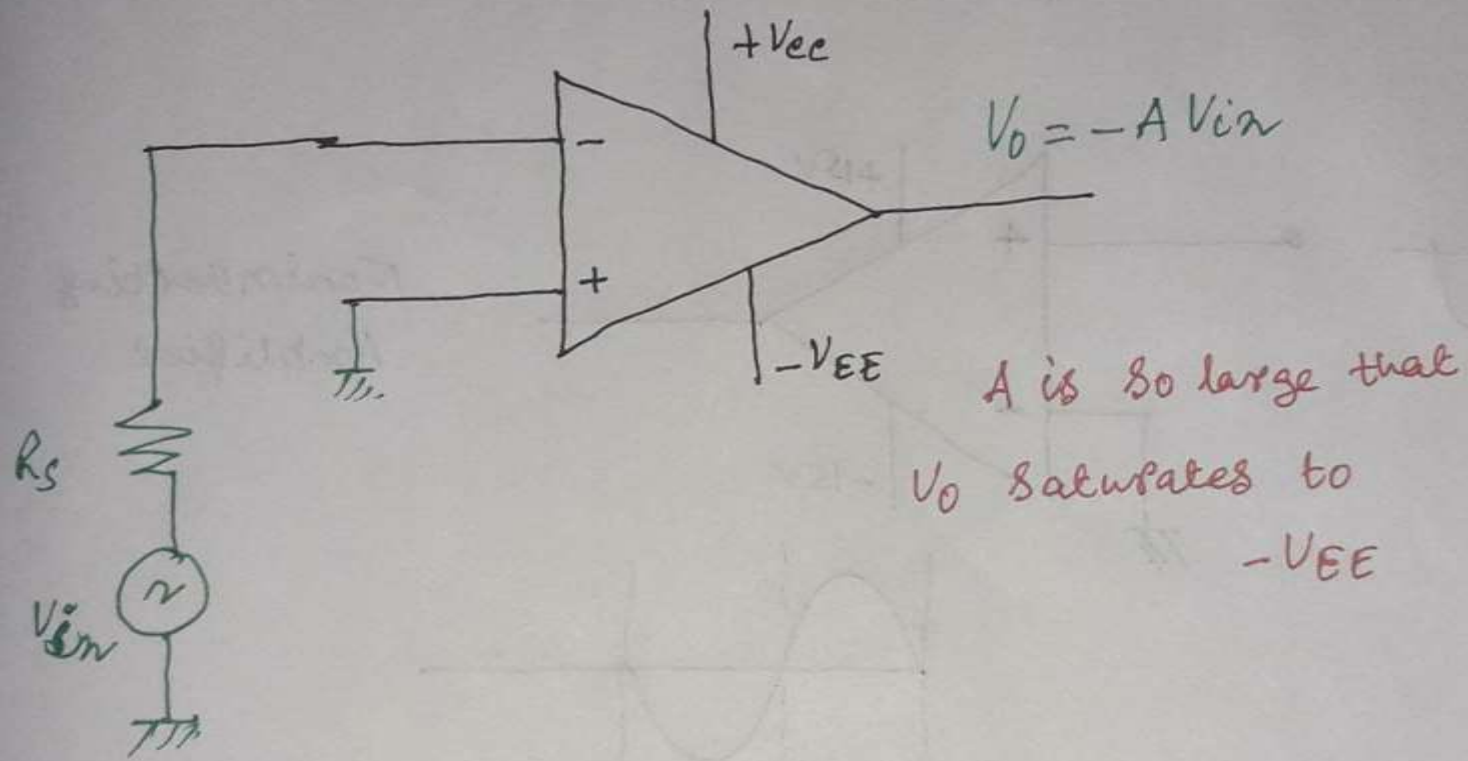


OP AMP

Noninverting Amplifier

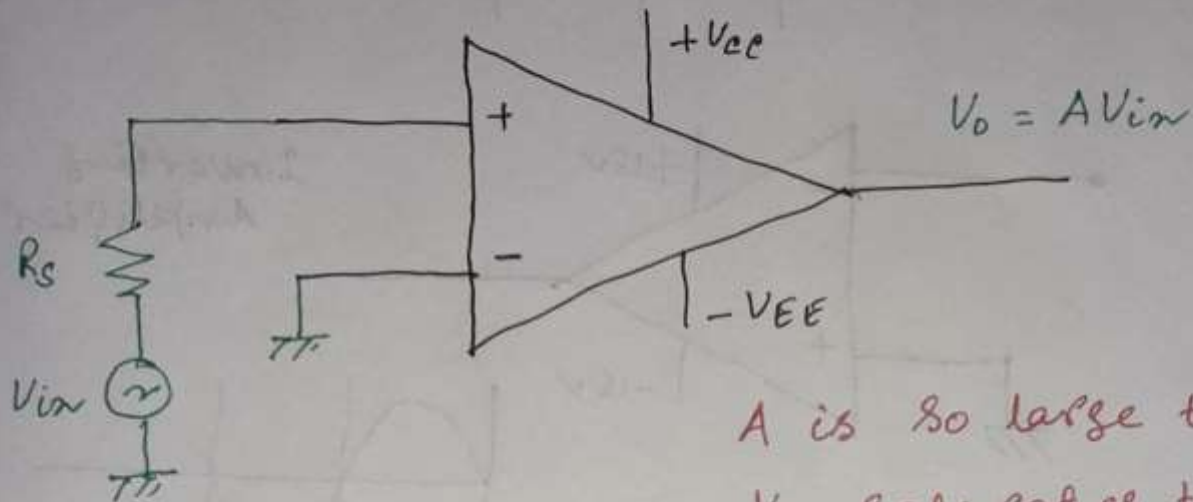


A is so large that
 V_o saturates to
 $+V_{cc}$.

OP AMP

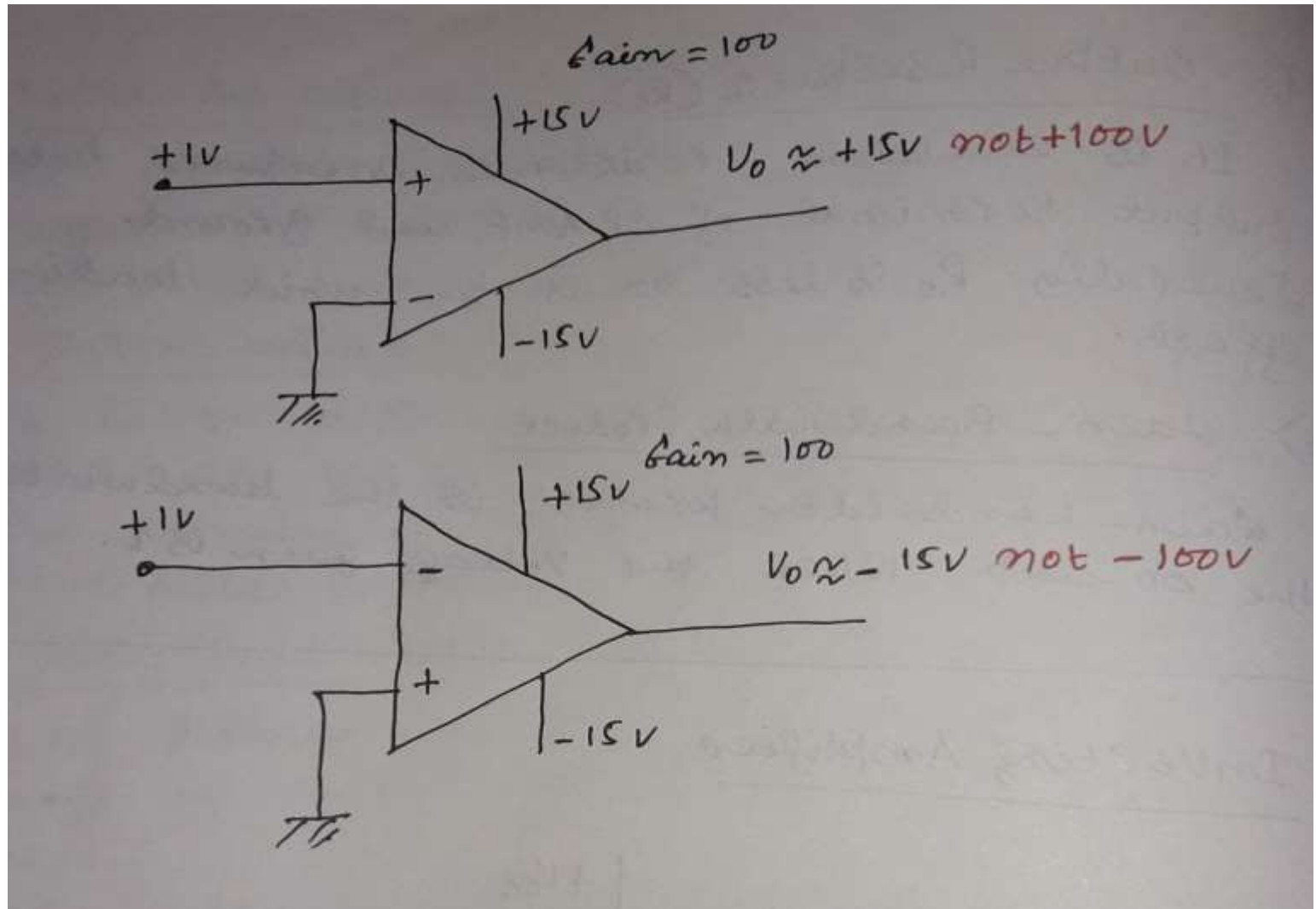

OP AMP

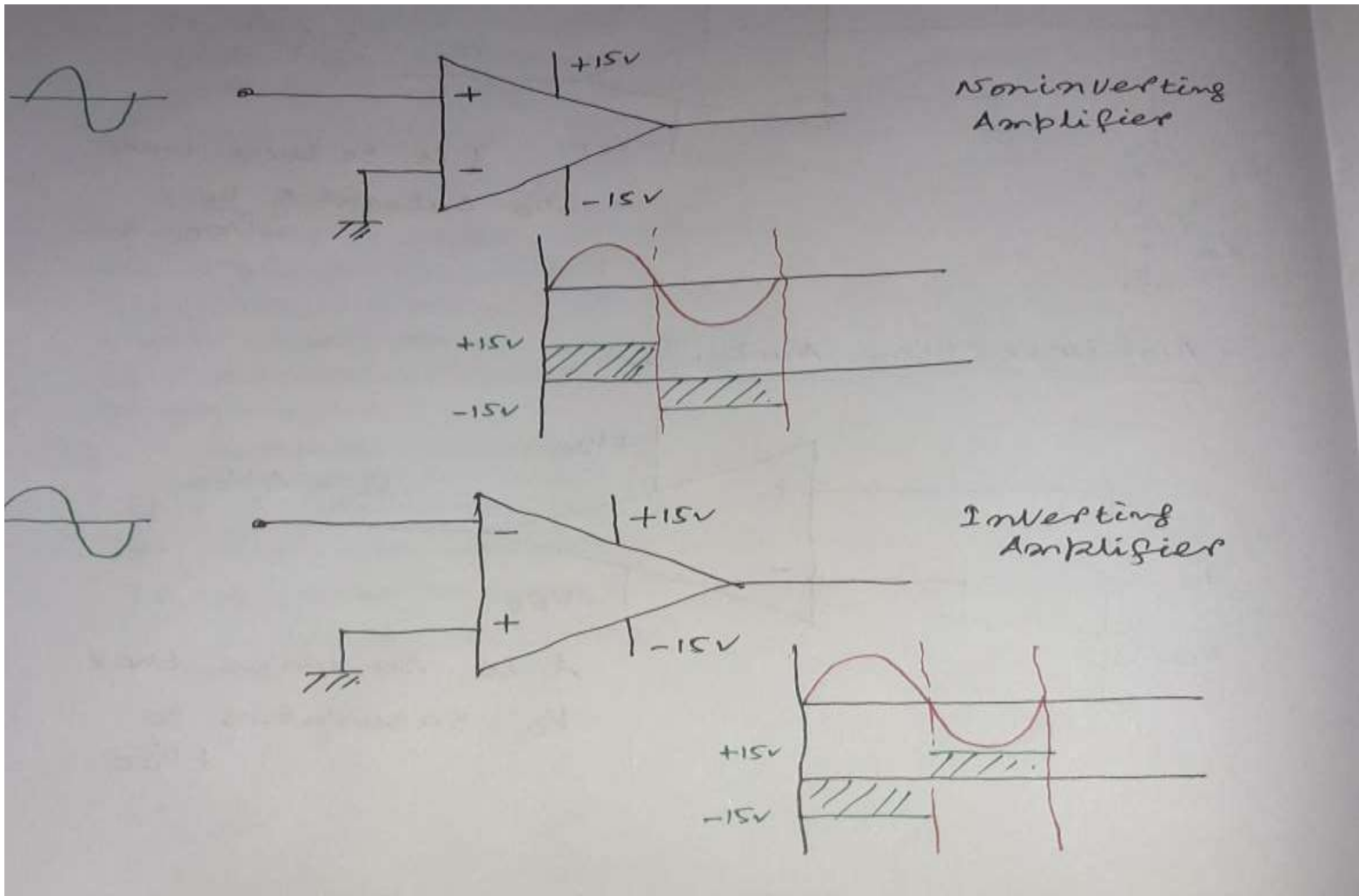

OP AMP

- > Here Amplification is not happening.
- > This is open loop application of OPAMP.
- > This is also called nonlinear applications of OPAMP.

OP AMP

Limitation of open loop configuration

1. In open-loop configuration even for small voltage also op-amp gets saturated.
2. open loop configuration can amplify micro volt signals with very low frequency. But such signals are very susceptible to noise.
3. open loop voltage gain is not constant. It changes with change in temperature and power supply. It is not suitable for linear applications.
4. Bandwidth (Band of frequencies for which the gain remains constant) of most open loop opamps is negligibly small almost zero. Hence this configuration is not suitable for ac applications.

To overcome these drawbacks closed loop configuration is used.


OP AMP

Concept of Feedback and Types of Feedback

In closed-loop configurations, there is a loop existing between output and input. The part of output is fed back to the input through a network. (may be resistance, resistance and capacitance etc.) This is called feedback.

Feedback Types

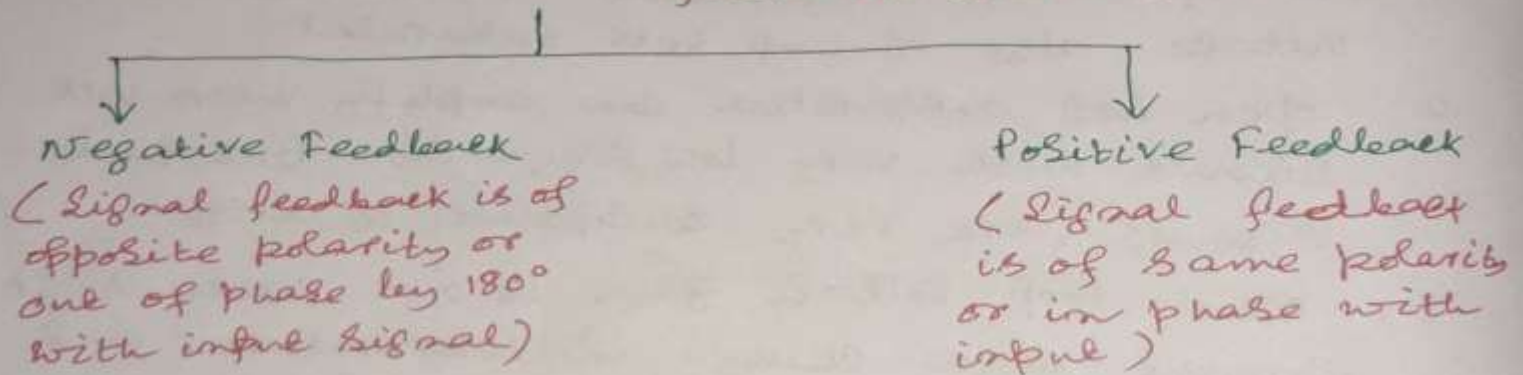(Based on the polarity of signal fed back to the input)



Difference between Negative and Positive Feedback

OP AMP

Negative Feedback	Positive Feedback.
<ol style="list-style-type: none">1. Signal feedback is of opposite polarity or out of phase by 180° with input.2. It is degenerative feedback i.e. output reduces.3. It is used in amplifiers.4. It has self correcting ability against any change in output caused by changes in environmental conditions. It opposes the input.5. It stabilizes the gain, increases bandwidth etc. but reduces the gain.	<ol style="list-style-type: none">1. Signal feedback is of same polarity or in phase with input.2. It is regenerative feedback i.e. output increases3. It is used in oscillators4. It feeds signal of same polarity and hence aids input signal.5. It continuously increases the gain of the amplifier.

OP AMP

Feedback Amplifier (closed-loop amplifiers)

Feedback Amplifiers using op-amp have two parts:


1. op-amp.
2. Feedback Circuit.

Feedback Topologies.

1. Voltage Series Feedback.
2. Voltage Shunt Feedback
3. Current Series Feedback
4. Current Shunt Feedback.

OP AMP

Inverting Amplifier with feedback

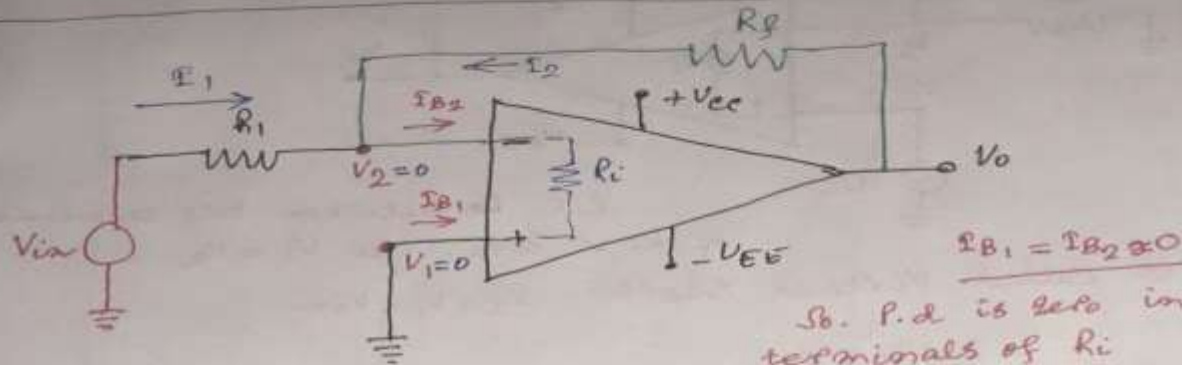

So, P.d is zero in two terminals of R_i

So $V_1 = V_2$, since V_2 is grounded, so V_1 is also having zero potential. This is called virtual ground.

$$I_1 + I_2 = 0$$


$$\therefore \frac{V_{in}}{R_1} + \frac{V_o}{R_f} = 0$$

$$\therefore \boxed{V_o = -\frac{R_f}{R_1} V_{in}}$$

$$\text{Gain} = -\frac{R_f}{R_1}$$


Gain is controllable.

OP AMP

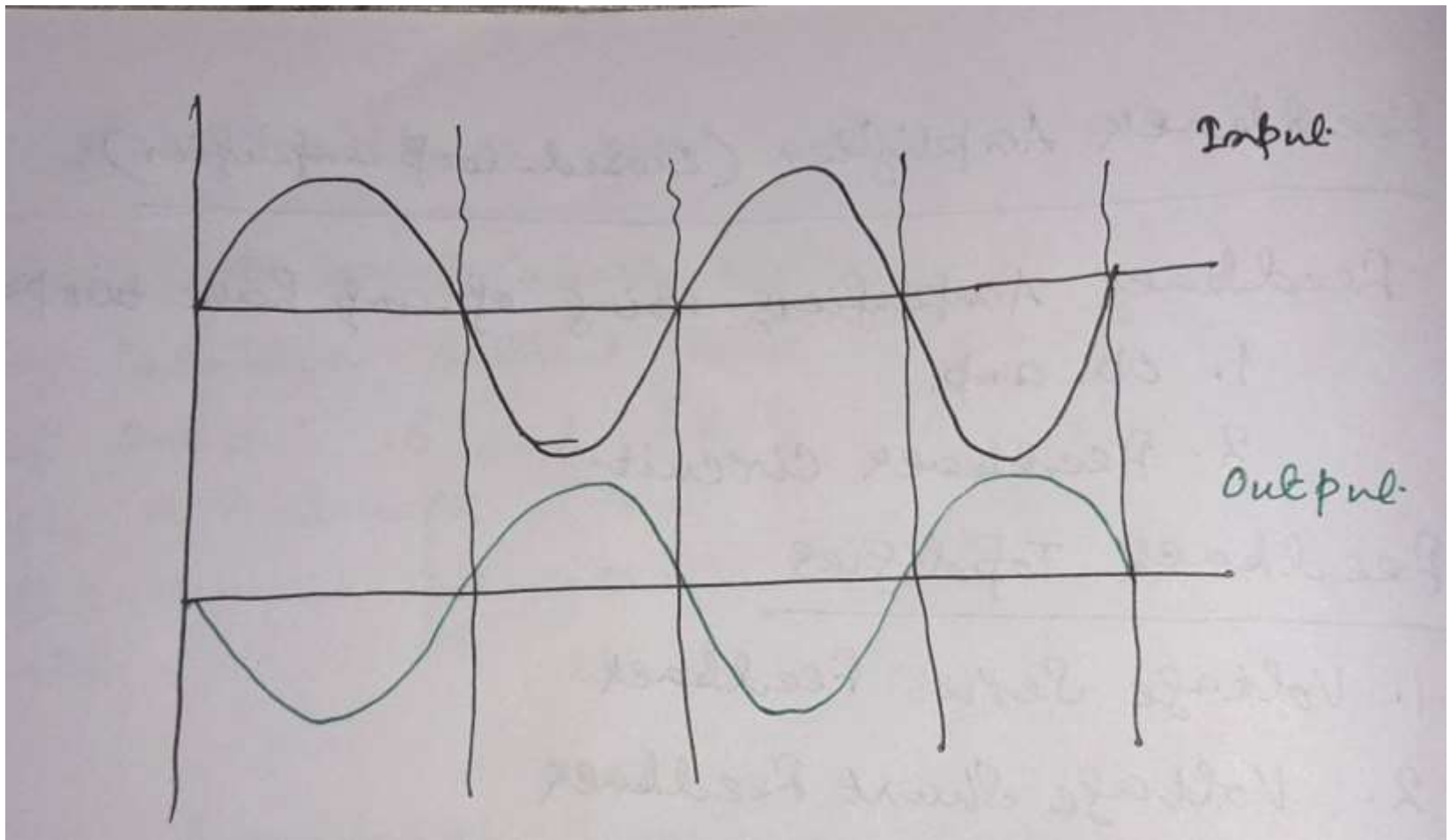

OP AMP

Closed Loop Non-Inverting Configuration

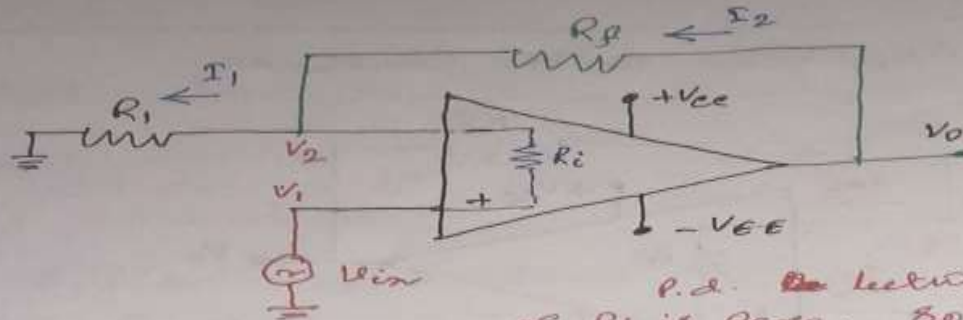

p.d. between two terminals of R_i is zero. So $V_1 = V_2$ is called Virtual Short. $V_2 = V_1 = V_{in}$

$$-I_1 + I_2 = 0.$$

$$\therefore -\left(\frac{V_{in}}{R_1}\right) + \frac{V_o - V_{in}}{R_f} = 0.$$

$$\therefore \frac{V_o}{R_f} = V_{in} \left(\frac{1}{R_f} + \frac{1}{R_1} \right)$$

$$\therefore \frac{V_o}{V_{in}} = R_f \left(\frac{1}{R_f} + \frac{1}{R_1} \right)$$


$$\therefore \boxed{V_o = \left(1 + \frac{R_f}{R_1} \right) V_{in}}$$

$$\text{Gain} = 1 + \frac{R_f}{R_1}$$

Gain is controllable.

OP AMP

Voltage Follower (Buffer)

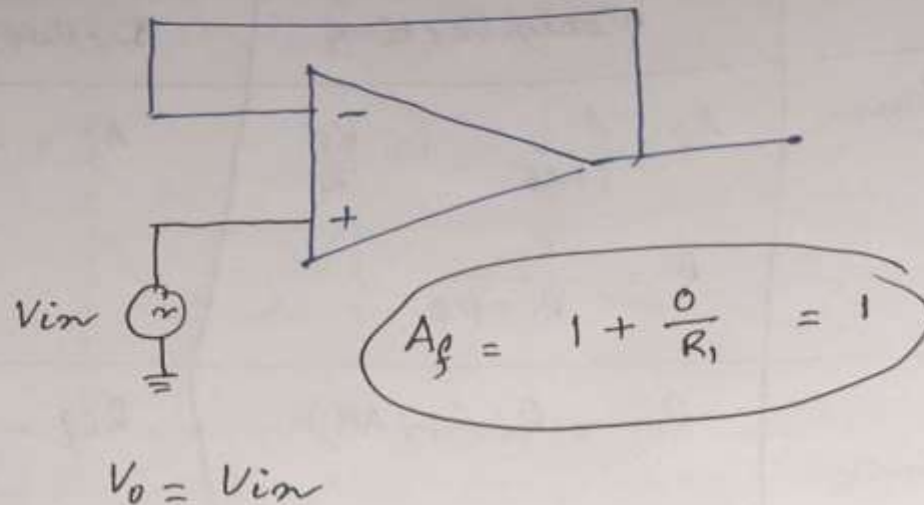

If in case inverting amplifier

$$R_f = R_1, \quad \boxed{V_o = -V_{in}} \quad \text{Inverter.}$$

OP AMP


Differential Amplifier

> It is a circuit that amplifies the difference between two input signals.


Differential Amplifiers are used in Instrumentation Systems because:

1. They are better able to reject common mode signals such as noise as compared to inverting and non inverting amplifiers. Thus it can be useful for millivolt signal amplification that is required in instrumentation.
2. They also present balanced input impedance.

OP AMP

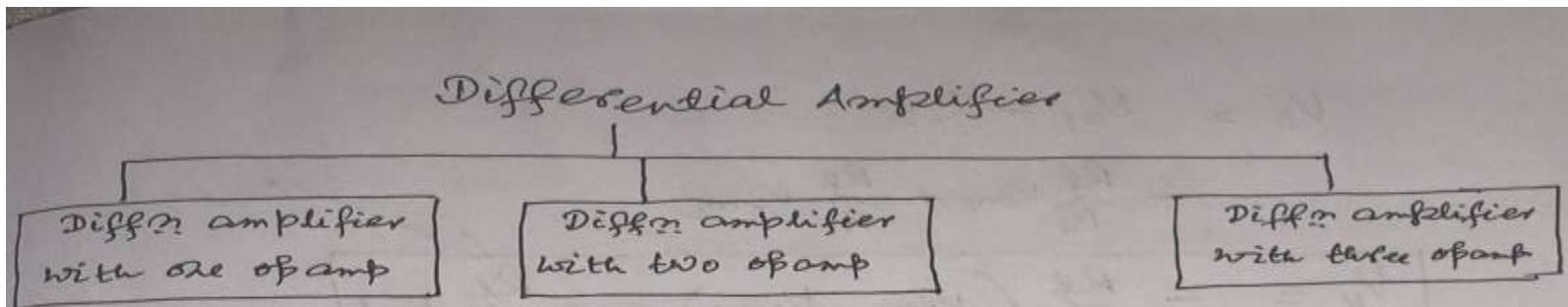

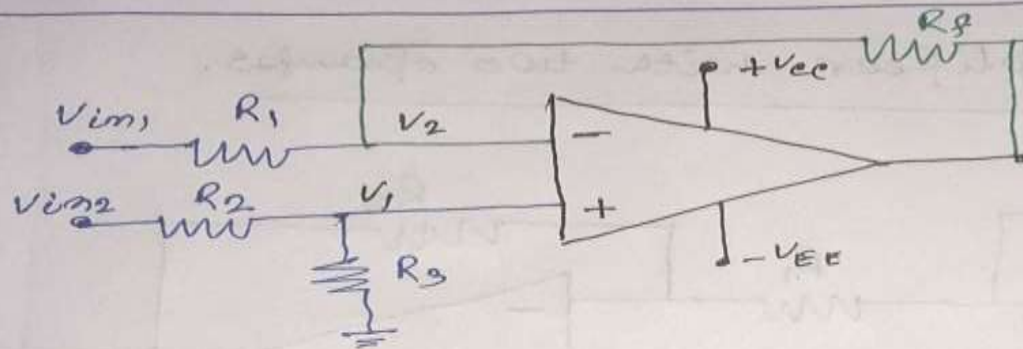Differential Amplifier with single op-amp.



1. with $V_{in1} = 0$ it acts as noninverting amplifier.
2. with $V_{in2} = 0$ it acts as inverting amplifier.

OP AMP

Use superposition theorem.

$$\text{Say, } V_{in2} = 0, \quad V_{o1} = - \frac{R_f}{R_1} V_{in1}$$

$$\text{When } V_{in1} = 0, \quad V_{o2} = \left(1 + \frac{R_f}{R_1}\right) V_1$$

$$V_1 = \frac{R_3}{R_2 + R_3} \cdot V_{in2}$$

$$\therefore V_{o2} = \left(1 + \frac{R_f}{R_1}\right) \frac{R_3}{R_2 + R_3} \cdot V_{in2}$$

$$\text{if } R_1 = R_2 \text{ \& } R_f = R_3$$

$$V_{o2} = \frac{R_f}{R_1} V_{in2}$$

OP AMP

$$V_o = V_{o1} + V_{o2}$$

$$= -\frac{R_f}{R_1} V_{in1} + \frac{R_f}{R_1} V_{in2}$$

$$V_o = -\frac{R_f}{R_1} (V_{in1} - V_{in2}) = -\frac{R_f}{R_1} V_{id}$$

Gain

OP AMP


$$V_o = V_{o1} + V_{o2}$$

$$= -\frac{R_f}{R_1} V_{in1} + \frac{R_f}{R_1} V_{in2}$$

$$V_o = -\frac{R_f}{R_1} (V_{in1} - V_{in2}) = -\frac{R_f}{R_1} V_{id}$$

Gain.

Differential Amplifier with two opamps.

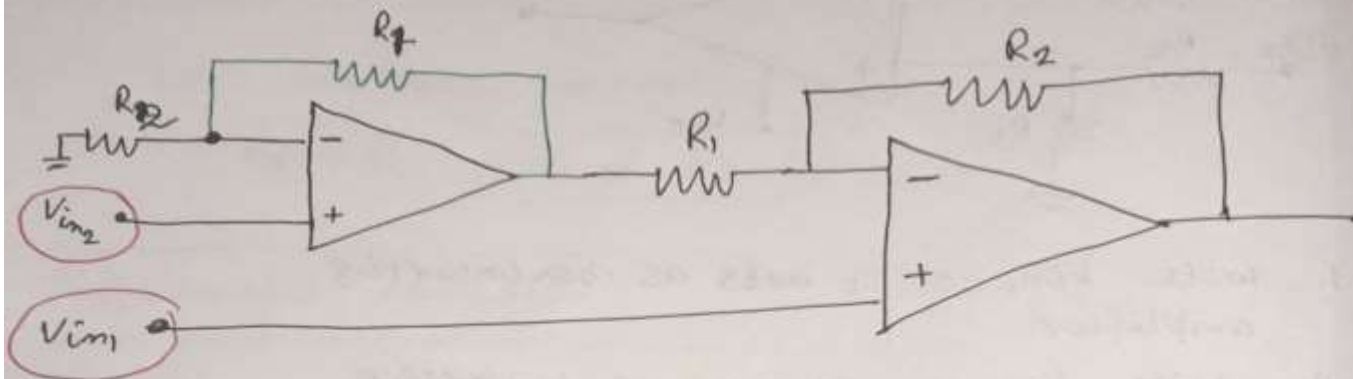

OP AMP

Differential Amplifier with two OPAMP.

$$V_{01} = V_{in2} \left(1 + \frac{R_1}{R_2} \right)$$

$$V_{02} = - \frac{R_2}{R_1} V_{in2} \left(1 + \frac{R_1}{R_2} \right)$$


$$= - V_{in2} \left(1 + \frac{R_2}{R_1} \right)$$

$$V_{03} = \left(1 + \frac{R_2}{R_1} \right) V_{in1}$$

$$V_0 = V_{02} + V_{03} = \left(1 + \frac{R_2}{R_1} \right) (V_{in1} - V_{in2}).$$

OP AMP

Differential Amplifier with three OPAMP.

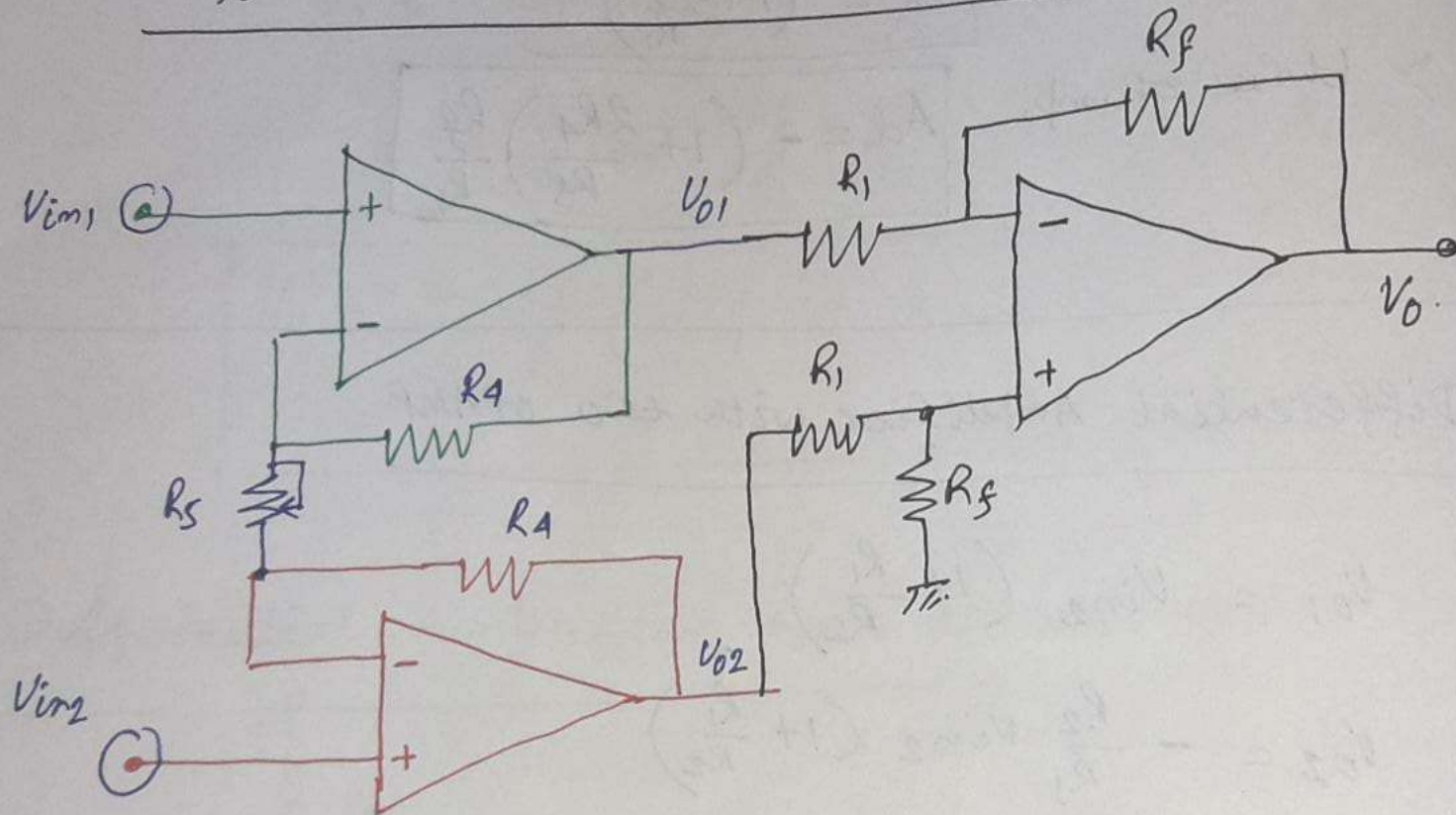

OP AMP

$$V_{o1}' = V_{in1} \left(1 + \frac{R_A}{R_5}\right) \dots \dots \textcircled{V_{in2} = 0}$$

$$V_{o1}'' = -\frac{R_A}{R_5} V_{in2}$$

$$\begin{aligned} V_{o1} &= \frac{R_A + R_5}{R_5} V_{in1} - \frac{R_A}{R_5} V_{in2} \\ &= \frac{(R_A + R_5)V_{in1} - R_A V_{in2}}{R_5} \\ &= \frac{R_A}{R_5} (V_{in1} - V_{in2}) + V_{in1} \end{aligned}$$

Similarly


$$V_{o2} = \frac{R_A}{R_5} (V_{in2} - V_{in1}) + V_{in2}$$

$$\begin{aligned} V_o &= \frac{R_f}{R_i} (V_{o2} - V_{o1}) \\ &= \frac{R_f}{R_i} \left[\frac{R_A}{R_5} (V_{in2} - V_{in1}) + V_{in2} - \frac{R_A}{R_5} (V_{in1} - V_{in2}) - V_{in1} \right] \end{aligned}$$

$$\boxed{V_o = -\left(\frac{R_f}{R_i}\right) \left(1 + \frac{2R_A}{R_5}\right) (V_{in1} - V_{in2})}$$


OP AMP

INSTRUMENTATION AMPLIFIER

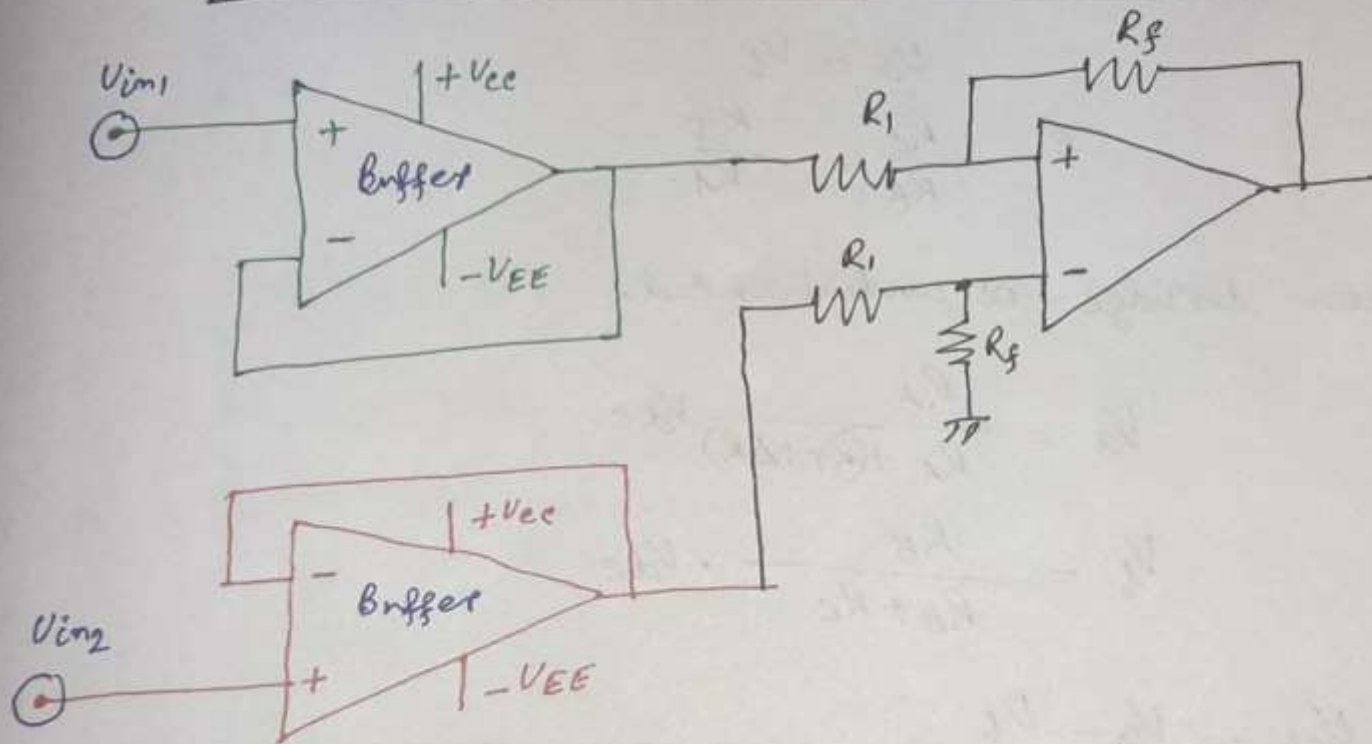

OP AMP

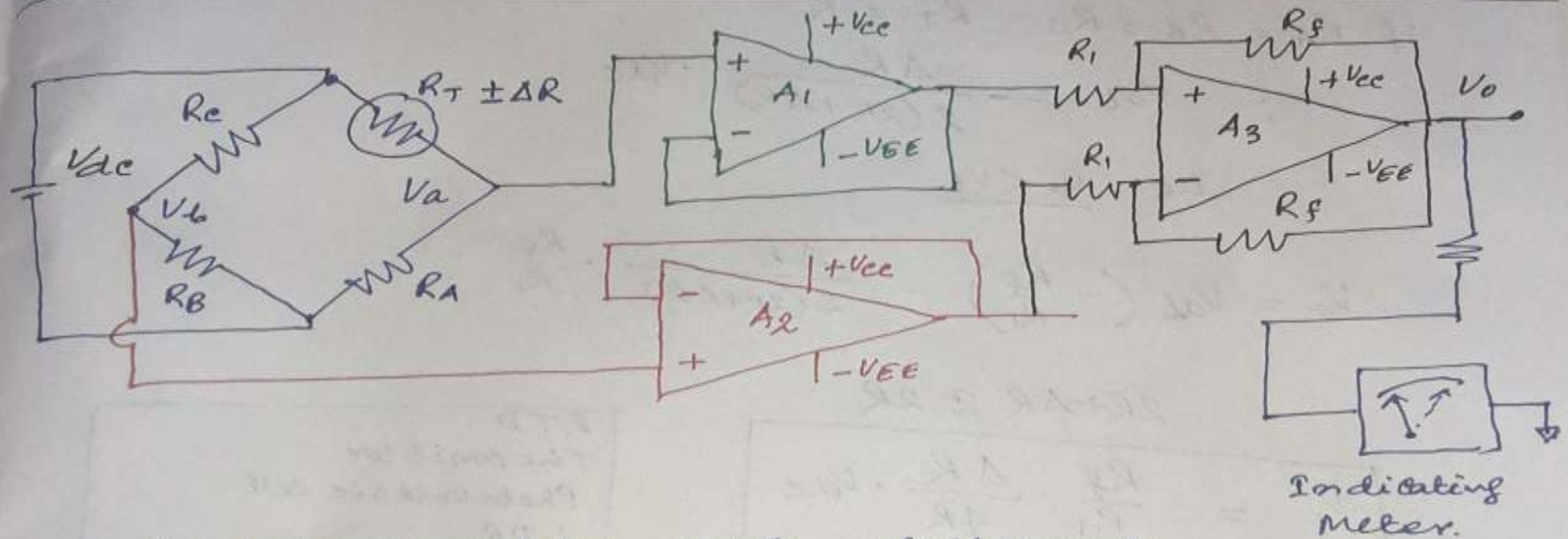Instrumentation Amplifier with Transducer Bridge.



> Resistive Transducer whose resistance changes as a function of some physical energy.

OP AMP

When the bridge is balanced,

$$V_a = V_b.$$
$$\therefore \frac{R_c}{R_B} = \frac{R_T}{R_A}.$$

When bridge is unbalanced,

$$V_a = \frac{R_A}{R_A + (R_T + \Delta R)} V_{dc}.$$

$$V_b = \frac{R_B}{R_B + R_c} \cdot V_{dc}.$$

$$\therefore V_{ab} = V_a - V_b.$$

$$= \frac{R_A}{R_A + R_T + \Delta R} V_{dc} - \frac{R_B V_{dc}}{R_B + R_c}.$$

$$\text{if } R_A = R_B = R_c = R_T = R$$

$$\therefore V_{ab} = - \frac{\Delta R}{2(2R + \Delta R)} \cdot V_{dc}.$$

$$\text{i.e. } \underline{V_a < V_b}$$

OP AMP

$$V_o = V_{ab} \left(-\frac{R_f}{R_i} \right) = \frac{\Delta R}{2(2R + \Delta R)} \cdot \frac{R_f}{R_i}$$

$$2R + \Delta R \approx 2R$$

$$V_o = \frac{R_f}{R_i} \cdot \frac{\Delta R}{4R} \cdot V_{dc}$$


$$\underline{V_o \propto \Delta R}$$

RTD
Thermistor
PhotoVoltaic cell
LDR
Strain Gauge
(Analog Weight Scale)

Temperature Indicator, Temperature Controller, Light Intensity meter, Measurement flow & Conductivity, Analog Weight Scale etc.

OP AMP

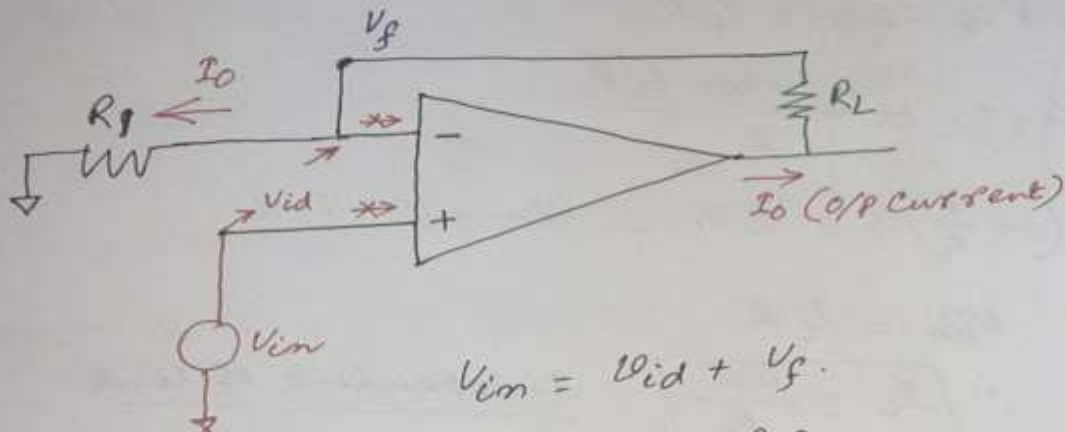Voltage to Current Converter with floating load



$$V_{id} = 0,$$

$$V_{in} = V_{id} + V_g.$$

$$V_{in} = V_g = R_1 I_o.$$


$$\therefore \boxed{I_o = \frac{V_{in}}{R_1}}$$

Output current is independent of load.

Applications — Low Voltage DC Voltmeter, Telemetry System.
Low Voltage AC Voltmeter, Zener Diode Tester,
Light emitting Diode Tester.

OP AMP

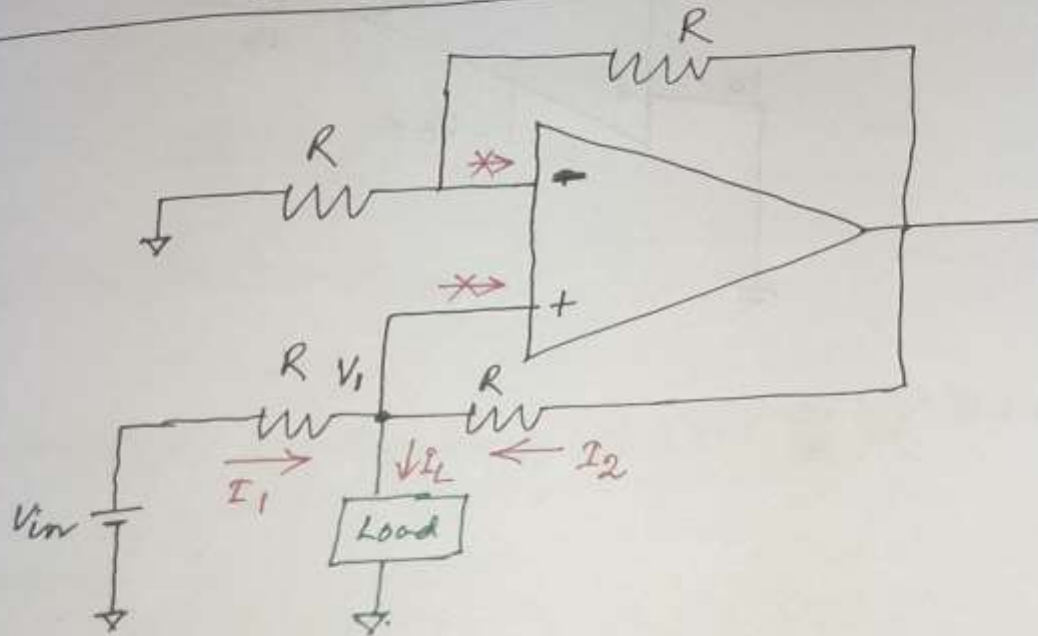Voltage to Current Converter with grounded load.



OP AMP

$$I_1 + I_2 = I_L$$

$$\therefore \frac{V_{in} - V_1}{R} + \frac{V_o - V_1}{R} = I_L$$

$$\therefore V_{in} + V_o - 2V_1 = I_L R$$

$$\therefore V_1 = \frac{V_{in} + V_o - I_L R}{2}$$


$$\therefore V_o = \left(1 + \frac{R}{R}\right) V_1 = 2V_1 = V_{in} + V_o - I_L R$$

$$\therefore V_{in} = I_L R$$

$$\therefore \boxed{I_L = \frac{V_{in}}{R}}$$

Independent of load.

OP AMP

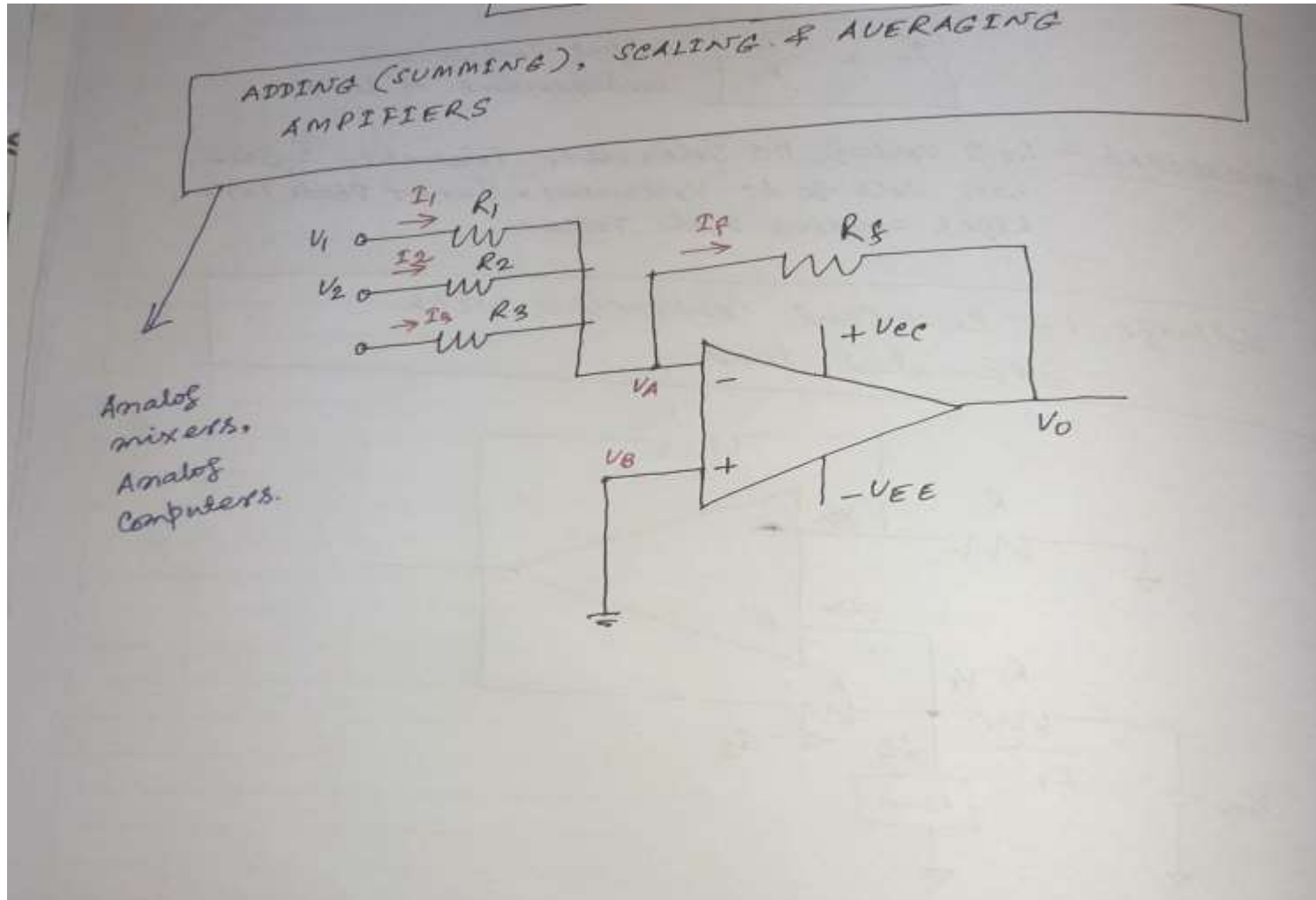

OP AMP

$$I_1 + I_2 + I_3 - I_f = 0.$$

$$\therefore V_A = V_B = 0$$

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} - \frac{V_A - V_0}{R_f} = 0.$$

$$\therefore V_0 = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

Scaling or Weighting Amplifier

Summing Amplifier

$$R_f = R_2 = R_3 = R$$

$$\therefore V_0 = - \left(\frac{R_f}{R_1} \right) (V_1 + V_2 + V_3)$$

OP AMP

Adder

$$R_1 = R_2 = R_3 = R_f = R.$$

$$\therefore V_o = -(V_1 + V_2 + V_3)$$

Averaging Circuit.

$$R_1 = R_2 = R_3 = R$$

$$\frac{R_f}{R} = \frac{1}{n}$$


Here $n=3$,
$$V_o = - \frac{V_1 + V_2 + V_3}{3}$$

Noninverting?

Summing
$$V_o = \left(1 + \frac{R_f}{R_1}\right) (V_1 + V_2 + V_3)$$


OP AMP

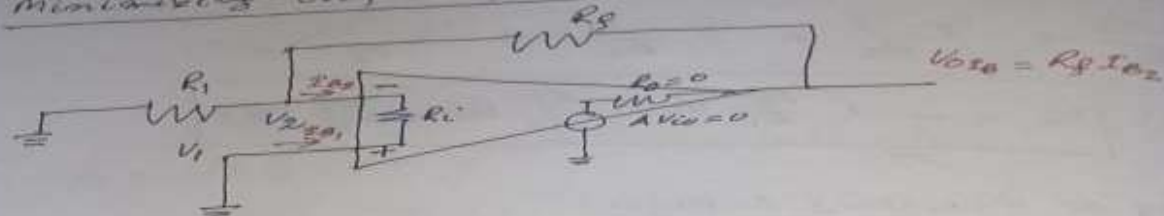~~OFFSET ADJUSTING TECHNIQUE~~
Minimizing output offset voltage



$$V_2 = (R_1 \parallel R_f) I_{B2}$$


$$V_{out} = R_f I_{B2}$$

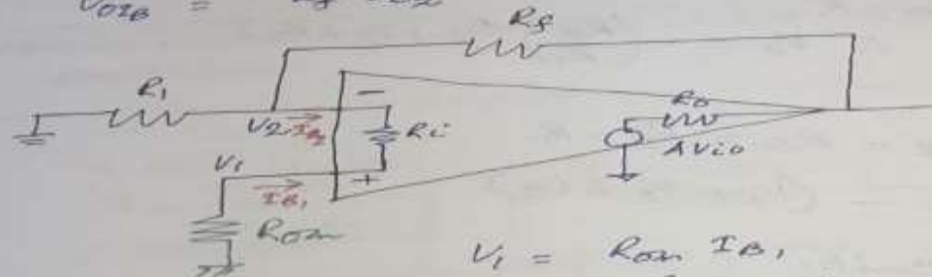

$$\therefore R_{eq} I_{B1} = (R_1 \parallel R_f) I_{B2}$$


$$\underline{I_{B1} = I_{B2}} \quad \therefore \boxed{R_{eq} = (R_1 \parallel R_f)}$$

OP AMP

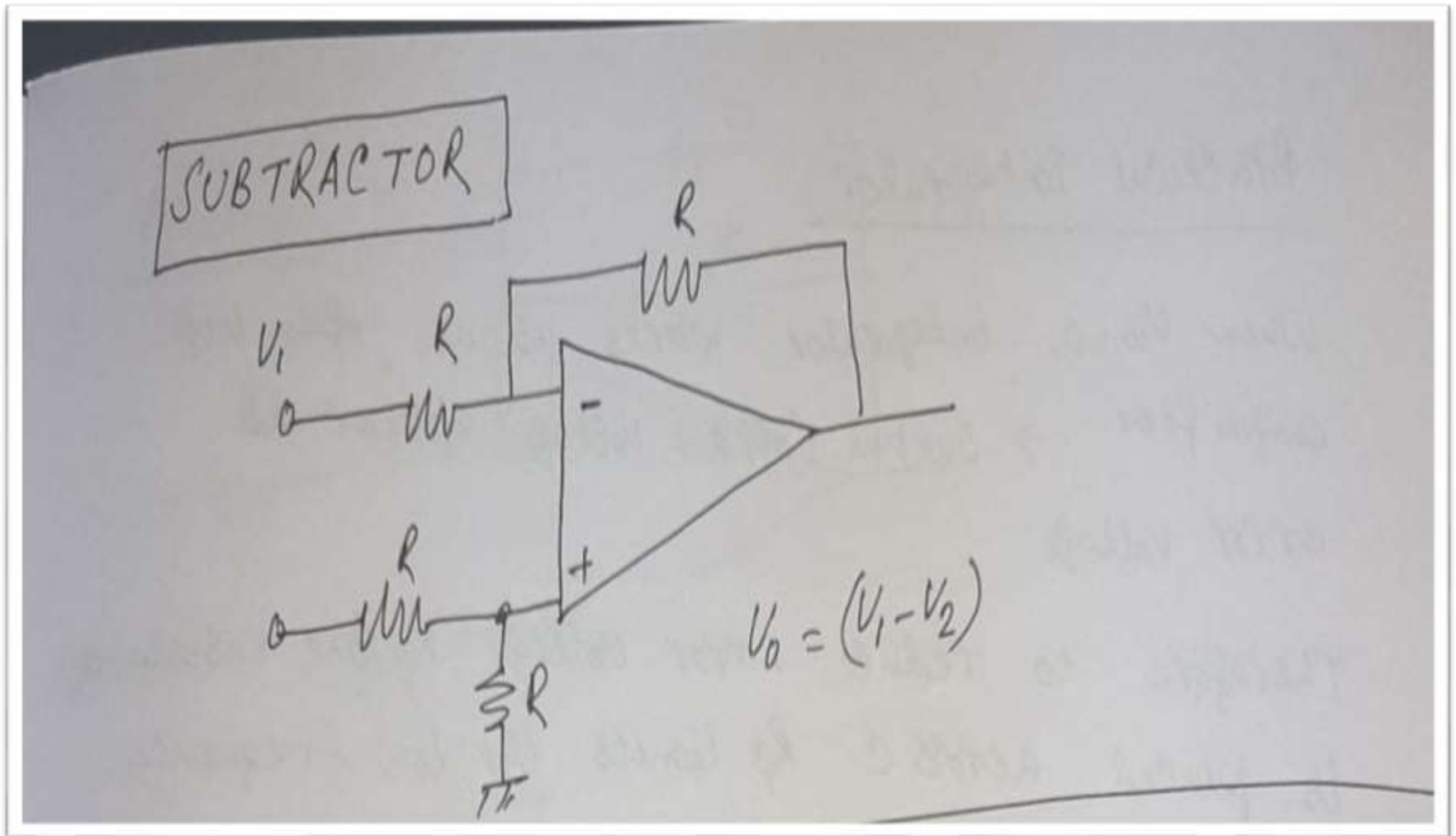

OP AMP

THE INTEGRATOR

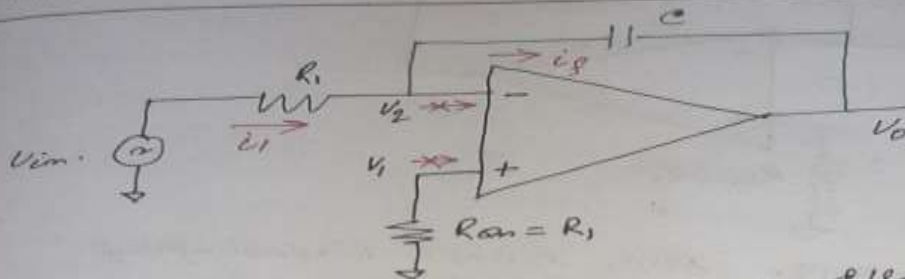

$$i_1 = i_2$$

$$i_c = C \frac{dV_o}{dt}$$

$$\therefore \frac{V_{in} - V_2}{R_1} = C \frac{d}{dt} (V_2 - V_o)$$

$$\therefore \frac{V_{in}}{R_1} = C \frac{d}{dt} (-V_o)$$

$$\therefore \int_0^t \frac{V_{in}}{R_1} dt = \int_0^t C \frac{d}{dt} (-V_o) dt$$

$$= C (-V_o) + V_o |_{t=0}$$

$$\therefore \boxed{V_o = -\frac{1}{R_1 C} \int_0^t V_{in} dt + C}$$


$$f_L = \frac{1}{2\pi R_1 C F}$$

OP AMP

Practical Integrator


When $V_{in}=0$, integrator works as an open loop amplifier. \rightarrow Output (offset voltage) appear as error voltage.

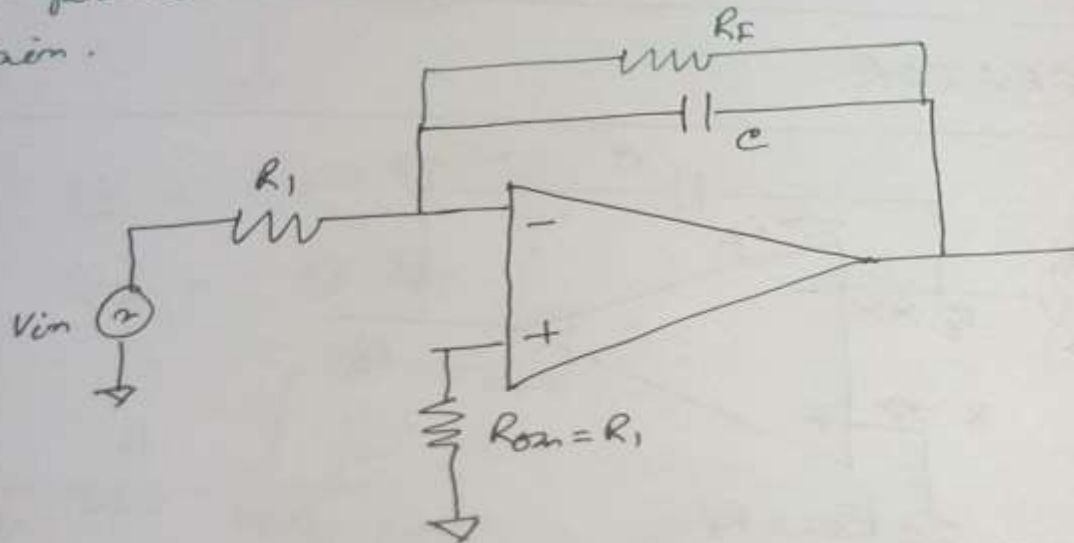Therefore to reduce error voltage R_f (one resistance) is placed across C . R_f limits the low frequency gain.




\rightarrow Analog Computers, ADC, Signal Waveshaping.

OP AMP

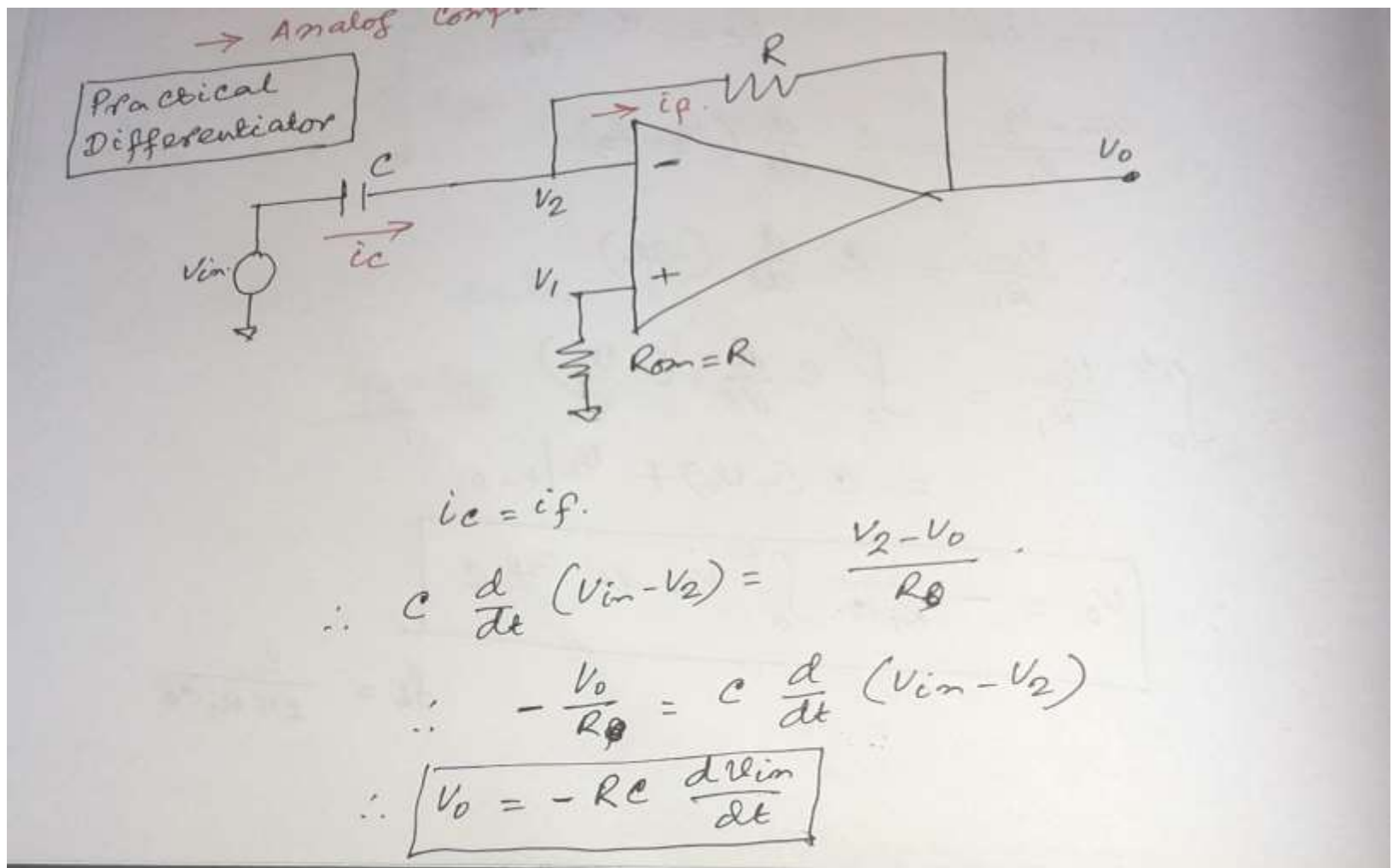


OP AMP

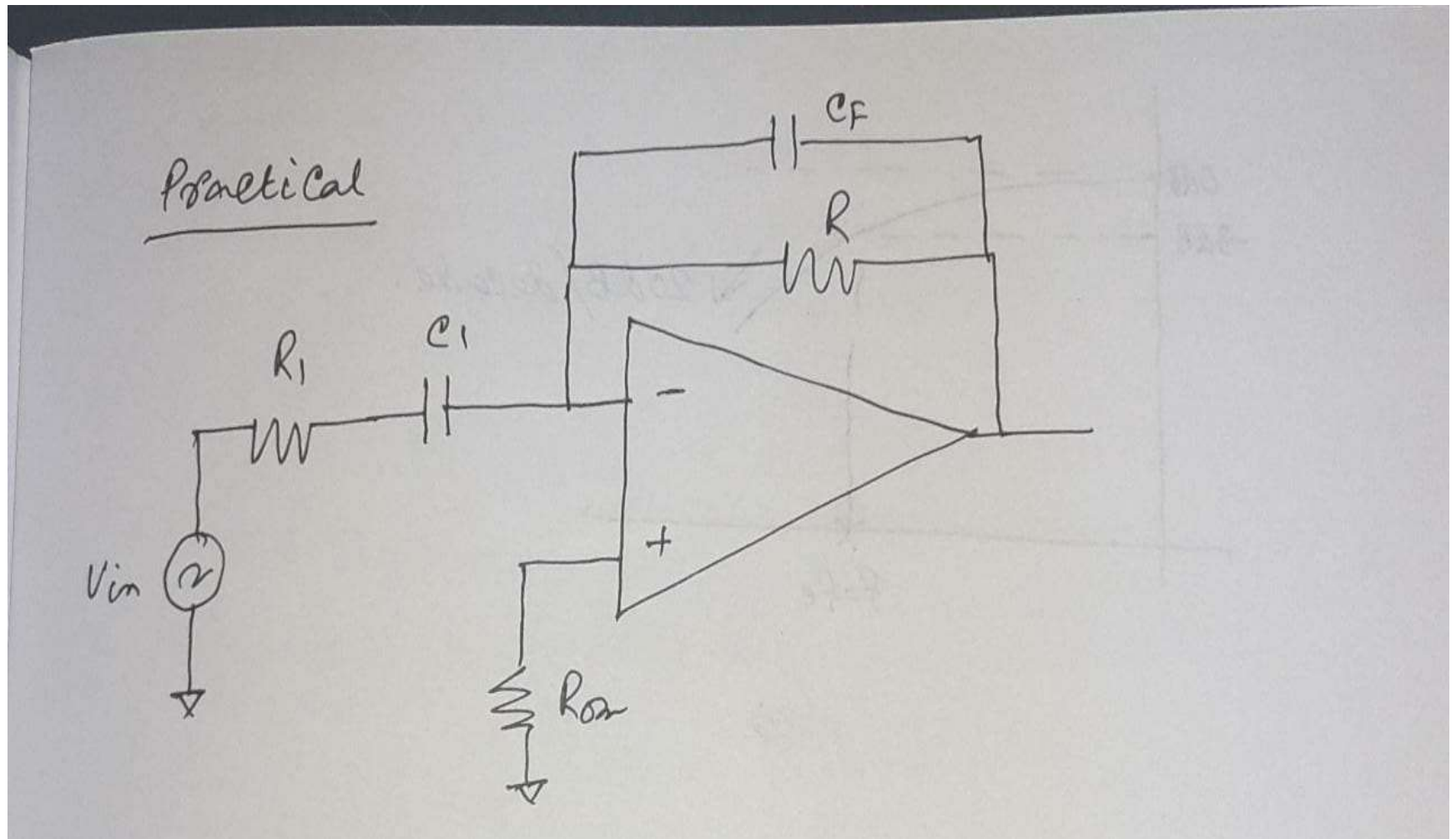

OP AMP

FREQUENCY RESPONSE OF AN OPAMP.

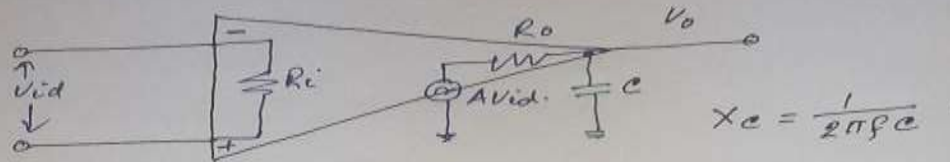

$$V_o = \frac{A V_{id} \cdot X_c}{R_o + X_c}$$

$$V_o = \frac{\frac{1}{j\omega c}}{R_o + \frac{1}{j\omega c}} (A V_{id})$$

$$= \frac{A V_{id}}{1 + j\omega c R_o}$$

$$= \frac{A V_{id}}{1 + j 2\pi f c R_o} = \frac{A V_{id}}{1 + j(f/f_c)} \quad \text{where } f_c = \frac{1}{2\pi c R_o}$$

$$\therefore A_f = \frac{V_o}{V_{id}} = \frac{A}{1 + j(f/f_c)}$$

$$\therefore |A_f| = \frac{A}{\sqrt{1 + (f/f_c)^2}}$$

OP AMP

FREQUENCY RESPONSE OF AN OPAMP.



$$V_o = \frac{\cancel{j\omega C} \cdot A V_{id}}{R_o - \cancel{j\omega C}} A V_{id}$$

$$V_o = \frac{\frac{1}{j\omega C}}{R_o + \frac{1}{j\omega C}} (A V_{id})$$

$$= \frac{A V_{id}}{1 + j\omega C R_o}$$


$$= \frac{A V_{id}}{1 + j 2\pi f C R_o}$$

$$= \frac{A V_{id}}{1 + j(f/f_c)} \quad \text{where } f_c = \frac{1}{2\pi C R_o}$$


$$\therefore A_f = \frac{V_o}{V_{id}} = \frac{A}{1 + j(f/f_c)}$$

$$\therefore |A_f| = \frac{A}{\sqrt{1 + (f/f_c)^2}}$$

OP AMP


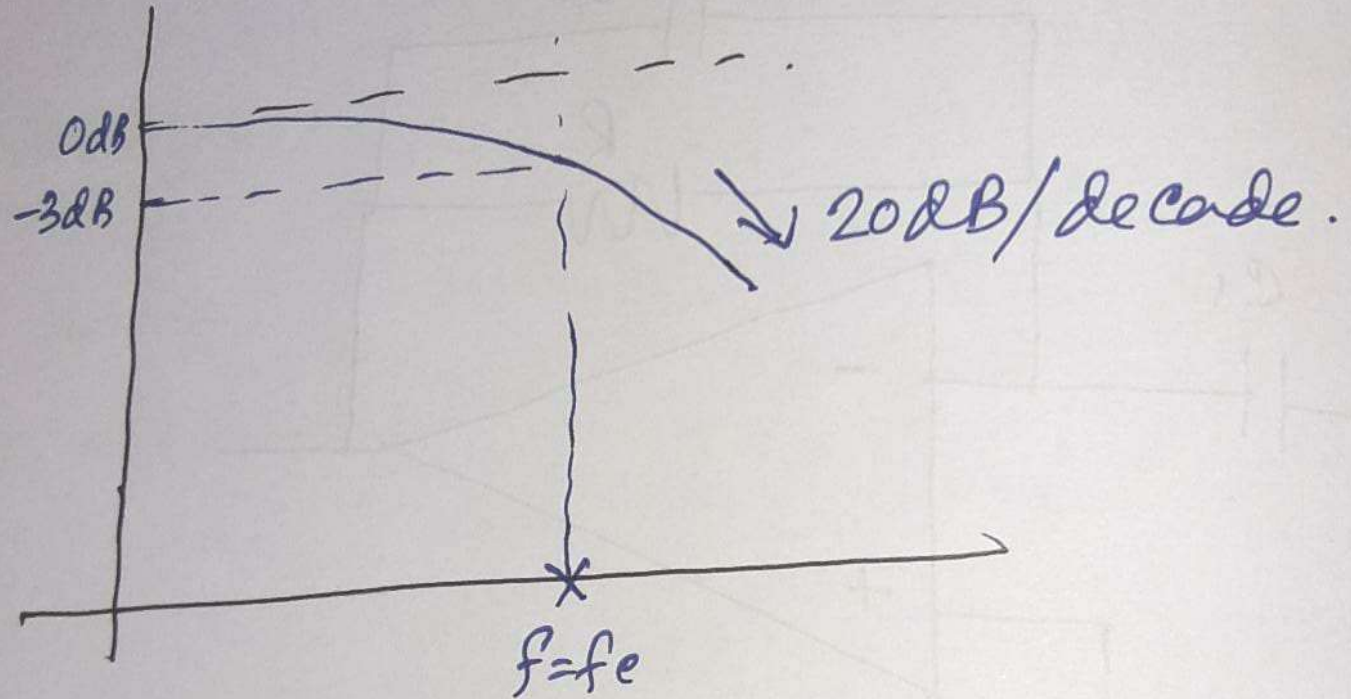


OP AMP

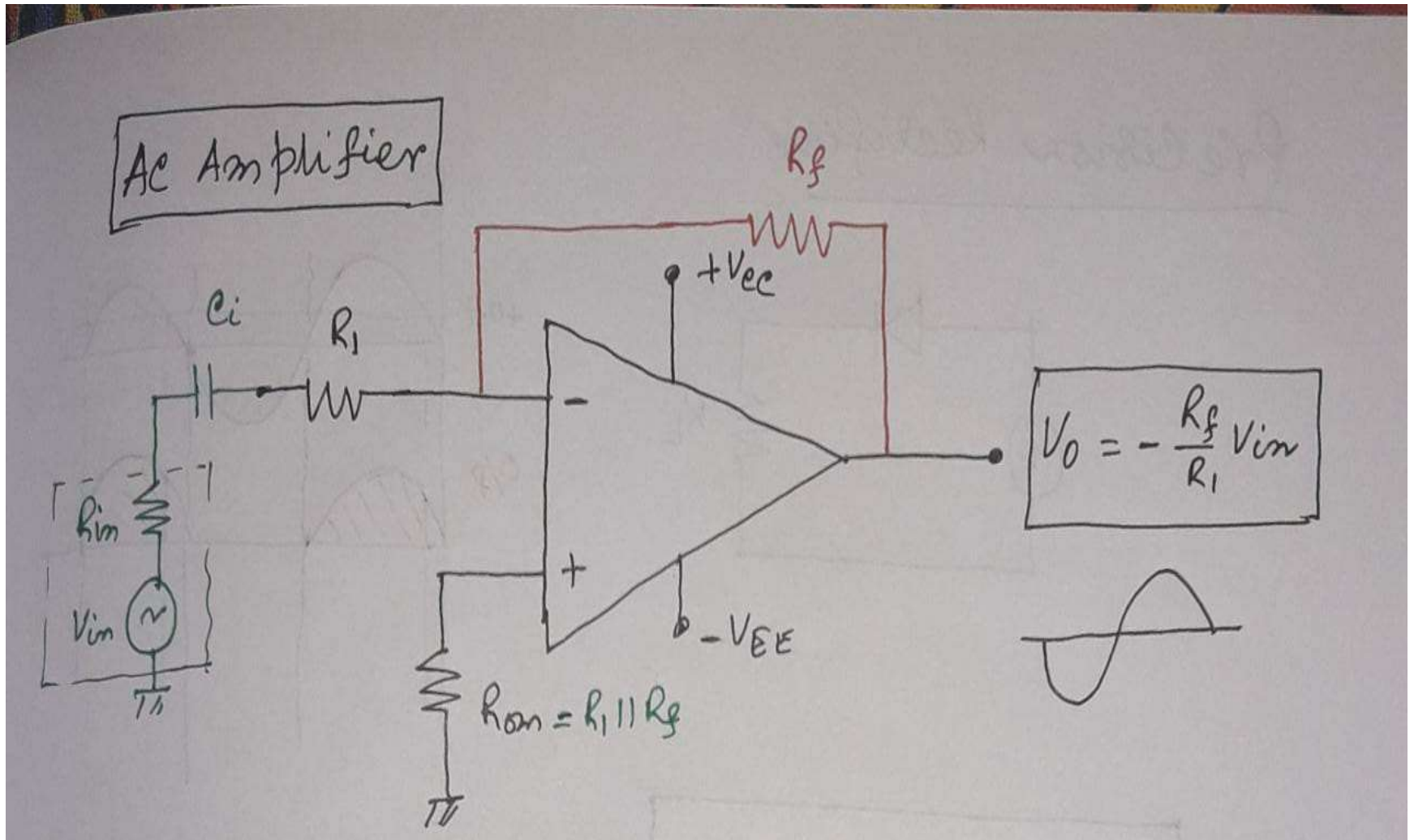



OP AMP

AC Amplifier with single power supply.

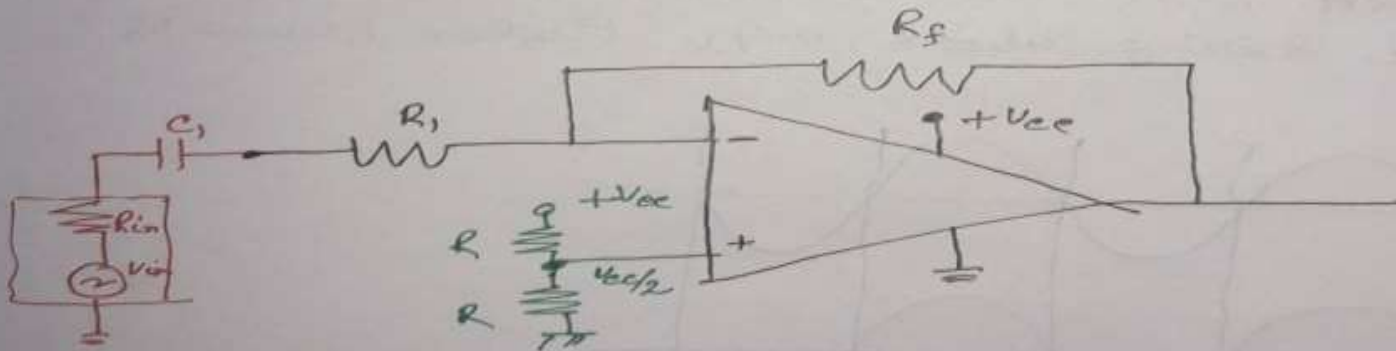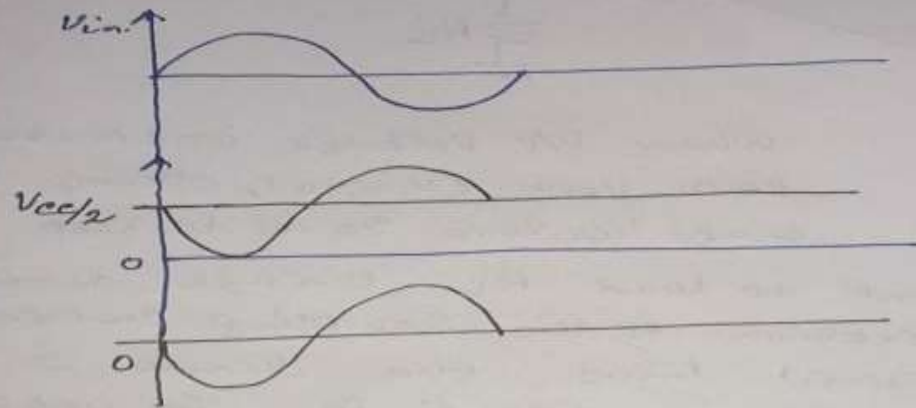


OP AMP

Precision Rectifier

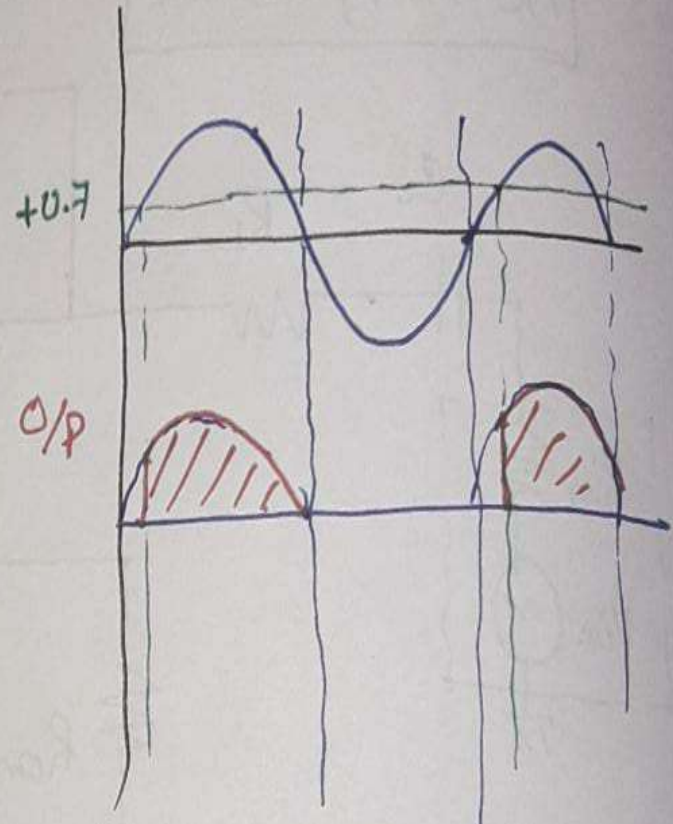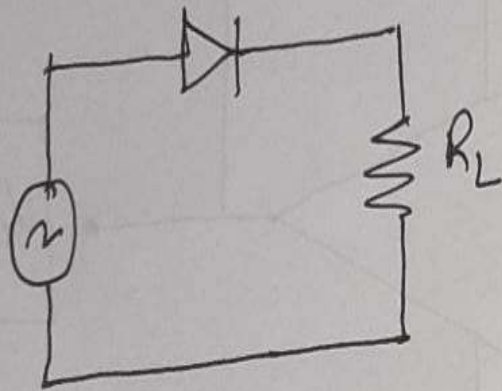


OP AMP

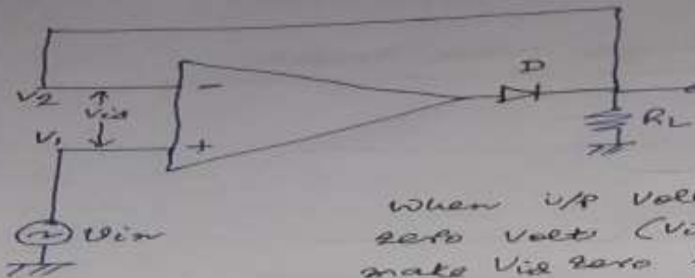

Half Wave


When i/p voltage increases above zero volt ($V_{in} > 0$), opamp tried to make V_{id} zero so as to keep V_1 equal to V_2 .

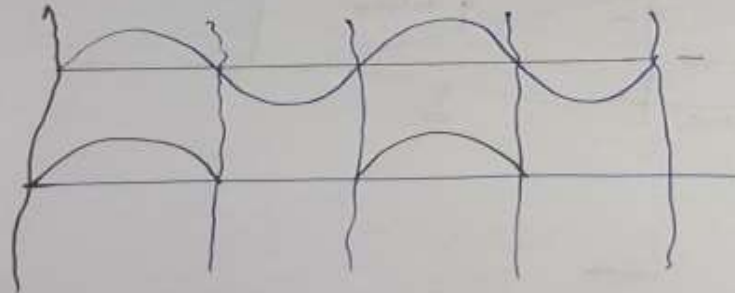If source current to load R_L through diode D is to ground. The direction of the sourcing current is opposite to forward bias the diode D which develops to drop $0.7V$ across diode. To achieve this opamp should swing about $0.7V$ higher than V_o .




OP AMP


Full wave Precision Rectifier

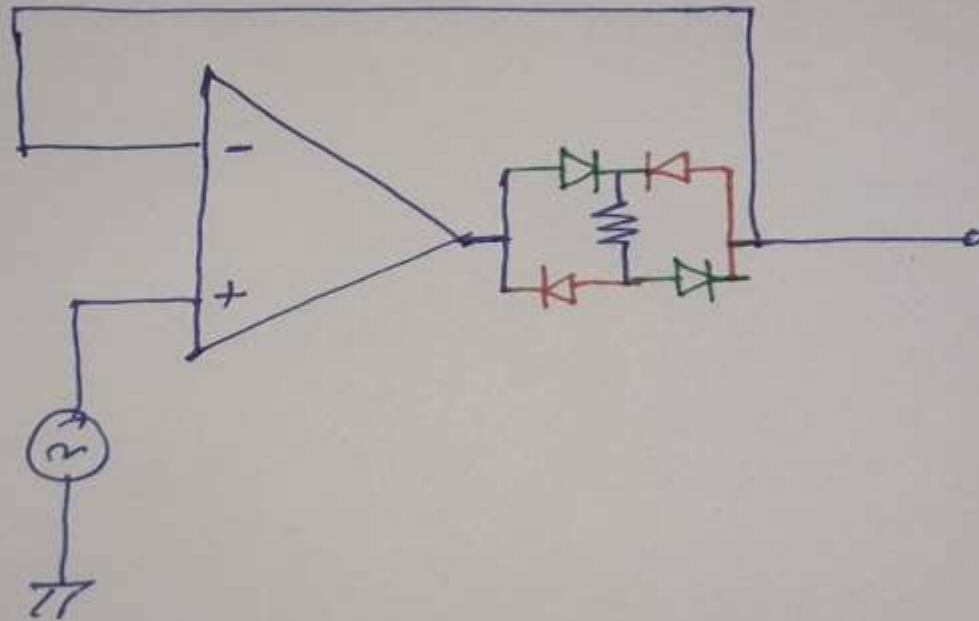


OP AMP

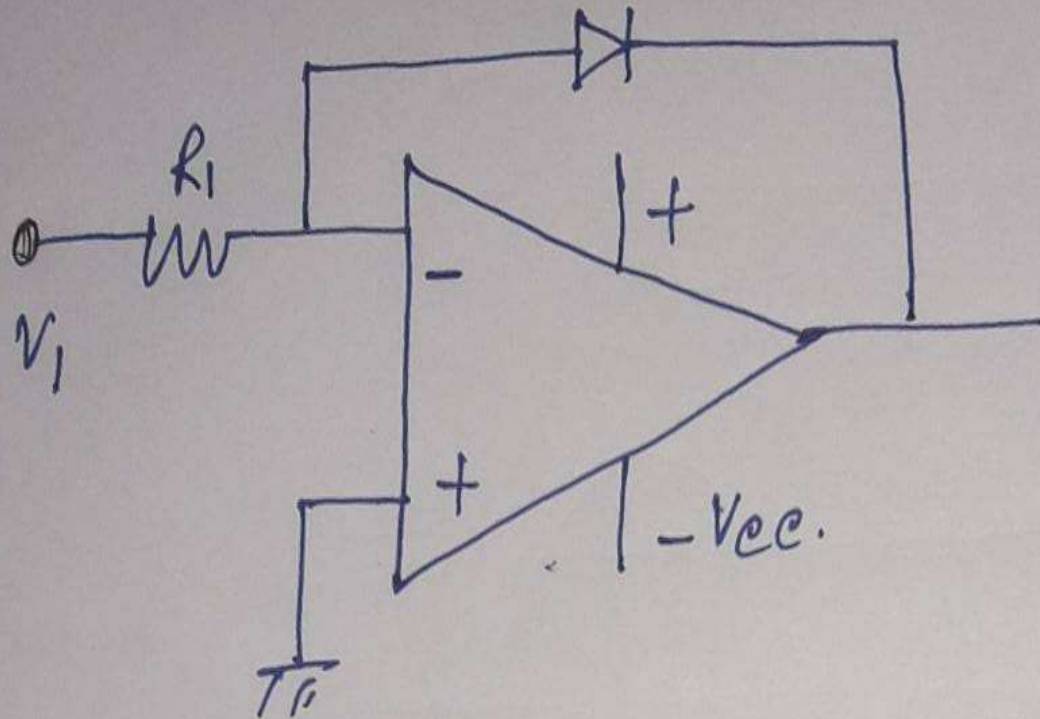

OP AMP

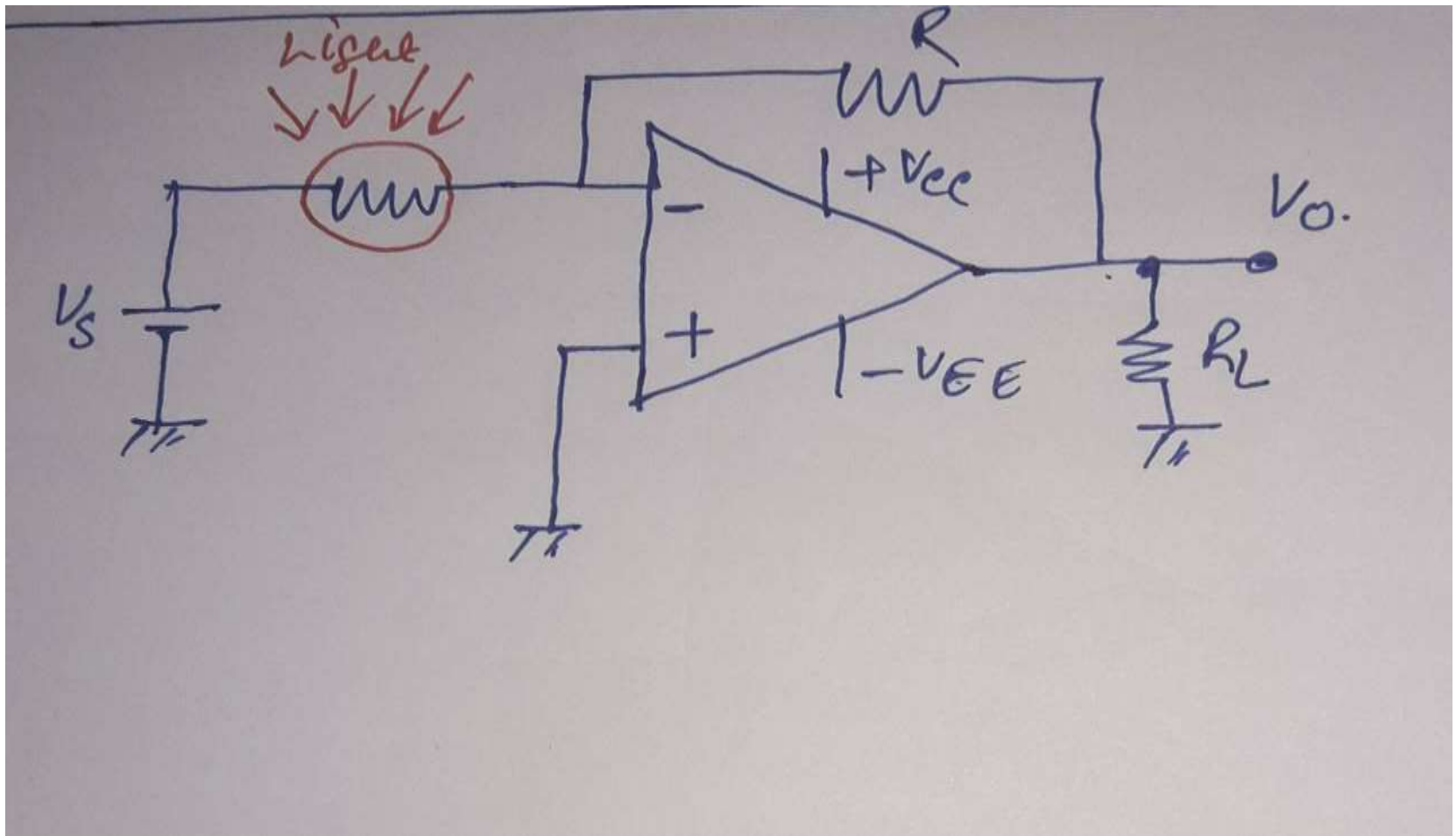

OP AMP

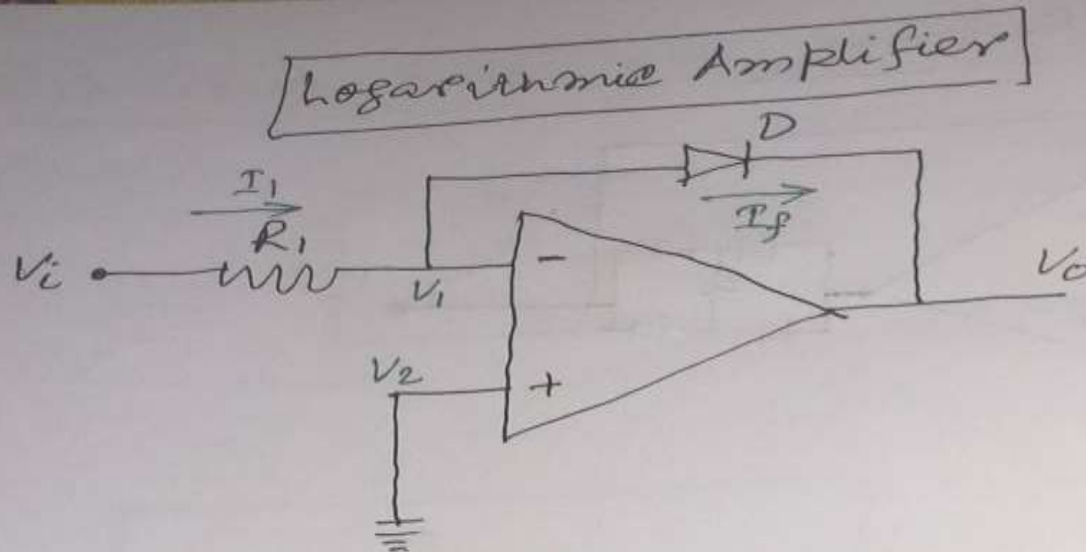

$$I_f = I_1 = V_i / R_1$$

$$I_f = I_s e^{(V_f / n V_T)}$$

I_s = Saturation Current of the diode

V_f = Voltage Drop across diode,
When it is in forward bias

V_T = diode's thermal equivalent voltage.

OP AMP

$$V_f = -V_o \quad (-V_o/nV_T)$$

$$\therefore I_f = I_S e$$


$$\therefore \frac{V_i}{R_1} = I_S e^{- (V_o/nV_T)}$$

$$\therefore \frac{V_i}{R_1 I_S} = e^{- (V_o/nV_T)}$$

$$\ln \left(\frac{V_i}{R_1 I_S} \right) = - \frac{V_o}{nV_T}$$

$$\therefore \boxed{V_o = -nV_T \ln \left(\frac{V_i}{R_1 I_S} \right)}$$

OP AMP

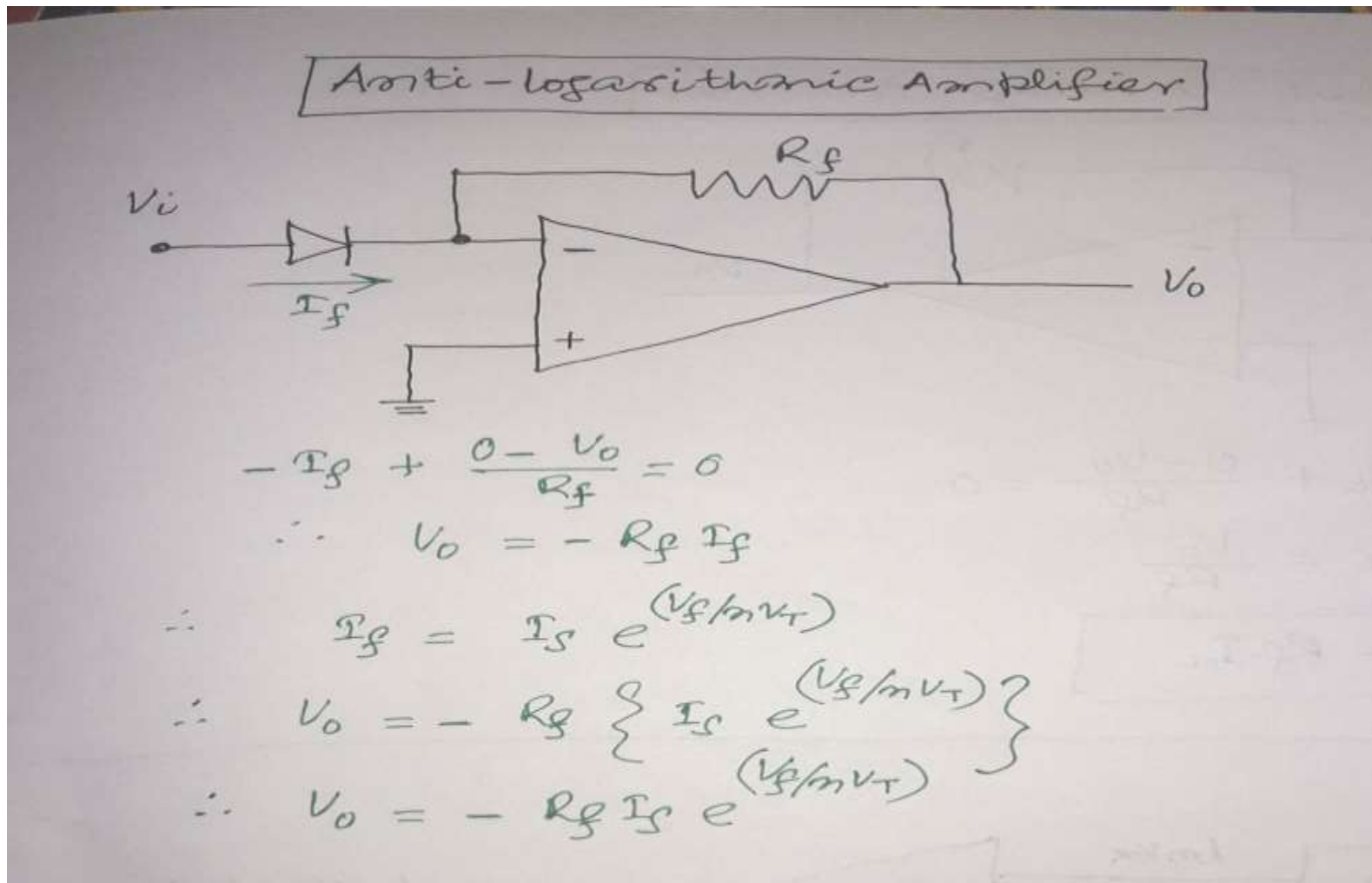

OP AMP


$$\cancel{e^{(V_g/nV_T)}} \quad e^{(V_g/nV_T)} = \frac{V_o}{-R_f I_s}$$

$$V_g/nV_T = \ln\left(\frac{V_o}{-R_f I_s}\right)$$

$$\boxed{\text{antilog}[V_g/nV_T] = -\frac{V_o}{R_f I_s}}$$


Analog Multiplier

OP AMP

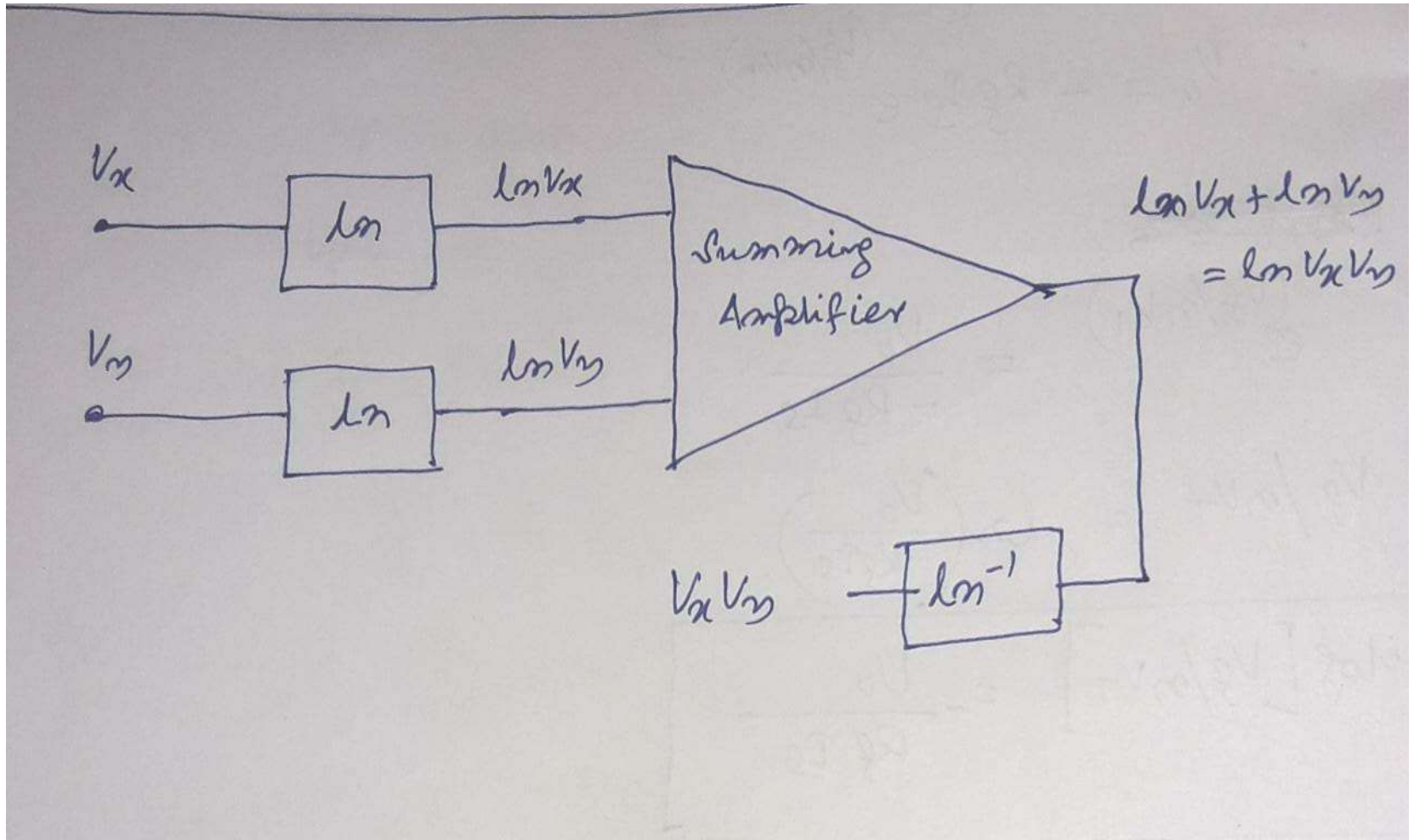

OP AMP

Current to Voltage Converter

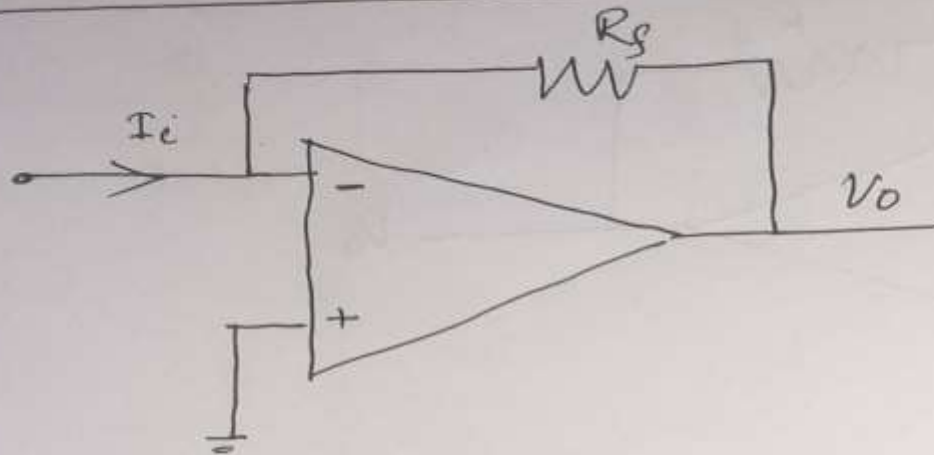

$$-I_i + \frac{0 - V_o}{R_f} = 0$$

$$-I_i = \frac{V_o}{R_f}$$

$$V_o = -R_f I_i$$

OP AMP

Solution to the 2nd Order Differential Equation


$$\frac{d^2V}{dt^2} + k_1 \frac{dV}{dt} + k_2 V = C(t)$$

with initial conditions

$$V(0) = 0 \quad \& \quad \frac{dV}{dt}(0) = 0.$$

$$\frac{d^2V}{dt^2} = -k_1 \frac{dV}{dt} - k_2 V + C(t)$$

OP AMP

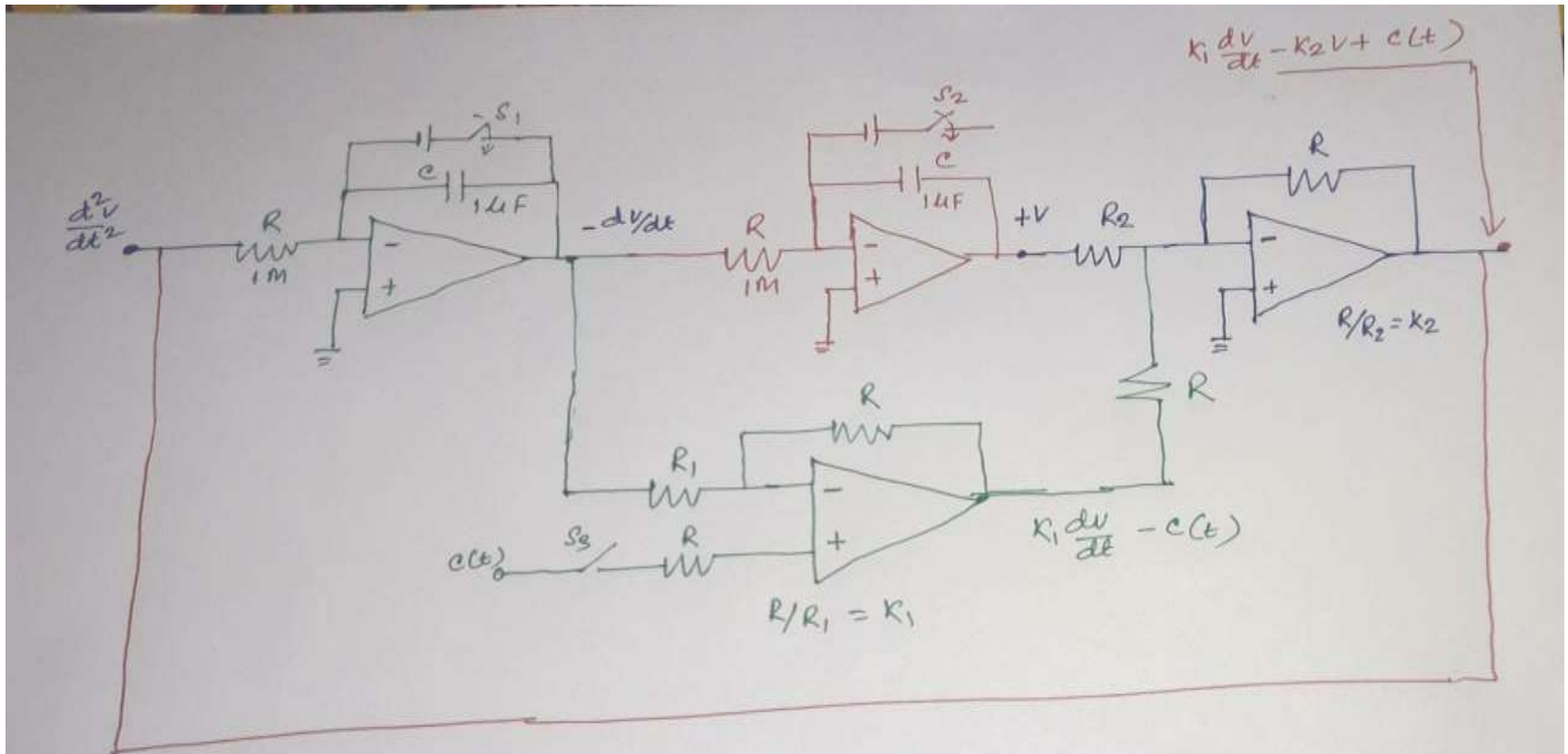

at $t=0$, S_1 & S_2 open, S_3 is closed.