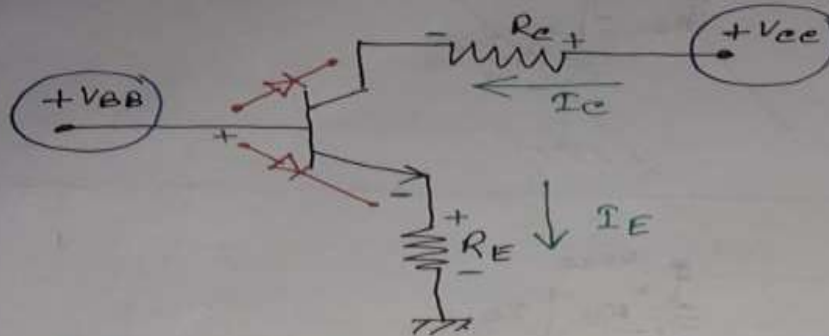


Emitter Bias

Emitter Bias

Emitter Bias

- To create the condition such that BJT can operate in the saturation region.
- To do the provisions for keeping I_{CQ} & V_{CEQ} independent of β .




Outcome — Favourable results are obtained.

Practical limitation


Use two power supplies i.e. V_{BB} & V_{CC} .

Remedy — To get same favourable result by optimizing the use of Power Supply.

1st Attempt

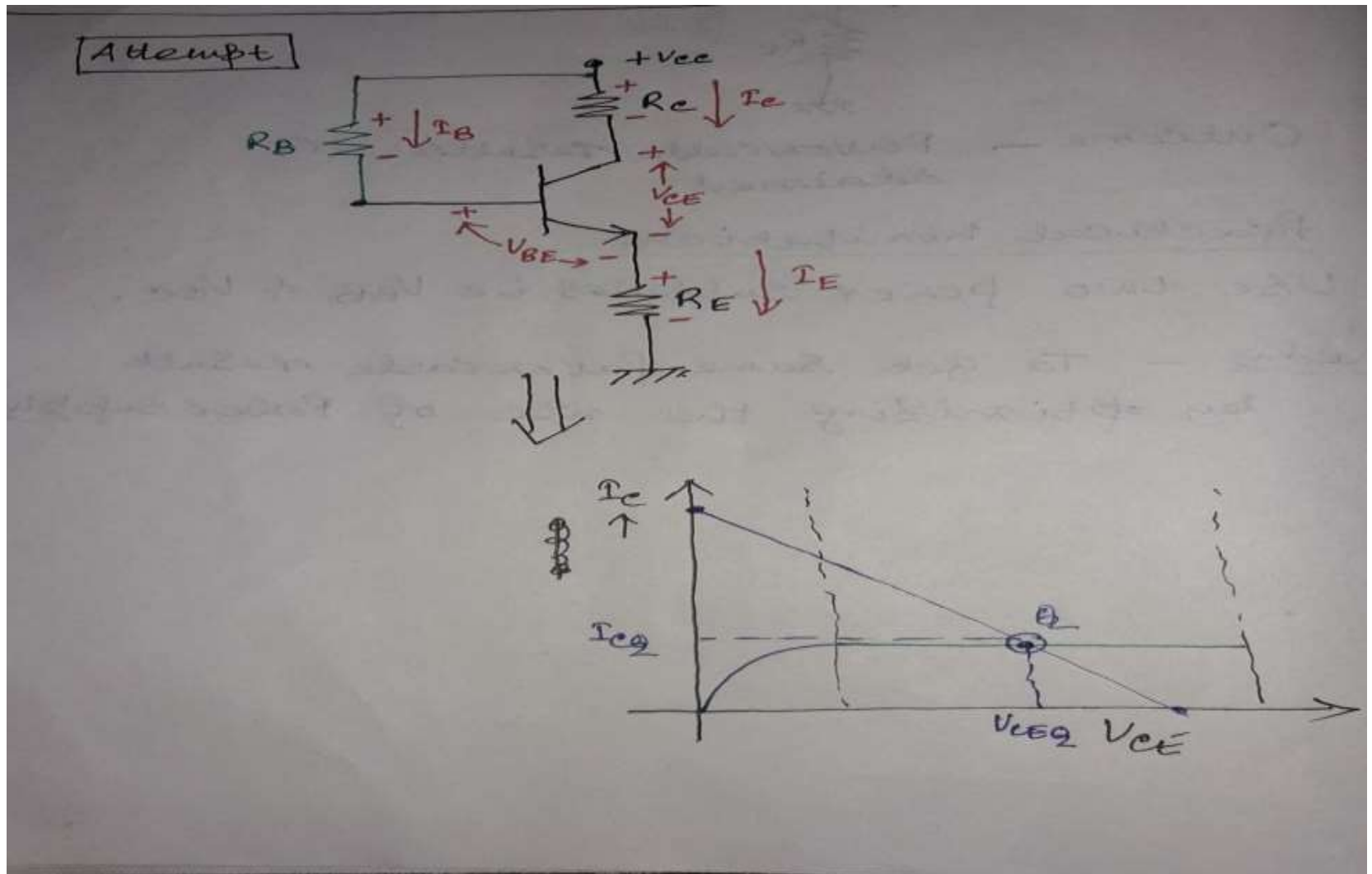

Analysis

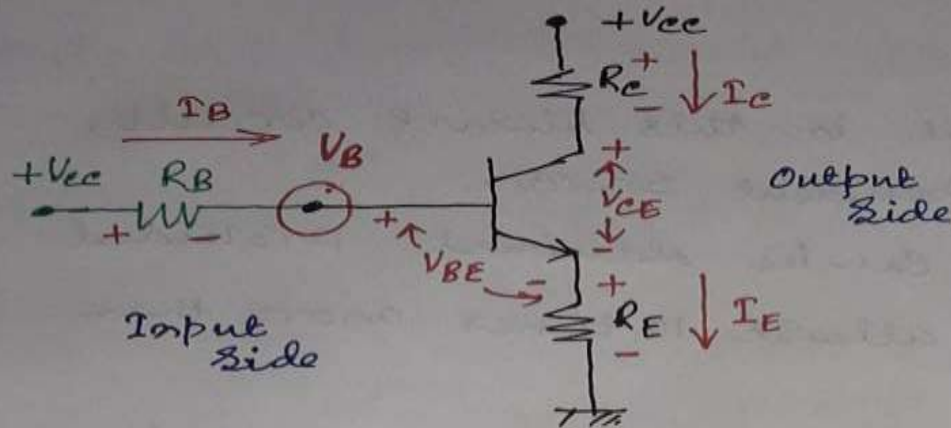

Input Side

$$V_{cc} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\therefore V_{cc} - \frac{I_E}{\beta + 1} R_B - V_{BE} - I_E R_E = 0$$

$$\therefore I_E \left(R_E + \frac{R_B}{\beta + 1} \right) = V_{cc} - V_{BE}$$

$$\therefore I_E = \frac{V_{cc} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} \approx I_C \rightarrow \text{Not independent of } \beta.$$

Analysis

$$\text{If } R_E \gg \frac{R_B}{\beta+1}, I_E \approx \frac{V_{CC} - V_{BE}}{R_E} \approx I_C \quad (\text{Independent of } \beta)$$

Practical Consideration.

$$\text{If } R_E = \frac{10 R_B}{\beta+1}, \quad I_E = \frac{V_{CC} - V_{BE}}{R_E + (1) R_E} = \frac{V_{CC} - V_{BE}}{1.1 R_E} = I_{EQ}$$

[Satisfactory]

Output Side

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\therefore V_{CC} - V_{CE} - I_C (R_C + R_E) = 0 \quad [I_C \approx I_E]$$

$$\begin{aligned} \therefore V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= V_{CC} - \frac{V_{CC} - V_{BE}}{1.1 R_E} \cdot (R_C + R_E) \end{aligned}$$

$$\boxed{V_{CE} = V_{CC} - (0.9) (V_{CC} - V_{BE}) \left(1 + \frac{R_C}{R_E}\right)} = V_{CEQ}$$


Inference

Observations

- <1> In general in this biasing circuit, V_B is a dependent source.
- <2> I_{CQ} , V_{CEQ} can be obtained provided R_E is atleast 10 times more than $R_B/(\beta+1)$.
- <3> If V_B is fixed then Q pt will be obtained. But getting fixed V_B is solely dependent on resistance R_B . Since resistances are available in discrete values, so getting a Q pt. finally is a challenge.
- <4> This biasing ckt. is also known as ~~Self bias~~ Emitter Bias with a base resistance or Fixed Bias.

2nd Attempt

Another Attempt.

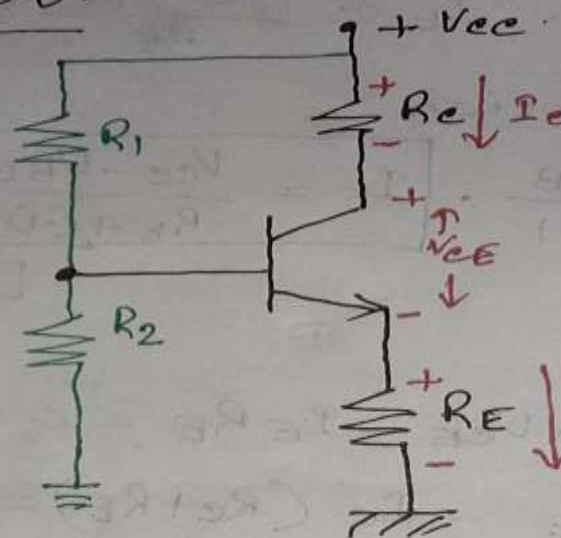


I/p side of this circuit has to be simplified.

$$\left(\frac{R_2}{R_1 + R_2} + 1 \right) (V_{cc} - V_{CE}) (I_C) - V_{CE} = 0$$

Simplification

Simplify this biasing circuit by using Thevenin's Theorem.


① To get Thevenin's Voltage V_{TH}

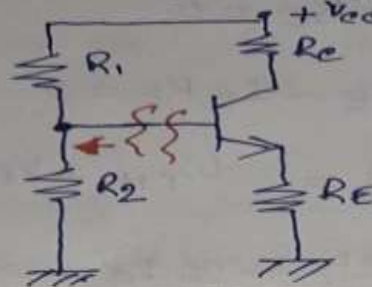

Load is removed, then subsequently voltage has to be measured as indicated.

$$V_{TH} = \frac{V_{CC}}{R_1 + R_2} \cdot R_2$$

② To get Thevenin's Resistance R_{TH}

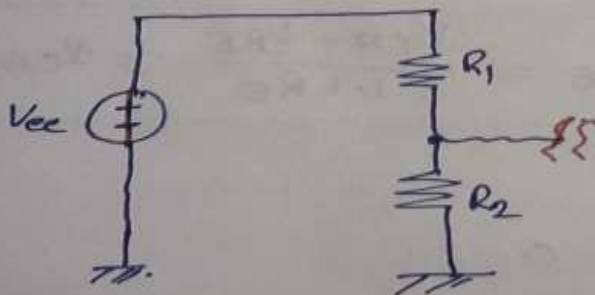


Deactivated the voltage source,

$\leftarrow R_{TH}$

$$R_{TH} = R_1 \parallel R_2$$

Equivalent Circuit

The Equivalent circuit.

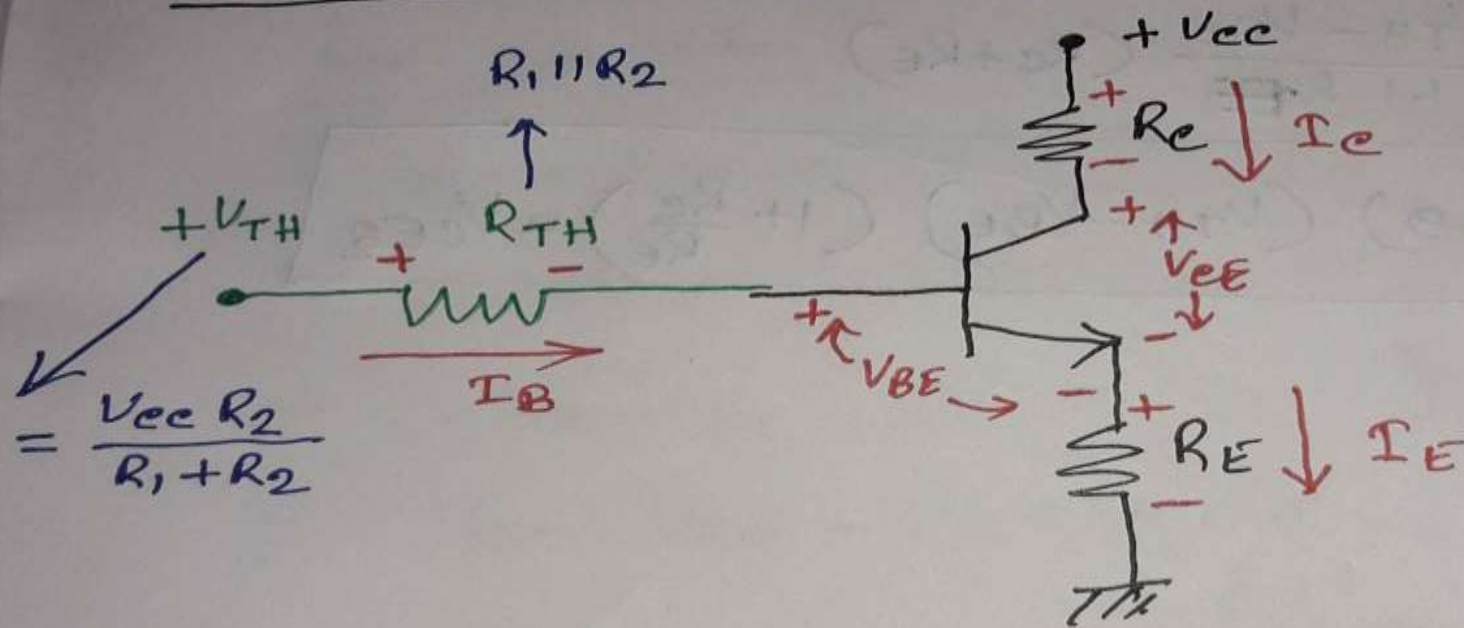

Analysis

Analysis of the circuit.

For I/P side.

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$\therefore V_{TH} - \frac{I_E}{\beta + 1} \cdot R_{TH} - V_{BE} - I_E R_E = 0$$

$$\therefore I_E \left(R_E + \frac{R_{TH}}{\beta + 1} \right) = V_{TH} - V_{BE}$$

$$\therefore I_E = \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{\beta + 1}} \approx I_C \rightarrow \text{not independent of } \beta$$

$$\text{If } R_E \gg \frac{R_{TH}}{\beta + 1}, \text{ then } I_E \approx \frac{V_{TH} - V_{BE}}{R_E}$$

Analysis

Practical Consideration

$$\text{If } R_E = \frac{10 R_{TH}}{\beta + 1}, \text{ then } I_E = \frac{V_{TH} - V_{BE}}{1.1 R_E} \approx I_{CQ}$$

For o/p side

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\therefore V_{CC} - V_{CE} - I_C (R_C + R_E) = 0$$

$$\therefore V_{CE} = V_{CC} - \frac{V_{TH} - V_{BE}}{1.1 R_E} (R_C + R_E)$$

$$V_{CE} = V_{CC} - (0.9) (V_{TH} - V_{BE}) \left(1 + \frac{R_C}{R_E}\right) = V_{CEQ}$$


Observations

Observations

- ① I_{CQ} & V_{CEQ} can be obtained if R_E is at least 10 times more than $\frac{R_{TH}}{\beta+1}$
- ② Getting R_{TH} is much better way because $R_{TH} = R_1 \parallel R_2$ (nonstandard values can be obtained)
- ③ This biasing circuit is known as Voltage Divider Bias circuit.

A new type-analysis

The given circuit is

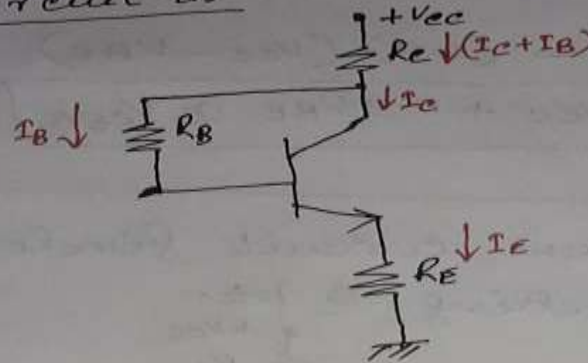

For I/P side

$$V_{cc} - R_C(I_C + I_B) - I_B R_B - I_E R_E - V_{BE} = 0$$

$$\therefore V_{cc} - V_{BE} - R_C I_B - I_B R_B - R_C I_C - I_E R_E = 0$$

$$\therefore V_{cc} - V_{BE} - (R_C + R_B)I_B - I_E(R_C + R_E) = 0$$

$$\therefore V_{cc} - V_{BE} - \frac{(R_C + R_B)I_E}{\beta + 1} - I_E(R_C + R_E) = 0$$

$$\therefore \boxed{I_E = \frac{V_{cc} - V_{BE}}{(R_C + R_E) + \frac{R_C + R_B}{\beta + 1}} \approx I_C}$$

Not independent
of β .

Analysis

$$\text{If } (R_C + R_E) = 10 \cdot \frac{R_C + R_B}{\beta + 1}$$

$$\text{then } \boxed{I_E = \frac{V_{CC} - V_{BE}}{1.1 (R_C + R_E)}} \approx I_{CQ}$$

For o/p side

$$V_{CC} - I_C R_C - I_E R_E - V_{CE} = 0.$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$


$$= V_{CC} - \frac{V_{CC} - V_{BE}}{1.1 (R_C + R_E)} \cdot (R_C + R_E)$$

$$V_{CE} = V_{CC} - (0.9) (V_{CC} - V_{BE})$$

$$\boxed{V_{CE} = 0.1 V_{CC} + 0.9 V_{BE} \approx V_{CEQ}}$$

Assignment

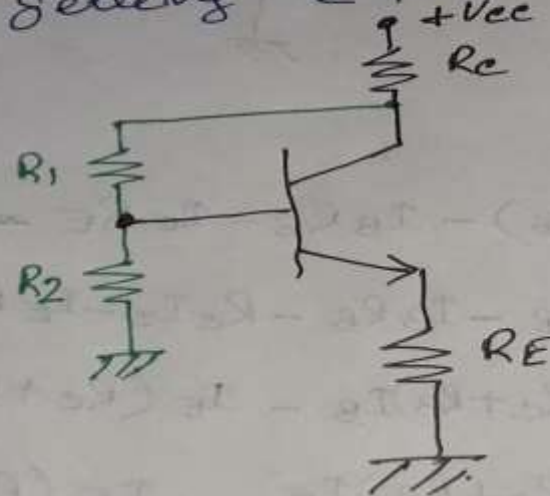For the given circuit find out the
condn. for getting Q pt.



$$V_{BE} = \frac{R_2 + \beta R_E}{R_1 + R_2 + (1 + \beta) R_E} V_{CC}$$