

Transistor Biasing

Transistor Biasing

Ground Rules

(1) Emitter Diode must be forward biased,
Whereas collector Diode must be reverse biased

(2)

NPN

Collector - Maxm. Potential

Base - Intermediate "

Emitter - Minm. "

PNP

Collector - Minm. Potential

Base - Intermediate "


Emitter - Maxm. "

Biassing ??

Biassing circuit should be re-designed to use BJT as ① SWITCH or ② CURRENT SOURCE or ③ AMPLIFIER

SWITCH — ON state or OFF state without having any intermediate state.

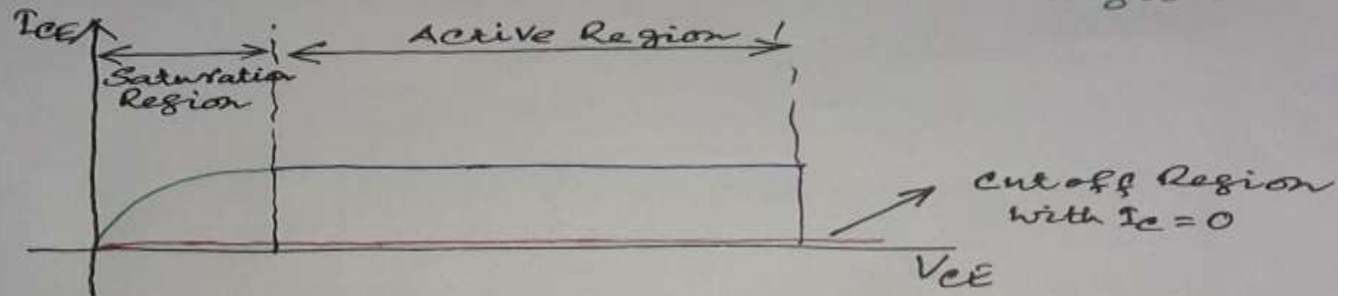[Saturated Transistor] — Saturation Region



CURRENT SOURCE OR AMPLIFIER


Q point should be kept fixed.

Evolution of Transistor Biasing

$$I_C = \beta I_B$$

As due to temperature change, β changes therefore I_C changes. So this equation cannot give a constant Q point.

Basic circuit

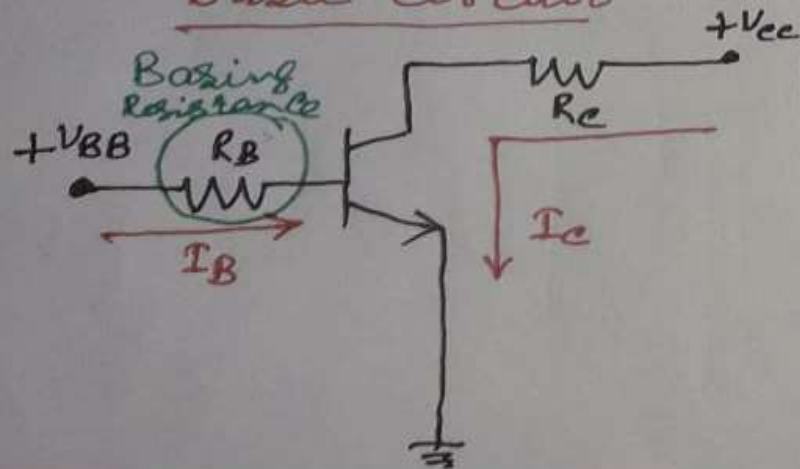


Basic Base Bias ckt.

$$I_C = \alpha I_E \approx \frac{\beta}{\beta + 1} I_E \approx I_E$$

Here change of β due to temperature hardly affects I_C . Possible to keep I_C constant


Basic circuit.

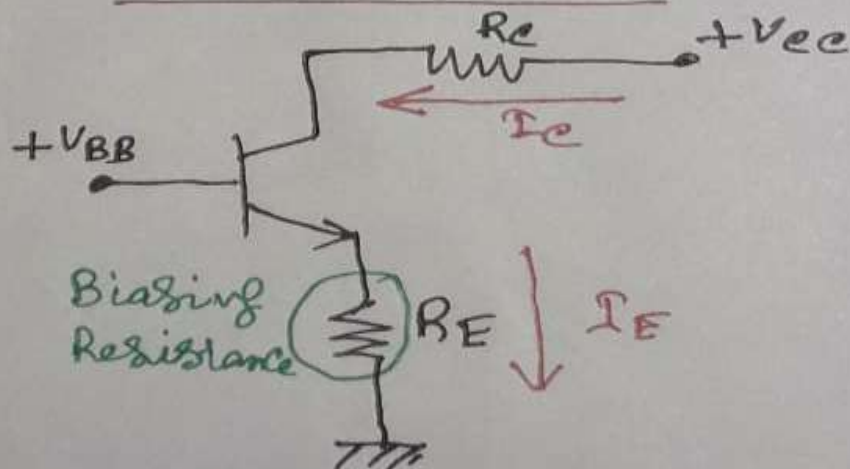

Basic Emitter Bias ckt.

Base Bias

Base Bias

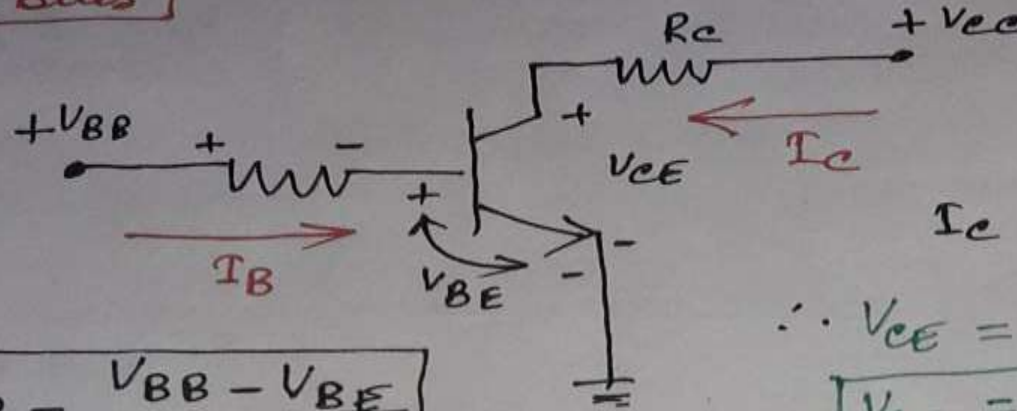

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$\therefore V_{CE} = V_{CC} - I_C \cdot R_C$$

$$V_{CE} = V_{CC} - \beta(V_{BB} - V_{BE}) \left(\frac{R_C}{R_B} \right)$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$


$$I_C = \beta I_B = \beta \cdot \frac{V_{BB} - V_{BE}}{R_B}$$

$$\beta \rightarrow I_C \rightarrow V_{CE}$$

May be used in saturation Region

Emitter Bias

Emitter Bias

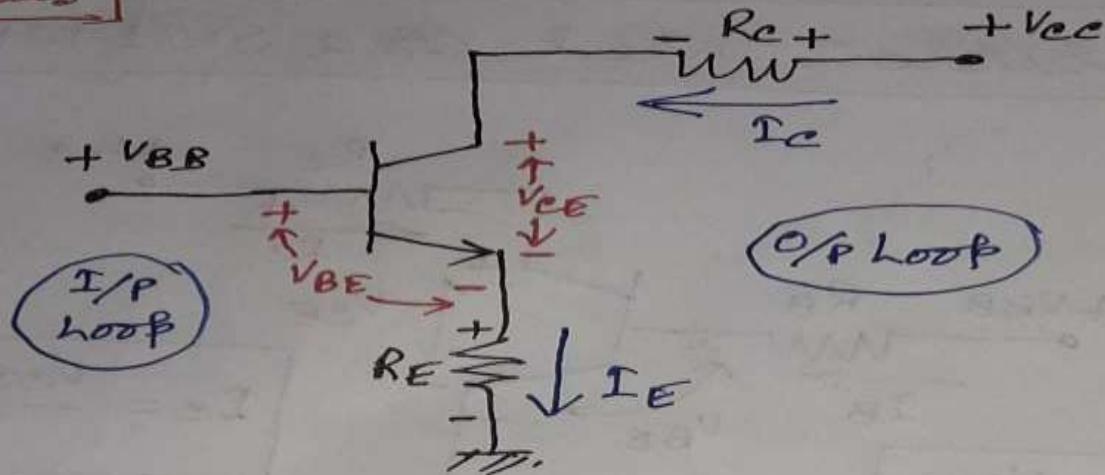

For I/P Loop

$$V_{BB} - V_{BE} - I_E R_E = 0$$

$$\therefore I_E = \frac{V_{BB} - V_{BE}}{R_E} = \frac{\beta + 1}{\beta} I_C$$

$$\boxed{I_E \approx I_C} = \frac{V_{BB} - V_{BE}}{R_E} \rightarrow \text{Independent of } \beta$$

Emitter Bias

For O/P Loop

$$V_{CC} - V_{CE} - I_C R_C - I_E R_E = 0$$

$$\therefore V_{CC} - V_{CE} - I_C (R_C + R_E) = 0$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$


$$= V_{CC} - \frac{V_{BB} - V_{BE}}{R_E} (R_C + R_E)$$

$$\boxed{V_{CE} = V_{CC} - (V_{BB} - V_{BE}) \left(1 + \frac{R_C}{R_E}\right)}$$

→ Independent of β .

If β changes due to temperature, it hardly affects I_C & V_{CE} . So it is possible to use it in the active region where Q pt. needs to be identified.

Transistor used as a SWITCH

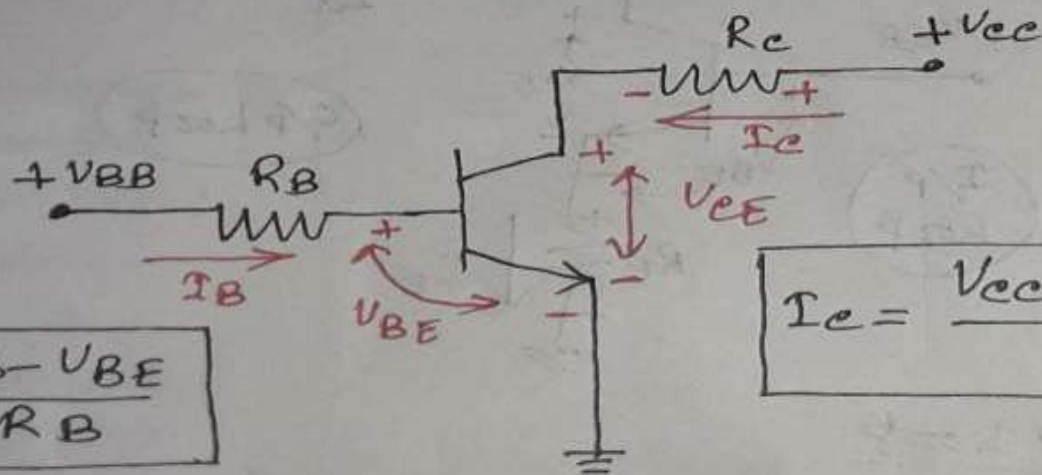


$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_B \approx \frac{V_{BB}}{R_B}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

Let the Transistor acts as a switch & in on condition.

$$V_{CE} = 0$$

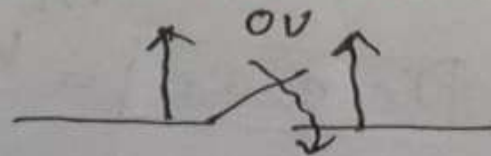

$$I_C = \frac{V_{CC}}{R_C} = \beta I_B = \beta \cdot \frac{V_{BB}}{R_B}$$

So

$$\frac{V_{CC}}{R_C} = \frac{V_{BB}}{R_B / \beta}$$

Transistor Switch

Since, Transistor is now on saturation region, so β value cannot be fixed.

Use 10% Rule & consider $\beta = 10$

So
$$\frac{V_{ce}}{R_c} = \frac{V_{BB}}{R_B/10}$$


$V_{ce} = V_{BB}$

$R_c = \frac{R_B}{10}$

condn for hard saturation

Switch (contd)


As an example

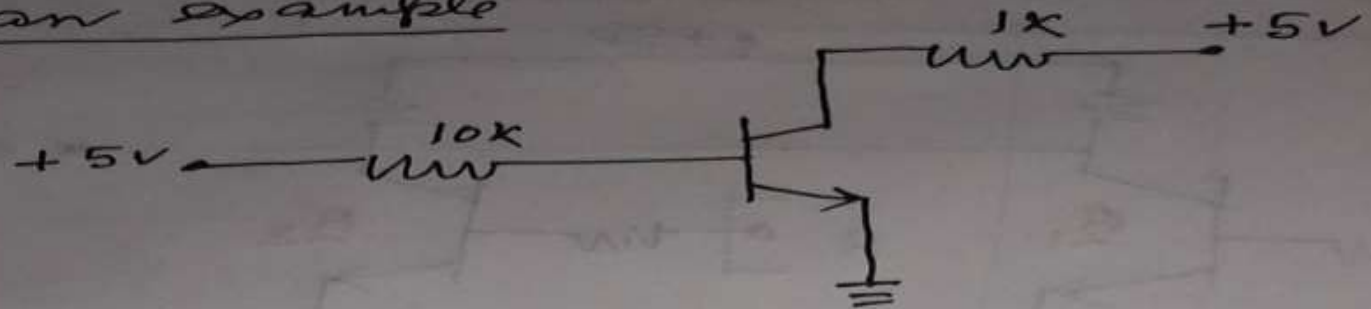


OFF State

$$I_c = 0, \quad V_{ce} = V_{CE} = +5V$$


For the given ckt.

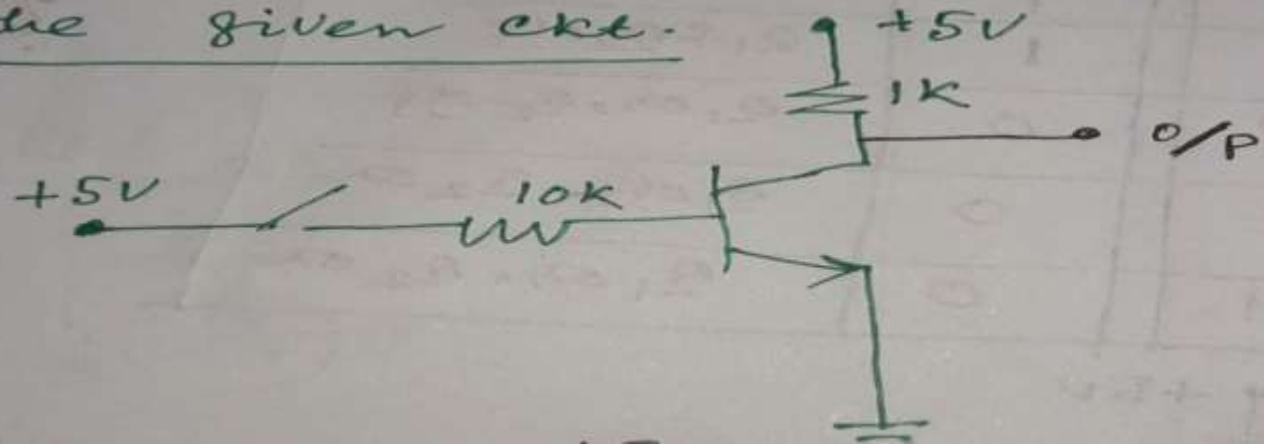

Switch ???

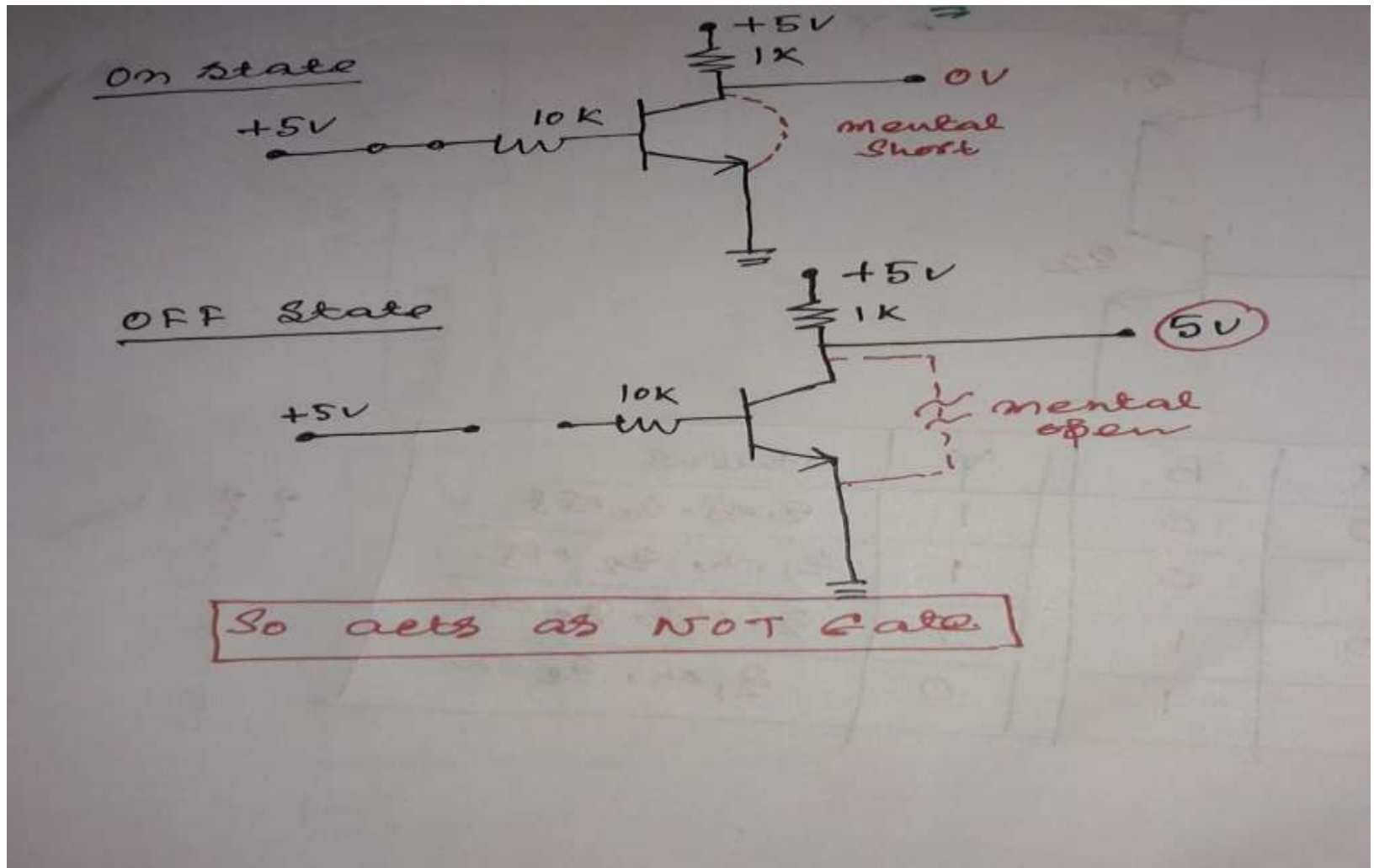


Applications

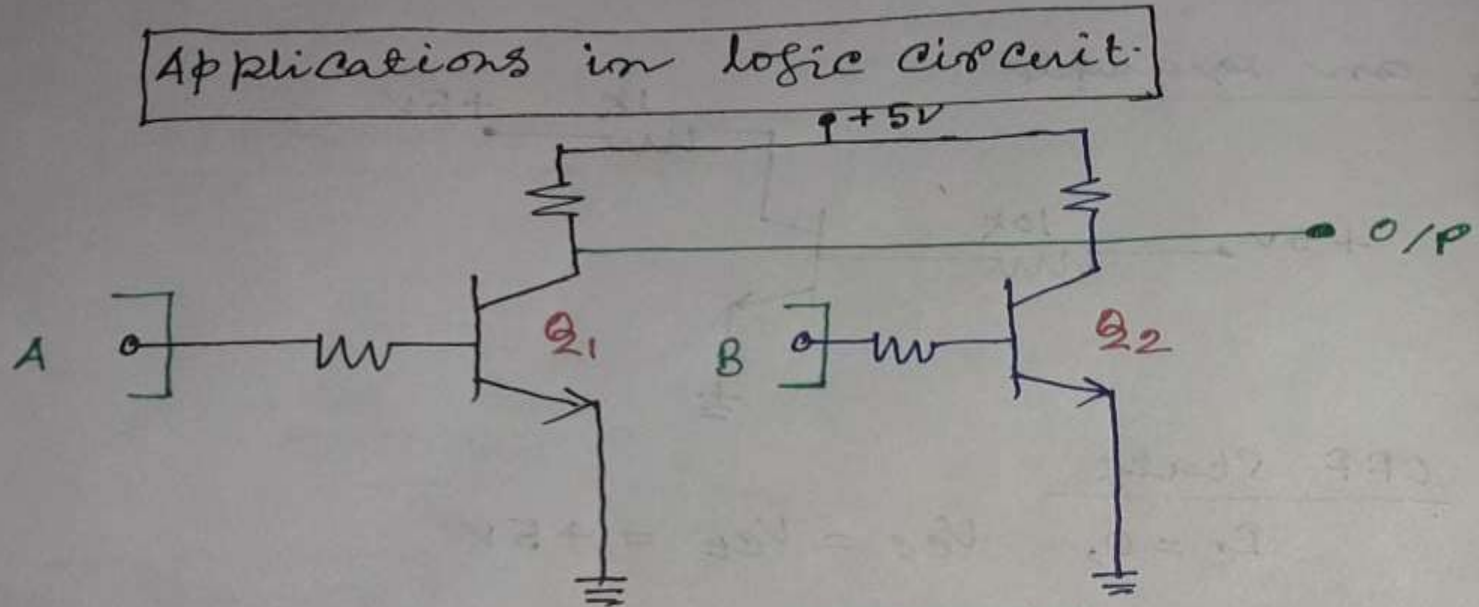

A	B	Y	Status
0	0	1	Q_1, Q_2 off
1	0	0	Q_1 on, Q_2 off
0	1	0	Q_1 off, Q_2 on
1	1	0	Q_1 on, Q_2 on

??

Applications

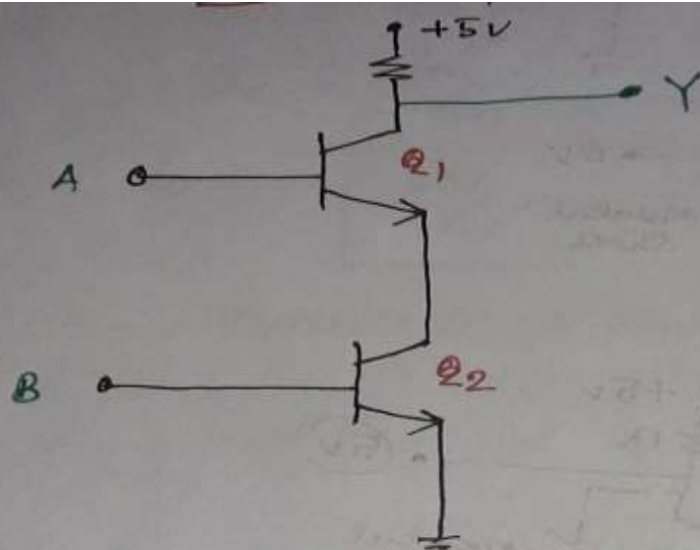

A	B	Y	Status
0	0	1	Q_1 off, Q_2 off
1	0	1	Q_1 on, Q_2 off
0	1	1	Q_1 off, Q_2 on
1	1	0	Q_1 on, Q_2 on

??

Applications = Temperature Control

