

# DIODE VOLTAGE MULTIPLIER

# What is VoltageMultiplier?

A voltage multiplier is an electrical circuit that converts AC electrical power from a lower voltage to a higher DC voltage, typically using a network of capacitors and diodes.

# Types of Voltage Multiplier

---

Depending on the output voltage, multipliers can be of different types


## ❖ Voltage Doublers

- Half wave voltage doubler
- Full wave voltage doubler



## ❖ Voltage Triplers

## ❖ Voltage Quadrupler
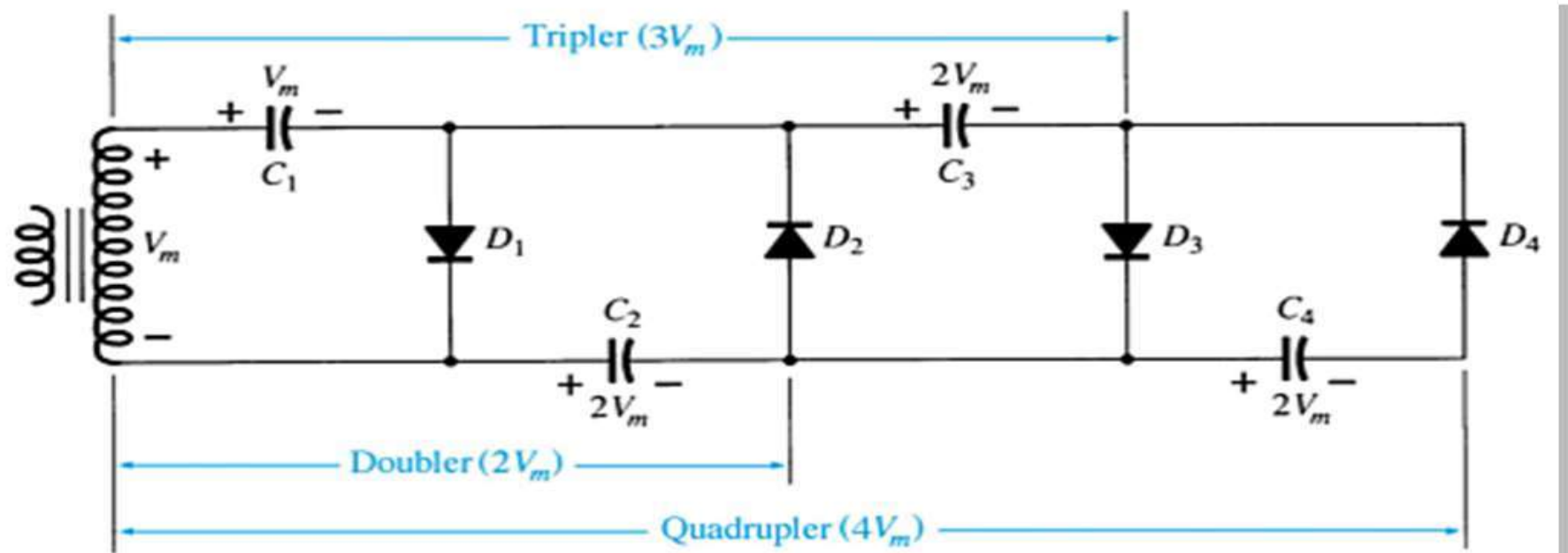
# Voltage Doubler, Tripler and Quadrupler



# Voltage Doubler

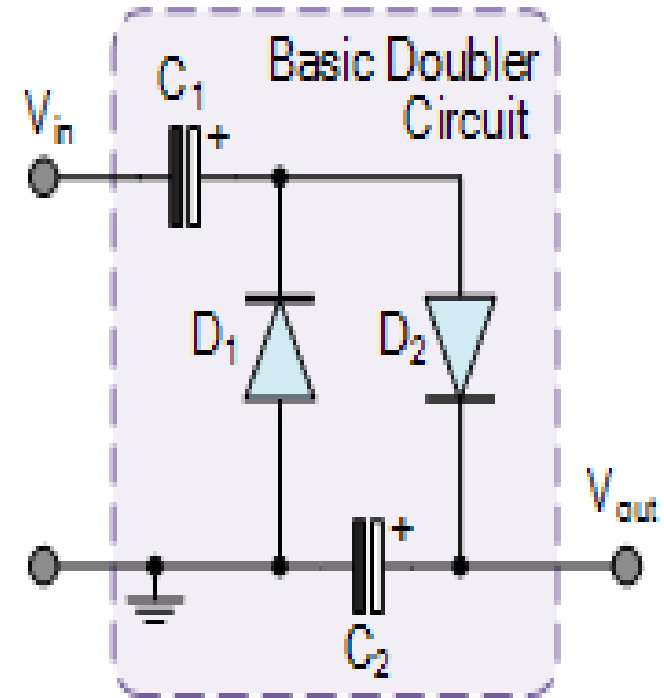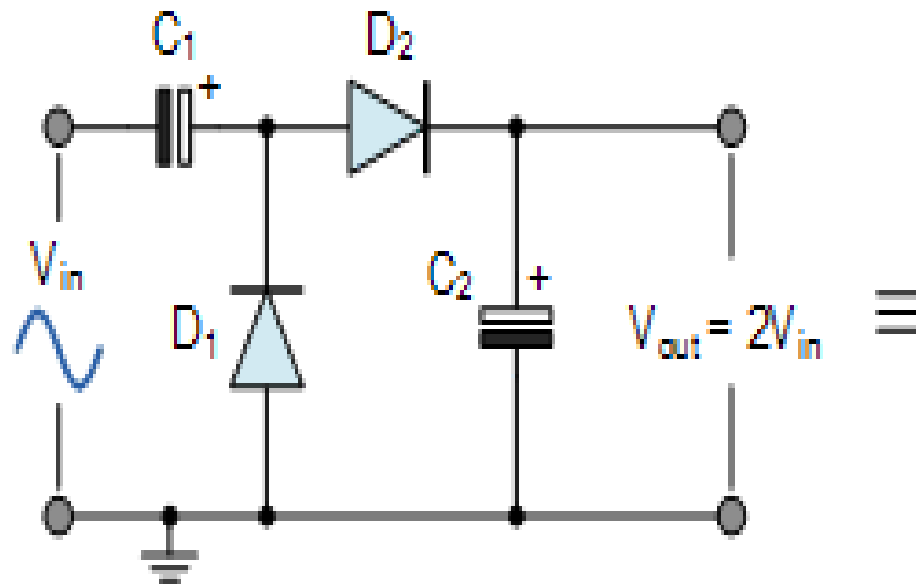

# Half wave Voltage Doubler


- **Positive Half-Cycle**

- o  $D_1$  conducts
- o  $D_2$  is switched off
- o Capacitor  $C_1$  charges to  $V_m$

- **Negative Half-Cycle**

- o  $D_1$  is switched off
- o  $D_2$  conducts
- o Capacitor  $C_2$  charges to  $2V_m$


$$V_{\text{out}} = V_{C2} = 2V_m$$

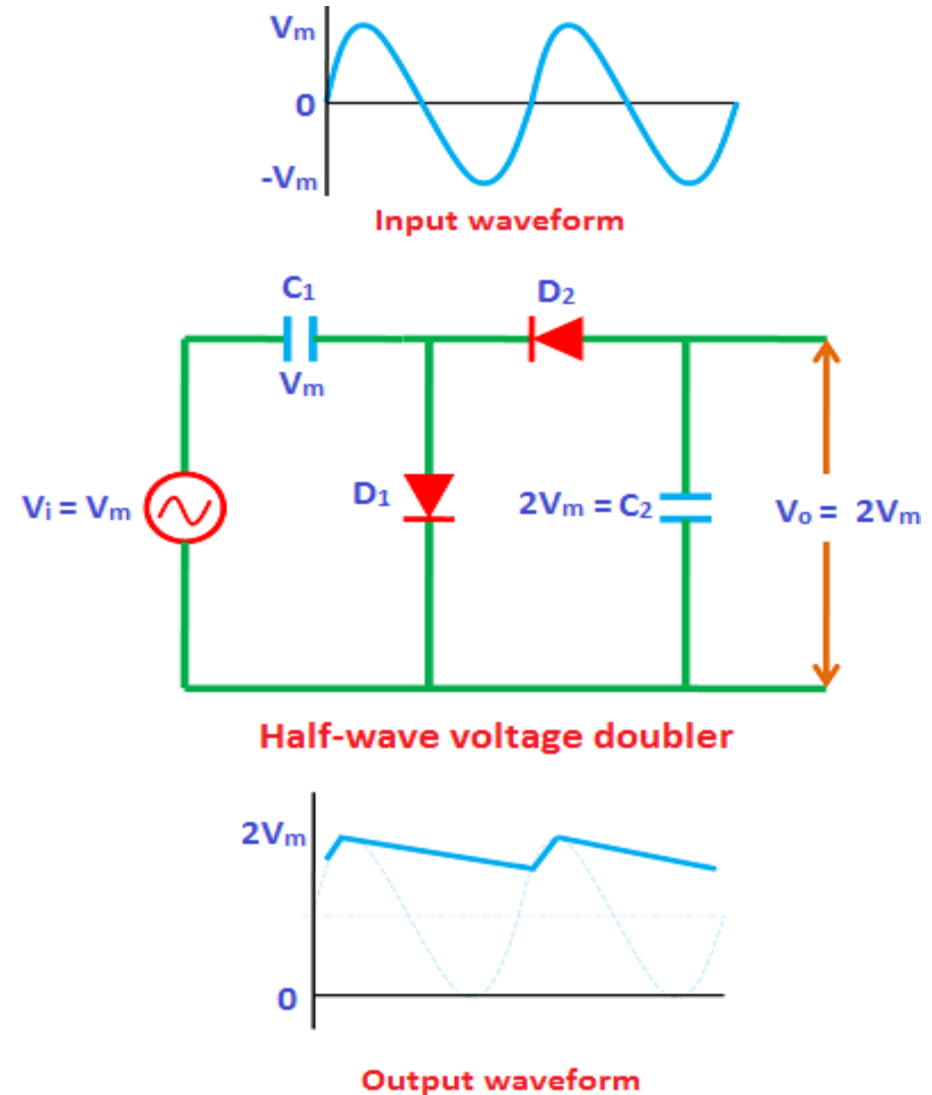
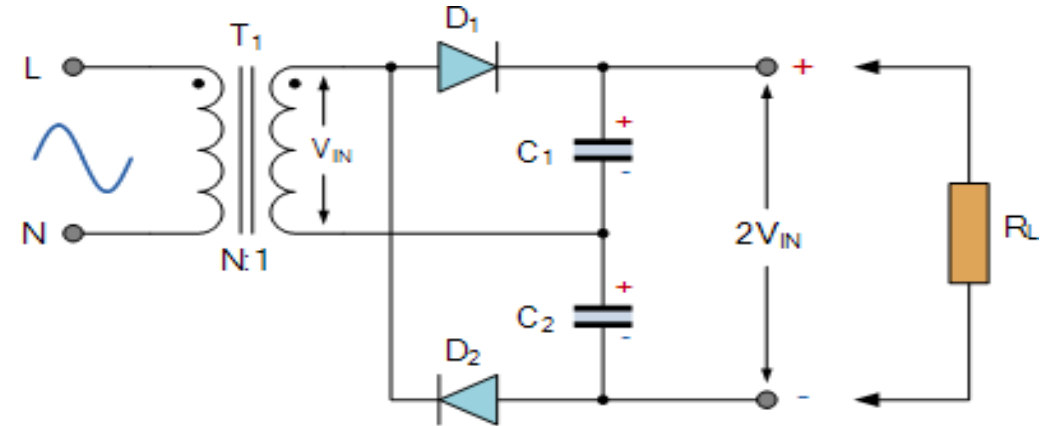
# Full Wave Voltage Multiplier

- **Positive Half-Cycle**



- $D_1$  conducts
- $D_2$  is switched off
- Capacitor  $C_1$  charges to  $V_m$




- **Negative Half-Cycle**

- $D_1$  is switched off
- $D_2$  conducts
- Capacitor  $C_2$  charges to  $V_m$

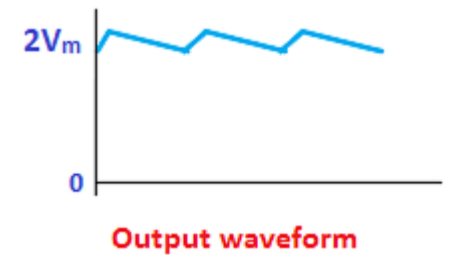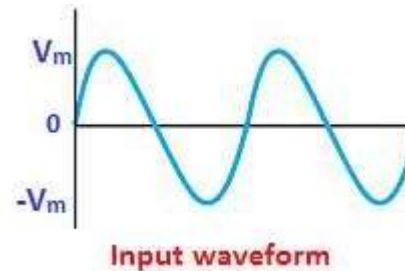
$$V_{\text{out}} = V_{C1} + V_{C2} = 2V_m$$



# Voltage Tripler

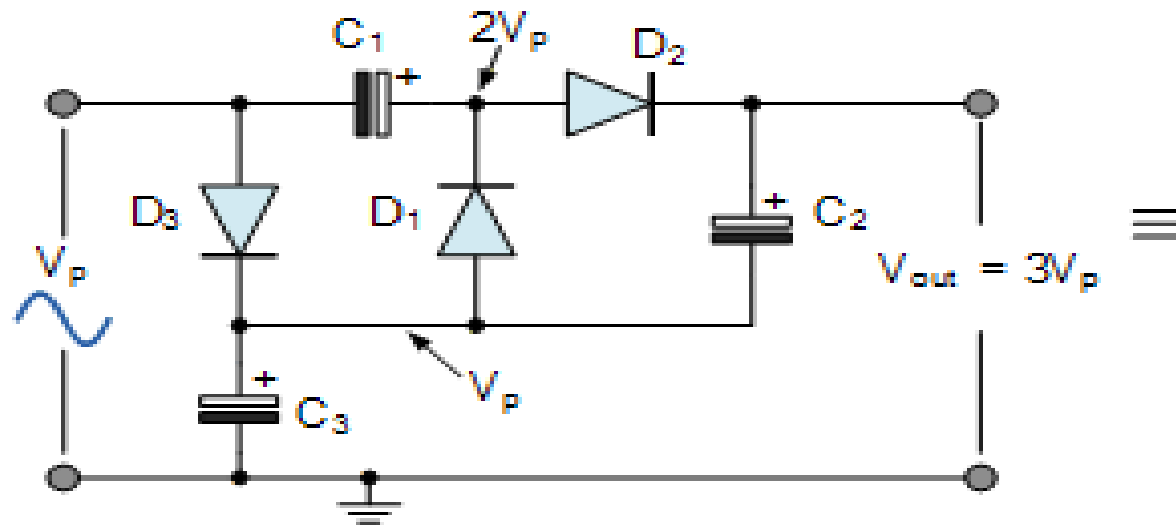

$\equiv$

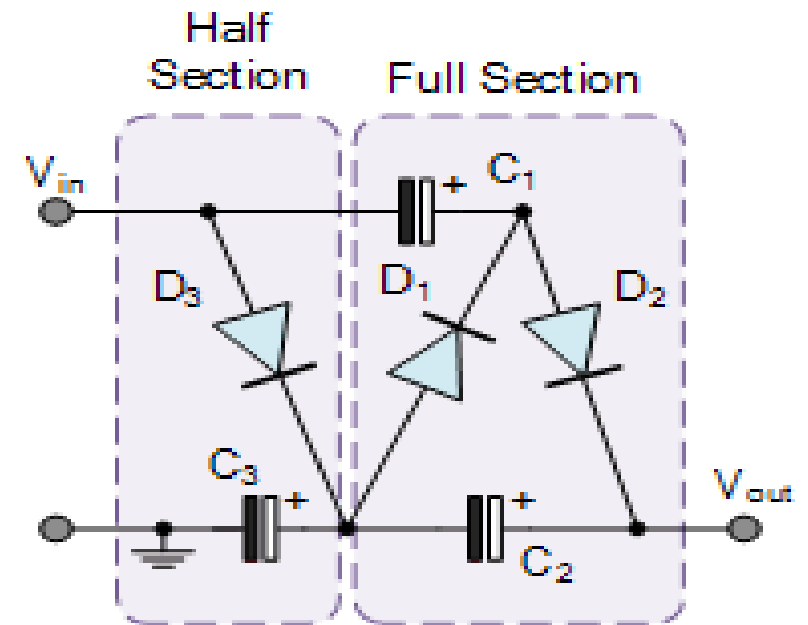



# Voltage Tripler

## **During first positive half cycle:**


- Diode  $D_1$  is forward biased whereas diodes  $D_2$  and  $D_3$  are reverse biased.
- Current will flow to the capacitor  $C_1$  and charges it to  $V_m$

## **During negative half cycle:**



- Diode  $D_2$  is forward biased whereas diodes  $D_1$  and  $D_3$  are reverse biased.
- Current will flow to the capacitor  $C_2$  and charges it. The capacitor  $C_2$  is charged to twice the peak voltage of the input signal ( $2V_m$ ). This is because the charge ( $V_m$ ) stored in the capacitor  $C_1$  is discharged during the negative half cycle.
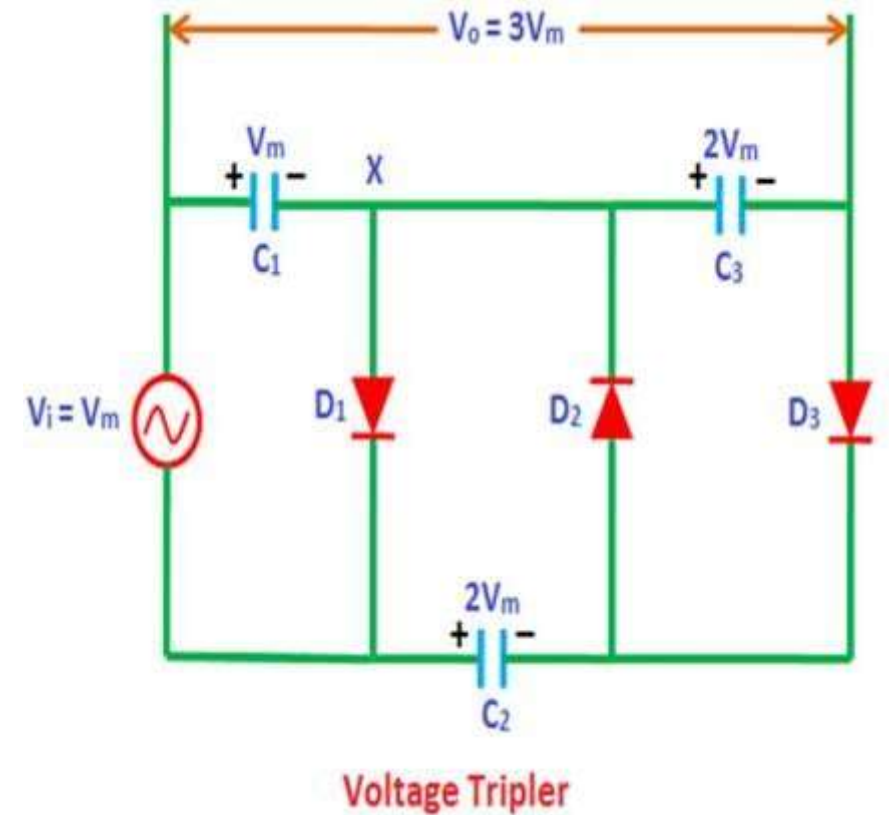
### During second positive half cycle:

- Diode  $D_3$  is forward biased whereas diodes  $D_1$  and  $D_2$  are reverse biased.
- As a result, the voltage ( $2V_m$ ) across capacitor  $C_2$  is discharged. This charge will flow to the capacitor  $C_3$  and charges it to the same voltage  $2V_m$ .
- The capacitors  $C_1$  and  $C_3$  are in series and the output voltage is taken across the two series connected capacitors  $C_1$  and  $C_3$ .
- The voltage across capacitor  $C_1$  is  $V_m$  and capacitor  $C_3$  is  $2V_m$ . So the total output voltage is equal to the sum of capacitor  $C_1$  voltage and capacitor  $C_3$  voltage  
i.e.  $C_1 + C_3 = V_m + 2V_m = 3V_m$ .




# Voltage Quadrupler

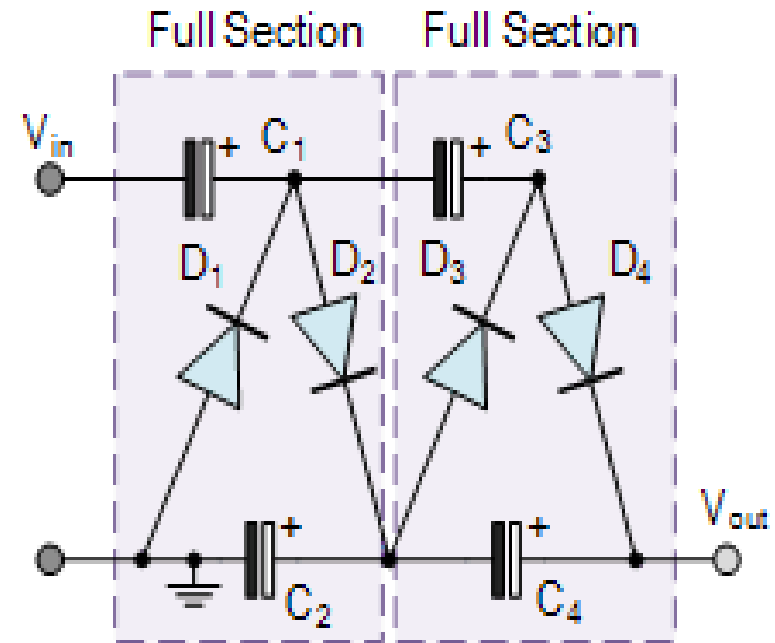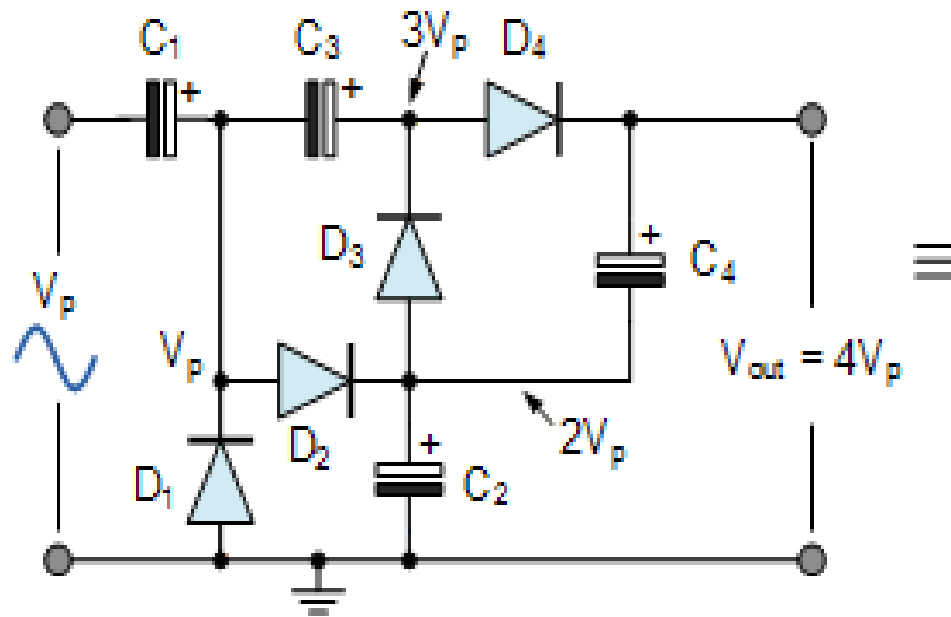

# Voltage Quadrupler
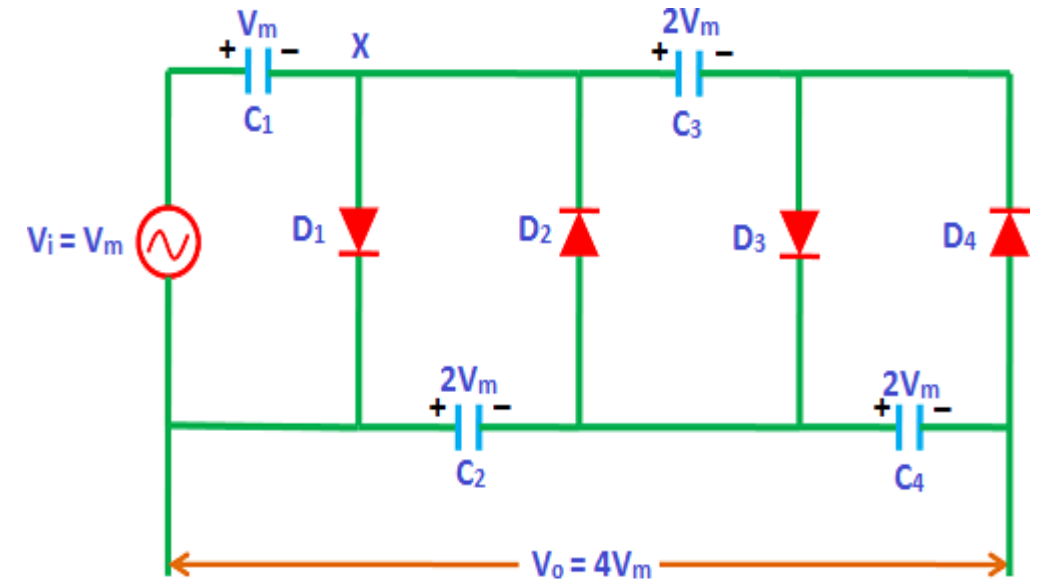
## During first positive half cycle:

- Diode  $D_1$  is forward biased whereas diodes  $D_2$ ,  $D_3$  and  $D_4$  are reverse biased.
- Current will flow to the capacitor  $C_1$  and charges it to the input voltage I.e.  $V_m$ .



Voltage Quadrupler

## During first negative half cycle:

- Diode  $D_2$  is forward biased and diodes  $D_1$ ,  $D_3$  and  $D_4$  are reverse biased.
- Current will flow to the capacitor  $C_2$  and charges it. The capacitor  $C_2$  is charged to twice the peak voltage of the input signal ( $2V_m$ ). This is because the charge ( $V_m$ ) stored in the capacitor  $C_1$  is discharged during the negative half cycle.
- Therefore, the capacitor  $C_1$  voltage ( $V_m$ ) and the input voltage ( $V_m$ ) is added to the capacitor  $C_2$  I.e. Capacitor voltage + input voltage =  $V_m + V_m = 2V_m$ . As a result, the capacitor  $C_2$  charges to  $2V_m$ .

### **During second positive half cycle:**

- Diode  $D_3$  is forward biased and diodes  $D_1$ ,  $D_2$  and  $D_4$  are reverse biased.
- As a result, the voltage ( $2V_m$ ) across capacitor  $C_2$  is discharged. This charge will flow to the capacitor  $C_3$  and charges it to the same voltage  $2V_m$ .

### **During second negative half cycle:**

- Diodes  $D_2$  and  $D_4$  are forward biased whereas diodes  $D_1$  and  $D_3$  are reverse biased.
- As a result, the charge ( $2V_m$ ) stored in the capacitor  $C_3$  is discharged. This charge will flow to the capacitor  $C_4$  and charges it to the same voltage ( $2V_m$ ).
- The capacitors  $C_2$  and  $C_4$  are in series and the output voltage is taken across the two series connected capacitors  $C_2$  and  $C_4$ .
- The voltage across capacitor  $C_2$  is  $2V_m$  and capacitor  $C_4$  is  $2V_m$ . So the total output voltage is equal to the sum of capacitor  $C_2$  voltage and capacitor  $C_4$  voltage I.e.  $C_2 + C_4 = 2V_m + 2V_m = 4V_m$ .

# PracticleApplications

---

Voltage multipliers are used in:

- Cathode Ray Tubes (CRTs)
- Laser systems
- X-ray systems
- LCD backlighting
- Power supplies
- Oscilloscopes
- Particle accelerators
- Copy machines

# Disadvantages

- ❖ Need Protection Circuit
- ❖ Low Current
- ❖ Delay Greater than transformer
- ❖ Cost depend upon Capacitors

# Advantages

- ❖ Low Cost
- ❖ Produce High Voltage
- ❖ Alternative of Transformer