

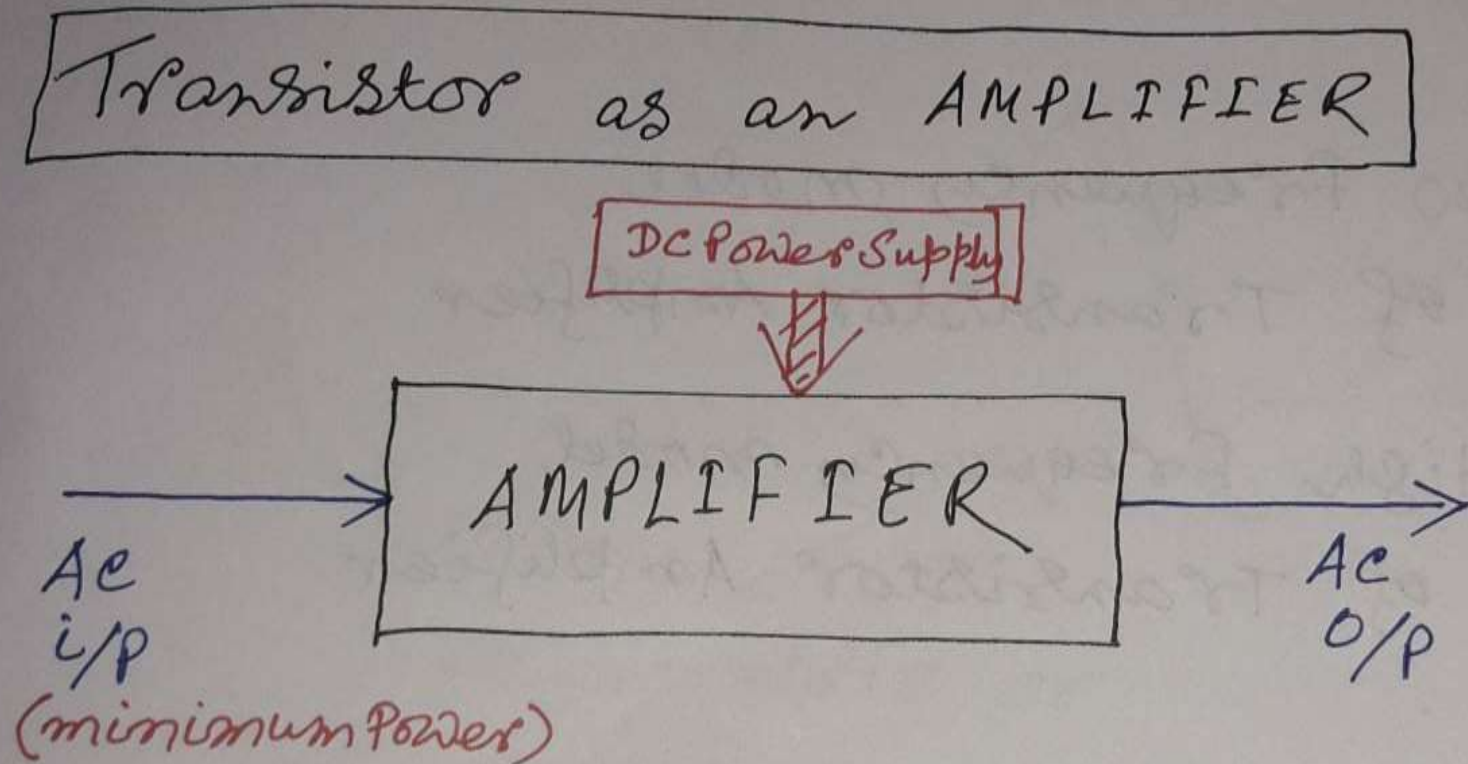


Transistor Amplifier

Transistor Amplifier

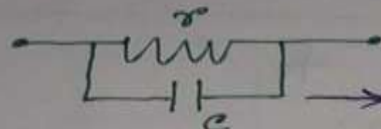

Transistor Amplifier

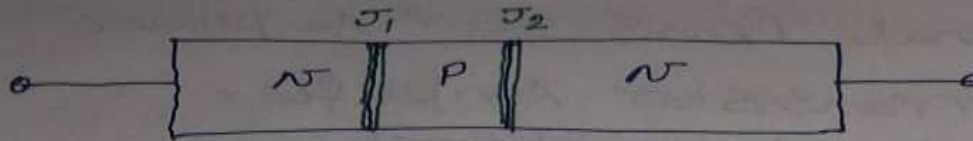

Junction Capacitance

$$X_c = \frac{1}{2\pi f c}$$

At low frequency
 $X_c \rightarrow \text{high}$
(so may be neglected)

At high frequency
 $X_c \rightarrow \text{low}$
(cannot be neglected)


Transistor Amplifier

- Low Frequency model of Transistor Amplifier
- High Frequency model of Transistor Amplifier


Another Consideration.

- Small Signal Transistor Amplifier
- Power Transistor Amplifier
[large signal amplifiers]

Transistor Amplifier

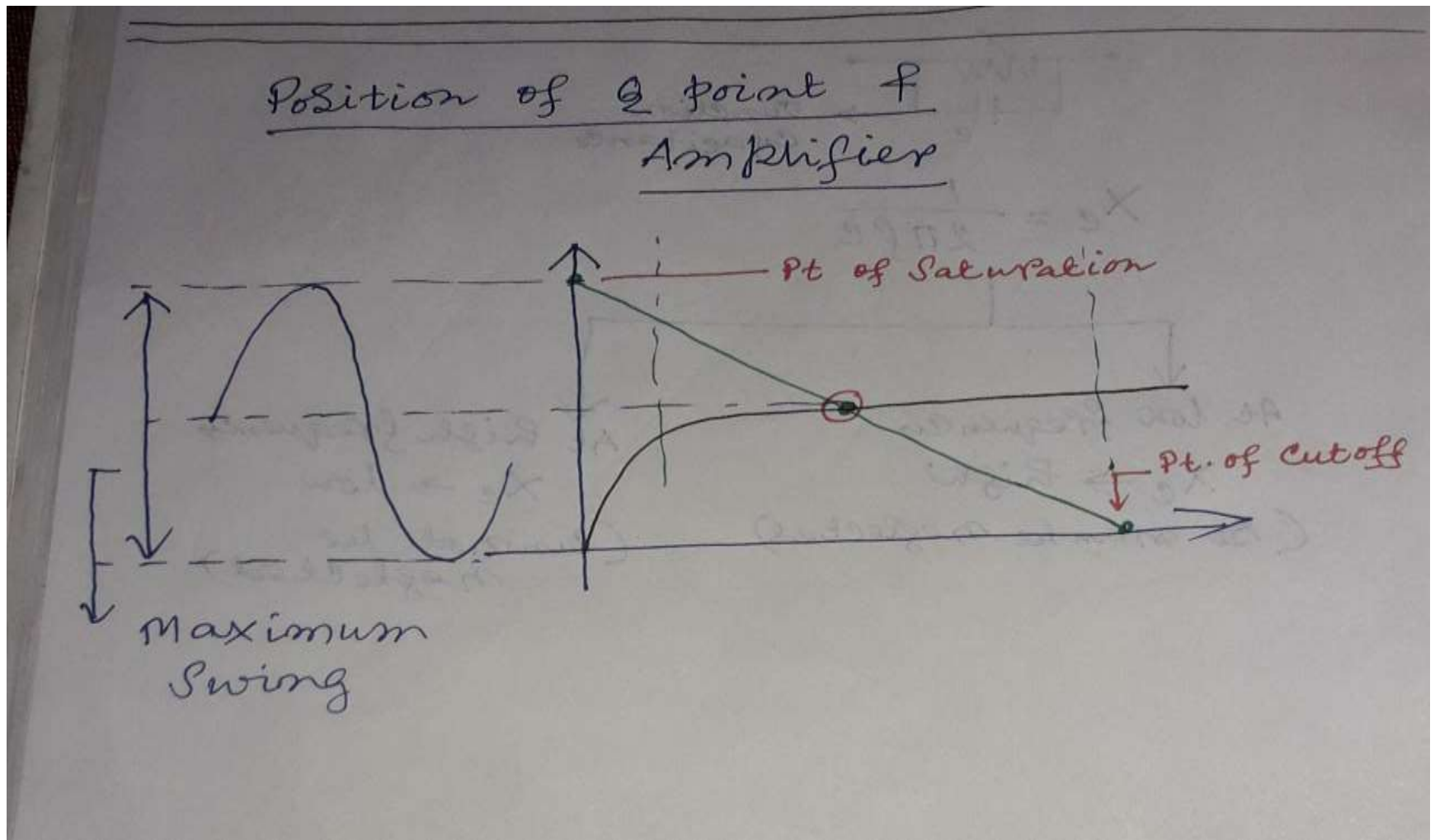


Transistor Amplifier

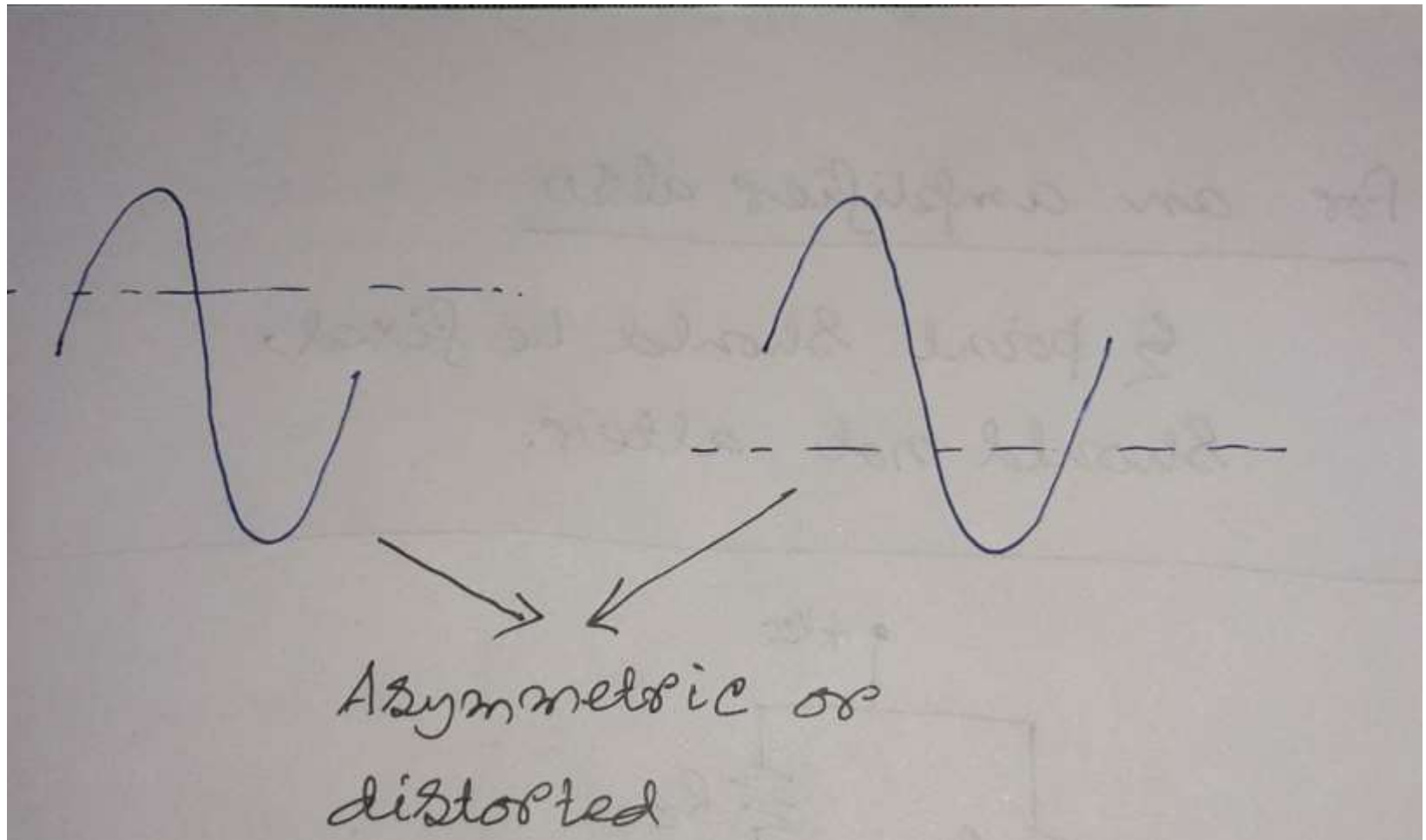


Transistor Amplifier

To get an Symmetrical.

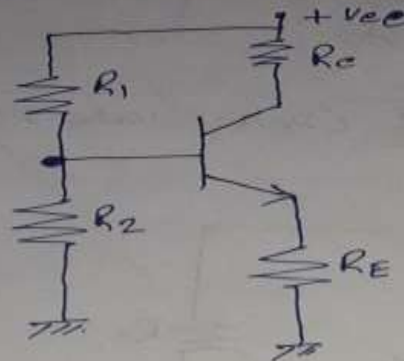The load line should pass through the middle.



Condn for maxm.
Symmetrical
Swing.

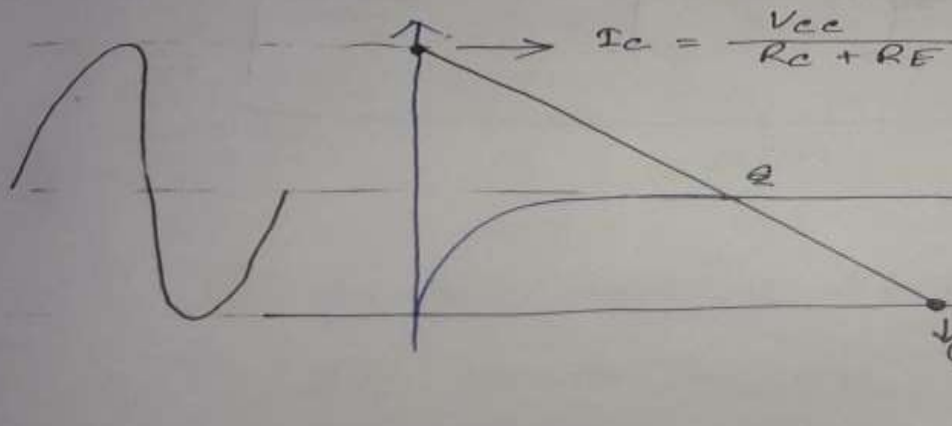


$$I_{CQ} = \frac{V_{CC}}{2(R_c + R_E)}$$
$$V_{CEQ} = \frac{V_{CC}}{2}$$

Transistor Amplifier


For an amplifier also

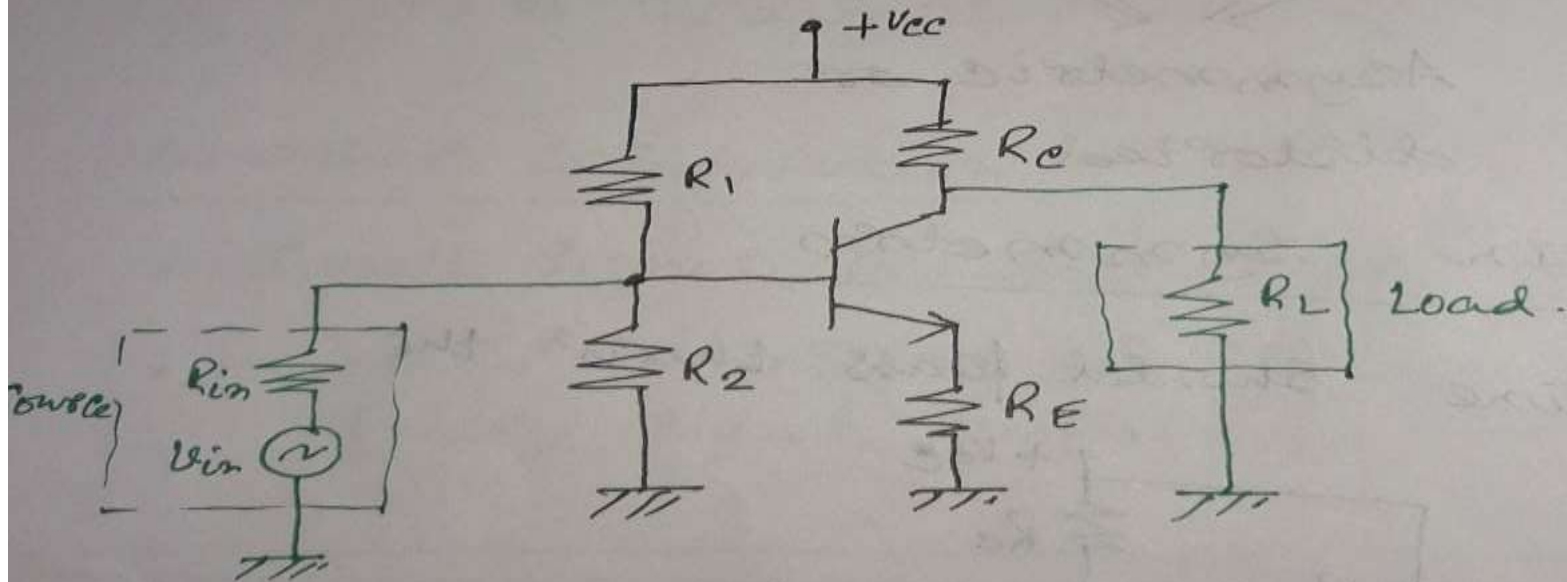Q point should be fixed,
should not alter.



Transistor Amplifier


DC Equivalent circuit.

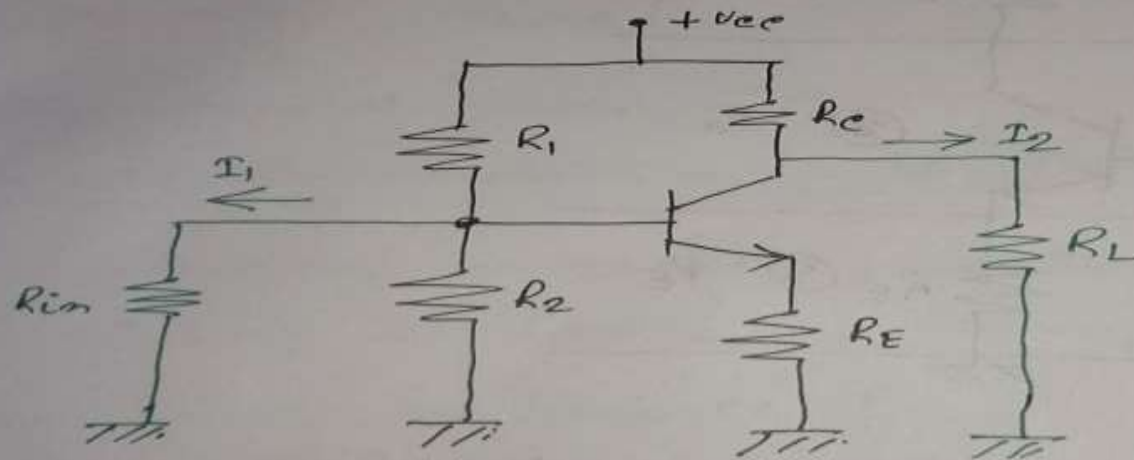


Additional currents (I_1, I_2) will cause the change of posn. of Q point.

By some means the posn. of the Q point should be as it is i.e. we have to stop the flow of I_1 & I_2 .

Transistor Amplifier

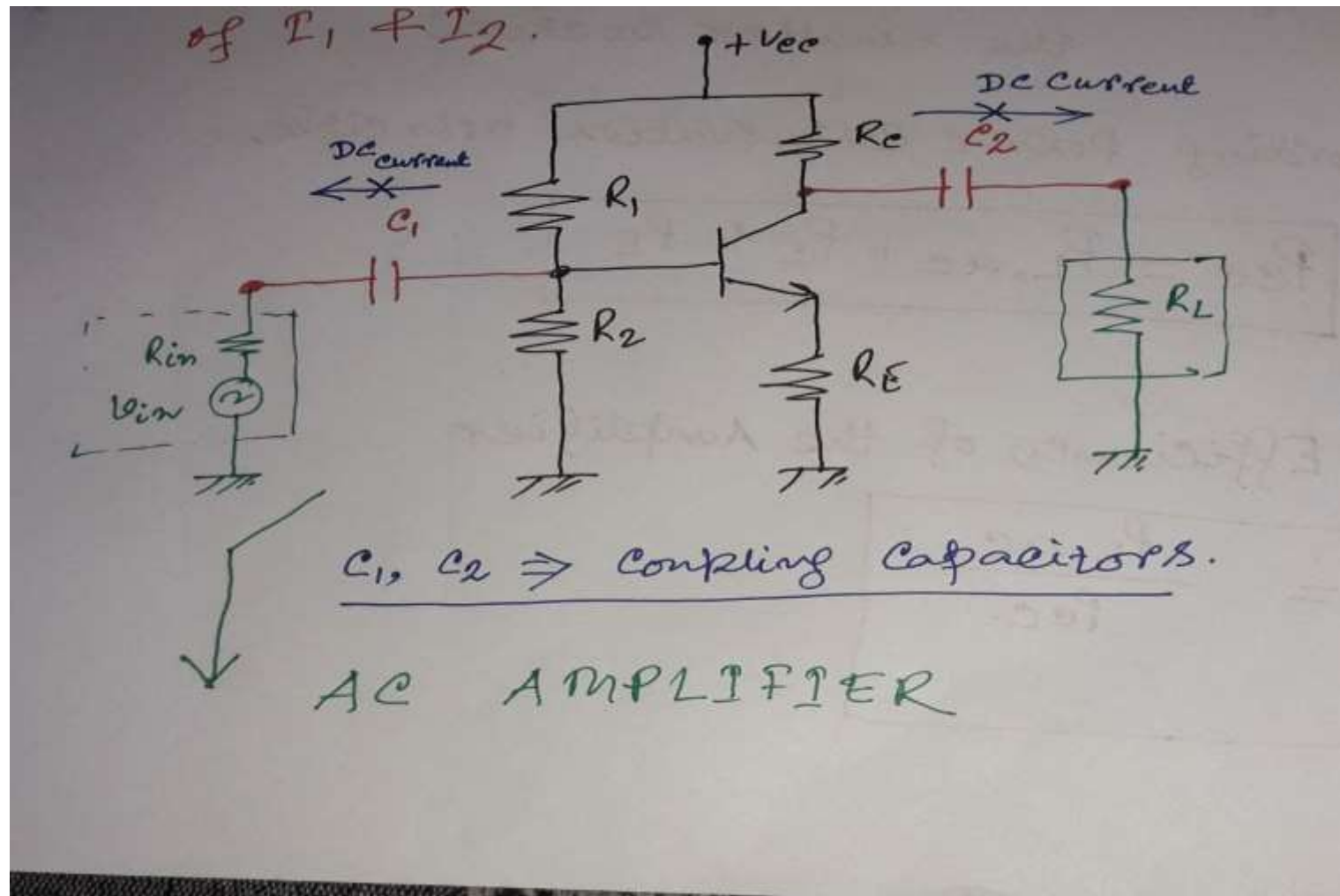

Transistor Amplifier

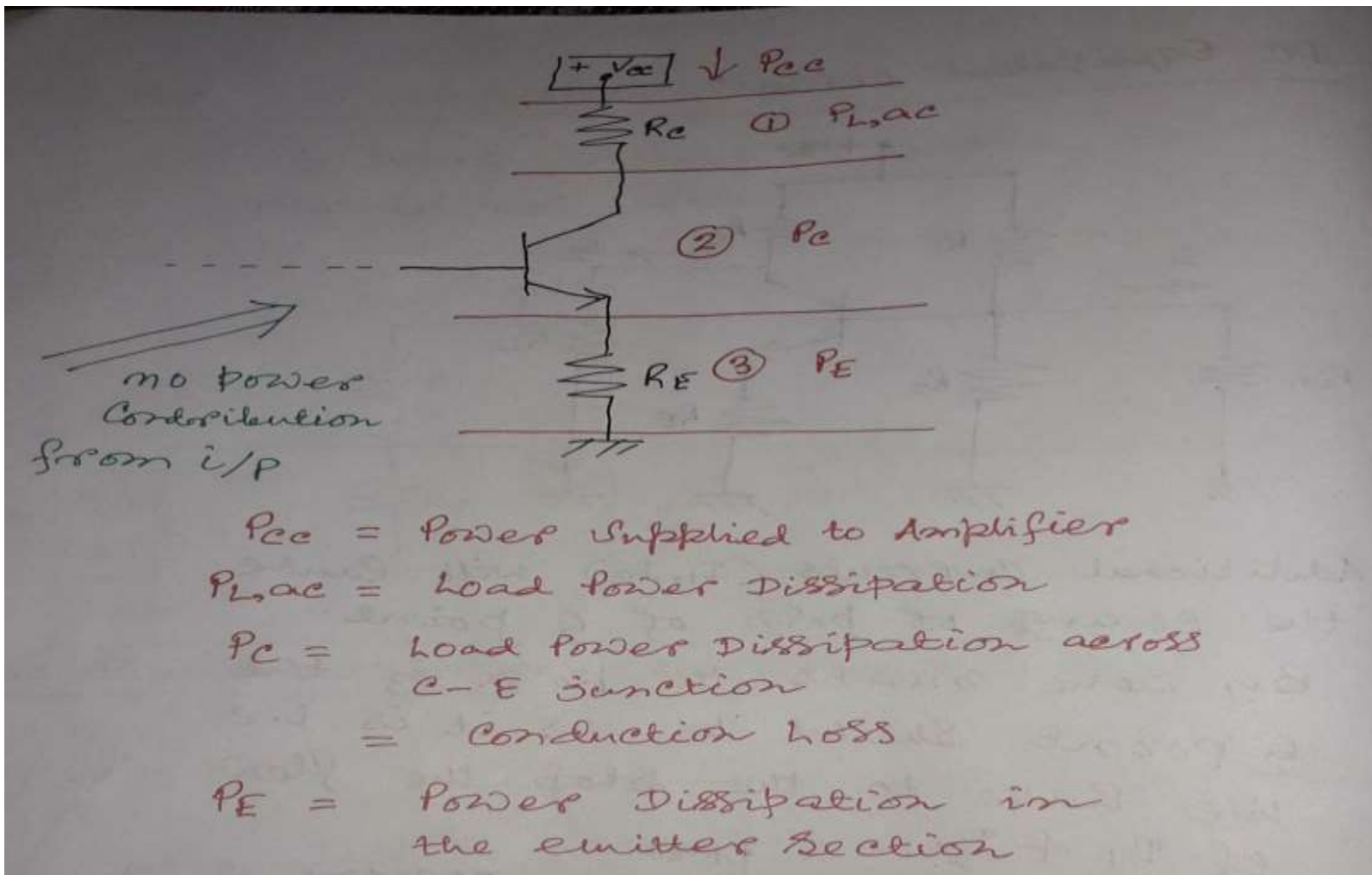

Transistor Amplifier

According to power conservation principle,

$$P_{cc} = P_{L,ac} + P_c + P_E$$

η = Efficiency of the Amplifier

$$\eta = \frac{P_{L,ac}}{P_{cc}}$$

Transistor Amplifier

As P_{CC} is fixed, $[P_{CC} = V_{CC} \cdot I_{CQ}]$

So $\eta \uparrow$ $P_{L,ac} \uparrow$

We cannot alter P_C .

So recommendation is to reduce P_E .

But, according to stability factor analysis,


R_E should be large $[S_V = -\frac{1}{R_E}]$

then how to reduce P_E

\downarrow
ac power dissipation
in the emitter section.

Transistor Amplifier


Solution.

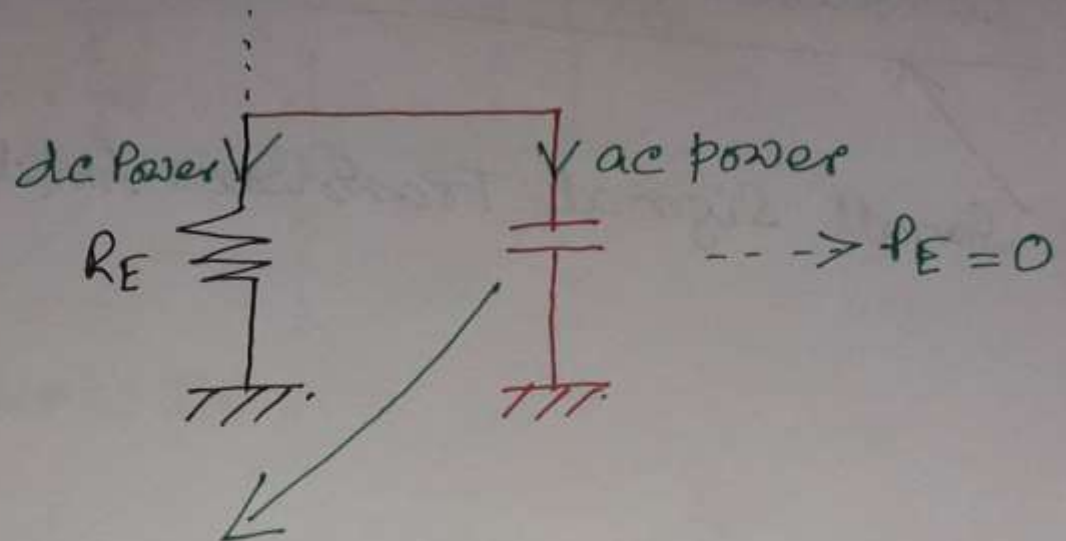

Bypass Capacitor

Transistor Amplifier

Final Design

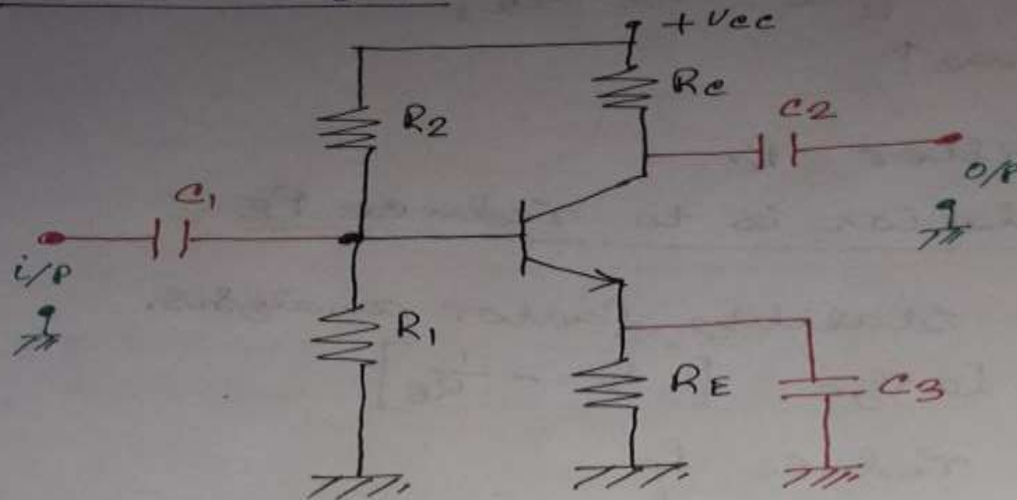

$C_1, C_2 \Rightarrow$ Coupling Capacitor

$C_3 \Rightarrow$ Bypass Capacitor

R-C Coupled Transistor Amplifier

Small Signal Transistor Amplifier

Transistor Amplifier

Low Frequency Model

Objective (1) To find out Gain


(2) To find out Gain vs. frequency i.e.
frequency response

[helps to get Bandwidth]

- Effect of the internal capacitances are not considered.

>> In the amplifier, frequency response of all components are known except Transistor.

Transistor Amplifier

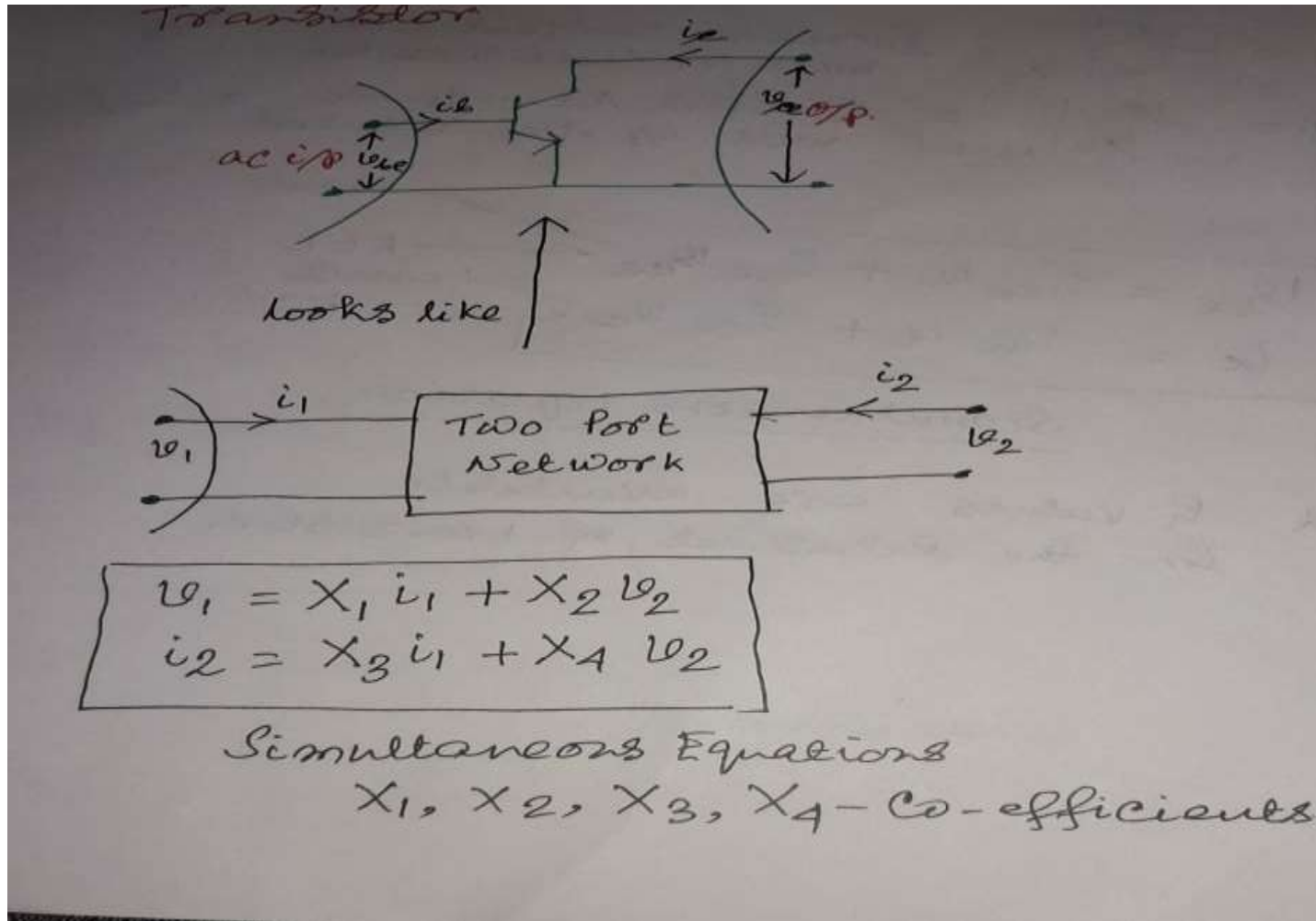

Transistor Amplifier

From fig.

$$V_1 = V_{be}, \quad i_1 = i_b$$

$$V_2 = V_{ce}, \quad i_2 = i_c$$

$$\begin{cases} V_{be} = X_1 i_b + X_2 V_{ce} \\ i_c = X_3 i_b + X_4 V_{ce} \end{cases}$$

--- Hybrid parameter

$$X_1 = \left. \frac{V_{be}}{i_b} \right|_{V_{ce}=0} = \text{Input Impedance with o/p short circuited} = h_{ie}$$

$$X_2 = \left. \frac{V_{be}}{V_{ce}} \right|_{i_b=0} = \text{Reverse Voltage gain with i/p open circuited} = h_{re}$$

$$X_3 = \left. \frac{i_c}{i_b} \right|_{V_{ce}=0} = \text{Forward Current gain with o/p short circuited} = h_{fe}$$

$$X_4 = \left. \frac{i_c}{V_{ce}} \right|_{i_b=0} = \text{Output Admittance with i/p open circuited} = h_{oe}$$

$$\begin{cases} V_{be} = h_{ie} i_b + h_{re} V_{ce} \\ i_c = h_{fe} i_b + h_{oe} V_{ce} \end{cases}$$

eqn ①
KVL
eqn ②
KCL

Simultaneous Equation.

* If values are available in the datasheet of transistor.

Transistor Amplifier

Handwritten equations for a transistor amplifier model, enclosed in a box. The equations are:

$$V_{be} = h_{ie} i_b + h_{re} V_{ce}$$
$$i_c = h_{fe} i_b + h_{oe} V_{ce}$$

Annotations on the right side of the box:


- eqn. ① points to the first equation.
- KVL points to the first equation.
- eqn. ② points to the second equation.
- KCL points to the second equation.

Simultaneous Equation.

* h values are available in the datasheet of transistor.

Transistor Amplifier


Equation 1

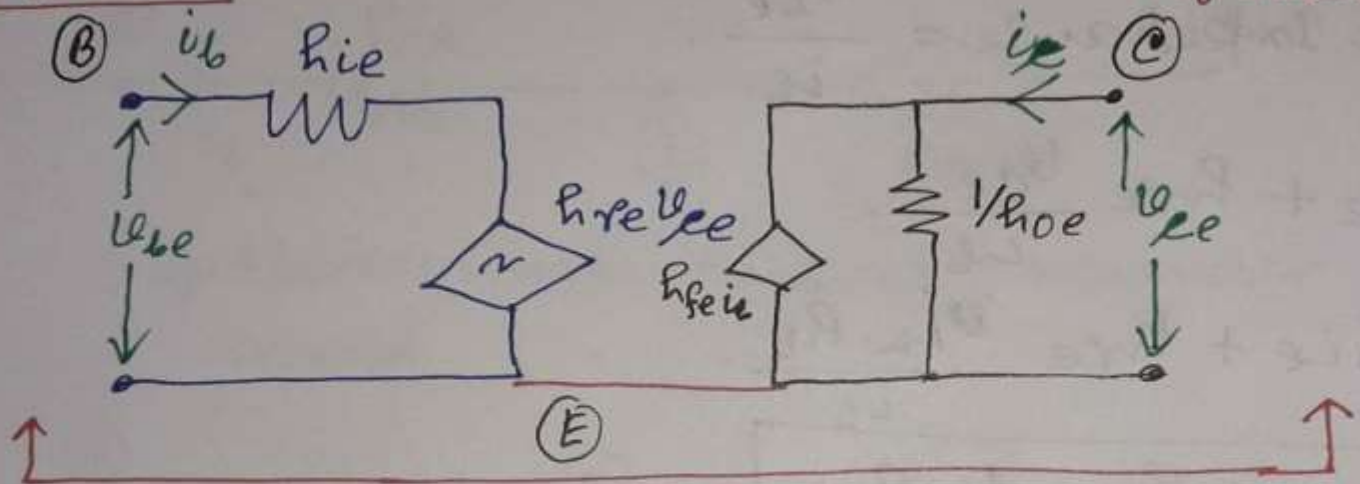

Equation 2

- BJT represented in low frequency hybrid parameter model.

Transistor Amplifier

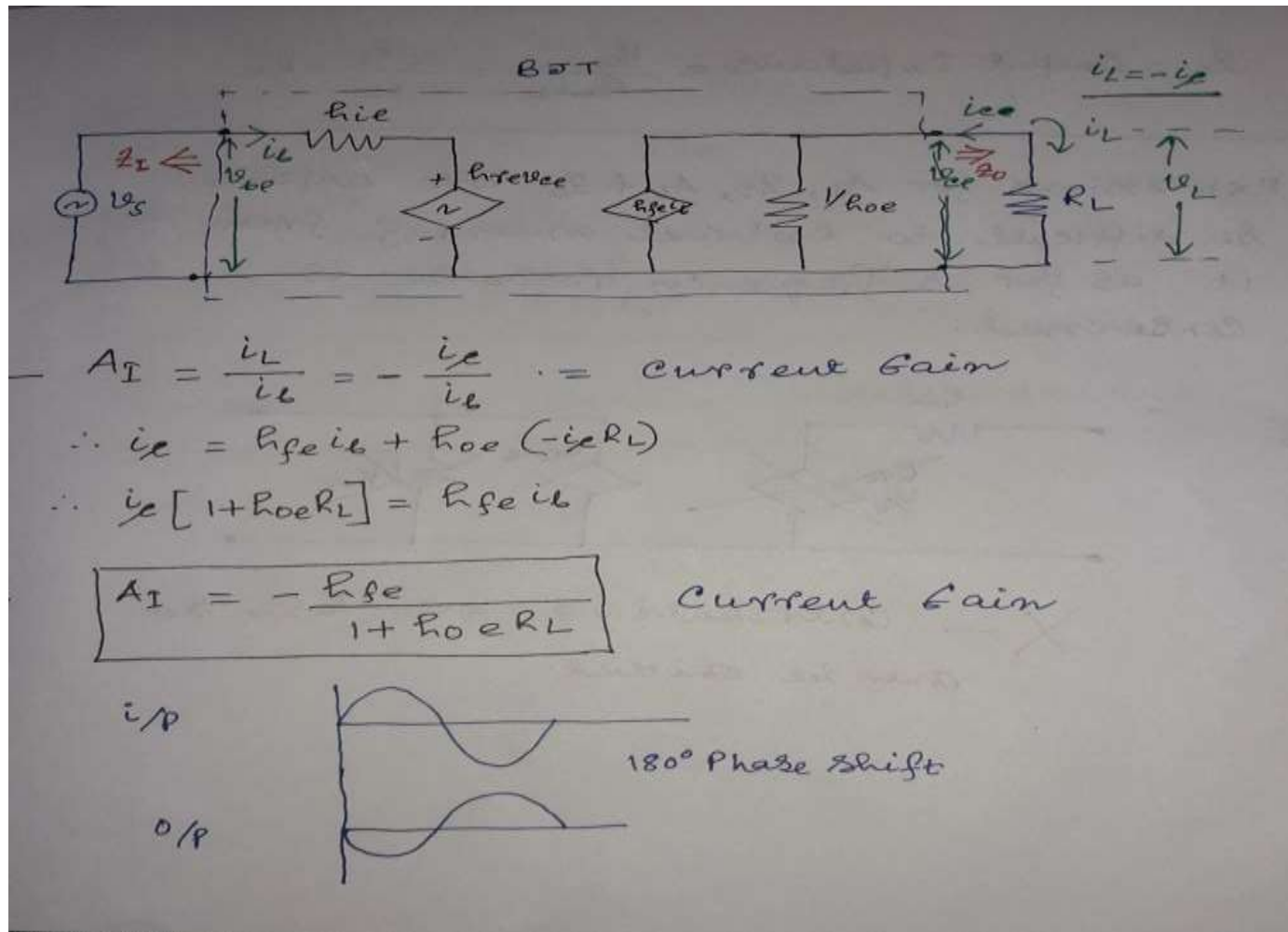

Transistor Amplifier

$$Z_I = \text{Input Impedance} = \frac{V_{ce}}{i_b}$$

$$= h_{ie} + h_{re} \frac{V_{ce}}{i_b}$$

$$= h_{ie} + h_{re} \frac{i_L R_L}{i_b}$$


$$\boxed{Z_I = h_{ie} + h_{re} A_I R_L}$$

$$A_V = \text{Voltage Gain} = \frac{V_{ce}}{V_{be}} = \frac{i_L R_L}{i_b Z_I} = A_I \frac{R_L}{Z_I}$$

$$Z_O = \text{Output Impedance} = \frac{V_{ce}}{i_L} = \frac{i_L R_L}{i_L} = R_L$$


Transistor Amplifier

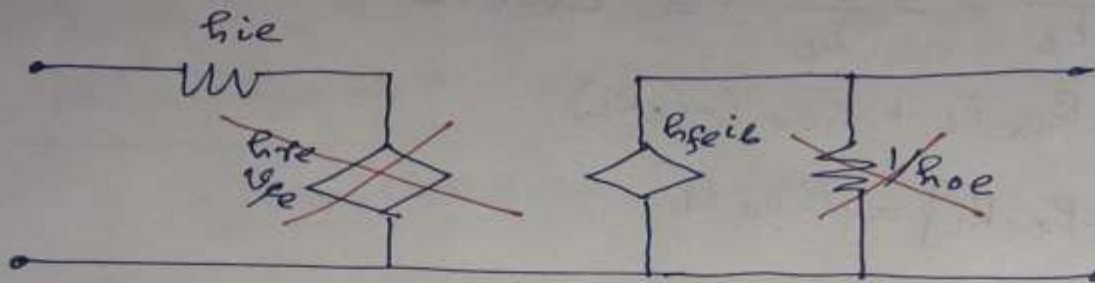Expressions for A_I , Z_I , A_V & Z_O are complex.
So difficult to extract meaning from
it as far as frequency response is
concerned.




X — Contributions are less, so
may be omitted.


Transistor Amplifier

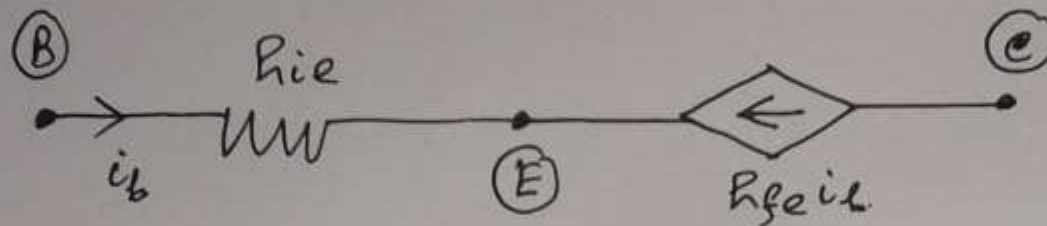

⇒ Approximate hybrid parameter model.

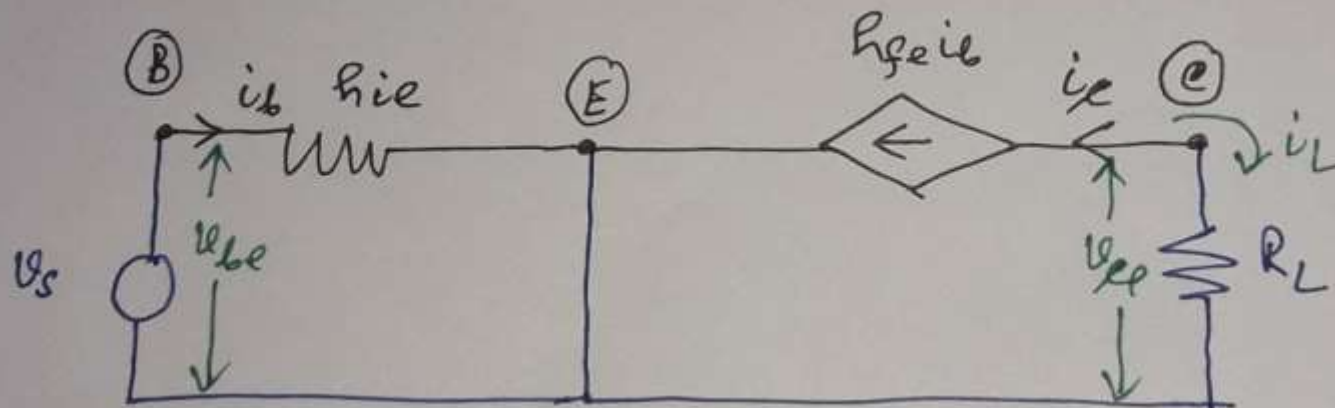

Transistor Amplifier

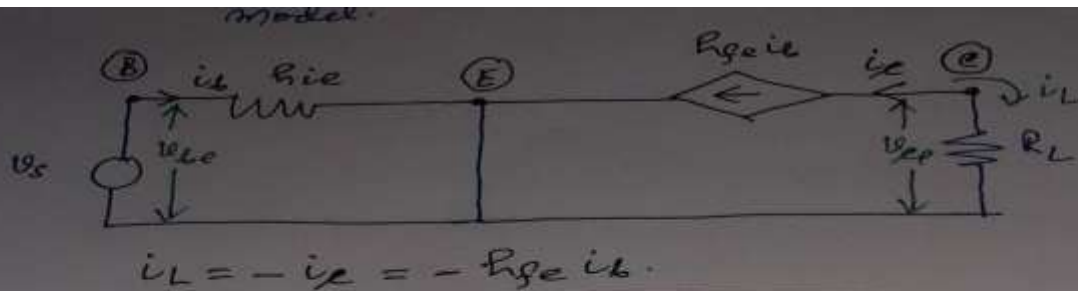

$$A_I = \text{Current Gain} = -h_{fe}$$

$$Z_I = \frac{v_{be}}{i_b} = \frac{h_{ie} i_b}{i_b} = h_{ie}$$


$$Z_O = \frac{v_{ce}}{i_c} = R_L$$

$$A_V = \frac{v_{ce}}{v_{be}} = \frac{i_c R_L}{i_b h_{ie}} = A_I \cdot \frac{R_L}{h_{ie}}$$

Available in the datasheet, mostly dependent of transistor parameters.

Transistor Amplifier

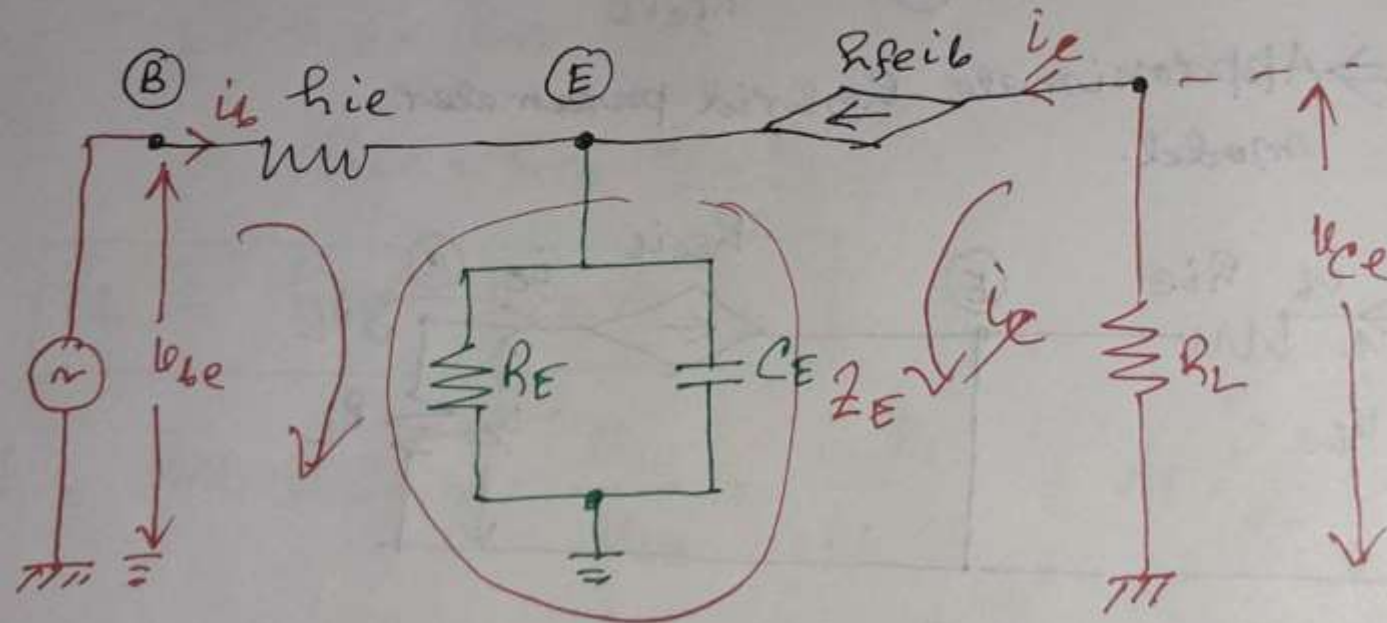Frequency Response of BJT Amplifier
- Low frequency



Transistor Amplifier

~~SWCE~~

$$i_c = h_{fe} i_b$$

$$v_{be} = h_{ie} i_b + i_b Z_E + i_c Z_E$$

$$= i_b [h_{ie} + Z_E + h_{fe} Z_E]$$

$$= i_b [h_{ie} + Z_E (1 + h_{fe})]$$

$$v_{ce} = i_L R_L = -i_c R_L$$

$$= -h_{fe} i_b R_L$$

$$A_v = \frac{v_{ce}}{v_{be}} = - \frac{h_{fe} i_b R_L}{i_b [h_{ie} + Z_E (1 + h_{fe})]} = \text{Voltage Gain}$$


Transistor Amplifier

$$Z_E = \frac{R_E \cdot \frac{1}{j\omega C_E}}{R_E + \frac{1}{j\omega C_E}}$$
$$= \frac{R_E / j\omega C_E}{\frac{j\omega C_E R_E + 1}{j\omega C_E}}$$


$$Z_E = \frac{R_E}{1 + j\omega C_E R_E}$$

Transistor Amplifier
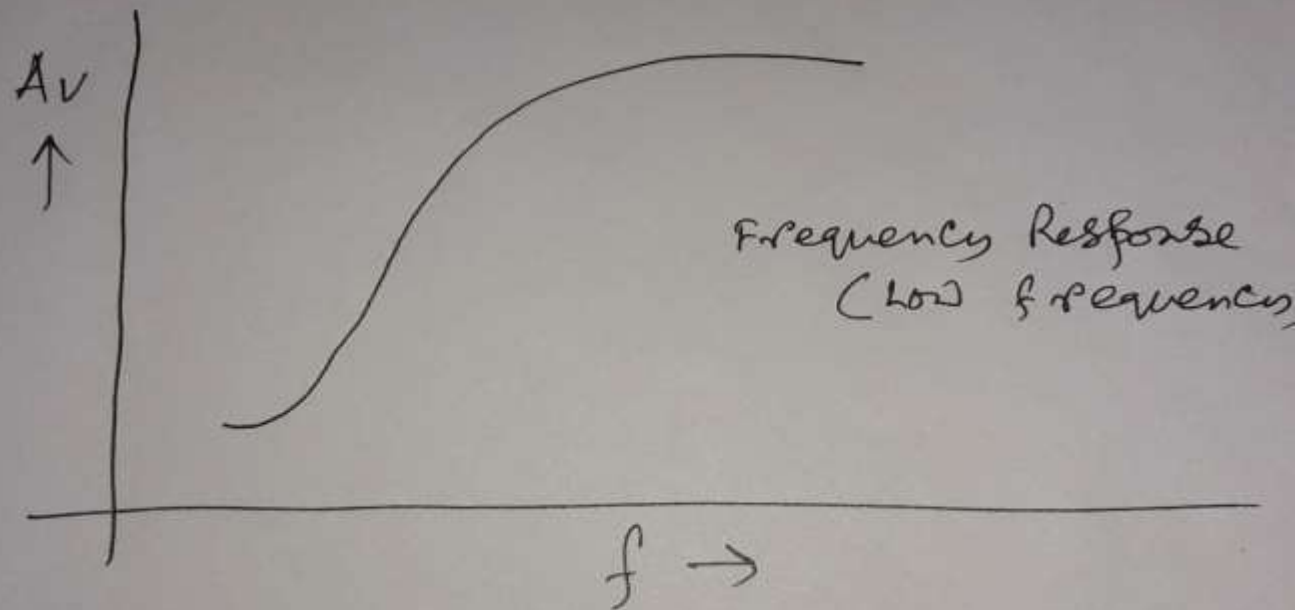
$$A_v = - \frac{h_{fe} R_L}{h_{ie} + \frac{(1+h_{fe}) R_E}{1+j\omega C_E R_E}}$$



High Frequency Model

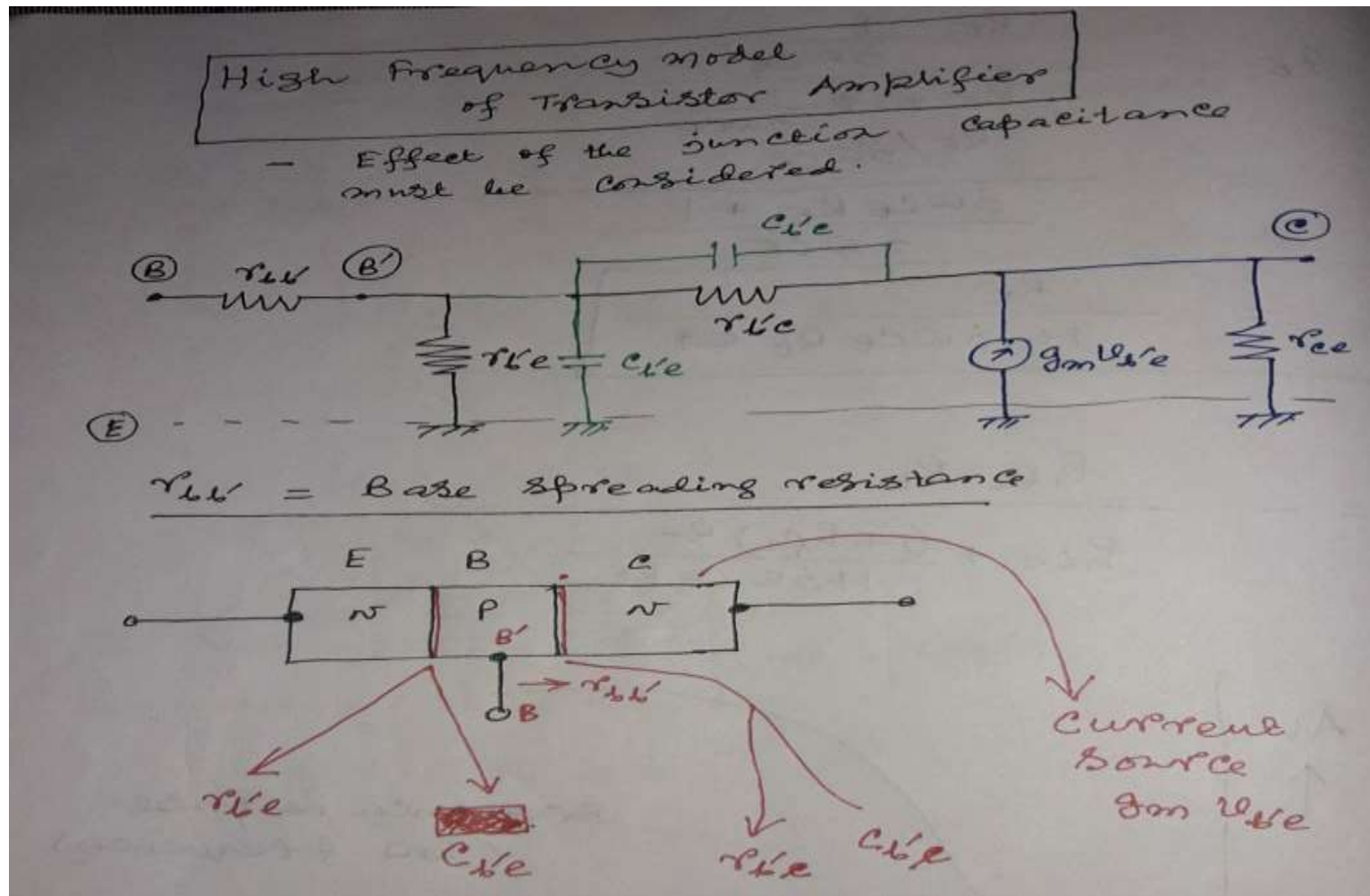


High Frequency Model

r values & g_m are not available in the datasheet.

$$g_m = \text{trans conductance} = \frac{i_e}{v_{be}} = \frac{di_e}{v_{be}} \\ = \frac{2}{v_{be}/i_e} = \frac{2}{r_e}$$

$$r_e = \frac{25\text{mV}}{I_E}$$

High Frequency Model

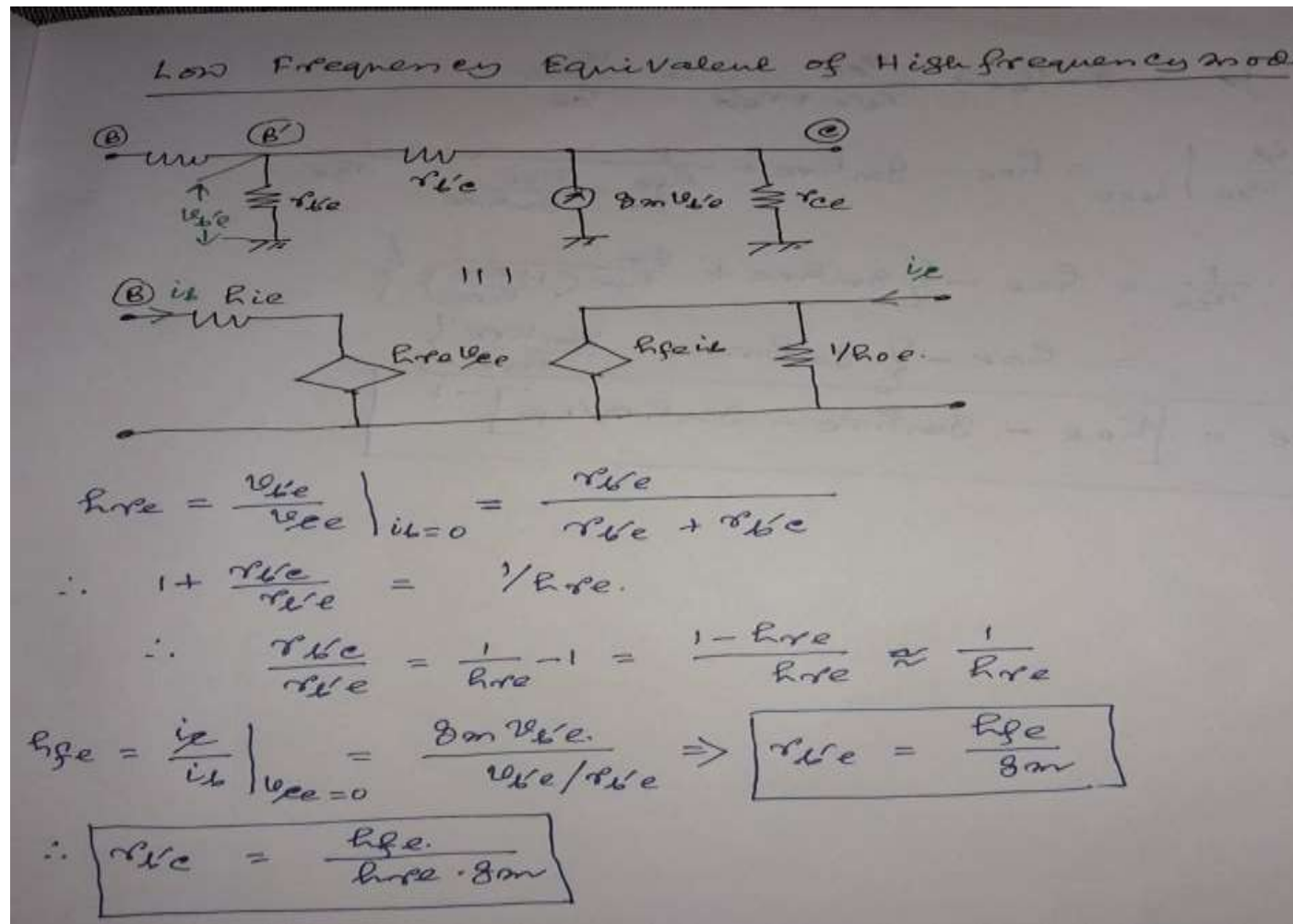

High Frequency Model

$$r_{bb'} + r_{b'e} = h_{ie}$$

$$\therefore r_{bb'} = h_{ie} - r_{b'e} \Rightarrow r_{bb'} = h_{ie} - \frac{h_{fe}}{g_m}$$

High Frequency Model

$$i_e = g_m v_{be} + \frac{v_{ce}}{r_{be} + r_{be}} + \frac{v_{ce}}{r_{ce}}$$

$$\therefore \left. \frac{i_e}{v_{ce}} \right|_{i_b=0} = h_{oe} = g_m h_{re} + \frac{1}{\frac{h_{fe}}{g_m} + \frac{h_{fe}}{g_m h_{re}}} + \frac{1}{r_{ce}}$$


$$\therefore \frac{1}{r_{ce}} = h_{oe} - \left\{ g_m h_{re} + \frac{g_m}{h_{fe} \left(\frac{1+h_{re}}{h_{re}} \right)} \right\}$$

$$= h_{oe} - \left\{ g_m h_{re} + \frac{g_m h_{re}}{h_{fe}} \right\}$$


$$r_{ce} = \left[h_{oe} - g_m h_{re} - g_m h_{re} / h_{fe} \right]^{-1}$$

High Frequency Model

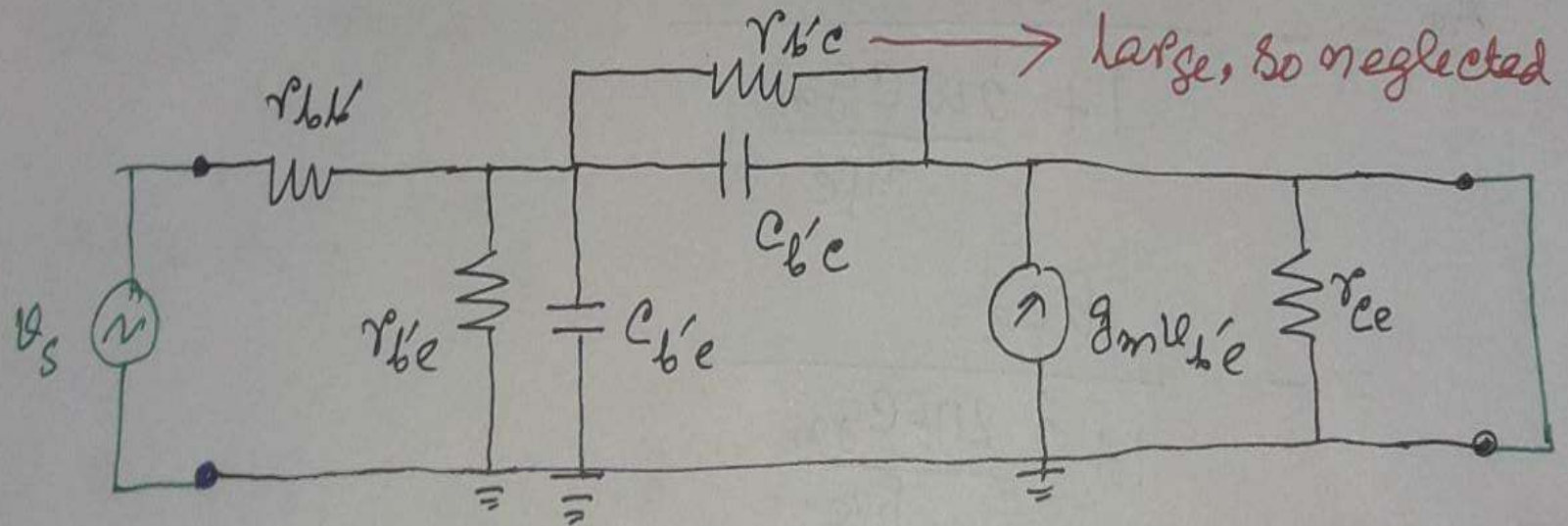
Frequency Response When o/p Short Circuited



High Frequency Model

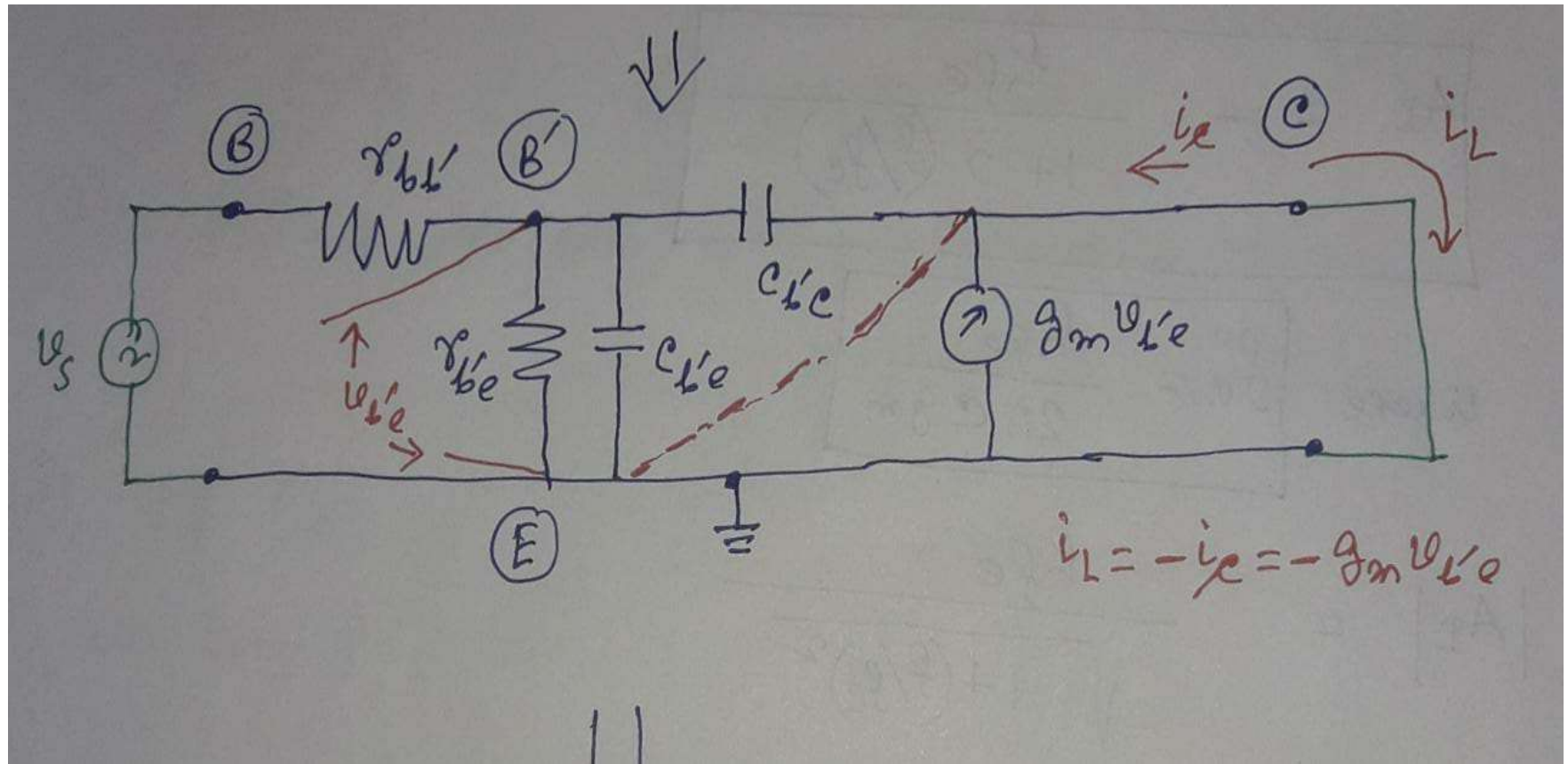

High Frequency Model

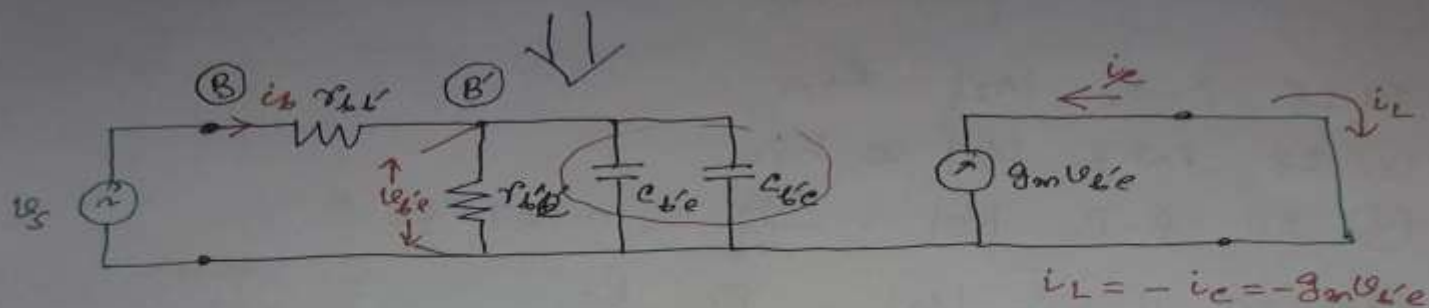

$$C = C_{be} + C_{bc}$$

$$i_b = v_{be} \left[\frac{1}{r_{be}} + j\omega C \right]$$

$$= v_{be} \left[\frac{g_m}{\beta_{fe}} + j\omega C \right]$$

$$\therefore A_T = \frac{i_L}{i_b} = - \frac{g_m v_{be}}{v_{be} \left[\frac{g_m}{\beta_{fe}} + j\omega C \right]}$$

High Frequency Model

$$A_I = - \frac{h_{fe}}{1 + j\omega C \frac{h_{fe}}{g_m}}$$

$$= - \frac{h_{fe}}{1 + j \frac{2\pi f C h_{fe}}{g_m}}$$

$$A_I = - \frac{h_{fe}}{1 + j(f/f_c)}$$

where $f_c = \frac{g_m}{2\pi C h_{fe}}$


$$f_c = \frac{g_m}{2\pi C h_{fe}}$$

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + (f/f_c)^2}}$$

High Frequency Model

$$|A_T| = \frac{R_{fe}}{\sqrt{1 + (f/f_c)^2}}$$

- ① If $f = 0$, $|A_T| = R_{fe}$
- ② If $f \ll f_c$, $|A_T| \approx R_{fe}$
- ③ If $f = f_c$, $|A_T| = \frac{R_{fe}}{\sqrt{2}} = 0.707 R_{fe}$
- ④ If $f \gg f_c$, $|A_T| = R_{fe} \cdot \frac{f_c}{f}$

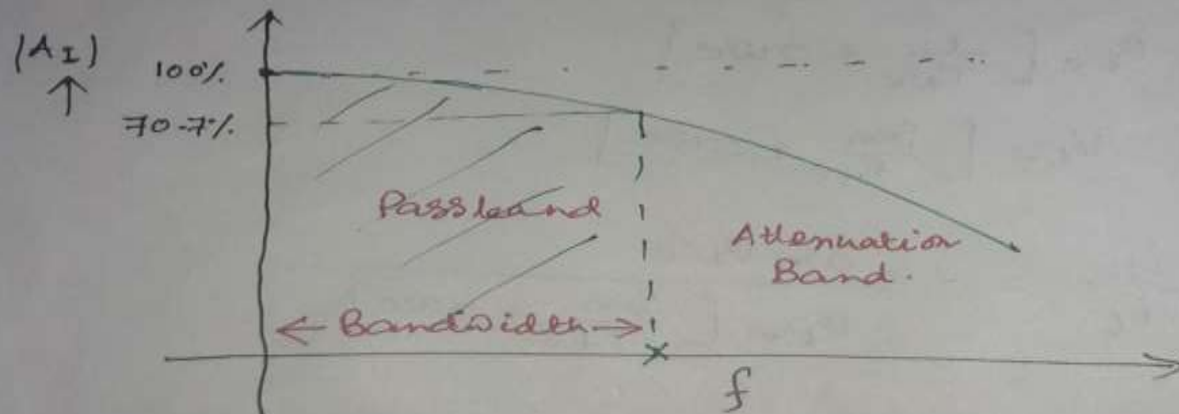

High Frequency Model

As $|A_I|$ is a large quantity, normally it is expressed in terms of dB.

$$|A_I|_{\text{in dB}} = 20 \log_{10} |A_I|$$


- ① If $f=0$, $|A_I|_{\text{in dB}} = 20 \log_{10} h_{fe} \dots \text{(max.)} \dots 10 \text{ dB}$
- ② If $f \ll f_c$, $|A_I|_{\text{in dB}} \approx 20 \log_{10} h_{fe} \dots \nearrow$
- ③ If $f=f_c$ $|A_I|_{\text{(dB)}} = 20 \log_{10} h_{fe} - 20 \log_{10} \sqrt{2}$
 $= 0 \text{ dB} - 3 \text{ dB} = -3 \text{ dB}$

High Frequency Model

① If $f \gg f_c$


lets say $f = 10 f_c$.
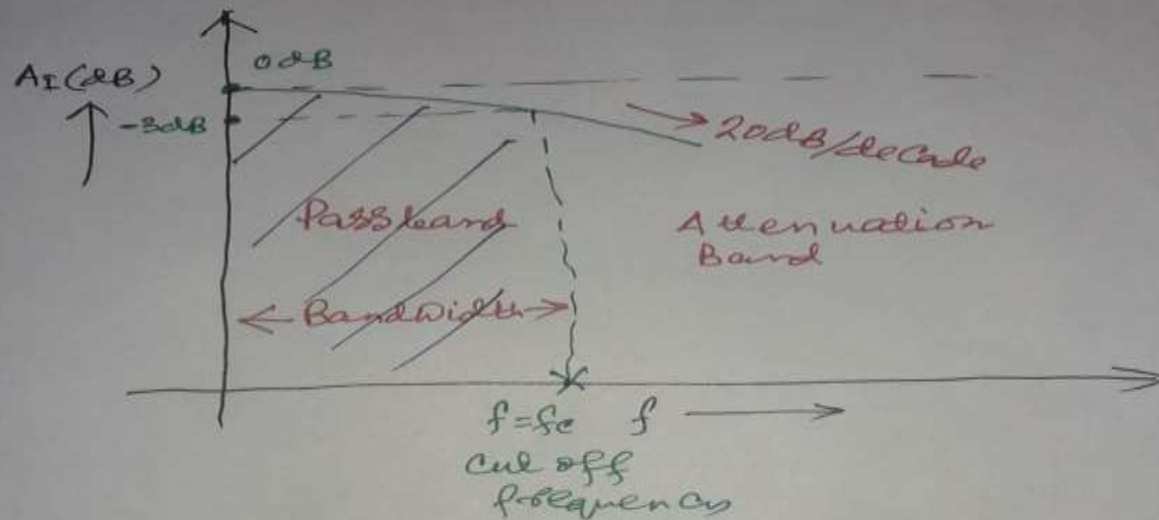
$$\begin{aligned} A_f(\text{in dB}) &= 20 \log_{10} f_{fc} - 20 \log_{10} 10 \\ &= -20 \text{ dB.} \end{aligned}$$






High Frequency Model

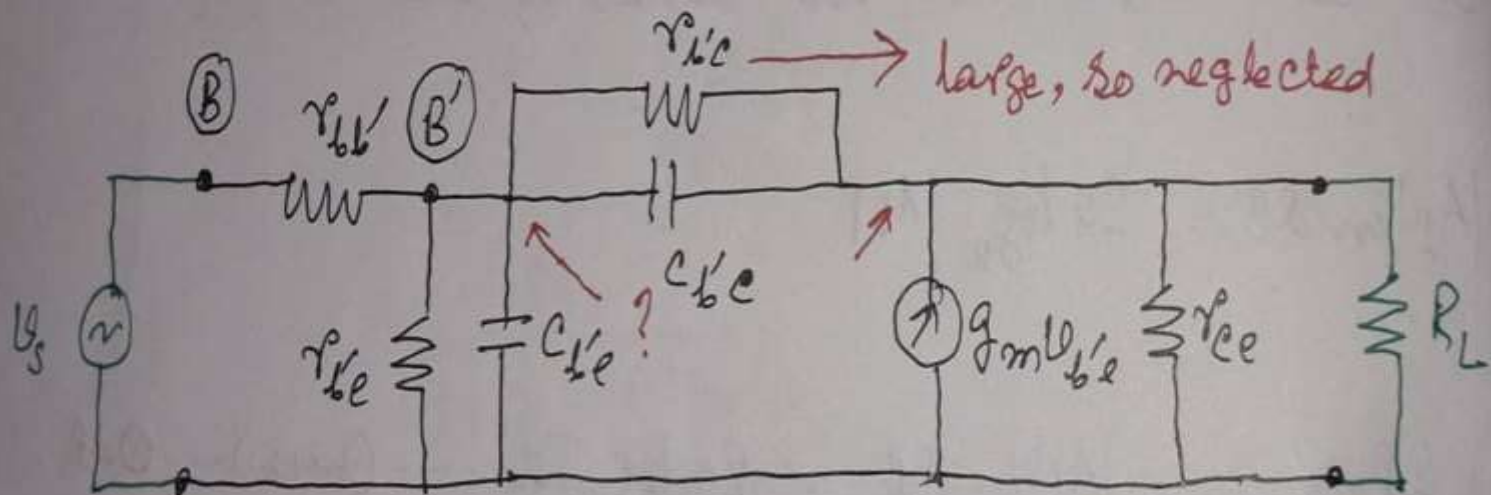Frequency Response when R_L is Connected at the load



High Frequency Model

Use Miller's Theorem

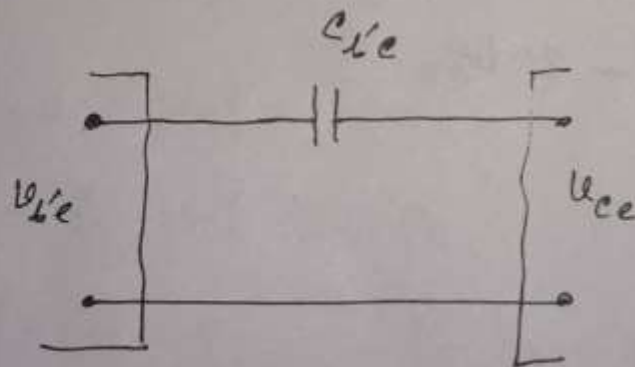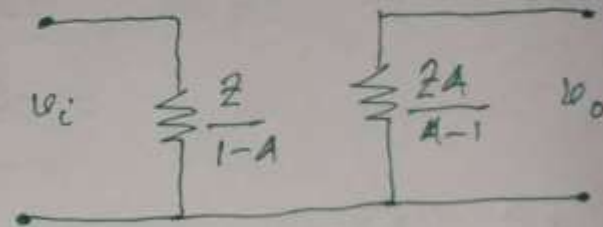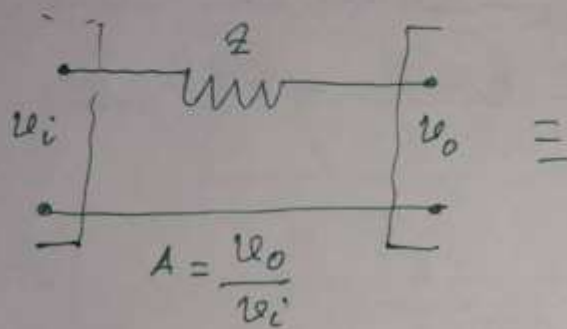

$$A = \frac{v_{ce}}{v_{be}} = - \frac{g_m v_{be} R_L}{v_{be}}$$

$$\boxed{A = -g_m R_L}$$


High Frequency Model

$$\frac{Z}{1-A} = \frac{\frac{1}{j\omega C_L'c}}{1+g_m R_L} = \frac{1}{j\omega C_L'c (1+g_m R_L)}$$
$$= \frac{1}{j\omega C_1}$$

where $C_1 = C_L'c (1+g_m R_L)$

$$\frac{Z_A}{A-1} = \frac{(-g_m R_L) \frac{1}{j\omega C_L'c}}{-g_m R_L - 1} \approx \frac{1}{j\omega C_L'c}$$

High Frequency Model

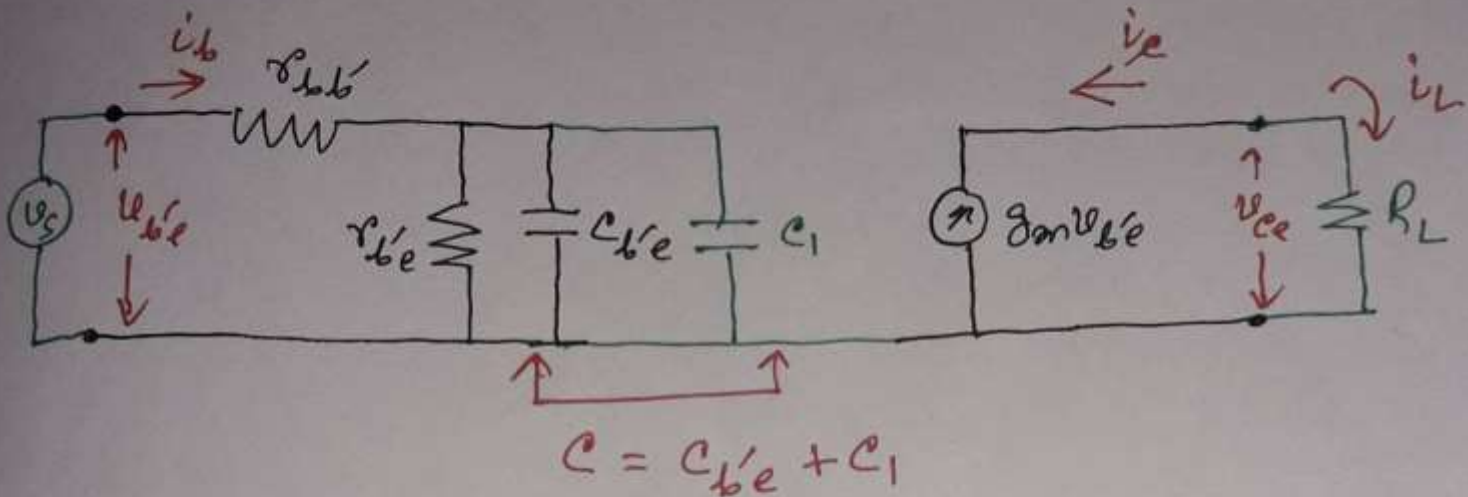

$$\begin{aligned}
 i_b &= v_{be'} \left[\frac{1}{r_{be'}} + j\omega C \right] \\
 &= v_{be'} \left[\frac{g_m}{h_{fe}} + j\omega C \right]
 \end{aligned}$$

High Frequency Model

$$A_I = \frac{i_L}{i_b} = \frac{-g_m v_{b'e}}{v_{b'e} \left[\frac{g_m}{h_{fe}} + j\omega C \right]}$$
$$= - \frac{h_{fe}}{1 + \frac{j\omega C h_{fe}}{g_m}}$$

$$A_I = - \frac{h_{fe}}{1 + j \left(\frac{f}{f_c} \right)}$$


where $f_c = \frac{g_m}{2\pi C h_{fe}}$

$$C = C_{b'e} + C_{b'c} (1 + g_m R_L)$$

High Frequency Model

$$|A_T| = \frac{R_{fe}}{\sqrt{1 + (f/f_c)^2}}$$


- ① If $f = 0$, $|A_T| = R_{fe}$
- ② If $f \ll f_c$, $|A_T| \approx R_{fe}$
- ③ If $f = f_c$, $|A_T| = \frac{R_{fe}}{\sqrt{2}} = 0.707 R_{fe}$
- ④ If $f \gg f_c$, $|A_T| = R_{fe} \cdot \frac{f_c}{f}$

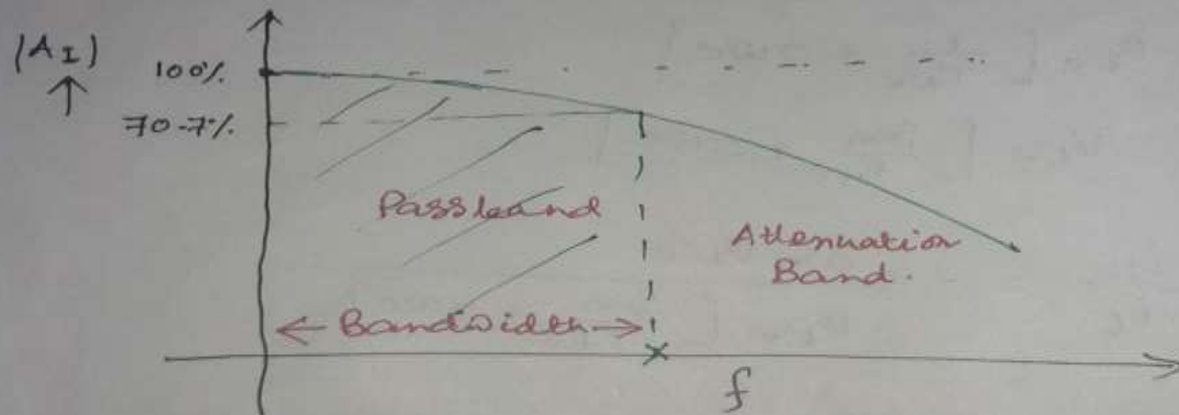

High Frequency Model

As $|A_I|$ is a large quantity, normally it is expressed in terms of dB.

$$|A_I|_{\text{in dB}} = 20 \log_{10} |A_I|$$

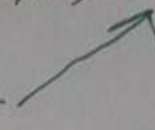- ① If $f=0$, $|A_I|_{\text{in dB}} = 20 \log_{10} h_{fe} \dots \text{(max.)} \dots 10 \text{ dB}$
- ② If $f \ll f_c$, $|A_I|_{\text{in dB}} \approx 20 \log_{10} h_{fe} \dots$ 
- ③ If $f=f_c$ $|A_I|_{\text{dB}} = 20 \log_{10} h_{fe} - 20 \log_{10} \sqrt{2}$
 $= 0 \text{ dB} - 3 \text{ dB} = -3 \text{ dB}$

High Frequency Model

① If $f \gg f_c$

lets say $f = 10 f_c$.

$$A_f(\text{in dB}) = 20 \log_{10} f_{fc} - 20 \log_{10} 10 \\ = -20 \text{ dB.}$$

