

The background of the slide is a deep blue color. It is decorated with numerous light blue butterfly silhouettes of various sizes, scattered across the entire surface. A pattern of thin, light blue radial lines emanates from the center, creating a subtle sunburst effect behind the text box.

# **THREE PHASE TRANSFORMERS**

# THREE PHASE SYSTEM


## BASICS

Line voltage  $V_L$  = voltage between lines

Phase voltage  $V_{ph}$  = voltage between a line and neutral

# THREE PHASE SYSTEM

## BALANCED STAR

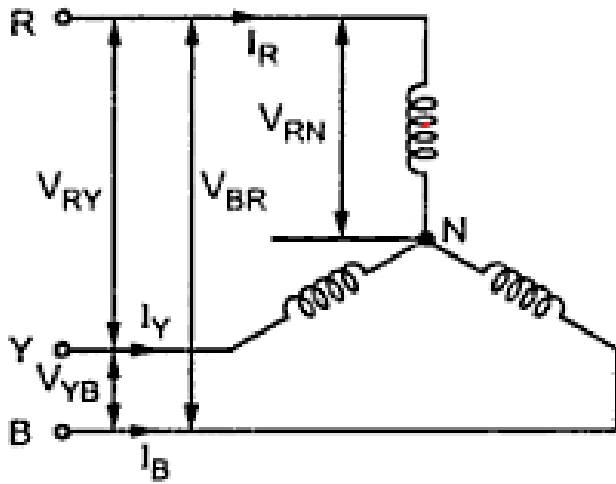


Line Voltage,

$$V_L = \sqrt{3} V_{ph}$$

Line current,  $I_L = I_{ph}$

# THREE PHASE SYSTEM

## BALANCED DELTA

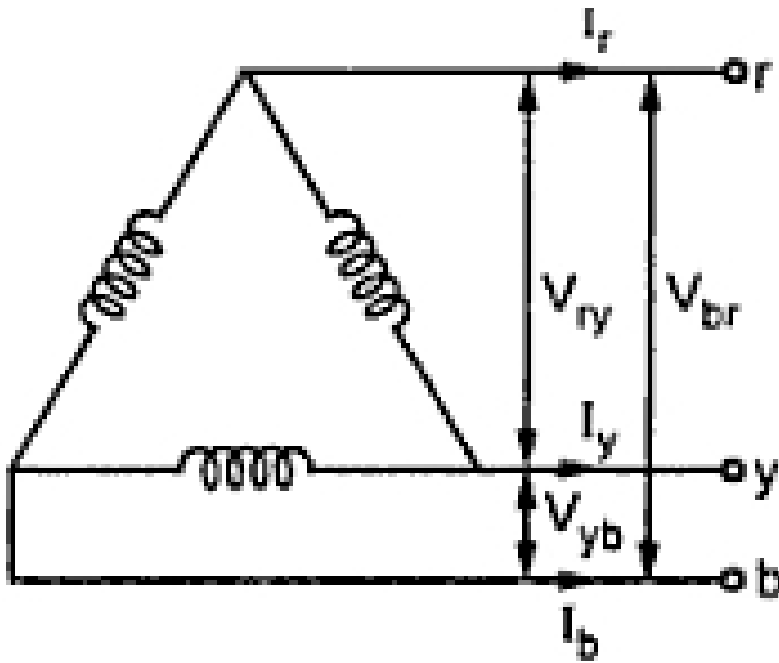

Line Voltage  $V_L = V_{ph}$

Line current  $I_L = \sqrt{3} I_{ph}$

# THREE PHASE TRANSFORMERS

**Almost all major generation & Distribution Systems in the world are three phase ac systems**  
**Three phase transformers play an important role in these systems**

**3 phase transformers can be constructed from**

- (a) 3 single phase transformers**
- (b) 2 single phase transformers**
- (c ) using a common core for three phase windings**

# 3 phase Transformer connections


**By connecting three single phase transformers**

- 1. Star- Star connection**
- 2. Delta- Delta connection**
- 3. Star – Delta connection**
- 4. Delta – Star connection**

$$\text{Phase transformation ratio, } K = \frac{\text{Secondary phase voltage}}{\text{Primary phase voltage}} = \frac{N_2}{N_1}$$



# Star- Star connection

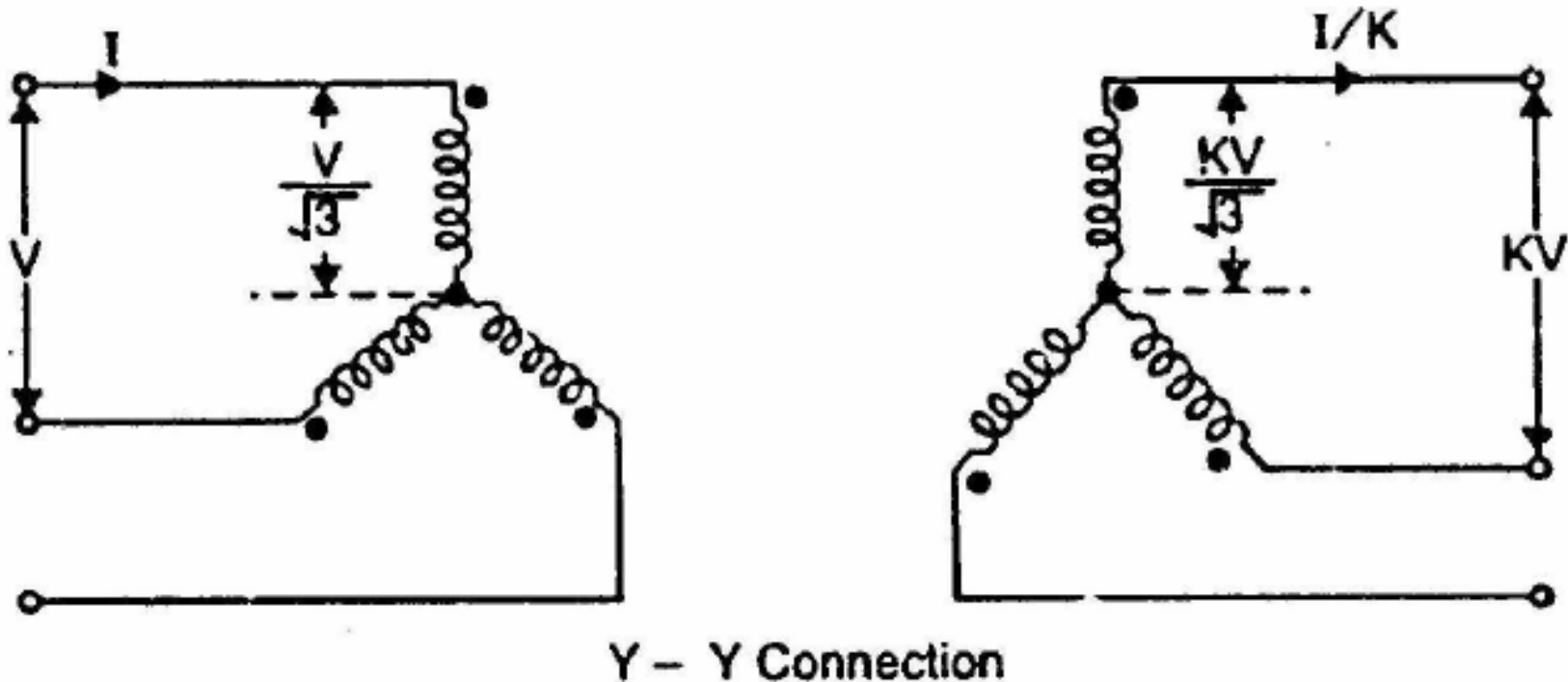

- This connection satisfactory only in balanced load otherwise neutral point will be shifted.

# Star- Star connection

## Advantages

- 1.Requires less turns per winding i.e. cheaper**  
*Phase voltage is  $1/\sqrt{3}$  times of line voltage*
- 2.Cross section of winding is large i.e. stronger to bear stress during short circuit**  
*Line current is equal to phase current*
- 3. Less dielectric strength in insulating materials**  
*phase voltage is less*





# Star- Star connection

## Disadvantages

- 1.If the load on the secondary side **unbalanced** then the **shifting of neutral point** is possible
- 2.The **third harmonic present** in the alternator voltage may appear on the secondary side. This causes distortion in the secondary phase voltages
3. Magnetizing current of transformer has **3<sup>rd</sup> harmonic** component

# Delta - Delta connection

(i)

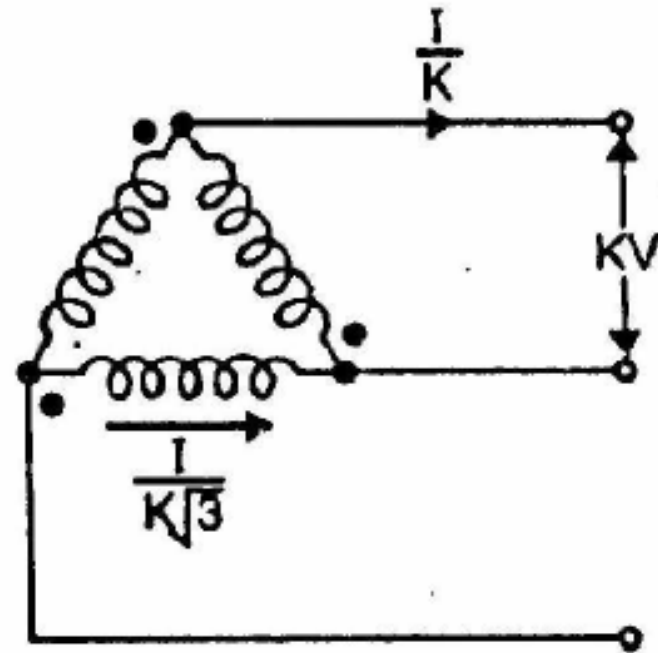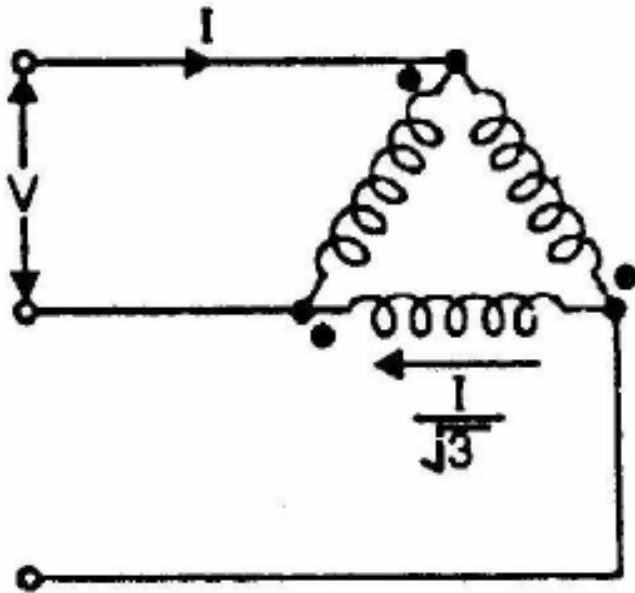

$\Delta - \Delta$  Connection

➤ This connection is used for moderate voltages

# Delta - Delta connection

## Advantages


- 1. System voltages are more stable in relation to unbalanced load**
- 2. If one t/f is failed it may be used for low power level i.e. V-V connection**
- 3. No distortion of flux i.e. 3<sup>rd</sup> harmonic current not flowing to the line wire**

# Delta - Delta connection

## Disadvantages

1. Compare to Y-Y require more **insulation**.
2. Absence of star point i.e. fault may severe.

# Star- Delta connection

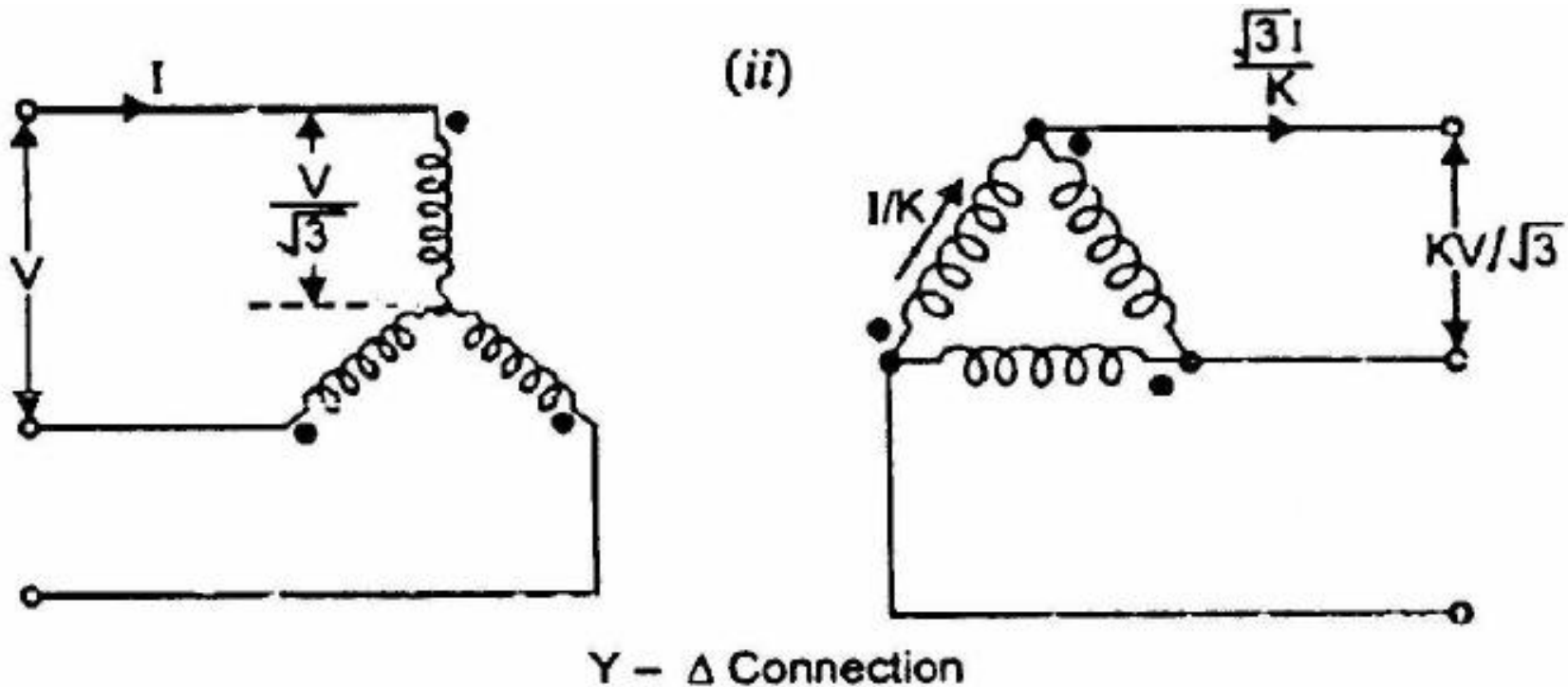

- Used to step down voltage i.e. end of transmission line

# Star- Delta connection

## Advantages

1. The primary side is star connected. **Hence fewer number of turns are required.** This makes the connection **economical**
2. The neutral available on the primary can be **earthed to avoid distortion.**
3. Large **unbalanced** loads can be handled satisfactory.




# Star- Delta connection

## Disadvantages

The secondary voltage **is not in phase** with the primary. ( $30^\circ$  phase difference )

Hence it is not possible to operate this connection in **parallel** with star-star or delta-delta connected transformer.

# Delta - Star connection

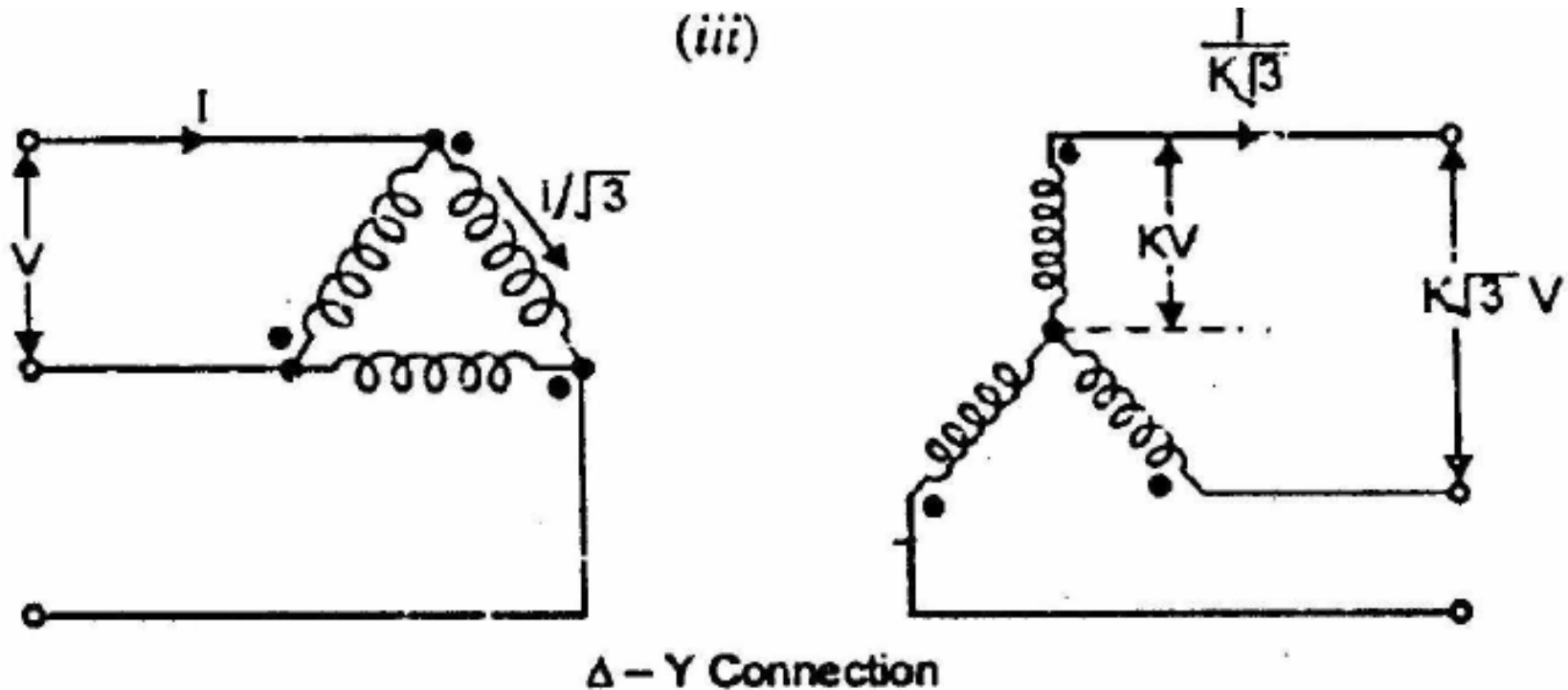

- This connection is used to step up voltage ie. Beginning of high tension line

# Delta - Star connection

## Features

- secondary Phase voltage is  $1/\sqrt{3}$  times of line voltage.
- neutral in secondary can be grounded for 3 phase 4 wire system.
- Neutral shifting and 3<sup>rd</sup> harmonics are there.
- Phase shift of  $30^\circ$  between secondary and primary currents and voltages.

# Open Delta or V-V Connection


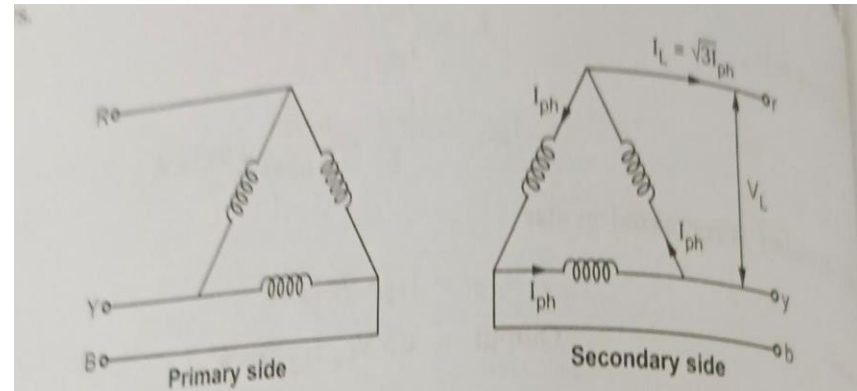
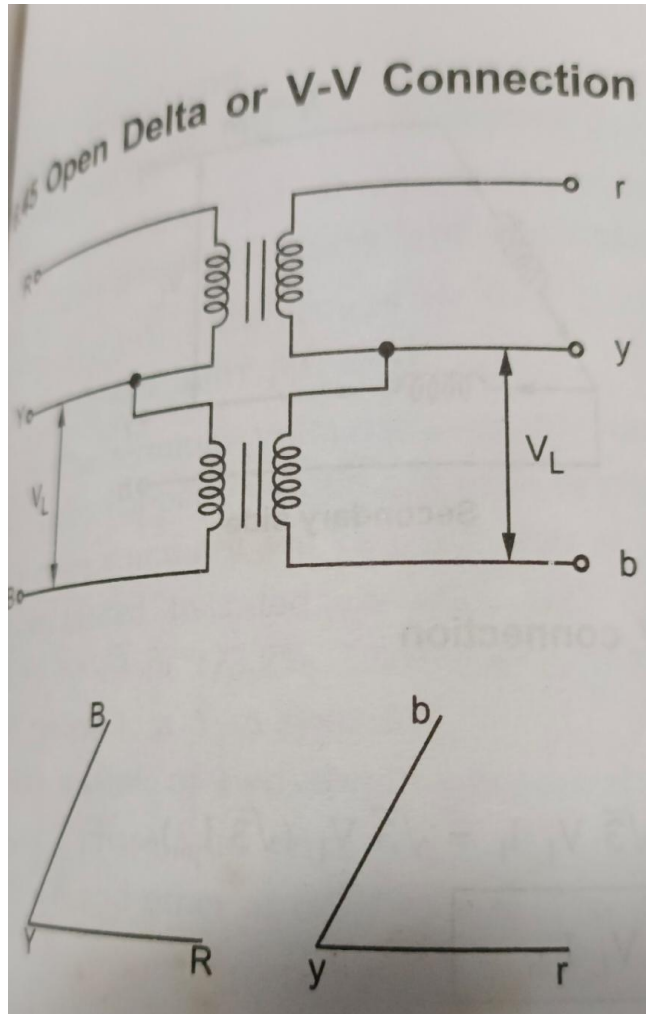


Fig. 6.85 (a)  $\Delta - \Delta$  connection

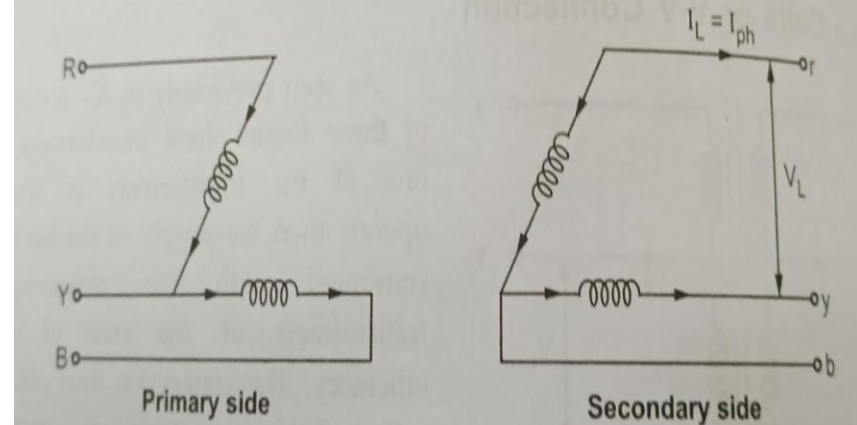

# Open Delta or V-V Connection

$$\Delta - \Delta \text{ capacity} = \sqrt{3} V_L I_L = \sqrt{3} V_L (\sqrt{3} I_{ph})$$

$$\Delta - \Delta \text{ capacity} = 3 V_L I_{ph}$$

# Open Delta or V-V Connection

Electrical Machines

It can also be noted from the Fig. 6.85 (b) that the secondary line current  $I_L$  equal to the phase current  $I_{ph}$ .

$$V - V \text{ capacity} = \sqrt{3} V_L I_L = \sqrt{3} V_L I_{ph} \quad \dots (2)$$

Dividing equation (2) by equation (1)

$$\frac{V - V \text{ capacity}}{\Delta - \Delta \text{ capacity}} = \frac{\sqrt{3} V_L I_{ph}}{3 V_L I_{ph}} = \frac{1}{\sqrt{3}} = 0.577 \approx 57.7 \% \quad \dots (3)$$

Thus the three phase load that can be carried without exceeding the ratings of the transformers is 57.7 % of the original load. Hence it is not 66.7 % which was expected otherwise.

The reduction in the rating can be calculated as  $\frac{66.67 - 57.735}{57.735} \times 100 = 15.476$

Suppose that we consider three transformers connected in  $\Delta - \Delta$  fashion and supplying their rated load. Now one transformer is removed then each of the remaining two transformers will be overloaded. The overload on each transformer will be given as

$$\frac{\text{Total load in V-V}}{\text{V A / transformer}} = \frac{\sqrt{3} V_L I_{ph}}{V_L I_{ph}} = \sqrt{3} = 1.732$$

**Key Point:** This overload can be carried temporarily if provision is made to reduce the load if overheating and breakdown of the remaining two transformers is to be avoided.



# Open Delta or V-V Connection

## 6.45.1 Limitations

The limitations with V-V connection are given below :

1. The average p.f. at which V-V bank is operating is less than that with the load. This power p.f is 86.6% of the balanced load p.f.
2. The two transformers in V-V bank operate at different power factor except for balanced unity p.f. load.
3. The terminal voltages available on the secondary side become unbalanced. This may happen even though load is perfectly balanced.


Thus in summary we can say that if two transformers are connected in V-V fashion and are loaded to rated capacity and one transformer is added to increase the total capacity by  $\sqrt{3}$  or 173.2%. Thus the increase in capacity is 73.2% when converting from a V-V system to a  $\Delta$ - $\Delta$  system.

With a bank of two single phase transformers connected in V-V fashion supplying a balanced 3 phase load with  $\cos \phi$  as p.f., one of the transformer operates at a p.f. of  $\cos (30 - \phi)$  and other at  $\cos (30 + \phi)$ . The powers of two transformers are given by,


$$P_1 = \text{kVA} \cos (30 - \phi)$$

$$P_2 = \text{kVA} \cos (30 + \phi)$$

# T-T Connection

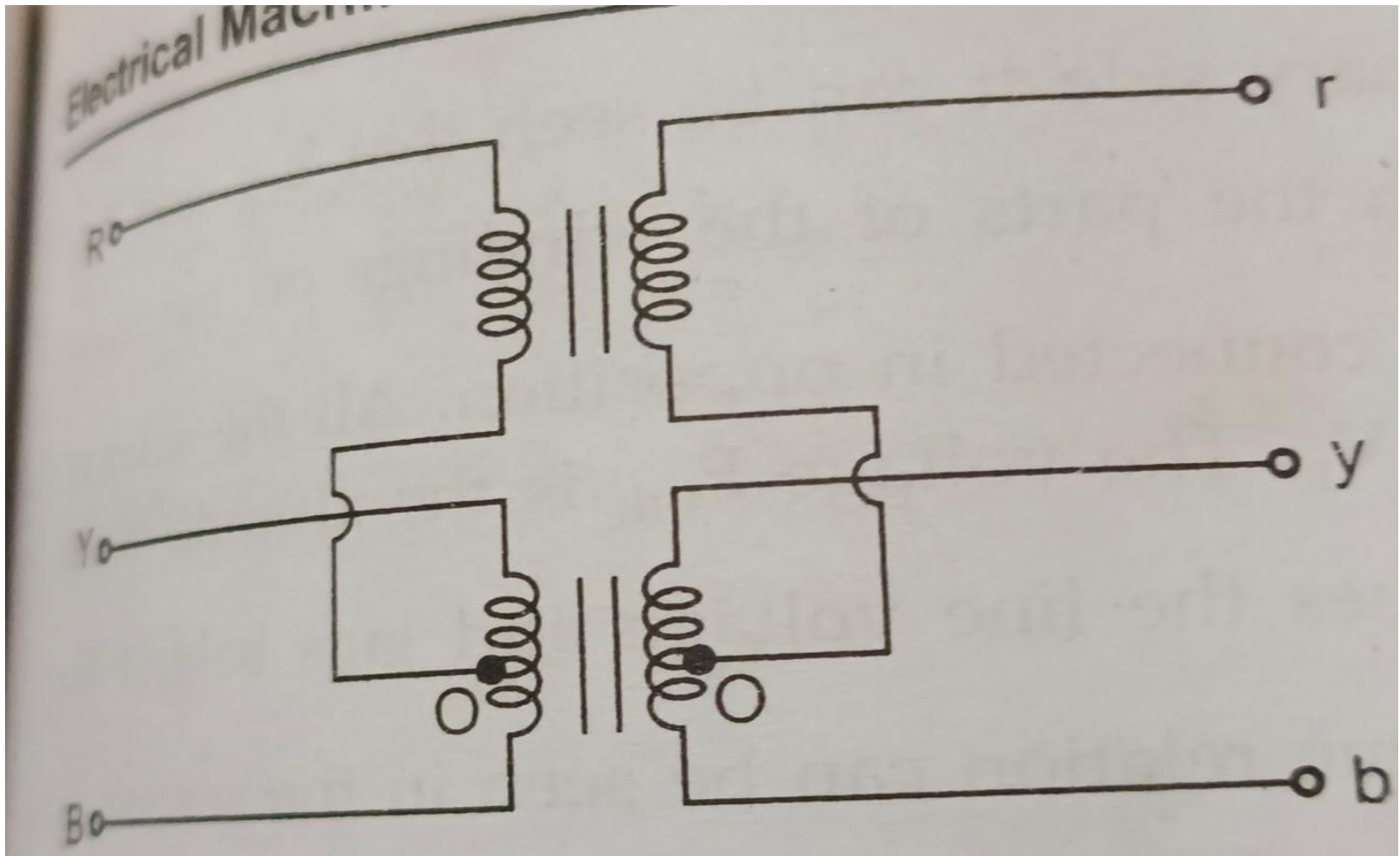

# T-T Connection

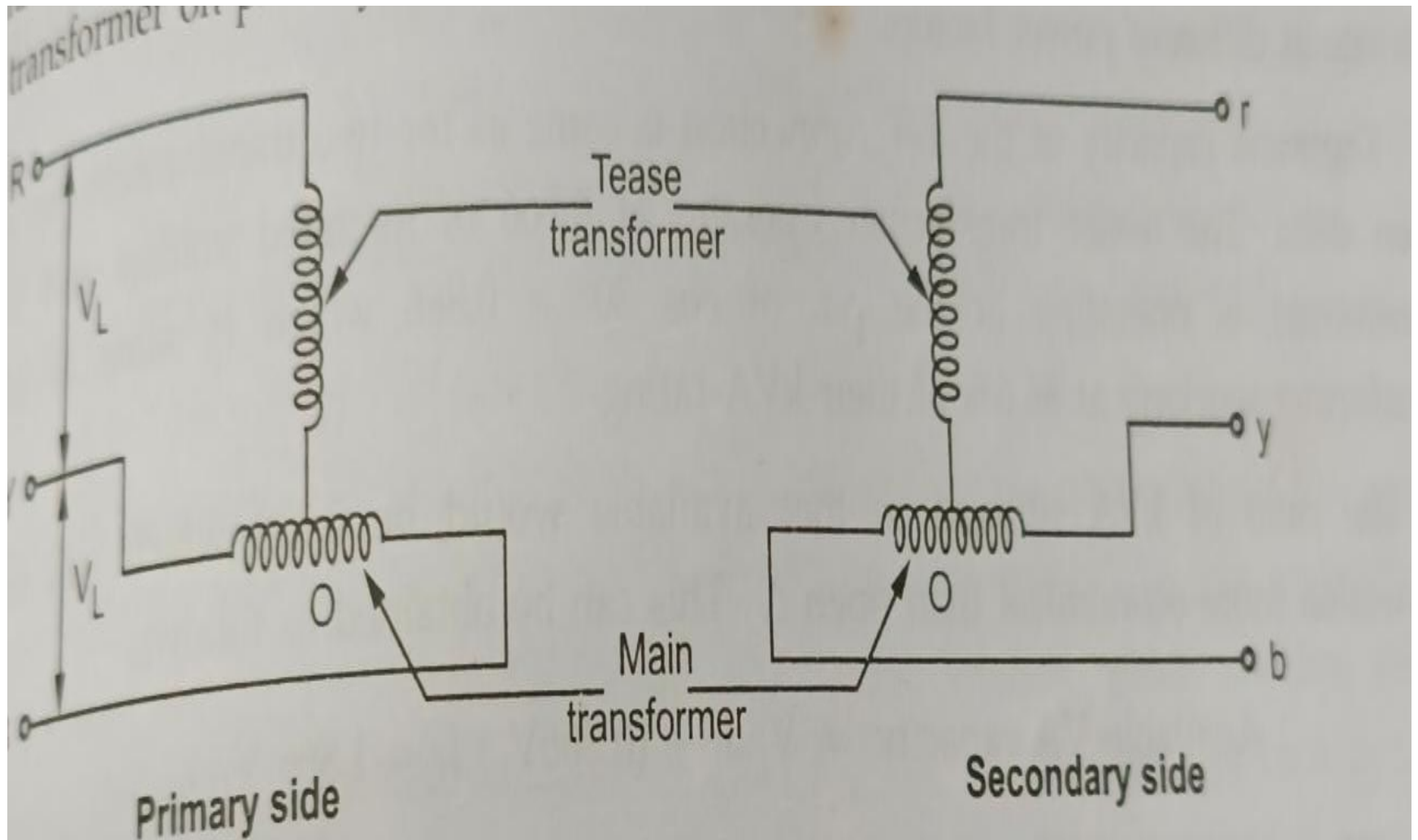

# T-T Connection

connection more economical


$$\text{Available VA capacity} = V_L I_L + (0.866 V_L) I_L = 1.866 V_L I_L$$

$$\text{VA actually utilized} = 1.732 V_L I_L \text{ since 3 phase power is supplied}$$


Taking the ratio of actual capacity to available capacity

$$\frac{\text{Actual capacity}}{\text{Available capacity}} = \frac{1.732 V_L I_L}{1.866 V_L I_L} = 0.928$$

# Scott Connection

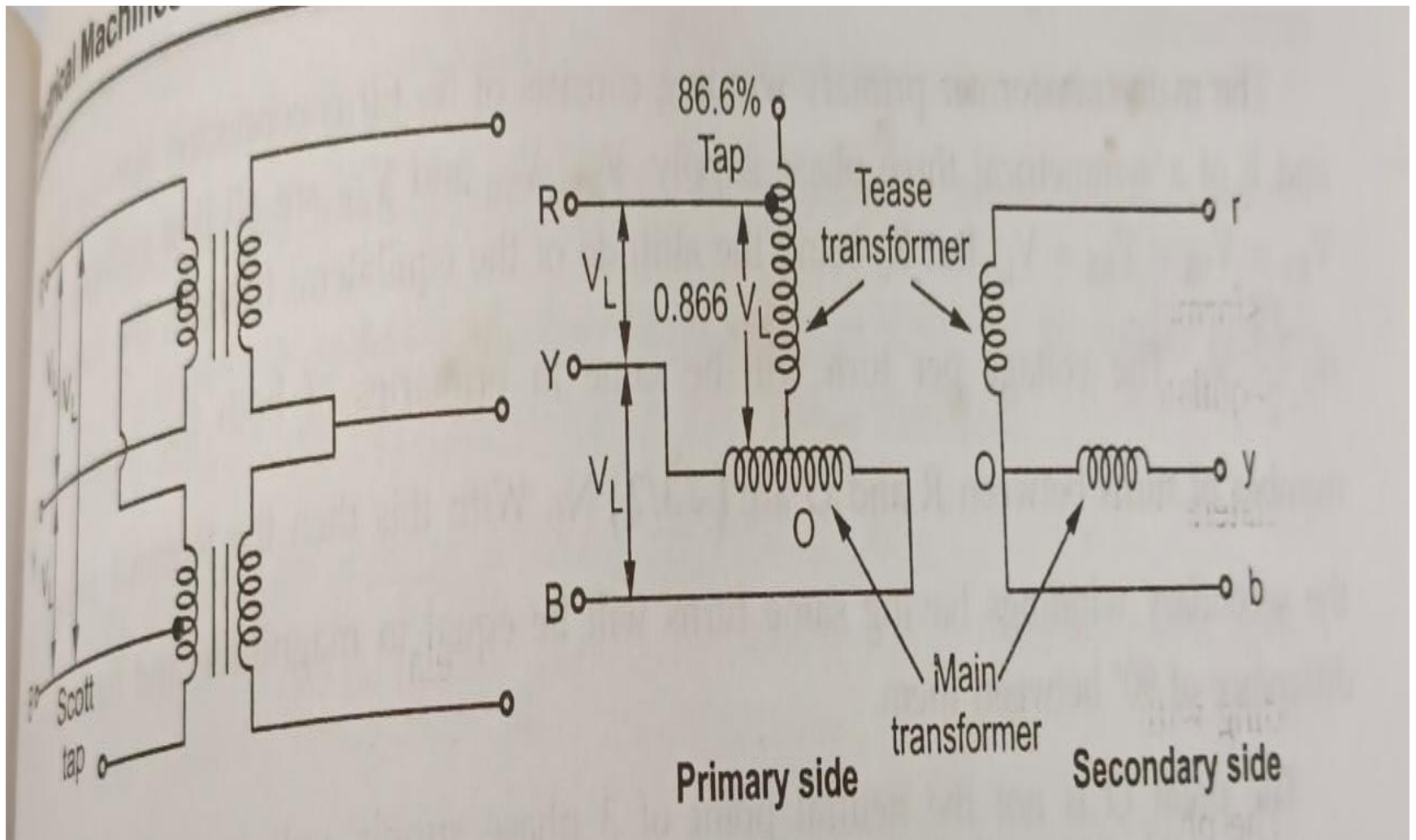


# Scott Connection

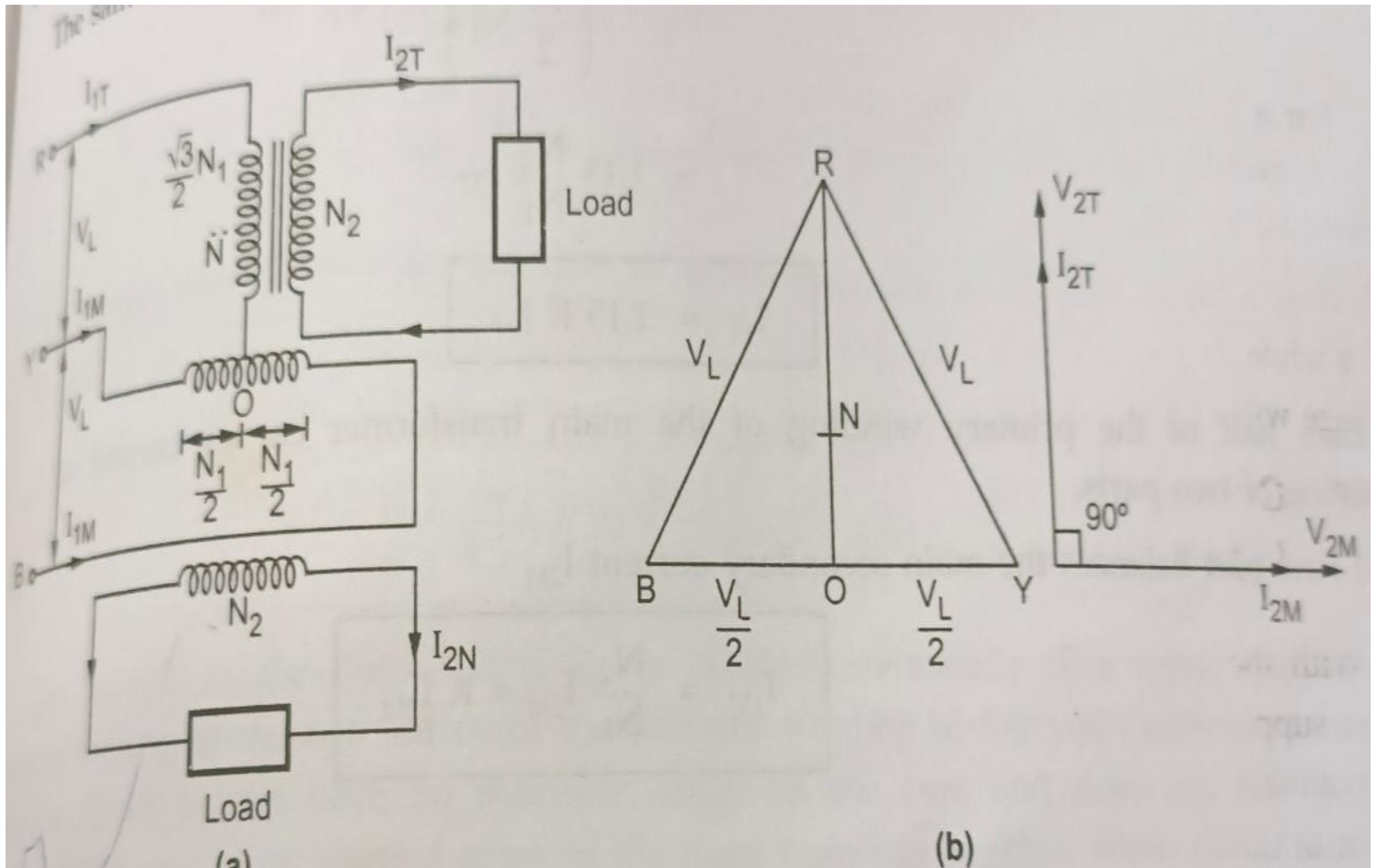



# Nomenclature of Transformer Phasor Groups

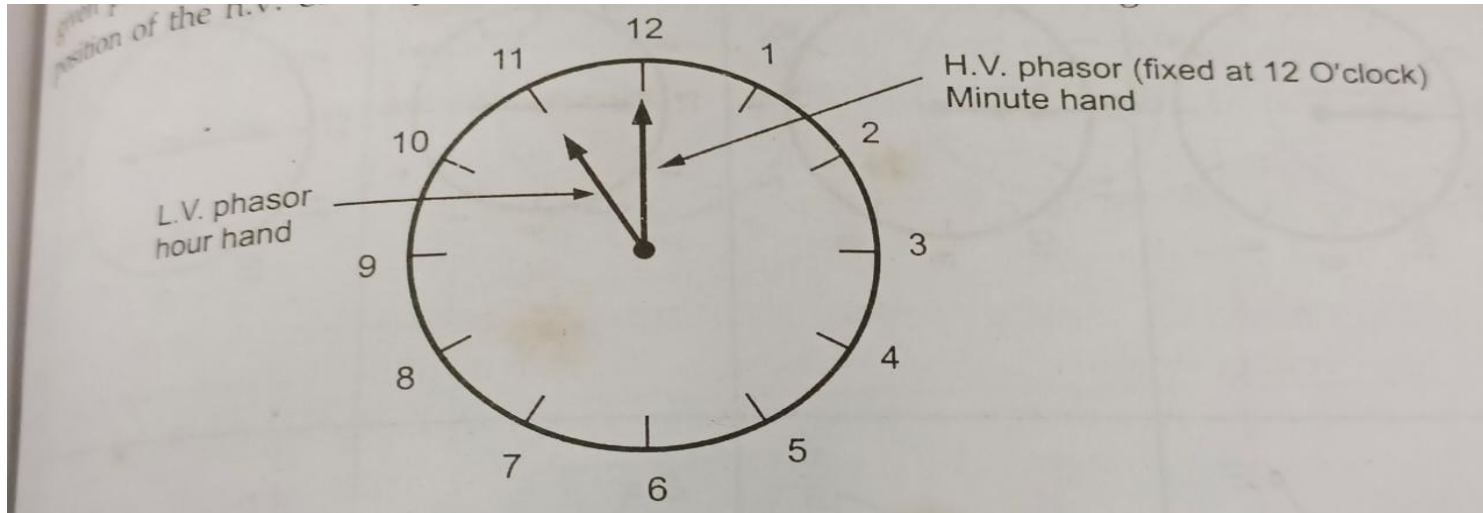

**Group 1 : Zero Displacement ( $Yy0, Dd0, Dz0$ )**

**Group 2 :  $180^\circ$  phase displacement ( $Yy6, Dd6, Dz6$ )**

**Group 3 :  $30^\circ$  lag phase displacement ( $Yd1, Dy1, Yz1$ )**

**Group 4 :  $30^\circ$  lead phase displacement ( $Yd11, Dy11, Yz11$ )**

# Nomenclature of Transformer Phasor Groups

| Sr. No. | Symbol        | Windings and terminals | EMF vector diagrams | Equivalent clock method representation |
|---------|---------------|------------------------|---------------------|--|
| 1.      | Y y 0<br>0°   |                        |                     |  |
| 2.      | D d 0<br>0°   |                        |                     |  |
| 3.      | Y y 6<br>180° |                        |                     |  |
| 4.      | D d 6<br>180° |                        |                     |  |

# Nomenclature of Transformer Phasor Groups

| Sr. No. | Symbol         | Windings and terminals | EMF vector diagrams | Equivalent clock method representation |
|---------|----------------|------------------------|---------------------|--|
| 5.      | D y 1<br>-30°  |                        |                     |  |
| 6.      | y d 1<br>-30°  |                        |                     |  |
| 7.      | D y 11<br>+30° |                        |                     |  |
| 8.      | Y d 11<br>+30° |                        |                     |  |