

Power Amplifier

Power Amplifier

POWER CALCULATION: Transistor Amplifier

In Transistor Amplifier, as all in sections both dc & ac current is flowing, so it has to be checked DC power & AC power are separable or not.

$$V(t) = V_{dc} + v(t)$$

$$I(t) = I_{dc} + i(t)$$

$$p = V(t) I(t) = \text{Instantaneous power}$$

$$P = \text{Average power} = \frac{1}{T} \int_0^T V(t) I(t) dt$$

$$= \frac{1}{T} \int_0^T [V_{dc} + v(t)] [I_{dc} + i(t)] dt$$

$$= \frac{1}{T} \int_0^T V_{dc} I_{dc} dt + \frac{1}{T} \int_0^T V_{dc} \underbrace{i(t) dt}_0 + \frac{1}{T} \int_0^T I_{dc} \underbrace{v(t) dt}_0 + \frac{1}{T} \int_0^T v(t) i(t) dt$$



$$= V_{dc} I_{dc} + \frac{1}{T} \int_0^T v(t) i(t) dt$$

$$P = P_{dc} + P_{ac}$$

- So they are separable. For power calculation ac power can be considered only.

Power Amplifier

For Small signal transistor amplifier

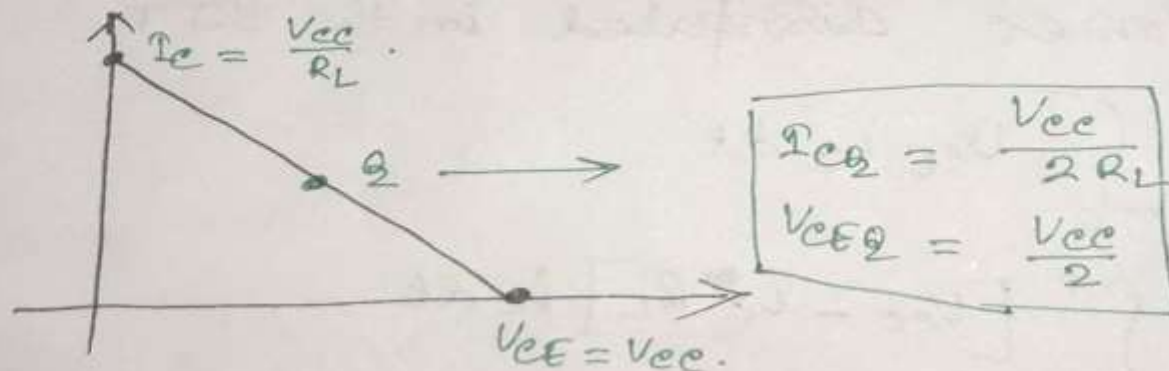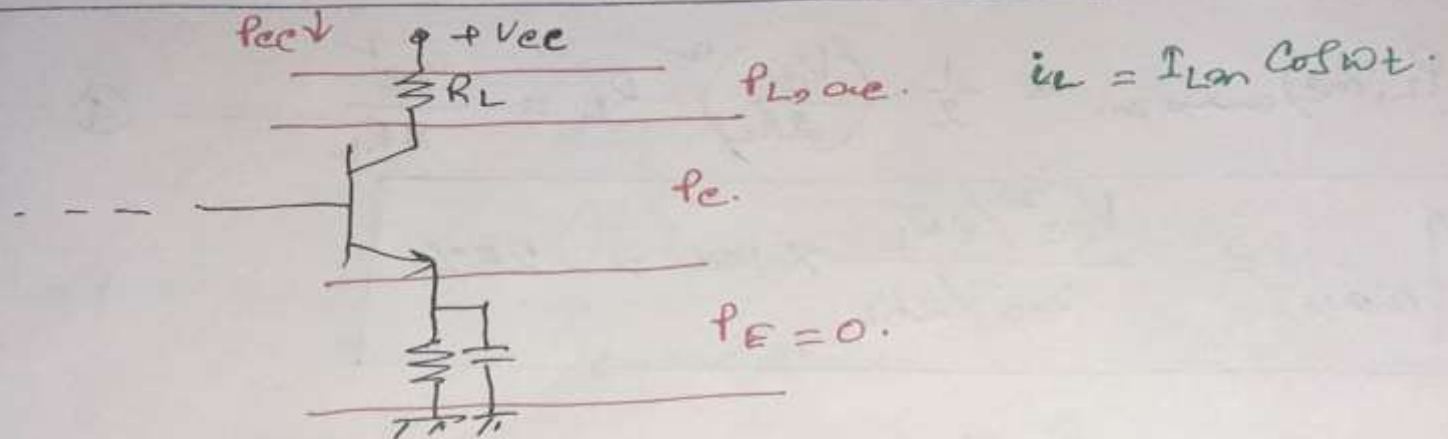

Power Amplifier

Power Calculations

$$\begin{aligned} P_{cc} &= \text{Power Supplied to the amplifier} \\ &= V_{cc} \cdot I_{C2} = \frac{V_{cc}^2}{2 R_L} \quad \dots \quad (1) \end{aligned}$$

$$\begin{aligned} P_{L,ae} &= \frac{1}{T} \int_0^T i_L^2 dt \cdot R_L = \text{load power dissipation} \\ &= \frac{1}{T} \int_0^T I_{Lm}^2 \cos^2 \omega t d(\omega t) \cdot R_L \end{aligned}$$

$$P_{L,ae} = \frac{1}{2} I_{Lm}^2 R_L \quad \dots \quad (2)$$

$$\eta = \frac{P_{L,ae}}{P_{cc}} = \text{Efficiency} = \frac{\frac{1}{2} I_{Lm}^2 R_L}{V_{cc}^2 / 2 R_L} \quad \dots \quad (3)$$

Power Amplifier

$P_{L,ac}$ will be max. when $I_{Lm} = \text{max. } I_{cq}$

$$(P_{L,ac})_{\text{max.}} = \frac{1}{2} \cdot \left(\frac{V_{cc}}{2R_L} \right)^2 \cdot R_L = \frac{V_{cc}^2}{8R_L} \quad \dots \quad (4)$$

$$\boxed{\eta_{\text{max.}} = \frac{V_{cc}^2/8R_L}{V_{cc}^2/2R_L} \times 100 = 25\%}$$

P_c = power dissipated in the BJT

$$= \frac{1}{T} \int_0^T V_{ce} i_c dt$$

$$= \frac{1}{T} \int_0^T [V_{cc} - i_c R_L] i_c dt$$

$$= \frac{1}{T} \int_0^T V_{cc} i_c dt - \frac{1}{T} \int_0^T i_c^2 R_L dt$$

$$\cancel{P_c} = \frac{1}{T} \int_0^T V_{cc} (I_{cq} + i_c) dt - \frac{1}{T} \int_0^T [I_{cq} + i_c]^2 R_L dt$$

$$= V_{cc} \cdot I_{cq} - I_{cq}^2 R_L - \frac{1}{T} \int_0^T i_c^2 R_L dt$$

$$P_c = \frac{V_{cc}^2}{2R_L} - \frac{V_{cc}^2}{4R_L} - \frac{1}{2} I_{Lm}^2 R_L$$

$$\therefore \boxed{P_c = \frac{V_{cc}^2}{4R_L} - \frac{1}{2} I_{Lm}^2 R_L} \quad \dots \quad (5)$$

Power Amplifier

P_c will be maxm. when $I_{Lm} = 0$.

$$\therefore (P_c)_{\max.} = \frac{V_{cc}^2}{4R_L}$$

$$\text{Figure of merit} = \frac{(P_c)_{\max.}}{(P_{L,ac})_{\max.}} = \frac{V_{cc}^2/4R_L}{V_{cc}^2/8R_L} = 2$$

Disadvantage

- ① $\eta_{\max} = 25\%$
- ② High Figure of merit
- ③ Power consumption by the transistor is maxm. when the i/p is zero.


Advantage.

This is the linear amplifier
i.e. O/P \propto i/p.

* The disadvantages are acceptable for small signal transistor amplifier, but for large signal improvements are necessary. For large signal amplifier this is known as Class A Amplifier.

Power Amplifier

Transformer Coupled class A Amplifier

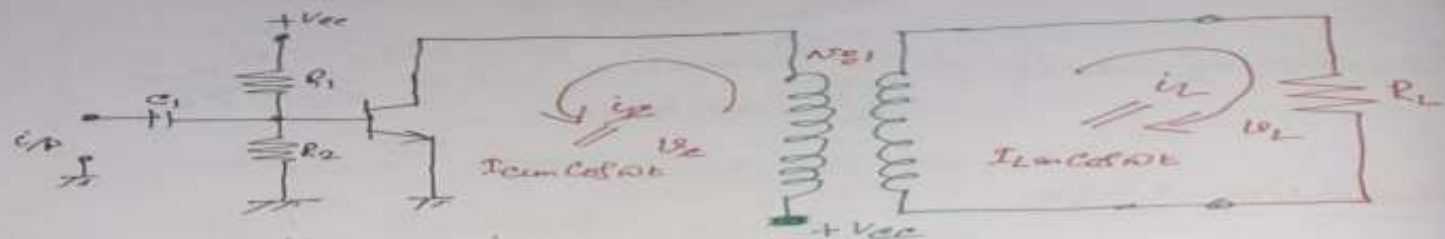

$$N = \frac{V_{ce}}{V_L} = \frac{I_L}{I_{cq}}$$

$$R_L = \frac{V_L}{I_L} = \frac{V_{ce}/N}{N I_{cq}} = \frac{1}{N^2} \left(\frac{V_{ce}}{I_{cq}} \right) \rightarrow R_L'$$

(Reflected impedance)

$$R_L' = N^2 R_L$$

$$P_{cc} = \text{Power Supplied} = V_{cc} \cdot I_{cq} = V_{cc} \cdot \frac{V_{cc}}{R_L'} = \frac{V_{cc}^2}{R_L'} \quad \text{--- (1)}$$

$$P_{L,ac} = \text{Load Power Dissipation} = \frac{1}{2} I_{Lm}^2 R_L$$

$$= \frac{1}{2} I_{cm}^2 R_L' \quad \text{--- (2)}$$

$$(P_{L,ac})_{max} = \frac{V_{cc}^2}{2 R_L'} \quad \text{--- (3)}$$

$$\eta_{max} = \frac{V_{cc}^2 / 2 R_L'}{V_{cc}^2 / R_L'} \times 100 = 50\%$$

Improvement

Power Amplifier

$$P_c = \frac{V_{cc}^2}{R_L'} - \frac{1}{2} I_{Lm}^2 \cdot R_L$$

$$(P_c)_{max} = \frac{V_{cc}^2}{R_L'} \quad \dots \dots \textcircled{4}$$

↓
maxm. power is consumed by the transistor when the i_p is zero

no improvement


↓

$$\text{Figure of merit} = \frac{(P_c)_{max}}{(P_{L,ac})_{max}}$$

$$= \frac{V_{cc}^2 / R_L'}{V_{cc}^2 / 2R_L'} = 2 \quad \text{no improvement}$$

Power Amplifier

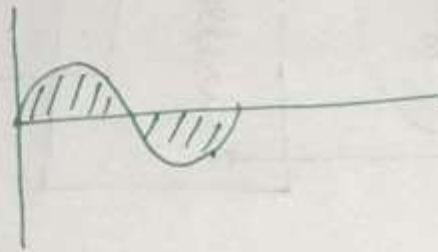
Since power consumed by the BJT is high, [moreover it is unwanted thus known as conduction loss]
Here transistor is always on




Conduction
Range = 0 to 360°

Power Amplifier

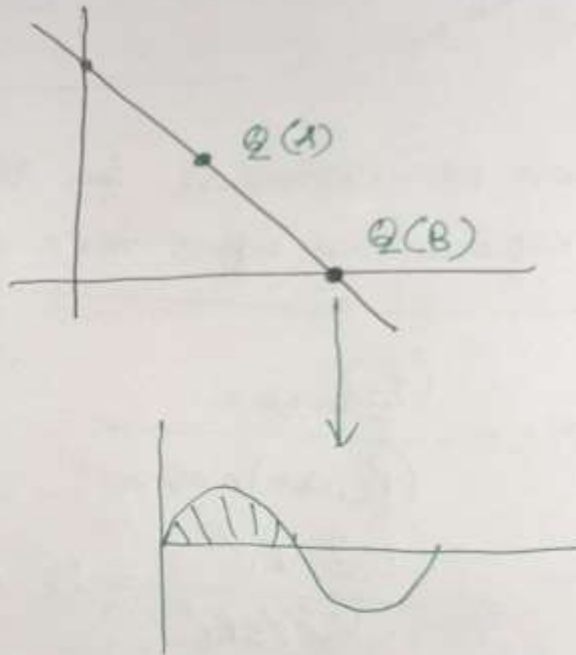In order to reduce P_c i.e. conduction loss
let us reduce conduction time or conduction
angle of transistor




Power Amplifier

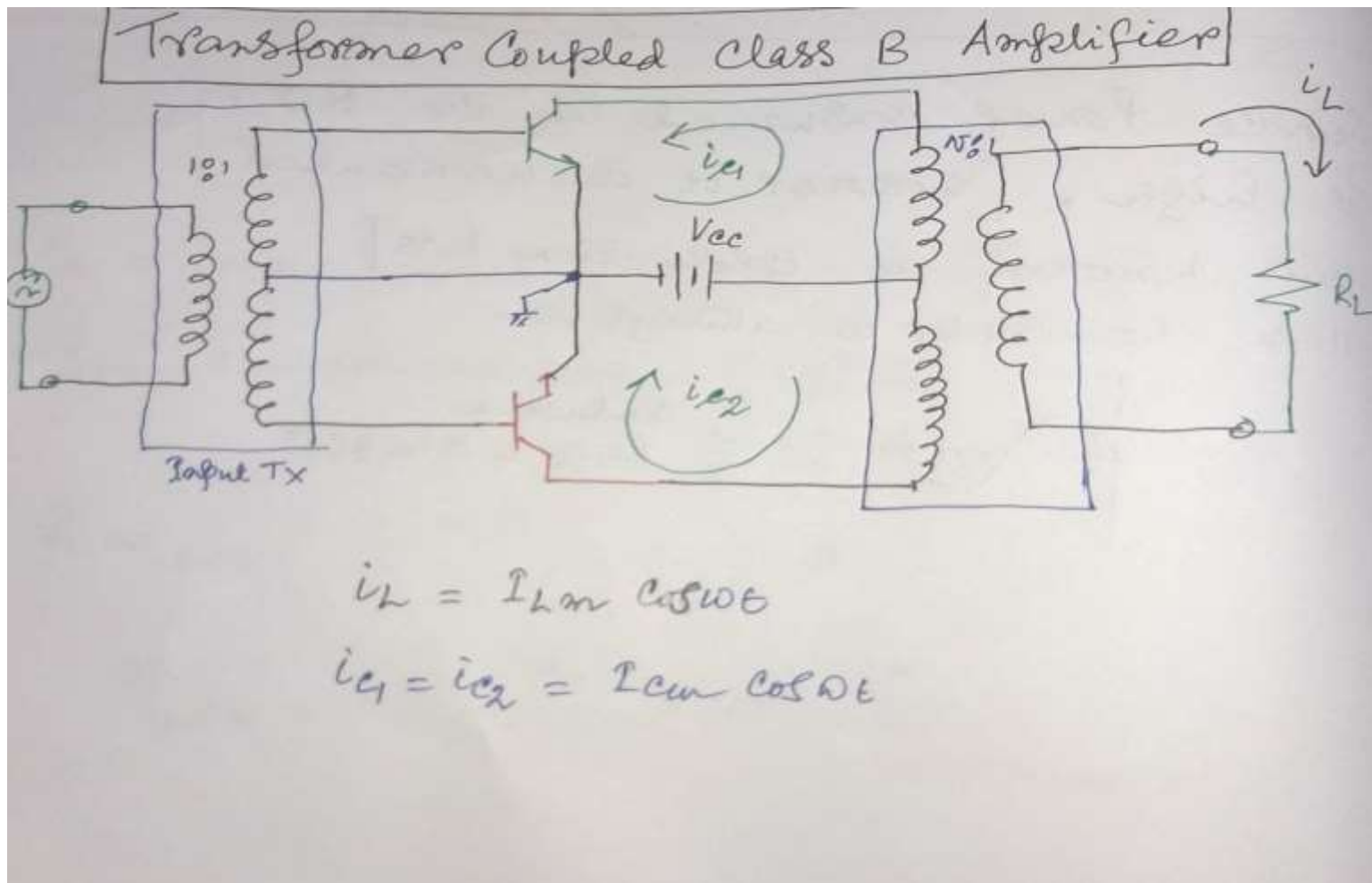

Power Amplifier

Current Characteristics.

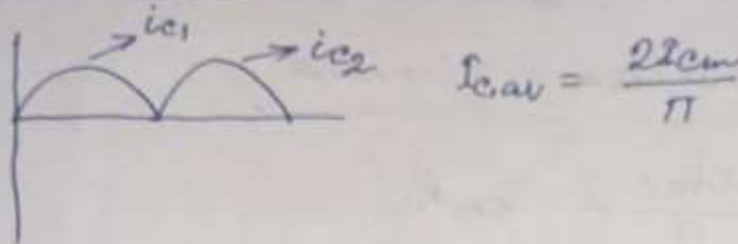

P_{cc} = Power Supplied to the Amplifier

$$= V_{cc} \cdot I_c = V_{cc} \cdot \frac{2I_{cm}}{\pi} \dots \dots \dots \textcircled{1}$$

$$(P_{cc})_{max} = V_{cc} \cdot \frac{2V_{cc}}{\pi R_L'}$$

$$\left[\begin{aligned} I_{cm} &= I_{CQ} \\ &= \frac{V_{cc}}{R_L'} \end{aligned} \right]$$

$$\boxed{(P_{cc})_{max} = \frac{2V_{cc}^2}{\pi R_L'}} \dots \dots \dots \textcircled{2}$$

Power Amplifier

$$(P_{L,ac})_{\text{max}} = \frac{1}{2} I_{Lm}^2 R_L$$
$$= \frac{1}{2} I_{cm}^2 R_L'$$

$$(P_{L,ac})_{\text{max}} = \frac{1}{2} \cdot \frac{V_{cc}^2}{R_L'^2} \cdot R_L' = \frac{V_{cc}^2}{2R_L'} \dots \textcircled{3}$$

$$\eta_{\text{max}} = \frac{(P_{L,ac})_{\text{max}}}{(P_{cc})_{\text{max}}} \times 100 = \frac{V_{cc}^2/2R_L'}{2V_{cc}^2/\pi R_L'} \times 100$$

$$= \frac{\pi}{4} \times 100$$

$$= 78.5\% \text{ Improvement}$$

Power Amplifier

$$P_c = \frac{2V_{cc}I_{cm}}{\pi} - \frac{1}{2}I_{cm}^2 R_L'$$

Use to find max. efficiency

$$\frac{dP_c}{dI_{cm}} = 0 = \frac{2V_{cc}}{\pi} - I_{cm} R_L'$$

$$\therefore I_{cm} = \frac{2V_{cc}}{\pi R_L'}$$

$$\therefore (P_c) = \frac{2V_{cc}}{\pi} \cdot \frac{2V_{cc}}{\pi R_L'} - \frac{1}{2} \cdot \frac{4V_{cc}^2}{\pi^2 R_L'} \cdot R_L'$$

$$= \frac{4V_{cc}^2}{\pi^2 R_L'} - \frac{2V_{cc}^2}{\pi^2 R_L'}$$

$$(P_c)_{max} = \frac{2V_{cc}^2}{\pi^2 R_L'}$$

$$\text{Figure of merit} = \frac{(P_c)_{max}}{(P_{L,ac})_{max}} = \frac{2V_{cc}^2/\pi^2 R_L'}{V_{cc}^2/2R_L'}$$


$$= \frac{4}{\pi^2} \approx \frac{2}{5} \quad \text{Improvement}$$

When $i/p = 0$, $I_{cm} = 0$.

So $P_c = 0$. . . Improvement.

Power Amplifier



Crossover Distortion

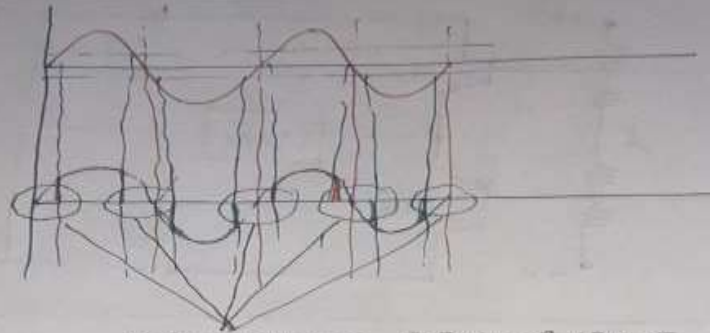


CROSSOVER DISTORTION

To solve this problem both the transistors should be slightly biased from the beginning


Class A Amplifier

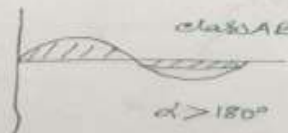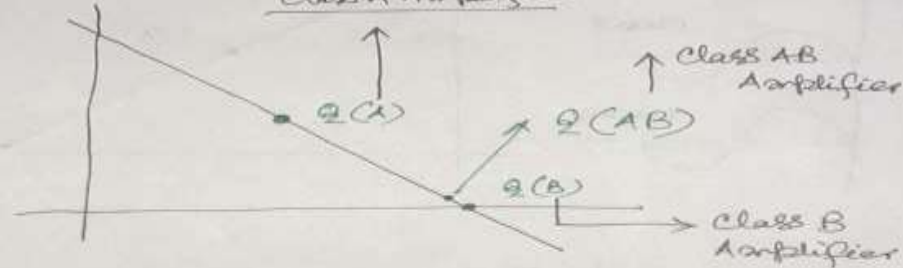



Power Amplifier

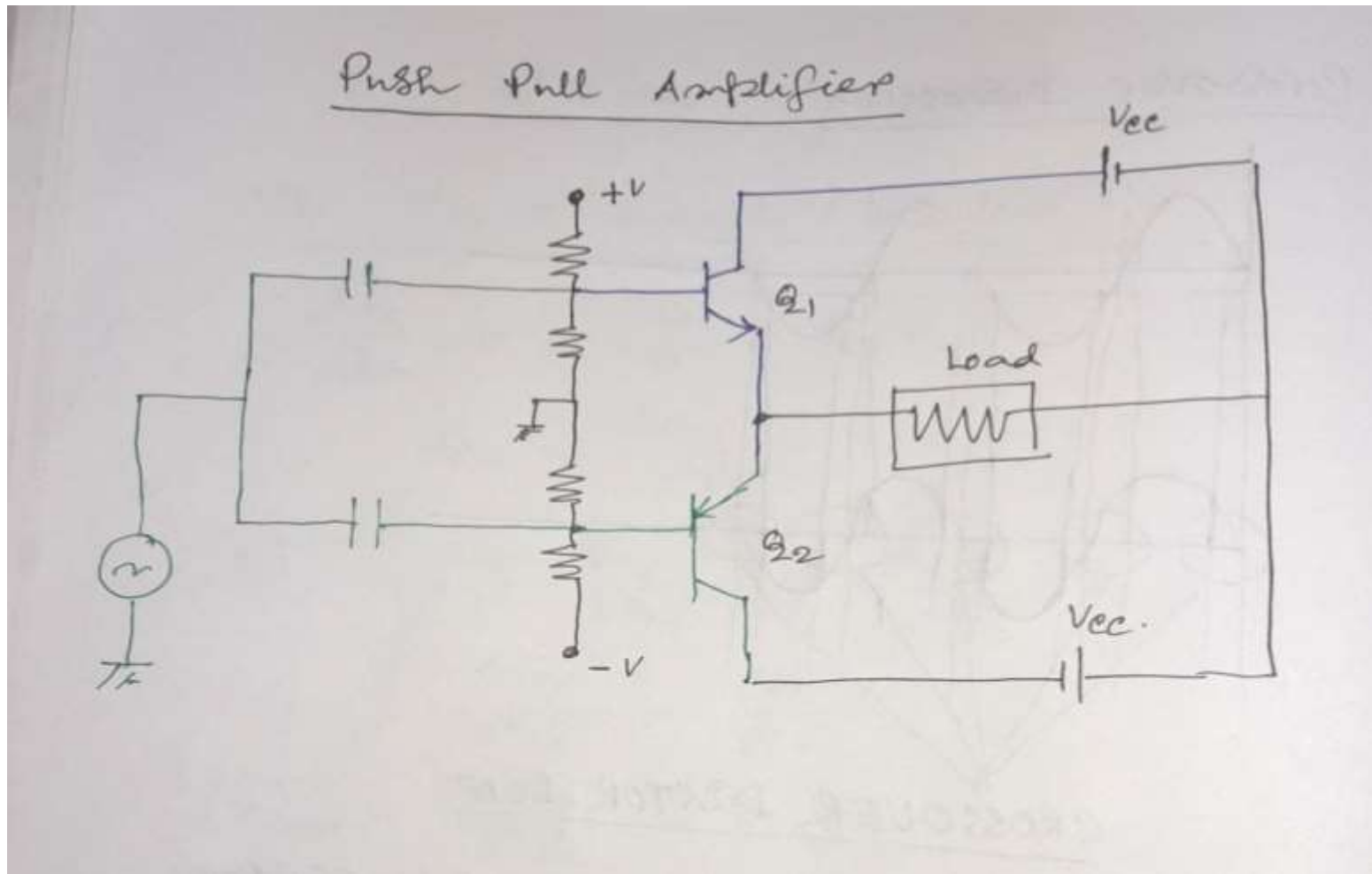

Power Amplifier

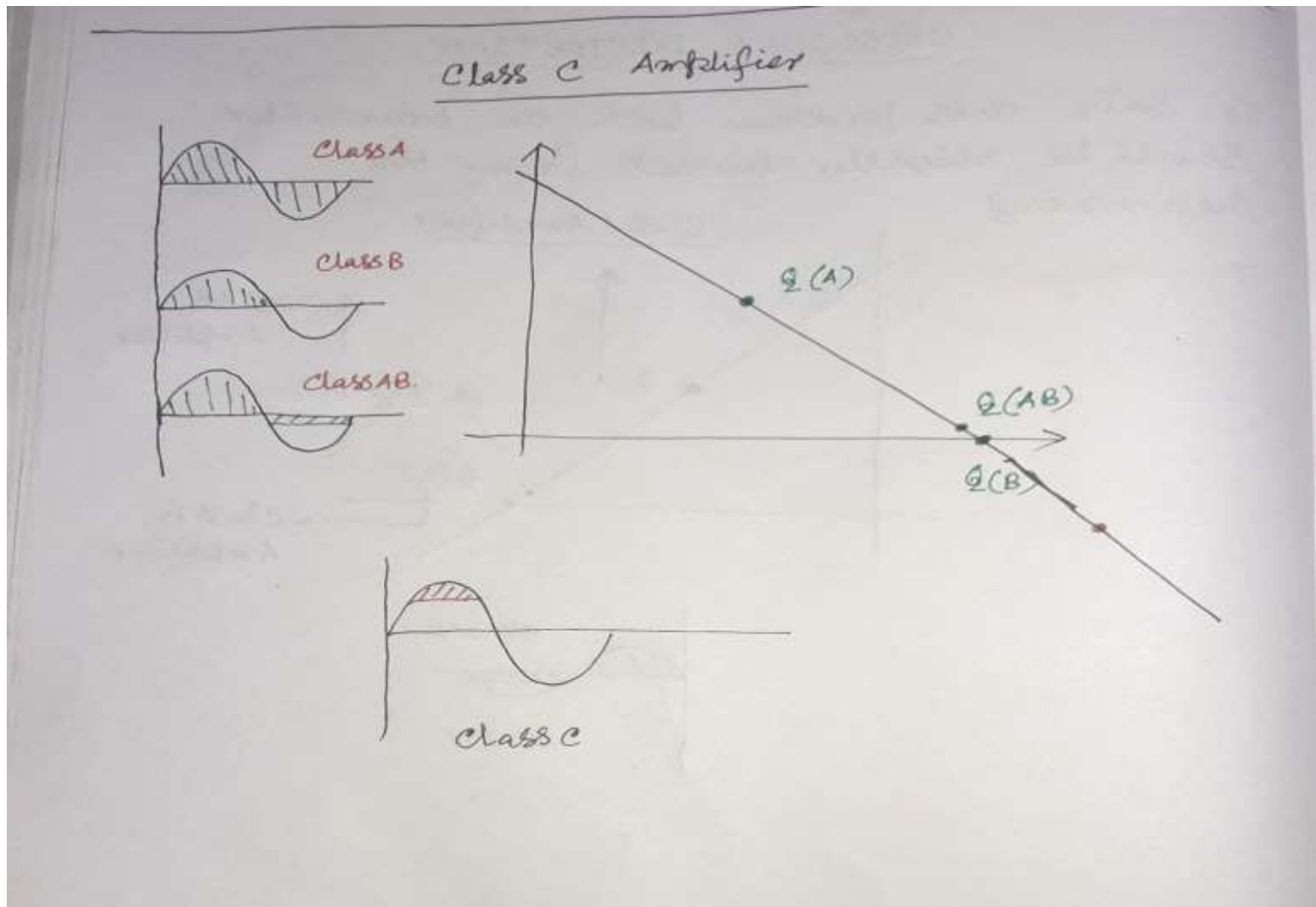

Power Amplifier

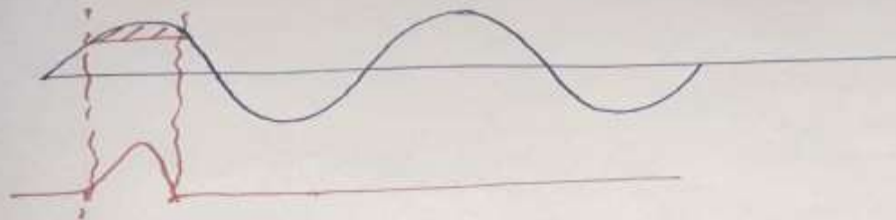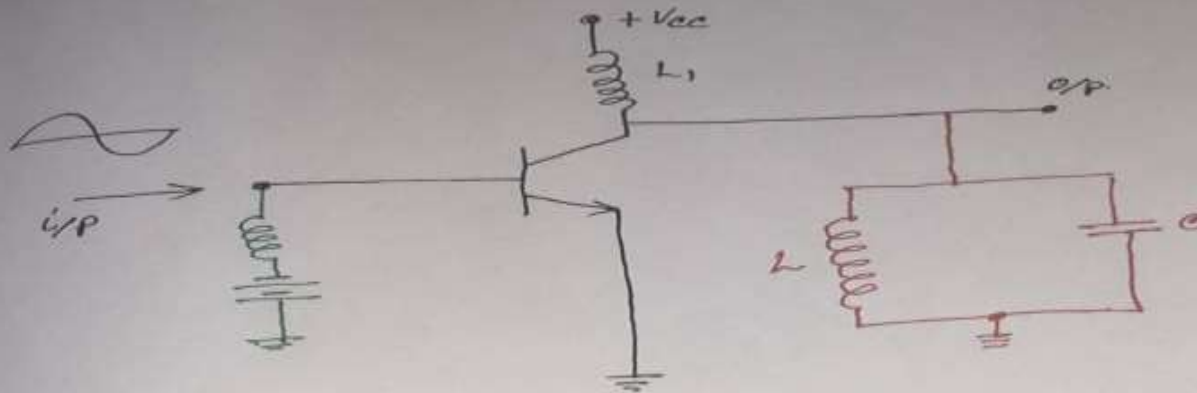

$$L \frac{di}{dt} + \frac{1}{C} \int i dt = V$$

Solve & find out the solution