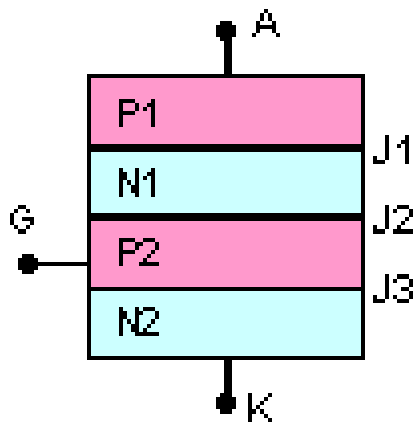


*Thyristor Characteristics, Two  
Transistor Model Of Thyristor &  
Thyristor Turn On And Off.*

# Thyristor Characteristics.

- A thyristor is a four layer, semiconductor device of p-n-p-n structure with three p-n junctions J1, J2 & J3 respectively.
- It has three terminals, the anode, cathode and the gate.

## Simplified Model Of SCR



## SCR Symbol



# CONTI.....

## Forward blocking or off state condition.

- ❖ Anode voltage is made +ve w.r.t. cathode, the junctions  $j_1$  &  $j_3$  are forward biased.
- ❖ Junction  $j_2$  becomes reverse biased & only small leakage current flows.
- ❖ The SCR is then said to be in the forward blocking or off state.


## Forward breakdown voltage $V_{bo}$ .

- ❖ If  $V_{ak}$  is further increased  $j_2$  will breakdown due to avalanche effect resulting in a large current through the device.
- ❖ The corresponding voltage is called the forward breakdown voltage  $V_{bo}$ .
- ❖ Now, the device is in forward conduction or ON state.


# CONTI.....

*Forward blocking or off state condition.*

*Forward breakdown voltage*

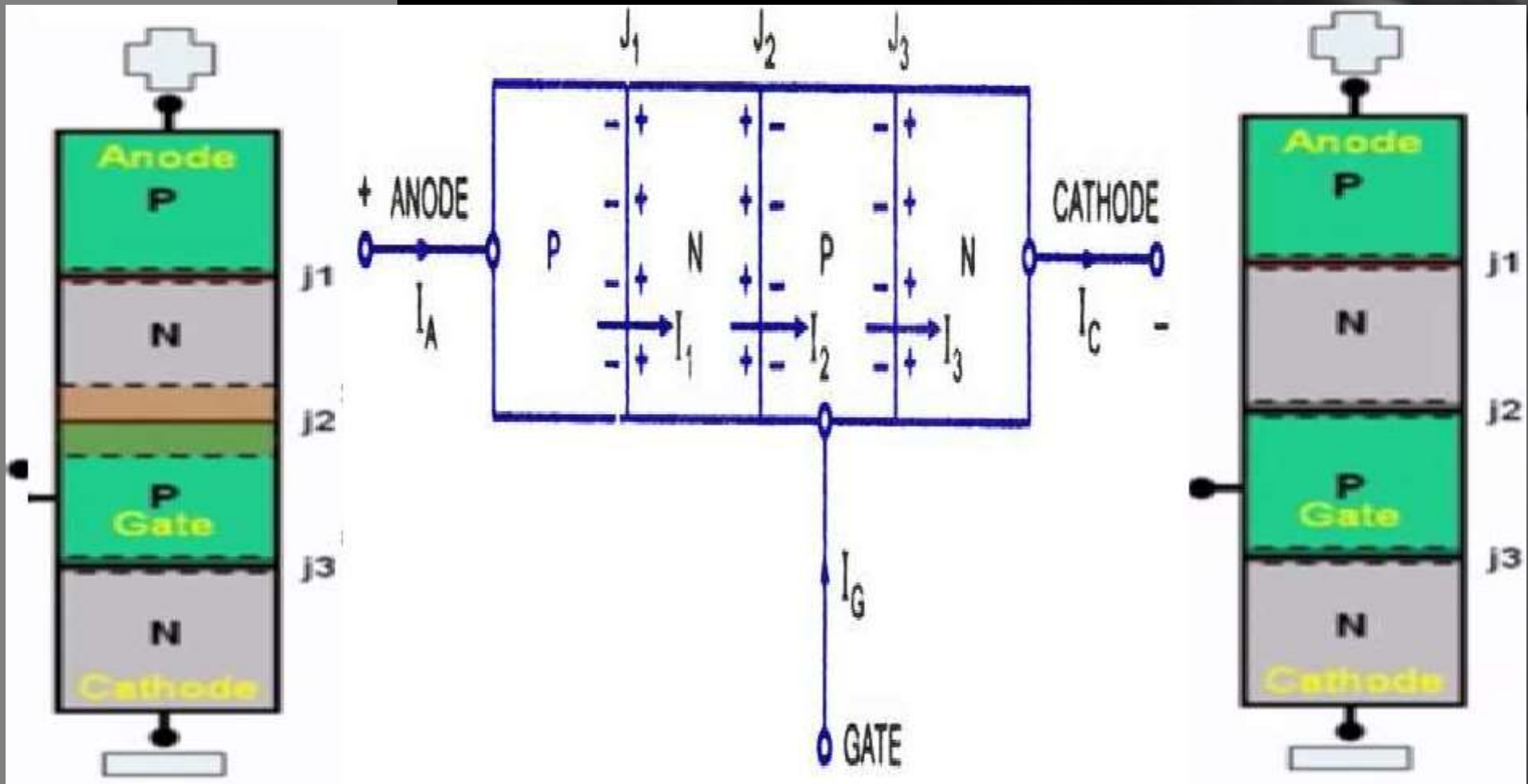

# Ideal Characteristic Of SCR

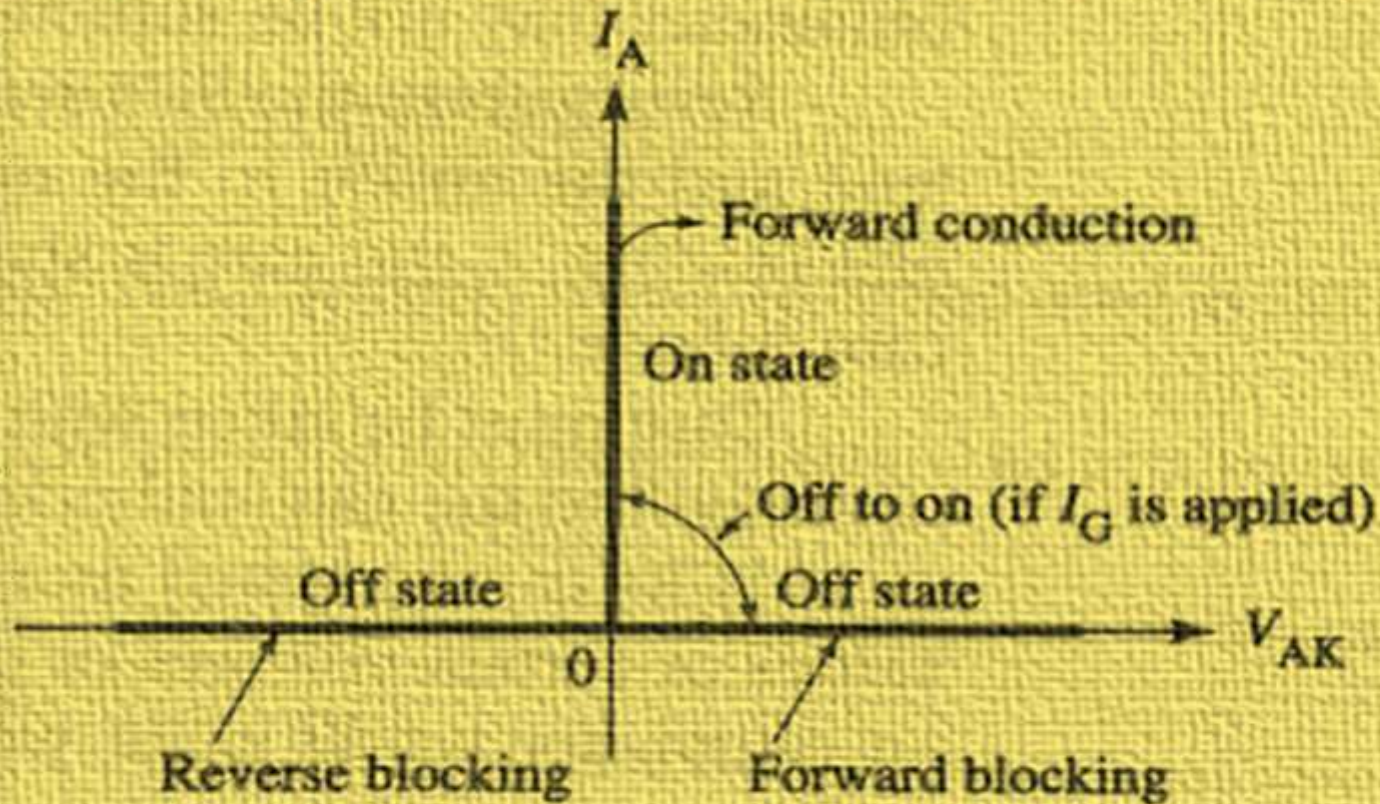




# V-I Characteristics

## Latching Current $I_L$

- After the SCR has switched on, there is a minimum current required to sustain conduction.
- This current is called the latching current  $I_L$ .
- Usually  $I_L$  is associated with turn ON of the device.
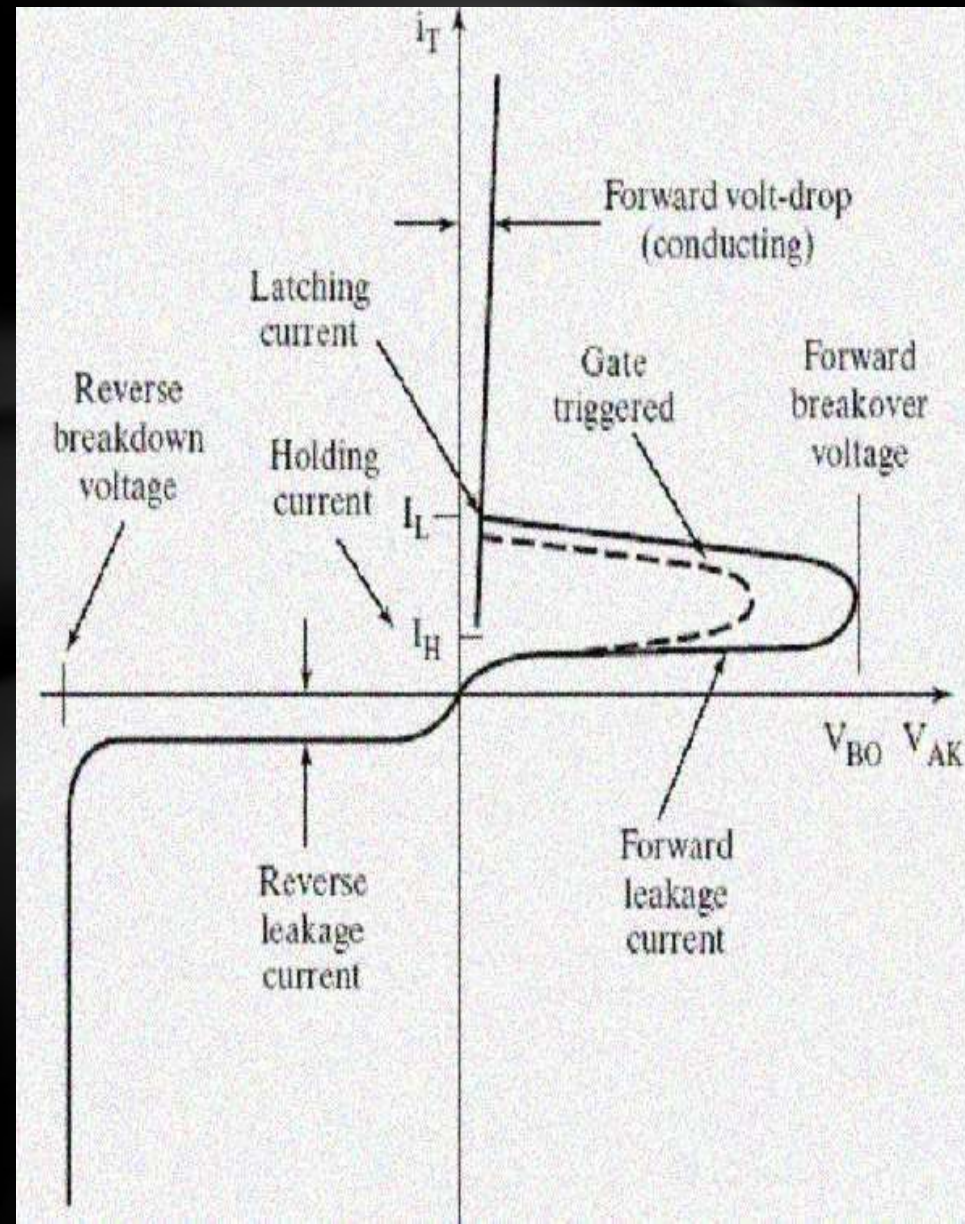
## Holding Current $I_H$


- SCR returns in its original off state if anode current falls below low level called holding current  $I_H$ .
- So, holding current  $I_H$  is minimum anode current to maintain thyristor in on state.
- Usually  $I_H$  is associated with turn off of the device.



# V-I Characteristics
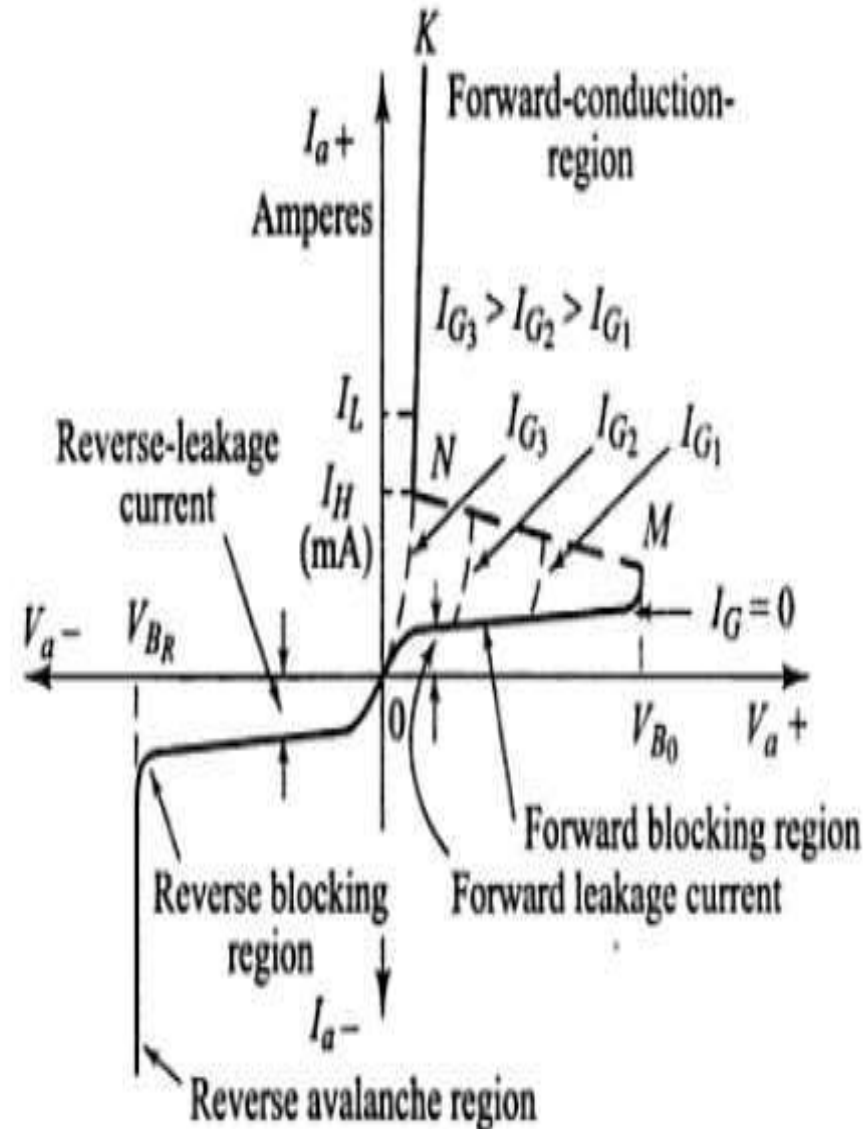
## Effects of gate current on $V_{bo}$ .

- ❑ If gate signal is applied, the thyristor turn on before  $V_{bo}$  is reached.
- ❑ So, forward voltage depends upon magnitude of gate current.
- ❑ Higher the gate current lower the forward breakover voltage.
- ❑ The typical gate current magnitudes are of order of 20 to 200mA.




# Thyristor Gate Characteristics

- $I_g(\text{max})$  and  $V_g(\text{max})$  are the maximum gate current and voltages that can flow through the thyristor without damaging it .
- $V_g(\text{min})$  and  $I_g(\text{min})$  are minimum gate voltage and current, below which thyristor will not be turned-on.
- Hence to turn-on the thyristor successfully

$$I_g(\text{min}) < I_g < I_g(\text{max})$$
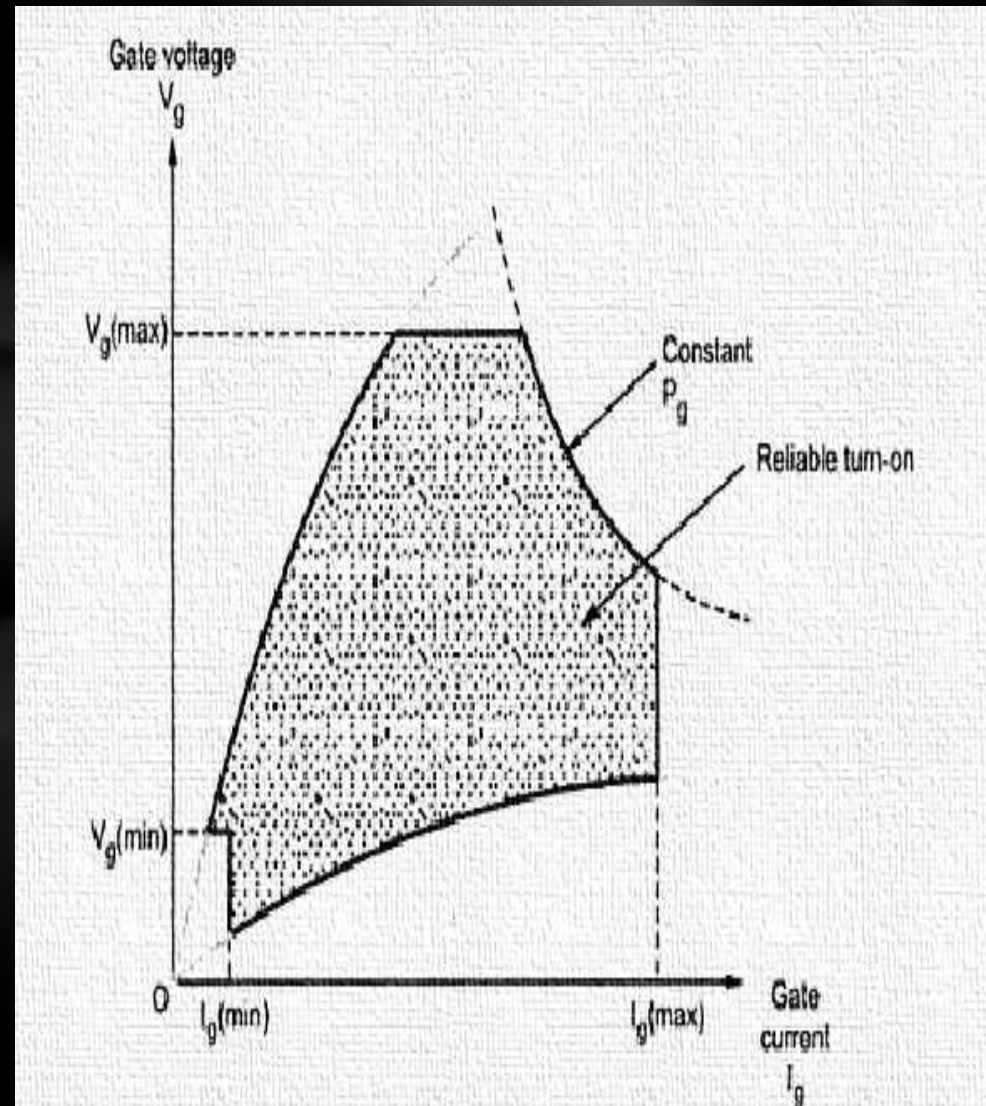
$$V_g(\text{min}) < V_g < V_g(\text{max})$$







# Two Transistor Model Of Thyristor

- The operation of thyristor can also be explained in a simple way by two transistor analogy.
- One transistor is pnp and second is npn.
- The collector of one is attached with base of other & vice versa.

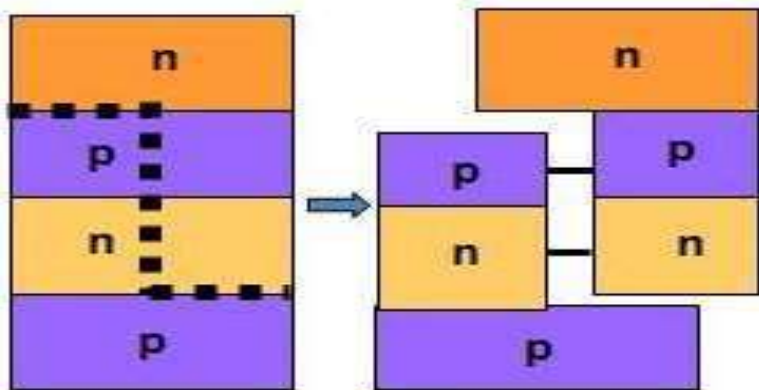**Splitting Thyristor into Two Transistors**



**Two transistor model of Thyristor**

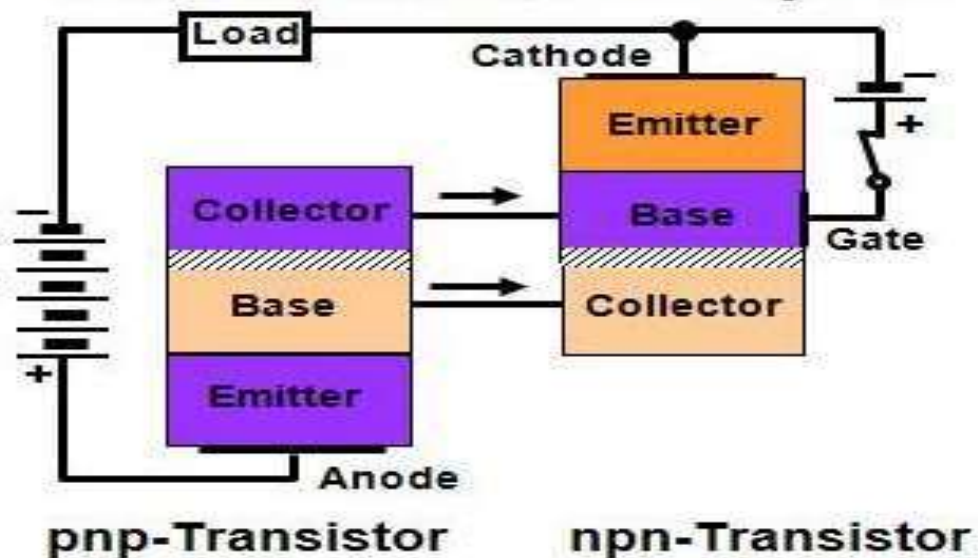

# CONTI.....

As from fig.b

## Derivation for anode current

General transistor equation is

$$I_C = \alpha I_E + I_{CBO}$$

For transistor 1

## General transistor equation is

$$I_C = \alpha I_E + I_{CBO} \quad I_{E1} = I_A$$


For transistor 2

$$I_{C2} = \alpha_2 I_{E2} + I_{CBO2};$$

$$I_{E2} = I_K \quad \text{and} \quad I_K = I_A + I_G$$

There fore      There fore
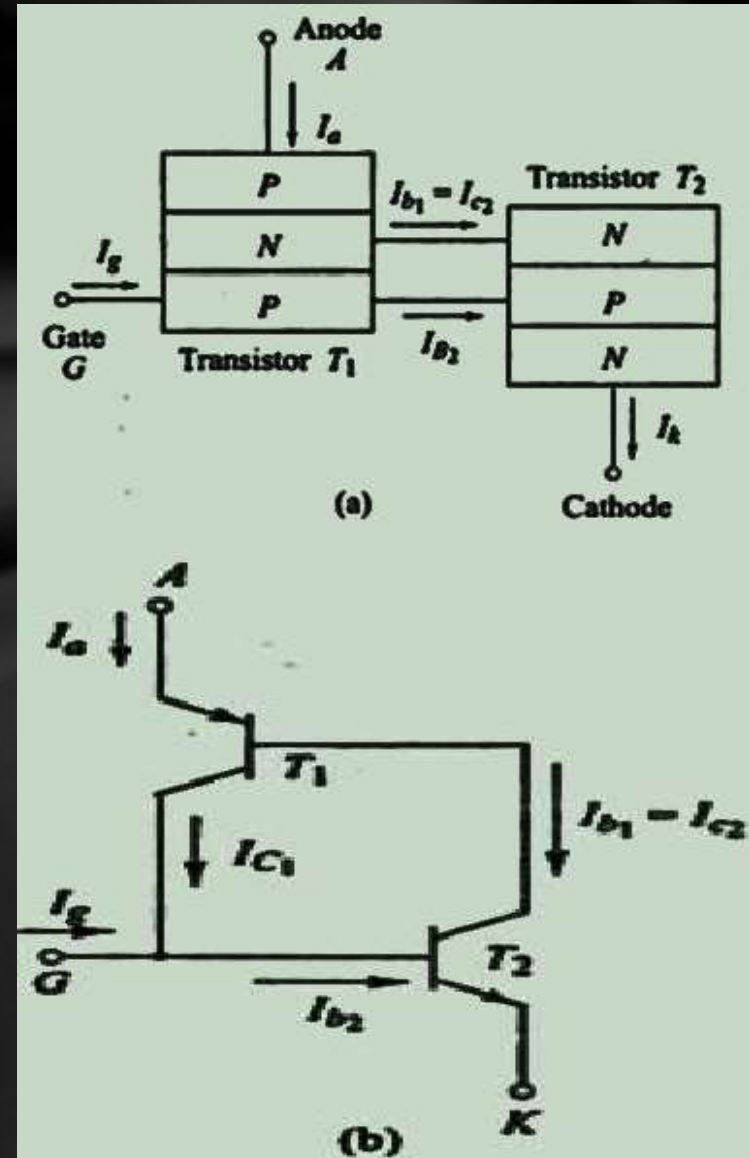
$$I_A = I_{C1} + I_{C2} \quad I_A = I_{C1} + I_{C2}$$




# CONTI.....

$$I_A = \alpha_1 I_A + I_{CBO1} + \alpha_2 (I_A + I_G) + I_{CBO2}$$

$$\therefore I_{C_2} = I_{B_1}$$
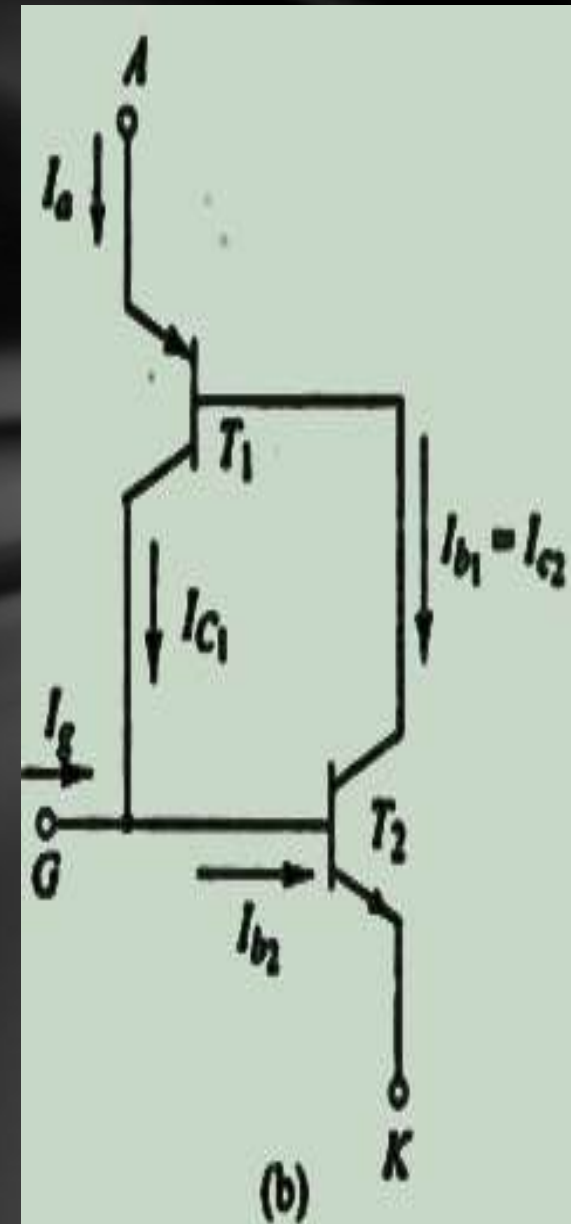
$$\Rightarrow I_A = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$




# CONTI.....

- ❑ If in equation
- ❑  $\alpha_1 + \alpha_2 = 1$
- ❑  $I_a = \infty$
- ❑ SCR suddenly latches to the ON state from OFF state condition
- ❑ This characteristic of device is called regenerative action.



# Two transistor model

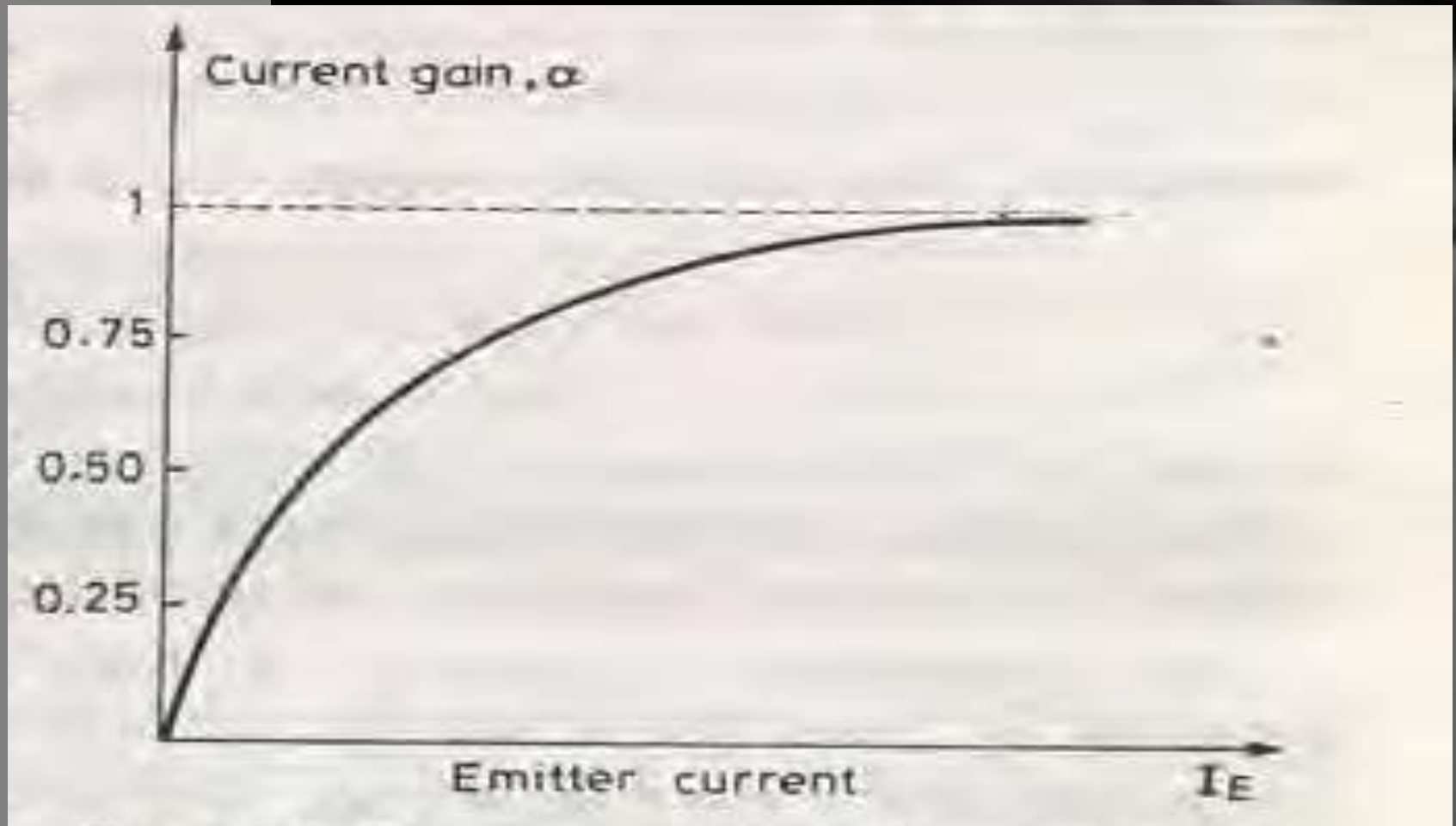

# Latching action of SCR

⑦

$$I_{C1} = \beta_1 I_{B1}$$

$$I_{C1} = I_{B2}$$

$$I_{C2} = \beta_1 \beta_2 I_{B1}$$

$$I_A \approx I_{C1} + I_{C2}$$

$$I_{C2} = I_{B1}$$

$$I_{C1} = \beta_1^2 \beta_2 I_{B1}$$

$$I_{C2} = \beta_1^2 \beta_2^2 I_{B1}$$

$$I_{C2} = \beta_1^2 \beta_2^2 I_{B1}$$

# Thyristor turn on Methods

The turning on Process of the SCR (turning the SCR from Forward-Blocking state to Forward-Conduction state )is known as Triggering.

The various SCR triggering methods are

- Forward Voltage Triggering
- Thermal or Temperature Triggering
- Radiation or Light triggering
- $dv/dt$  Triggering
- Gate Triggering

# CONTI.....

## Thermal Triggering (Temperature Triggering):

- Depletion layer of SCR decreases with increase in junction temp.
- In SCR when  $V_{ak}$  is very near its breakdown voltage, the device is triggered by increasing the junction temperature.
- By increasing the junction temperature the reverse biased junction collapses thus the device starts to conduct

## Radiation Triggering (or) Light Triggering

- For light triggered SCRs a special terminal niche is made inside the inner P layer instead of gate terminal.
- When light is allowed to strike this terminal, free charge carriers are generated.
- When intensity of light becomes more than a normal value, the thyristor starts conducting.
- This type of SCRs are called as LASCR



# dv/dt Triggering.

Junction J2 behaves as a capacitor, due to the charges existing across the junction.

If voltage across the device is  $V$ , the charge by  $Q$  and capacitance by  $C$  then

□  $i_c = dQ/dt$

$Q = CV$


□  $i_c = d(CV) / dt$

$$i_c = C \cdot \frac{dV}{dt} + V \cdot \frac{dC}{dt}$$

□  $dC/dt = 0$  ( $C = \text{constant}$ )

$i_c = C \cdot dV/dt$

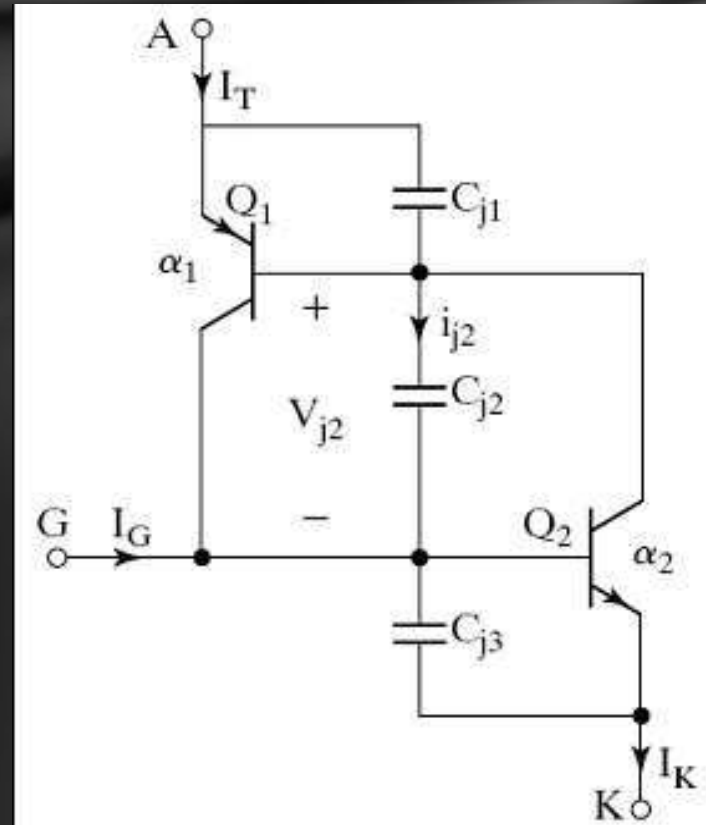❑ The  $dV/dt$  across the device becomes large & scr will turn on



# Gate Triggering

This is most widely used SCR triggering method.

Three types .

1. DC Gate Triggering:-

2. AC Gate Triggering:-

I. Resistance triggering:

II. RC Triggering

3. Pulse Gate Triggering:-

# DC gate triggering:-

- ❖ A DC voltage of proper polarity is applied between gate and cathode ( Gate terminal is positive with respect to Cathode).
- ❖ When applied voltage is sufficient to produce the required gate Current, the device starts conducting.

## Drawbacks :

- ❖ One drawback of this scheme is that both power and control circuits are DC and there is no isolation between the two.
- ❖ Another disadvantages is that a continuous DC signal has to be applied. So gate power loss is high.

# AC Gate Triggering:-

- Here AC source is used for gate signals.
- This scheme provides proper isolation between power and control circuit.

## Drawback:

- Drawback of this scheme is that a separate transformer is required to step down ac supply.

Two methods of AC voltage triggering namely


(i) R Triggering

(ii) RC triggering



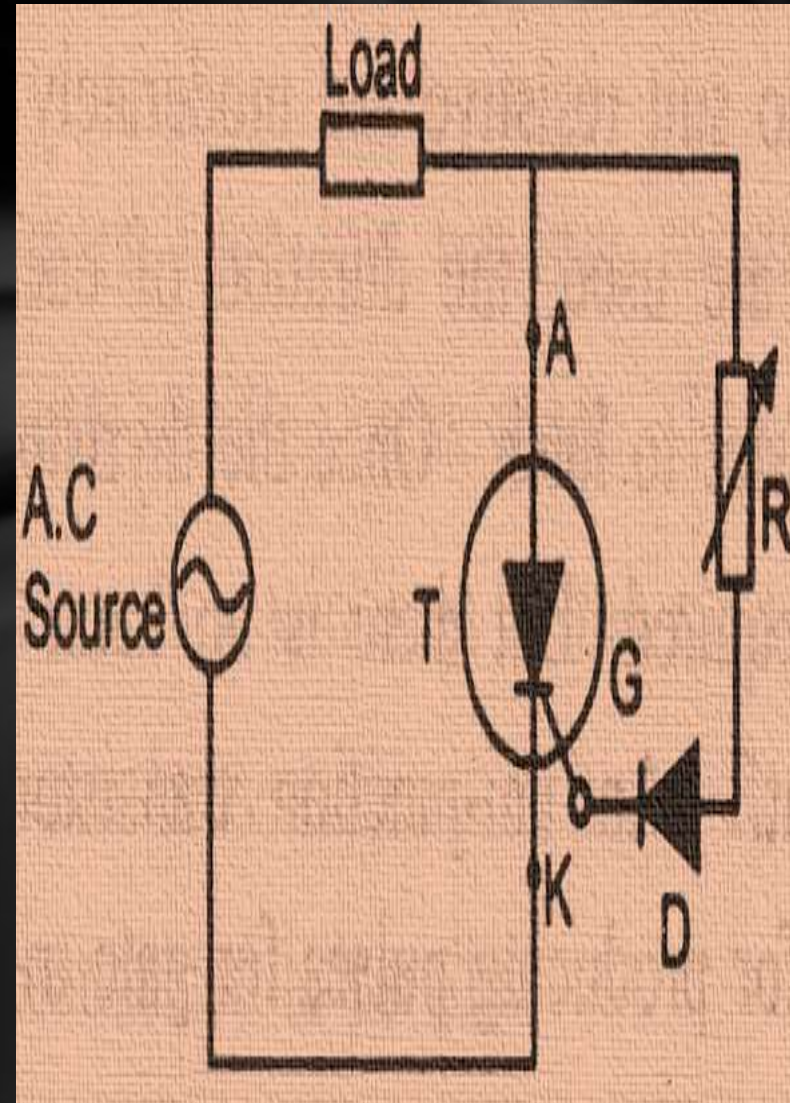
# Resistance triggering:

- R is used to control the gate current.
- Depending on R, when the gate current reaches the  $I_L$  (latching) the SCR starts to conduct.
- The diode D is called as blocking diode. It prevents the gate cathode junction from getting damaged in the negative half cycle.
- By considering that the gate circuit is purely resistive, the gate current is in phase with the applied voltage.
- By using this method we can achieve maximum firing angle up to  $90^\circ$ .



# Firing Angle

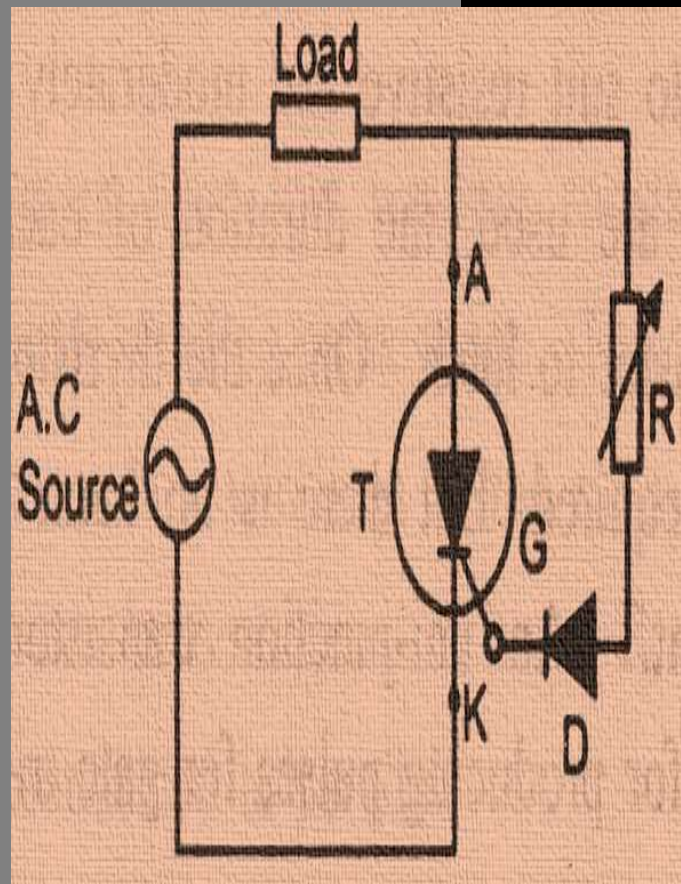

or

$$V_{gp} \sin \alpha = V_{gt}$$

$$\alpha = \sin^{-1} (V_{gt} / V_{gp})$$


Since

$$V_{gp} = \frac{V_m R}{R_1 + R_2 + R}$$

$$\alpha = \sin^{-1} \left[ \frac{V_{gt} (R_1 + R_2 + R)}{V_m R} \right]$$

As  $V_{gt}$ ,  $R_1$ ,  $R$  and  $V_m$  are fixed,  $\alpha \propto \sin^{-1} (R_2)$  or  $\alpha \propto R_2$ .

## Resistance Triggering

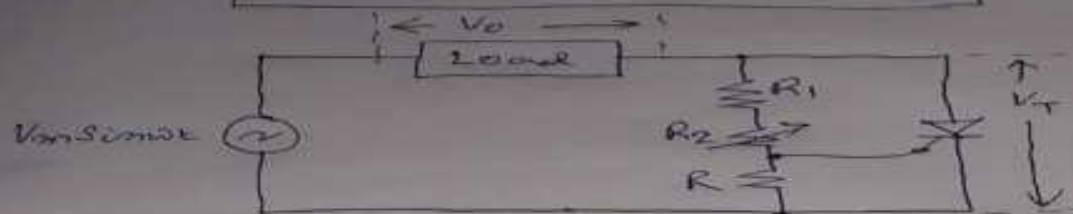

Resistance values are large

Initially  $R_2 \rightarrow 0$

$$I_{gp} = \frac{V_m}{R+R_1} < I_{gt}$$

$$V_{gp} = \frac{V_m}{R+R_1} \cdot R < V_{gt}$$

Let  $R_2$

$$I_{gp} = \frac{V_m}{R+R_1+R_2} \geq I_{gt}$$

$$V_{gp} = \frac{V_m}{R+R_1+R_2} \cdot R \geq V_{gt}$$

$$V_{gp} \sin \alpha = V_{gt} \quad , \quad \alpha = \text{Firing Angle}$$

$$\sin \alpha = \frac{V_{gt}}{V_{gp}} = \frac{V_{gt} [R+R_1+R_2]}{V_m \cdot R}$$

$$\alpha = \sin^{-1} \left[ \frac{V_{gt} (R+R_1+R_2)}{V_m \cdot R} \right]$$

$$\alpha \propto \sin^{-1} [R_2]$$


$$\boxed{\alpha \propto R_2}$$

Points to be noted.

- ① When SCR is off, negligible current thru' trig. ckt,  $V_0 \approx 0$ ,  $V_T \approx V_m \sin \omega t$
- ② When SCR is on,  $V_T \approx 1 \text{ to } 2 \text{ V}$   
 $V_0 \approx$  Higher load voltage




# Graphical Representation

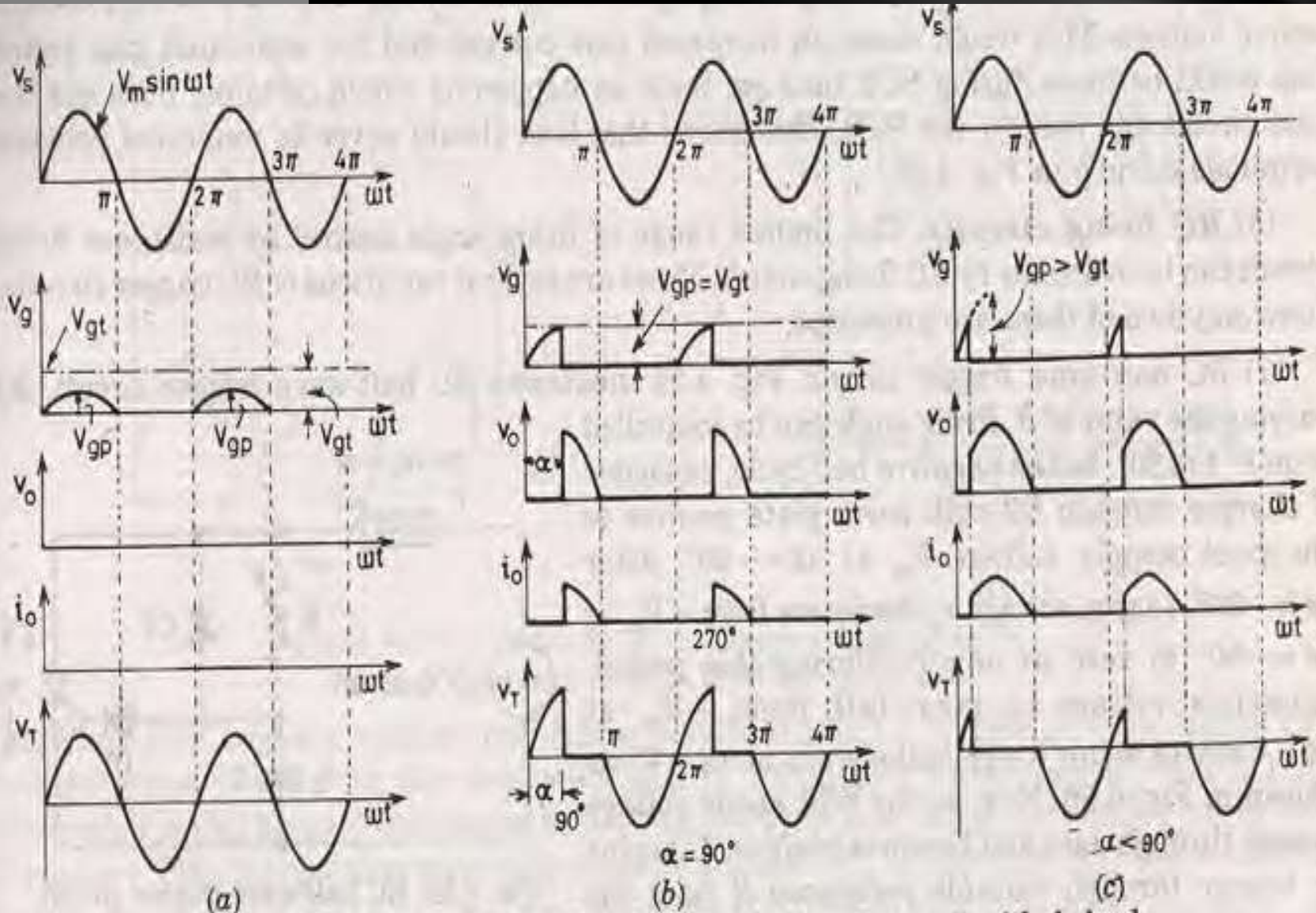



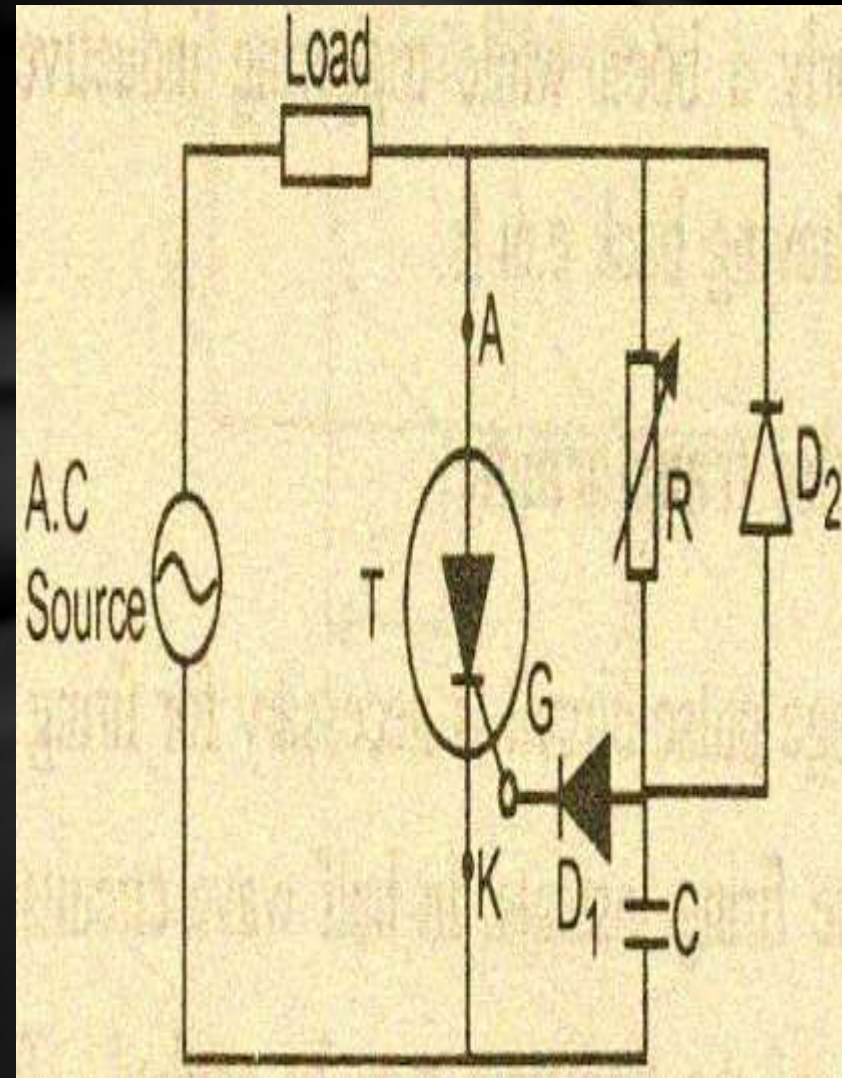
# RC Triggering [Half Wave ]


- ❑ Using this we can achieve firing angle more than  $90^\circ$ .
- ❑ In the positive half cycle, the capacitor is charged through the variable resistance  $R$  up to the peak value of the applied voltage.
- ❑ The variable resistor  $R$  controls the charging time of the capacitor.
- ❑ Depends on  $V_c$ , when sufficient amount of gate current will flow in the circuit, the SCR starts to conduct.
- ❑ In the negative half cycle, the capacitor  $C$  is charged up to the negative peak value through the diode  $D_2$ .




# Graphical Representation

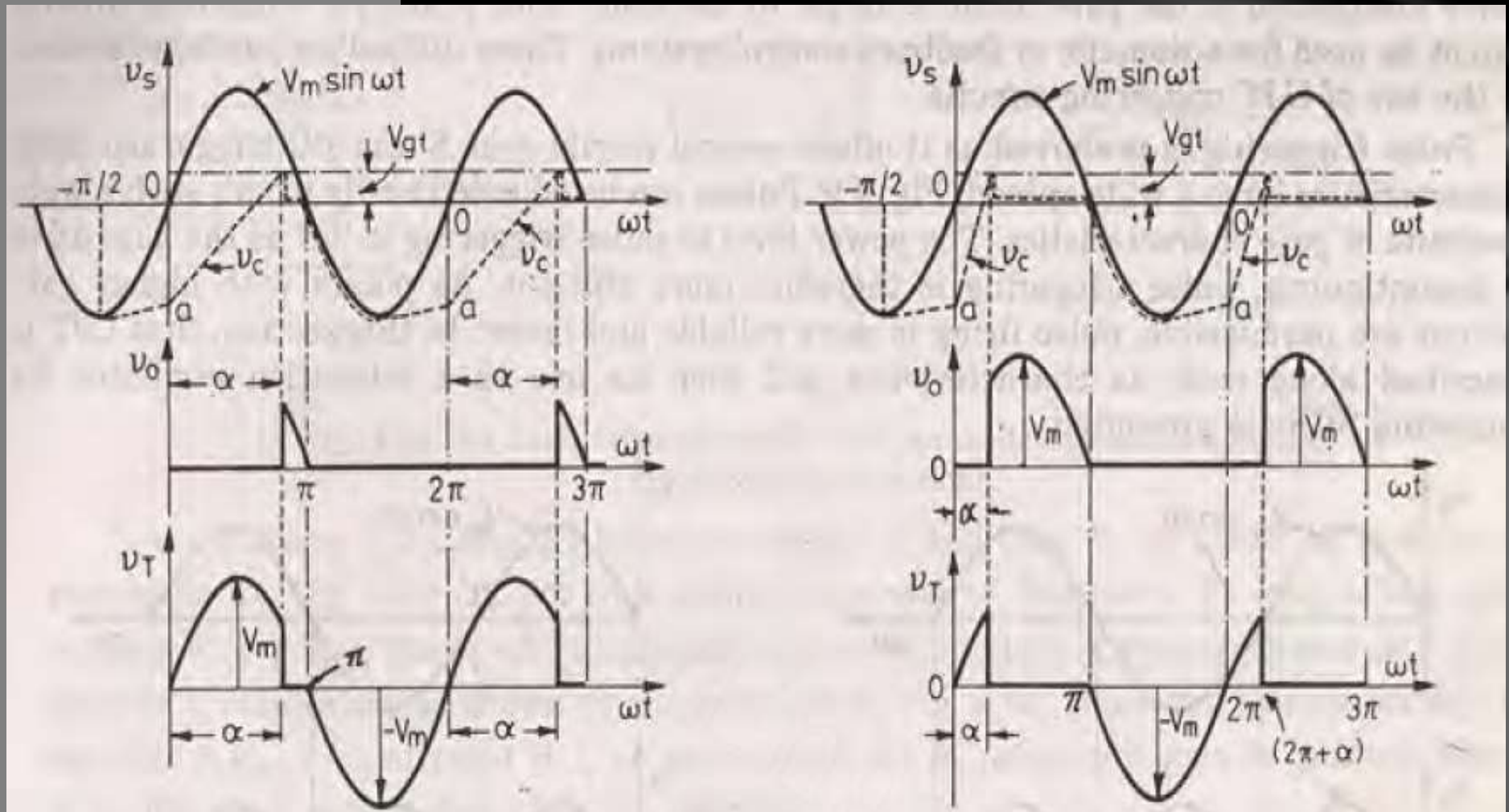

# RC Triggering Circuit [ Full Wave ]

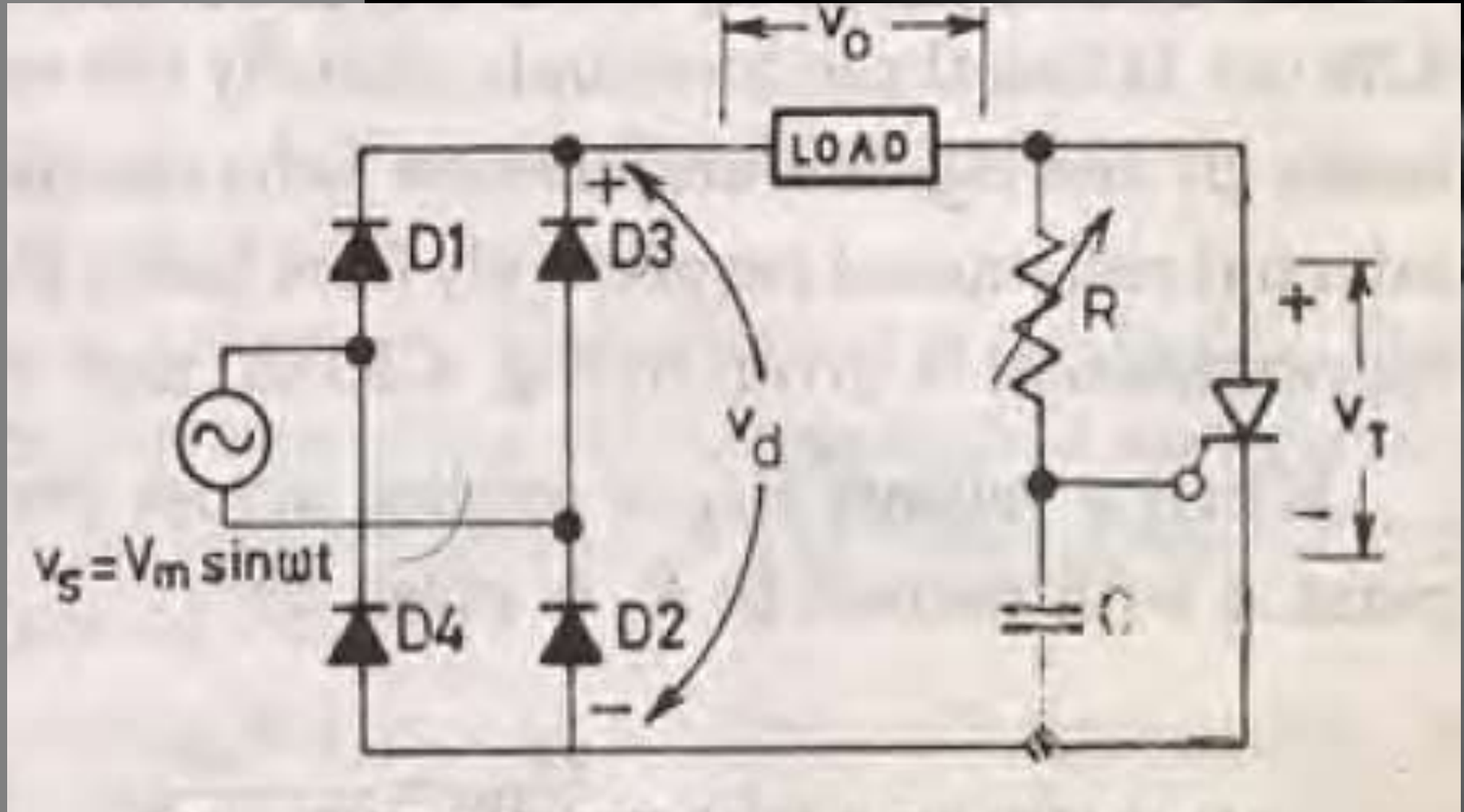


# Graphical Representation

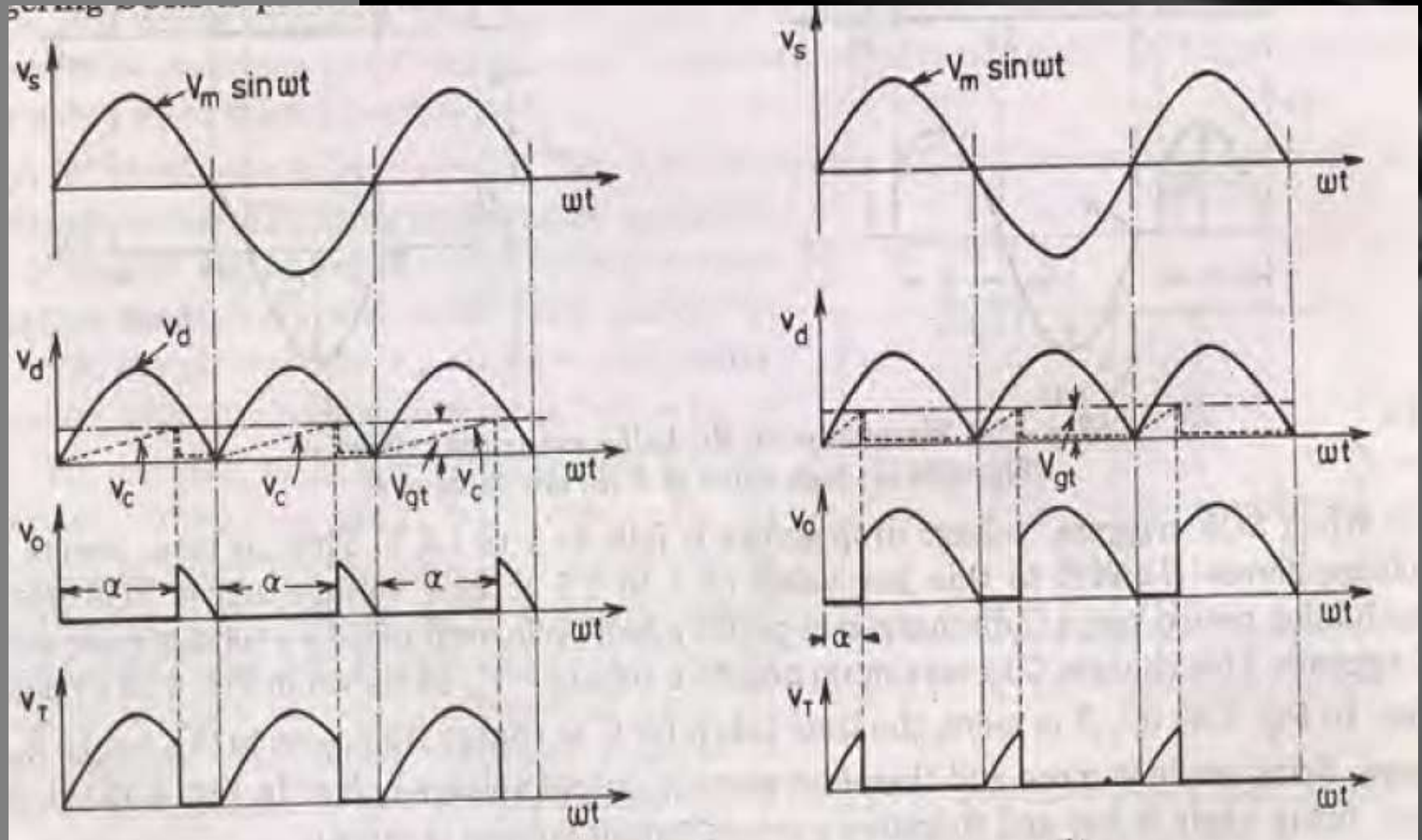


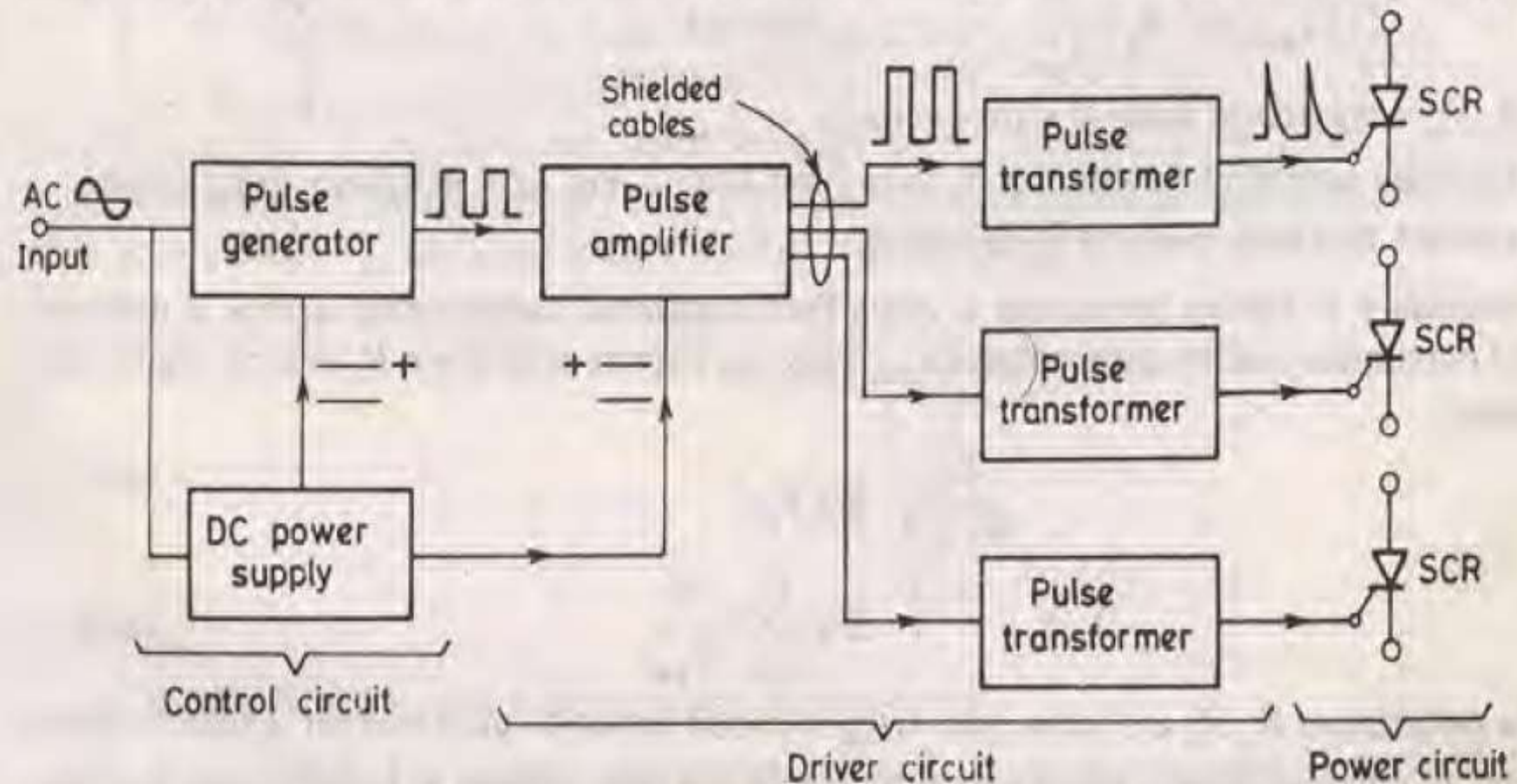
# General Layout of the firing circuit schemes for SCRs



# Pulse Gate Triggering:-

- In this method the gate drive consists of a single pulse appearing periodically (or) a sequence of high frequency pulses.
- This is known as carrier frequency gating.

## Advantages

1. Low gate dissipation at higher gate current.
2. Small gate isolating pulse transformer
3. Low dissipation in reverse biased condition is possible. So simple trigger circuits are possible in some cases
4. When the first trigger pulse fails to trigger the SCR, the following pulses can succeed in latching SCR.