

INVERTERS

Inverters

- DC to AC Conversion
- Applications : Adjustable speed ac drive , Induction heating, stand by air craft power supplies , UPS, HVDC Transmission lines etc
- Forced Commutated Inverters , Line commutated Inverters , Load Commutated Inverters , **Voltage Source Inverter** , **Current Source Inverter**

Inverters


Inverters are also classified depending upon the connection of commutating components with the main circuit.

- Series Inverter
- Parallel Inverter
- Bridge Inverter

Classification

- Broadly categorized into :
 - Voltage Source Inverter (VSI) or Voltage fed Inverters (VFI)
 - Current Source Inverter (CSI) or Current fed Inverters (CFI)
- Impedance of VSI and CSI are as per Voltage Source and Current Source


Single Phase Voltage Source Inverter

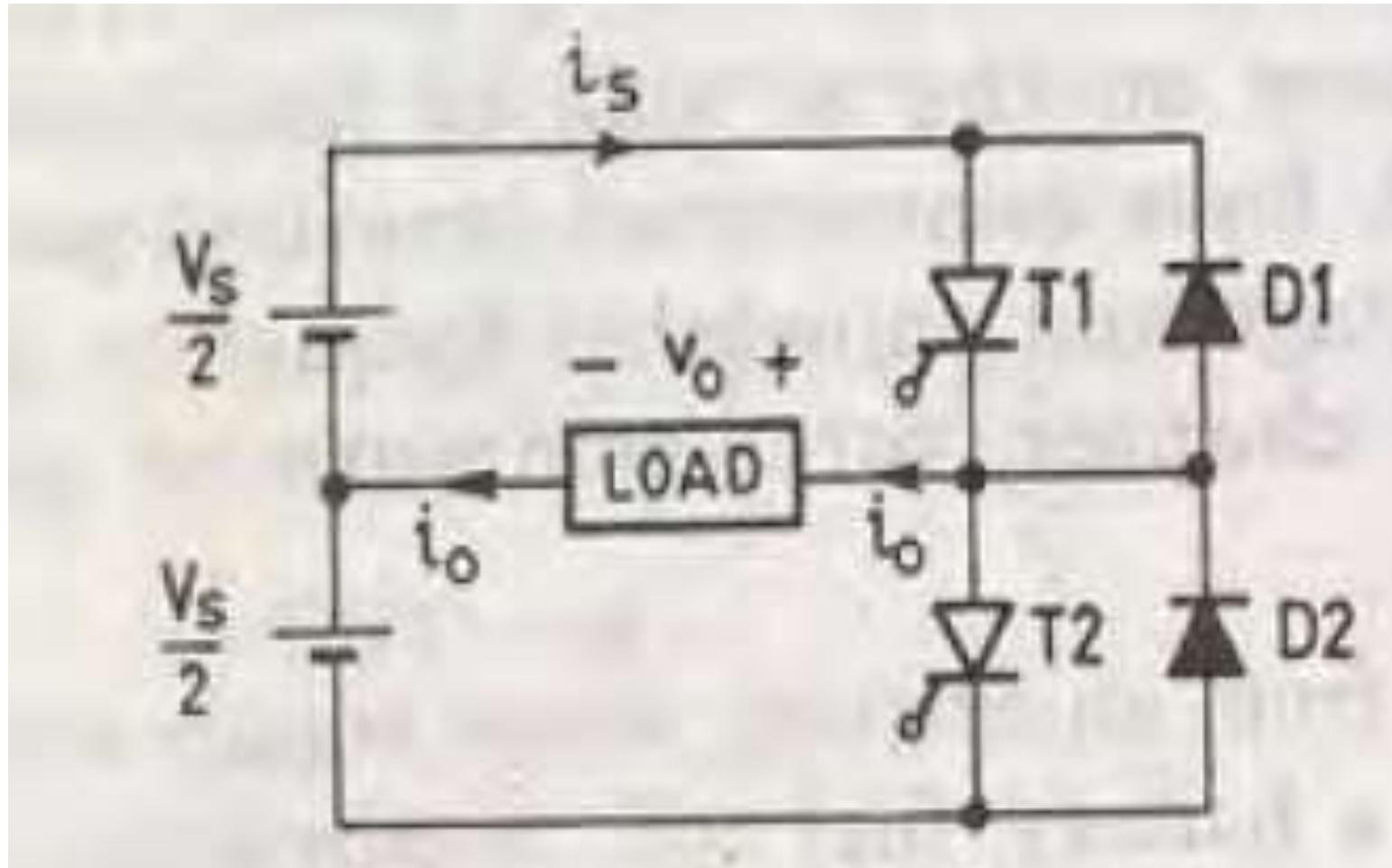


Single Phase VSI

Voltage Source Inverter


Mode I

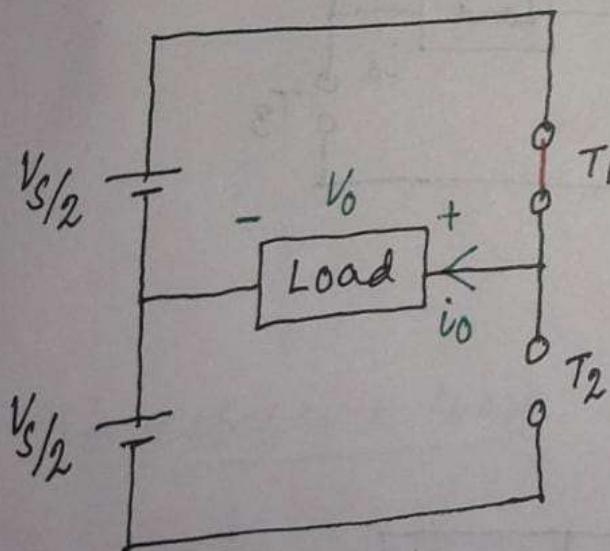

Mode II

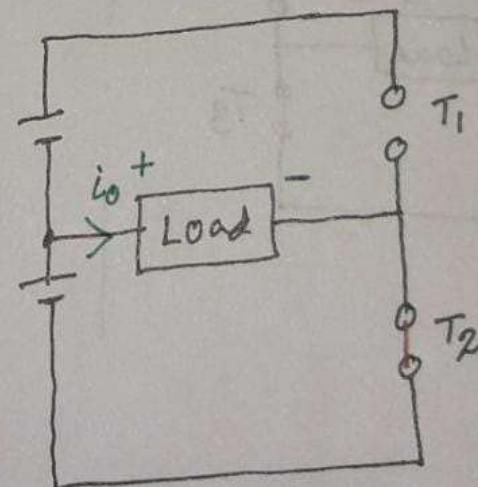

Single Phase Voltage Source Inverter

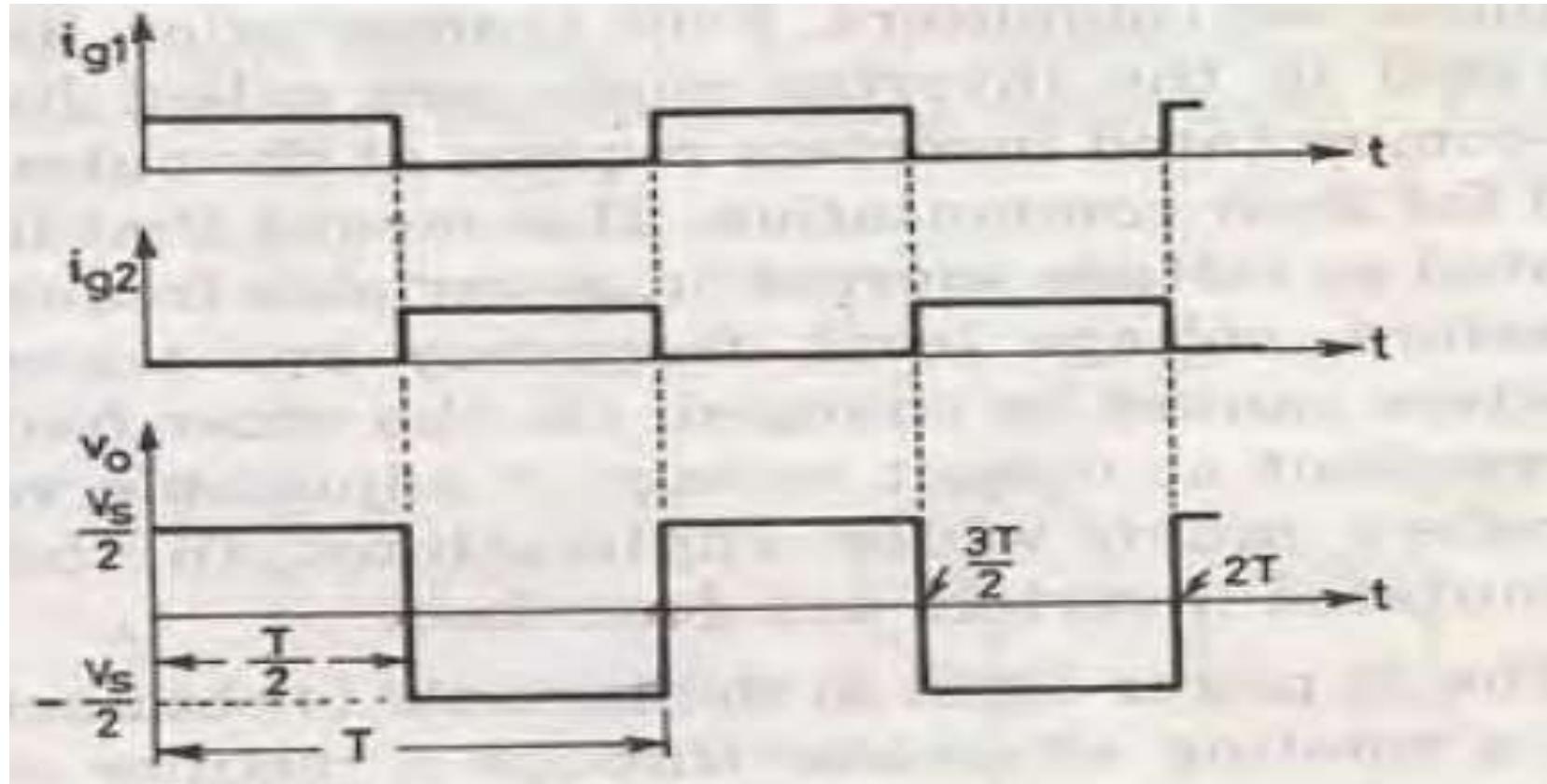

Half Bridge Configuration

Half Bridge VSI

For resistive load

$$V_0 = \frac{V_S}{2} \quad \dots \dots \text{for } 0 \leq t \leq T_0/2$$

$$V_0 = -\frac{V_S}{2} \quad \dots \dots \text{for } T_0/2 \leq t \leq T_0$$

$$I_0 = \frac{V_0}{R} = \frac{V_S}{2R} \quad \dots \text{for } 0 \leq t \leq T_0/2$$

$$I_0 = \frac{V_0}{R} = -\frac{V_S}{2R} \quad \dots \text{for } T_0/2 \leq t \leq T_0$$


$$\begin{aligned} V_{0\text{ RMS}} &= \left[\frac{1}{T_0/2} \int_0^{T_0/2} \left(\frac{V_S}{2}\right)^2 dt \right]^{1/2} \\ &= \frac{V_S}{2} \end{aligned}$$

$$I_{0\text{ RMS}} = \frac{V_S}{2R}$$

Limitations

- Requirement of 3 terminal DC Power Supply
- Output voltage is using half of the total voltage
- Full Bridge configuration eliminates the limitations
- Output nature is square wave.

Full Bridge VSI

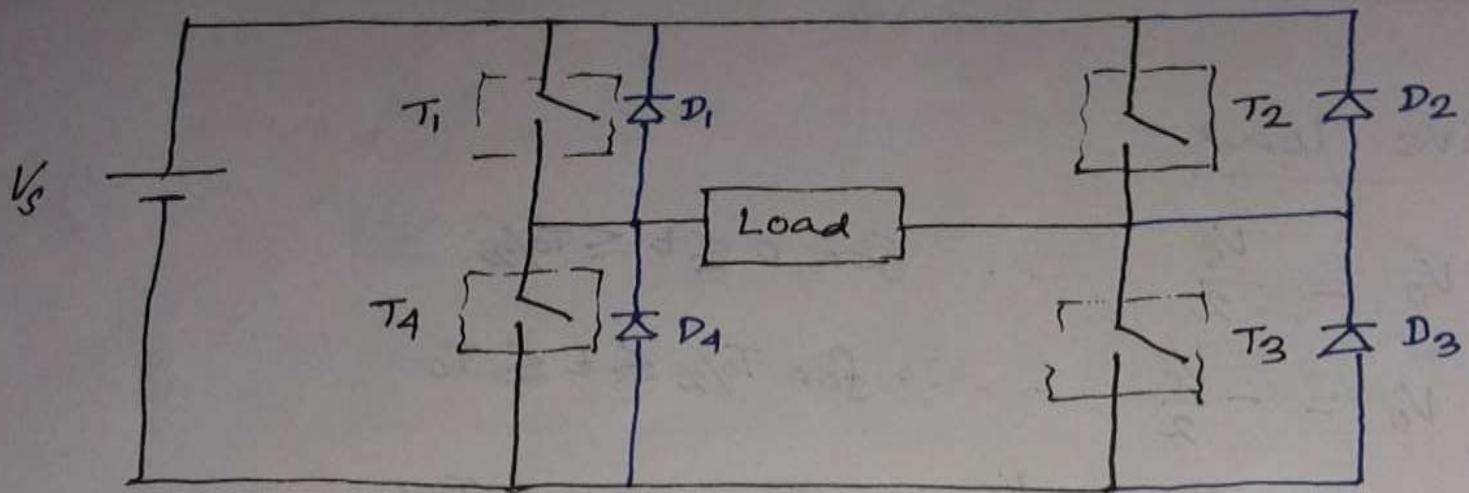


$T_1, T_3 \Rightarrow +ve$ group


$T_2, T_4 \Rightarrow -ve$ group

Full Bridge VSI


Mode I

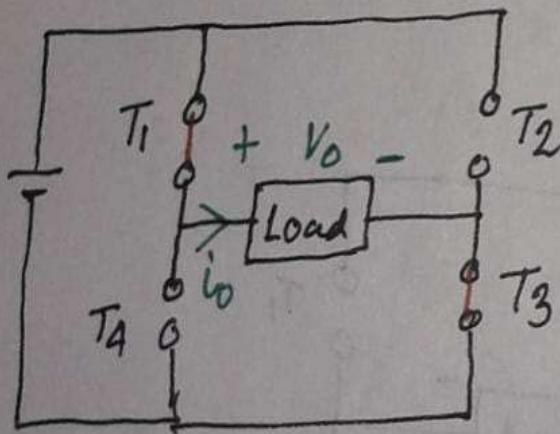

Mode II

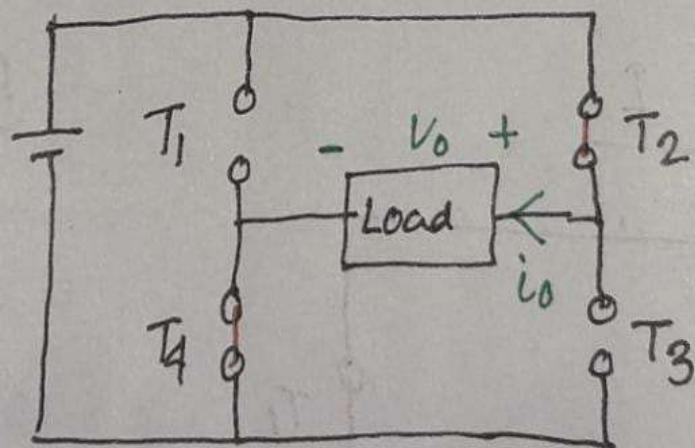

Full Bridge VSI

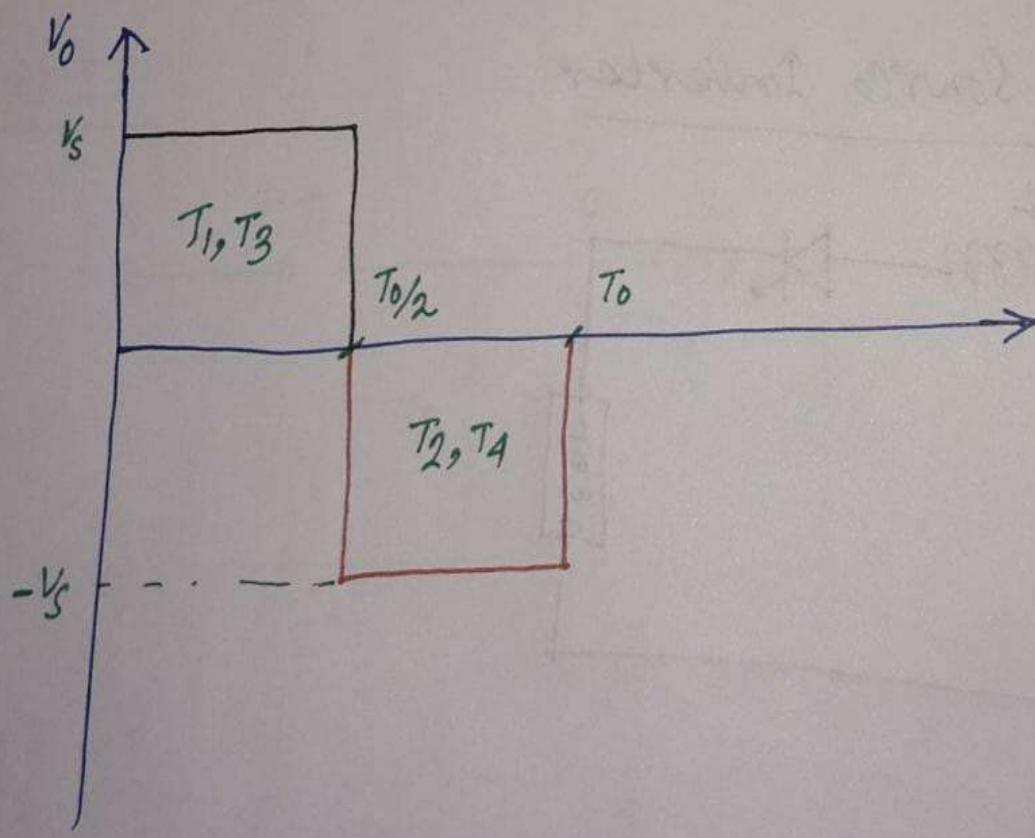

Full Bridge VSI

For resistive load

$$V_o = V_s \quad \dots \quad \text{for } 0 \leq t \leq T_0/2$$

$$V_o = -V_s \quad \dots \quad \text{for } T_0/2 \leq t \leq T_0$$

$$I_o = \frac{V_s}{R} \quad \dots \quad \text{for } 0 \leq t \leq T_0/2$$

$$I_o = -\frac{V_s}{R} \quad \dots \quad \text{for } T_0/2 \leq t < T_0$$

RMS O/P Voltage


$$V_{o\text{ RMS}} = \left[\frac{1}{T_0/2} \int_0^{T_0/2} V_s^2 dt \right]^{1/2}$$

$$= V_s$$


$$I_{o\text{ RMS}} = \frac{V_s}{R}$$

Current Source Inverter (CSI)


Current Source Inverter

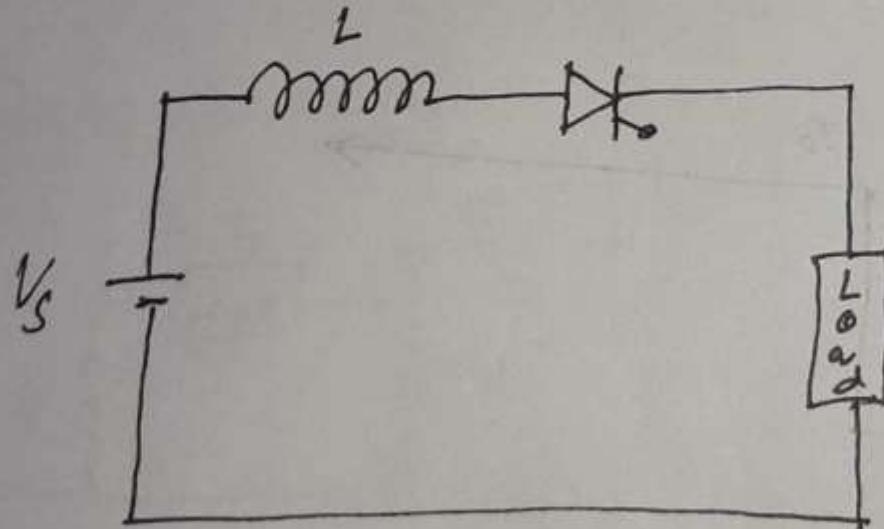

Current Source Inverter

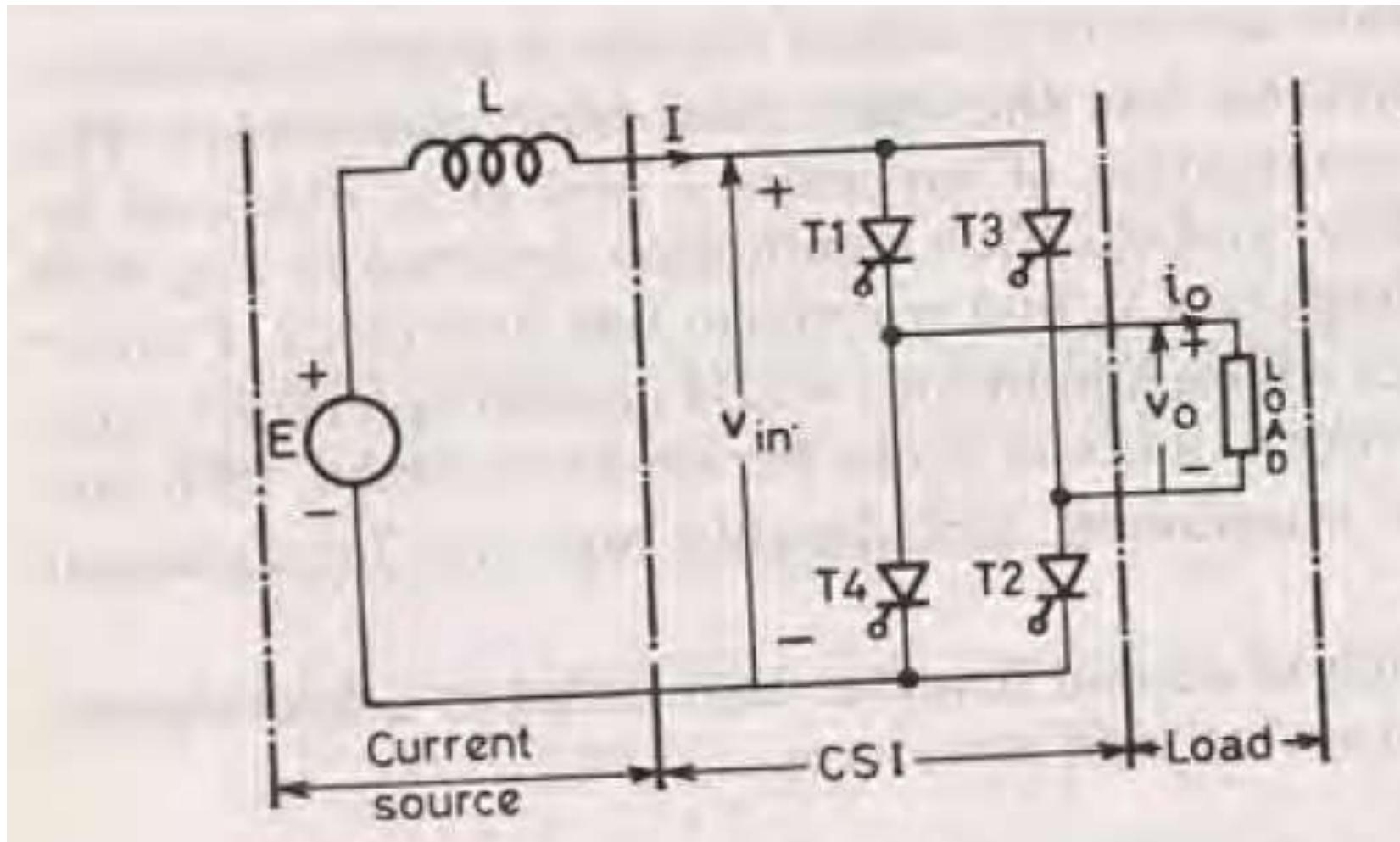


Current Source Inverter

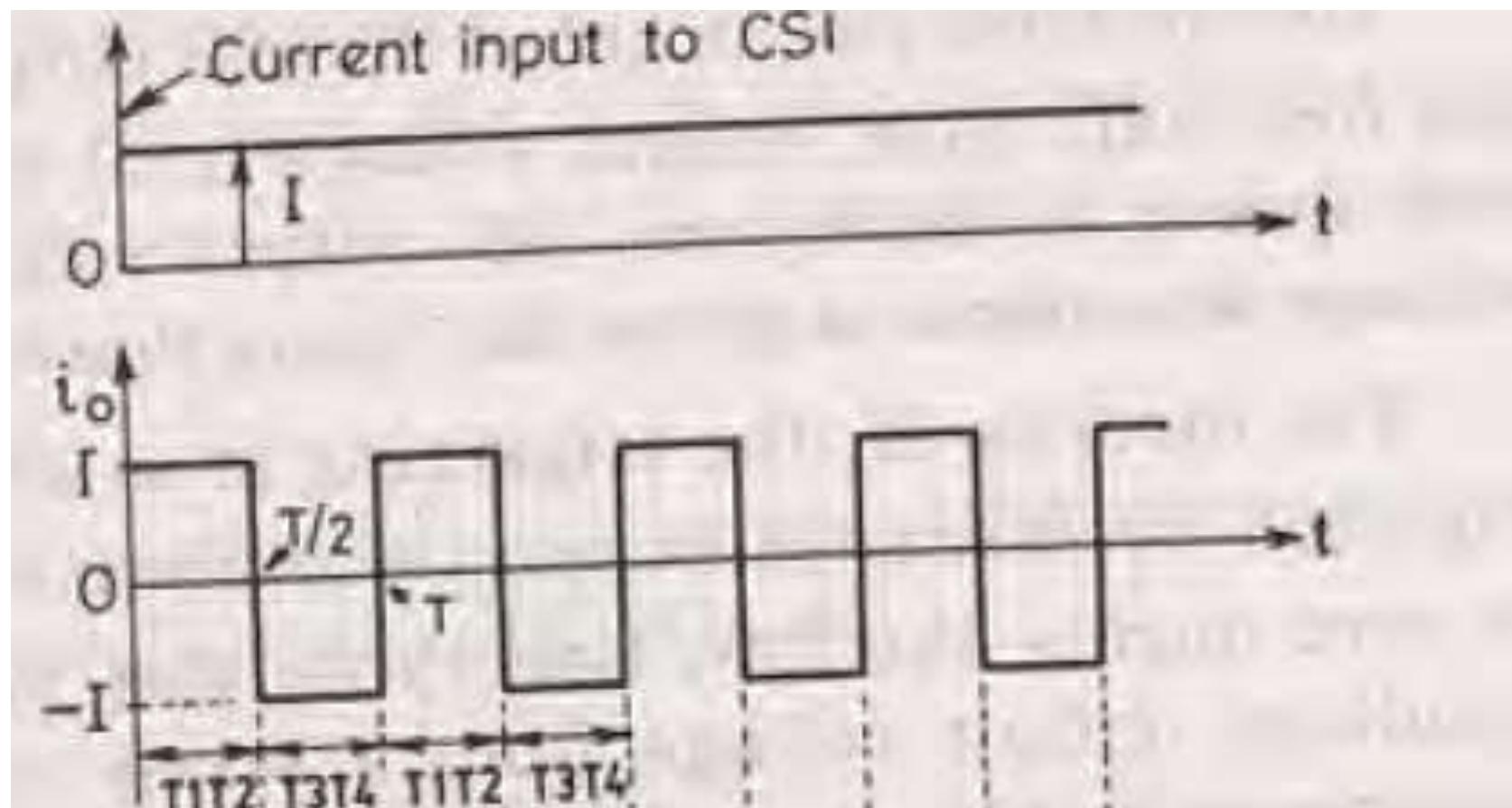


Series Inverter

Series Inverters

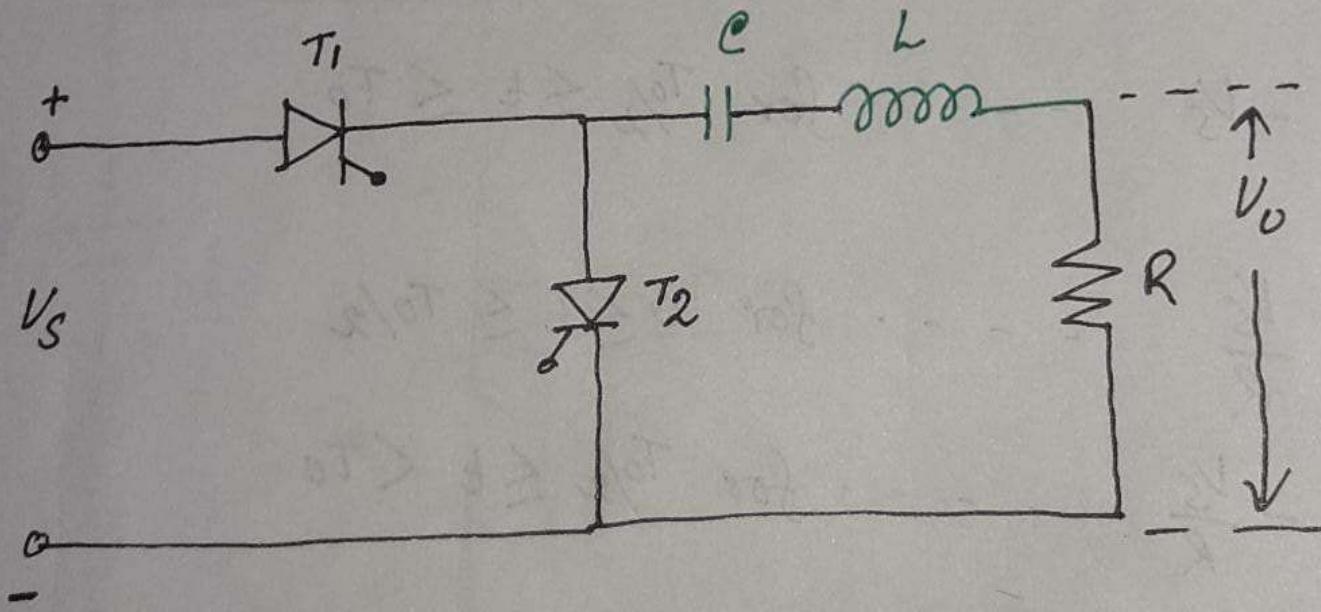



Series Inverter

Mode I

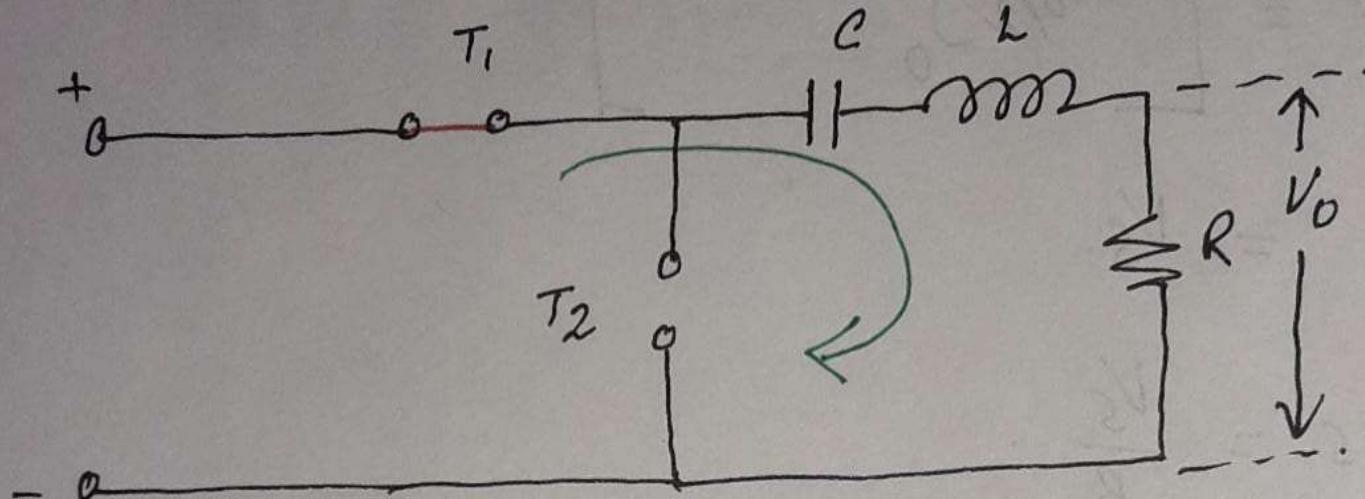

Series Inverter

Mode II

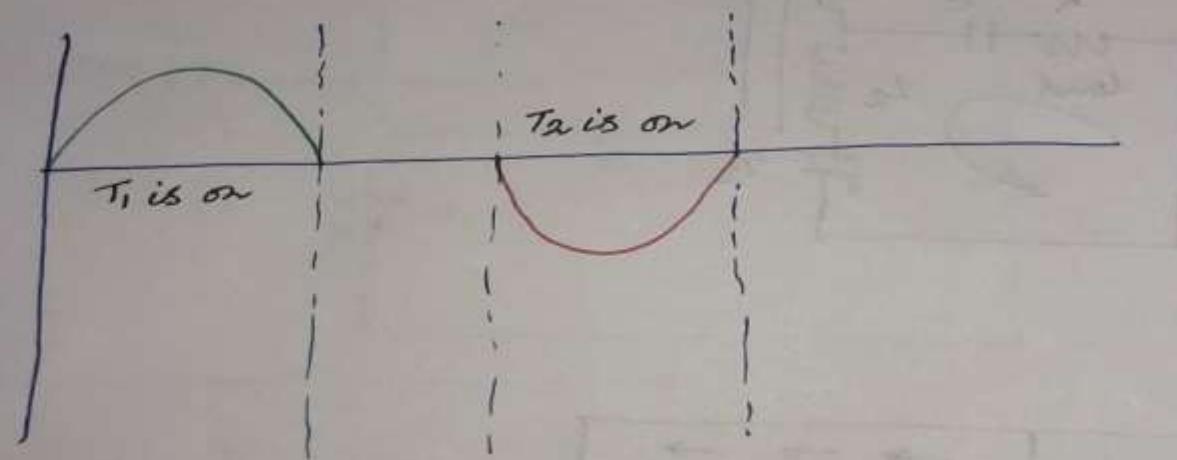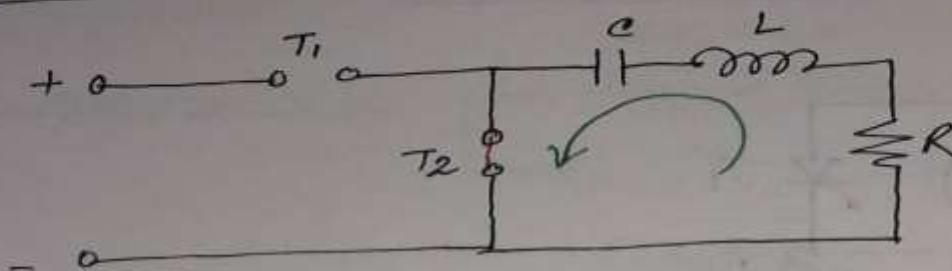


Series Inverter


Drawbacks

1. Power flow from the dc Supply is discontinuous.
2. DC Supply will have a high peak current and hence contains harmonics.
3. Proper Time delays.
4. Discontinuous current, thus ripples
5. Poor O/P regulation
6. Rating of the Commutation Components are high.


Modified Series Inverter

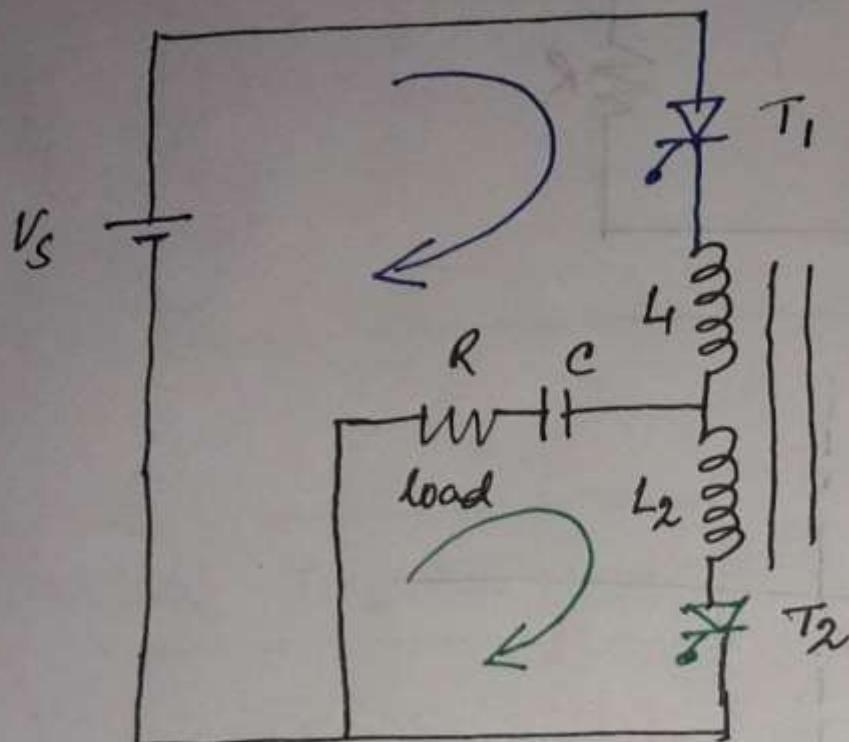


Modified Series Inverter

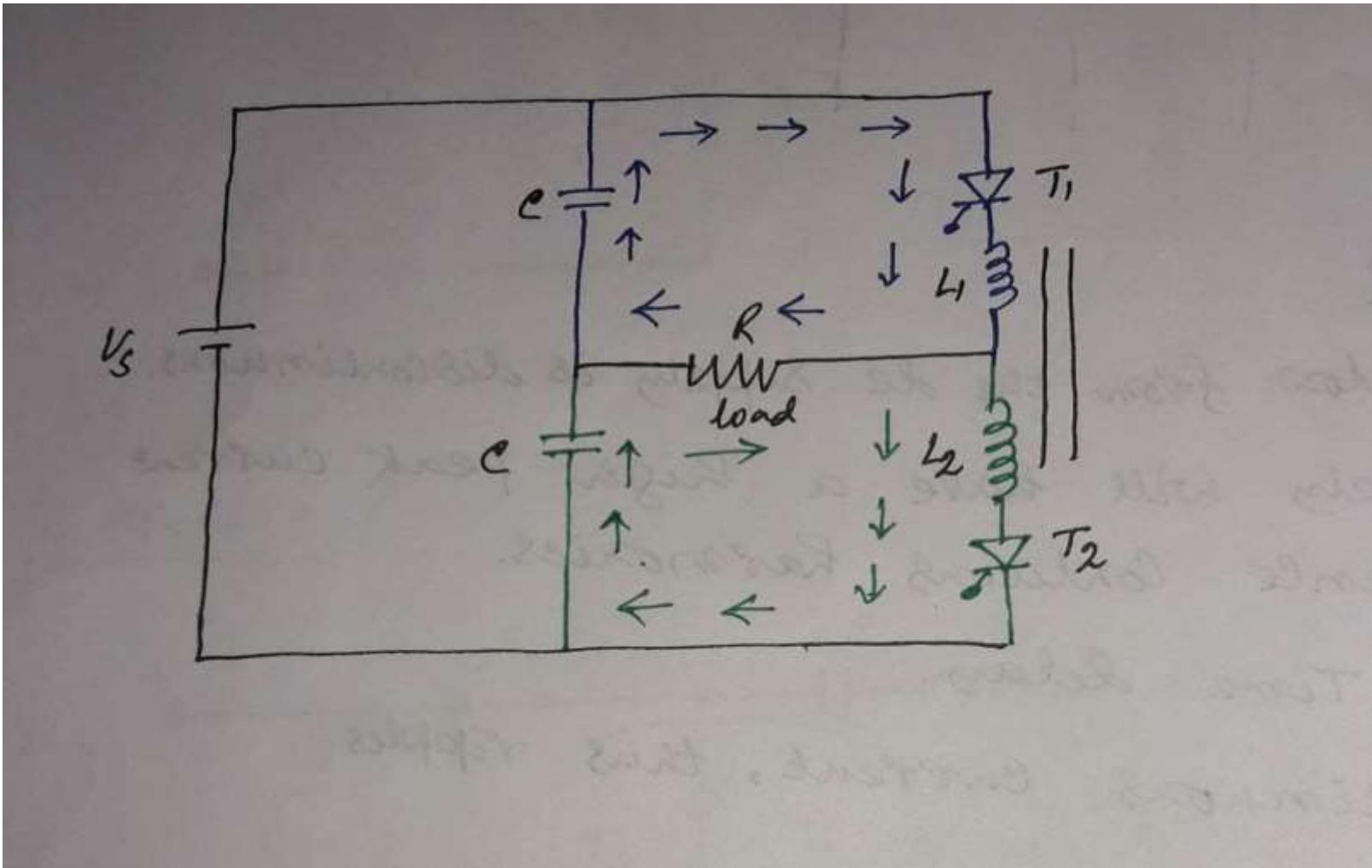


Parallel Inverter

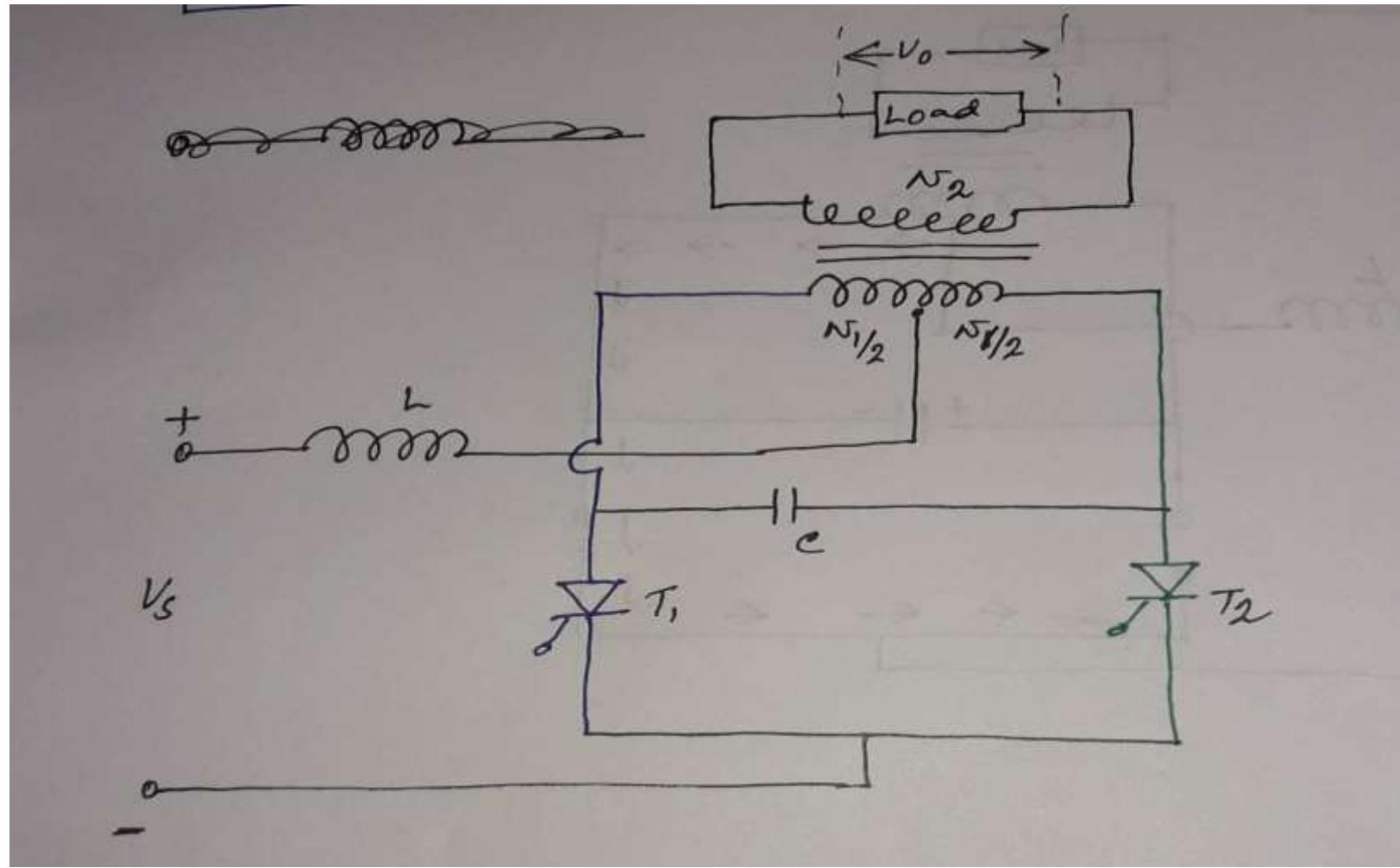

Parallel Inverter

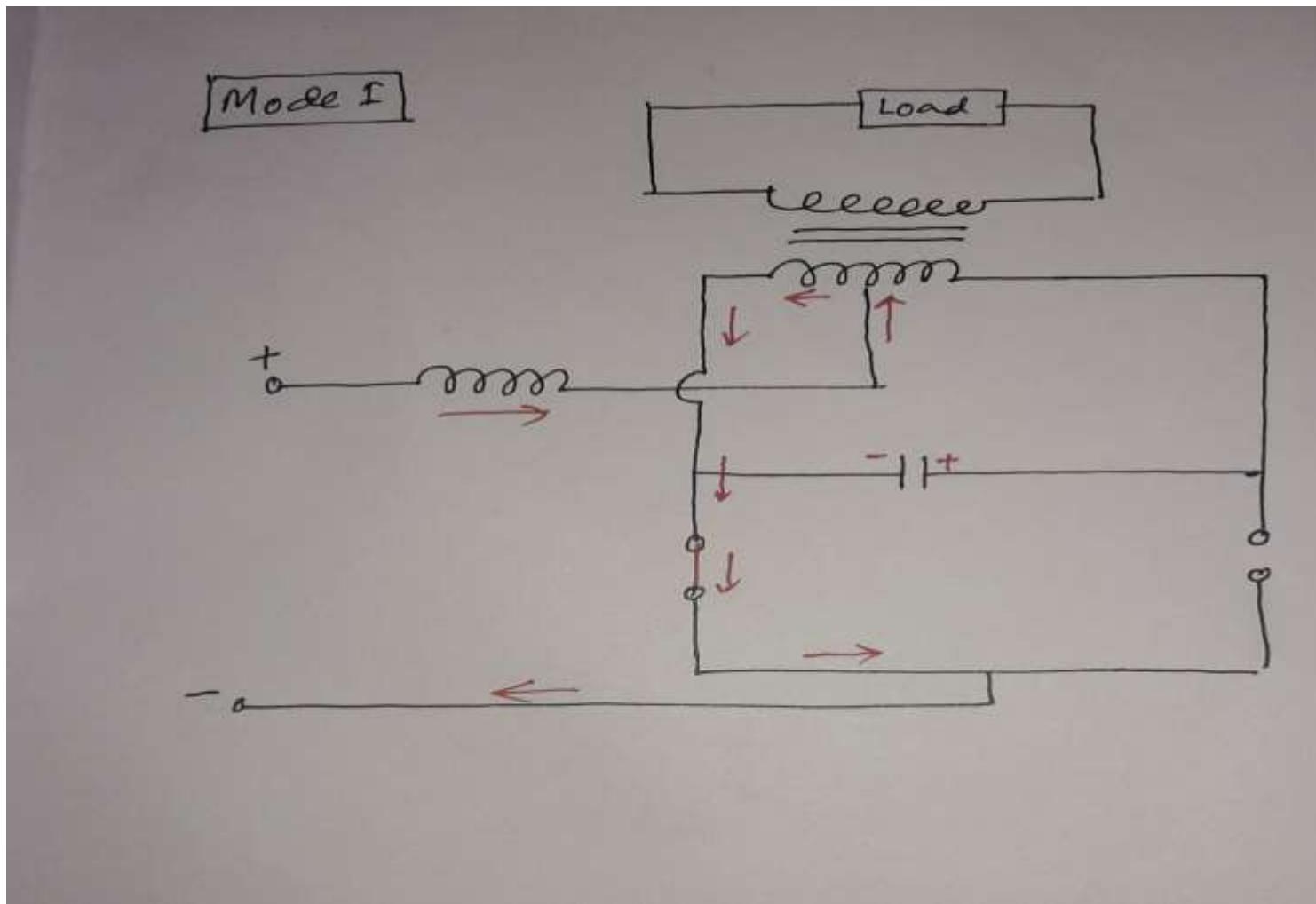


Parallel Inverter

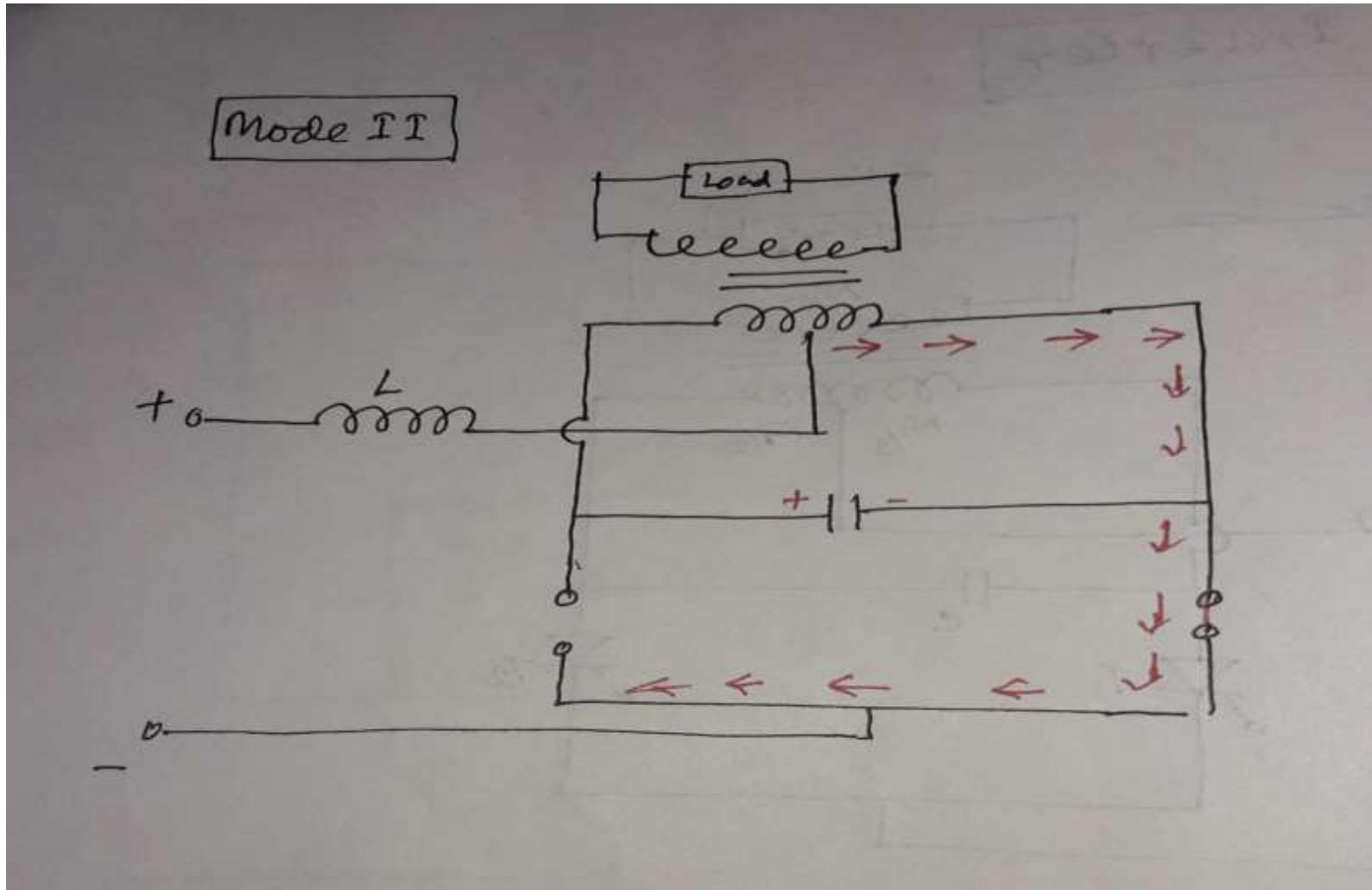

A few questions


- Applications of INVERTER
- What are the limitations of half bridge VSI ?
- Compare VSI & CSI
- Features of Series Inverter
- Features of Parallel Inverter

Forced Commutated Thyristor Inverter

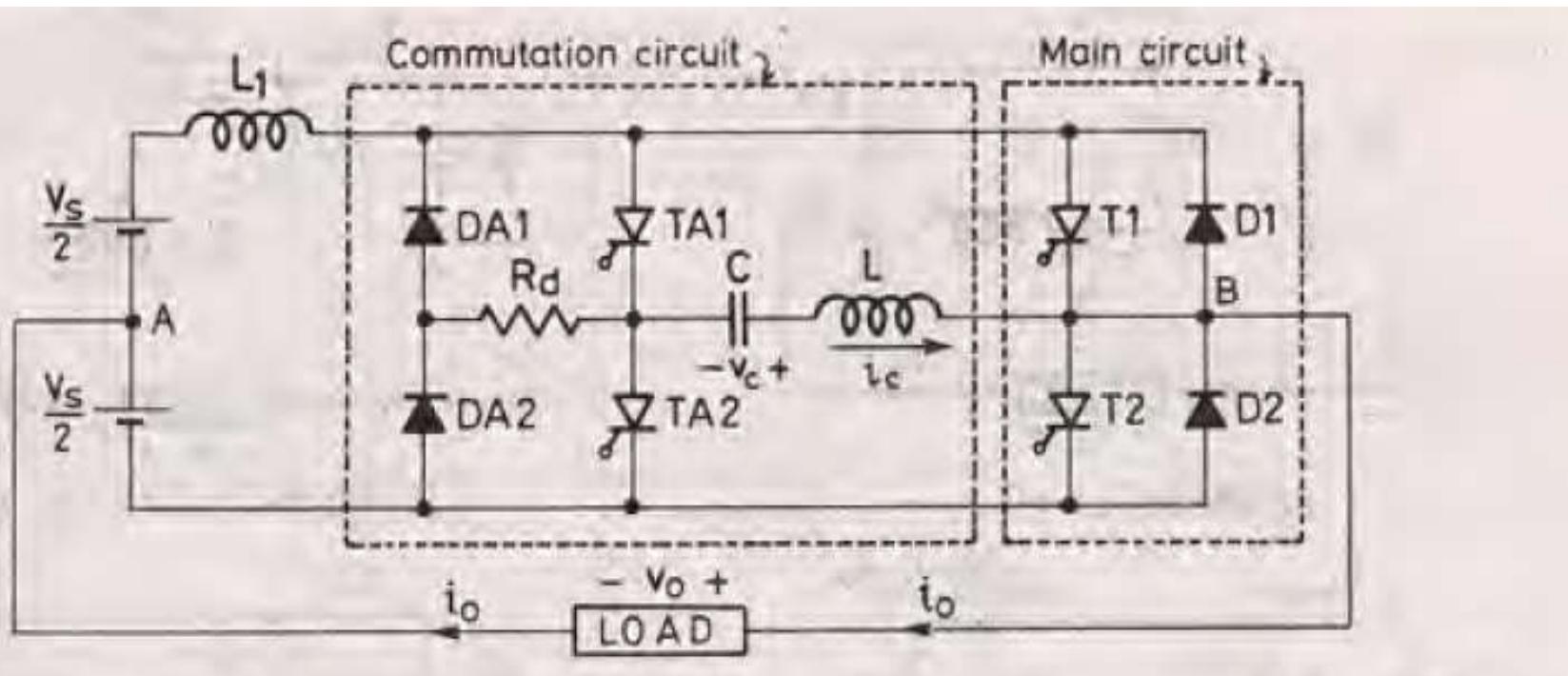


Modified McMurray Half Bridge Inverter

Understanding the operations

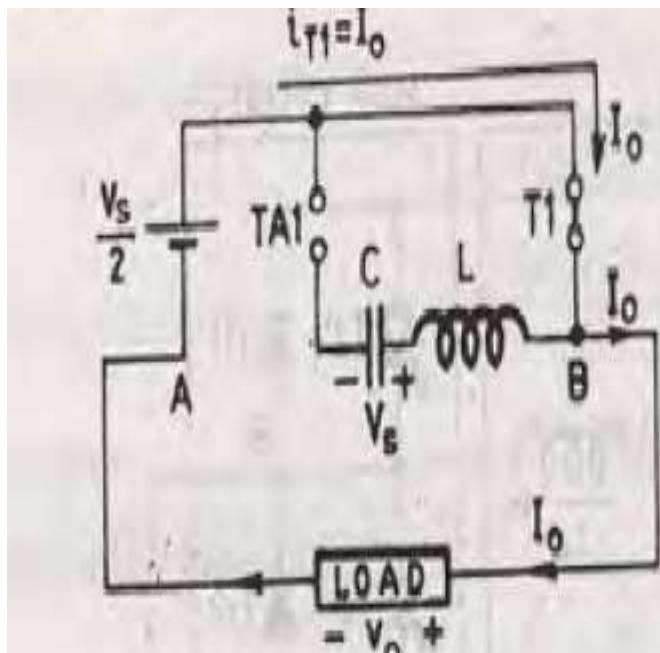


(a) Mode I, $t < 0$

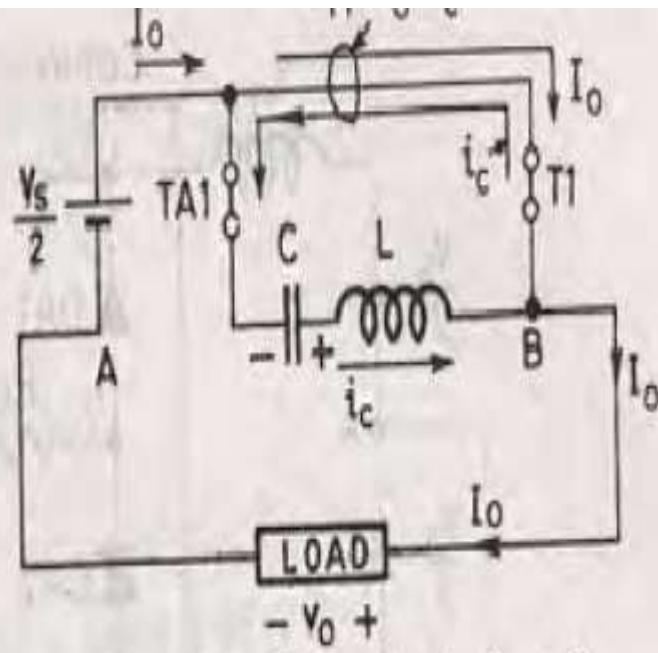


(b) Mode II, $0 < t < t_1$, $i_C < I_0$

Understanding the operations

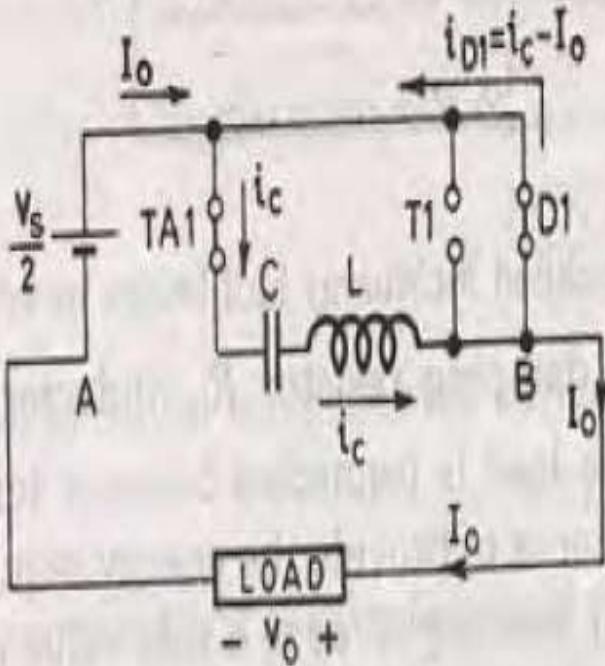


(c) Mode III, $i_c > I_0, t_1 < t < t_2$

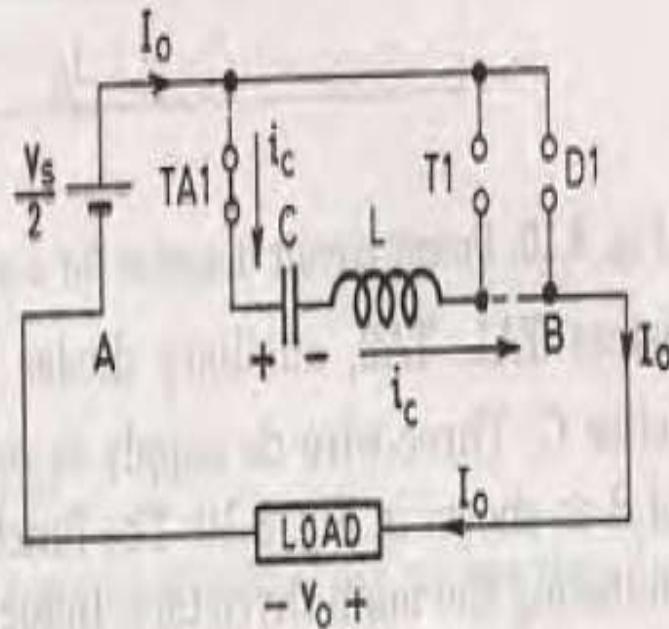


(d) Mode IV, $i_c = I_0, t_2 < t < t_3$


Understanding the operations

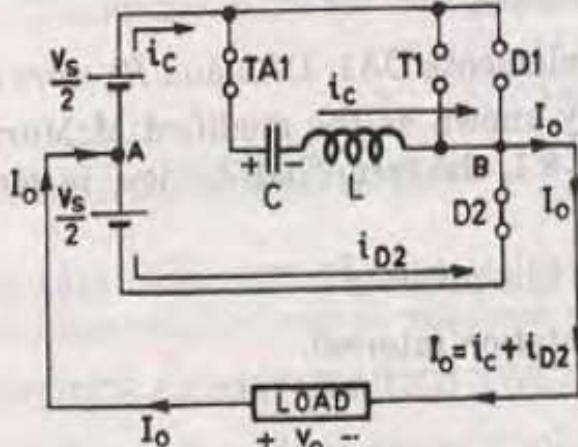

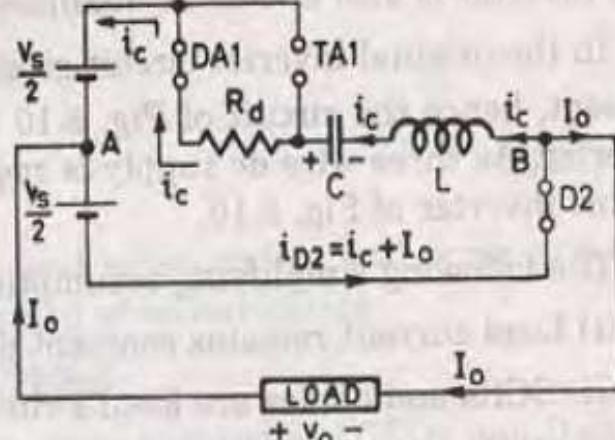(e) Mode V, $i_C < I_0$ and $i_C + i_{D2} = I_0$, $t_3 < t < t_4$




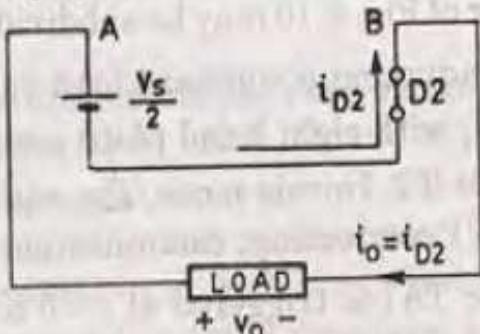(f) Mode VI, $i_{D2} > I_0$, $t_4 < t < t_5$




(g) Mode VII, $i_c = 0$, $i_{D2} = I_0$, $t_5 < t < t_6$


Waveforms

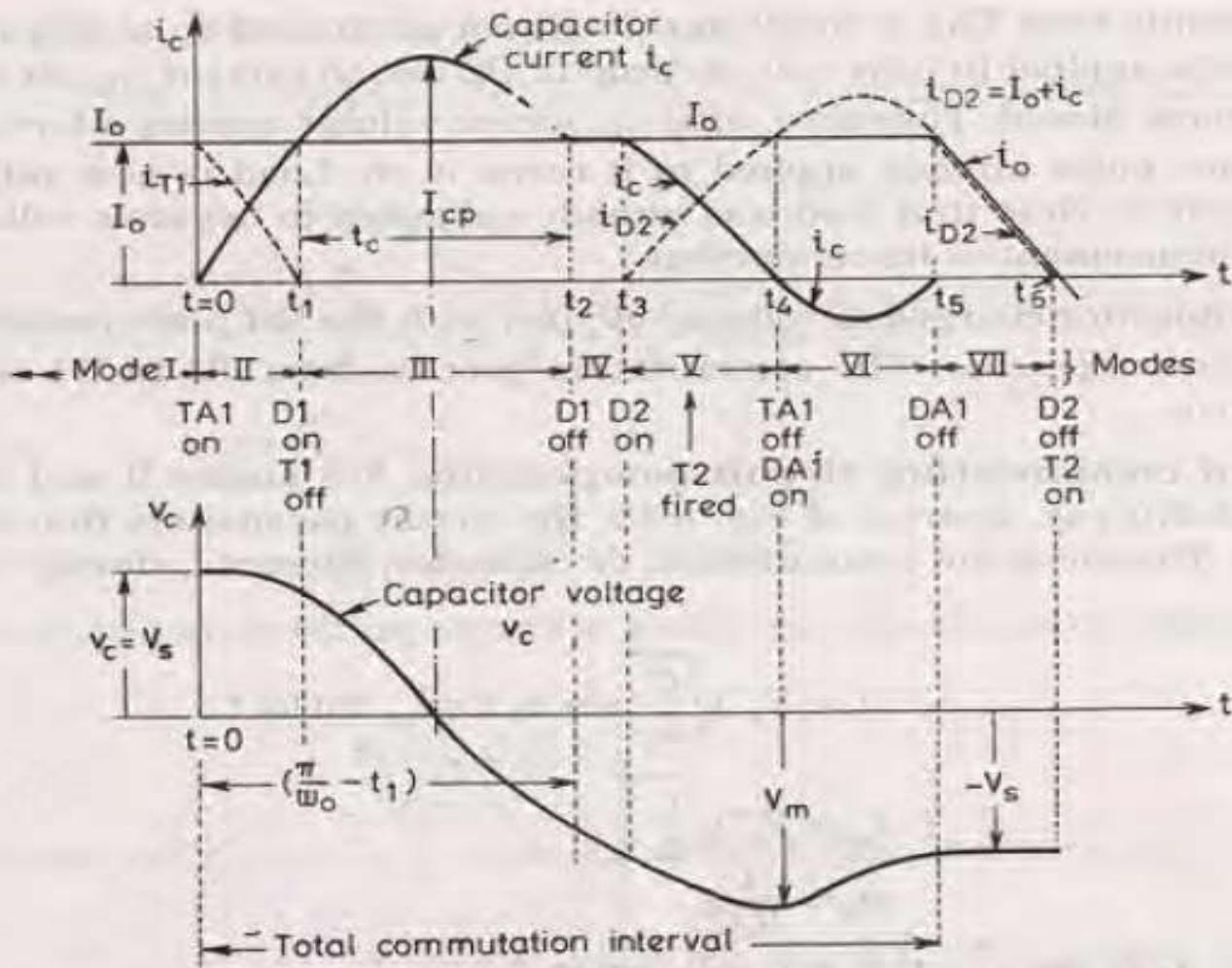

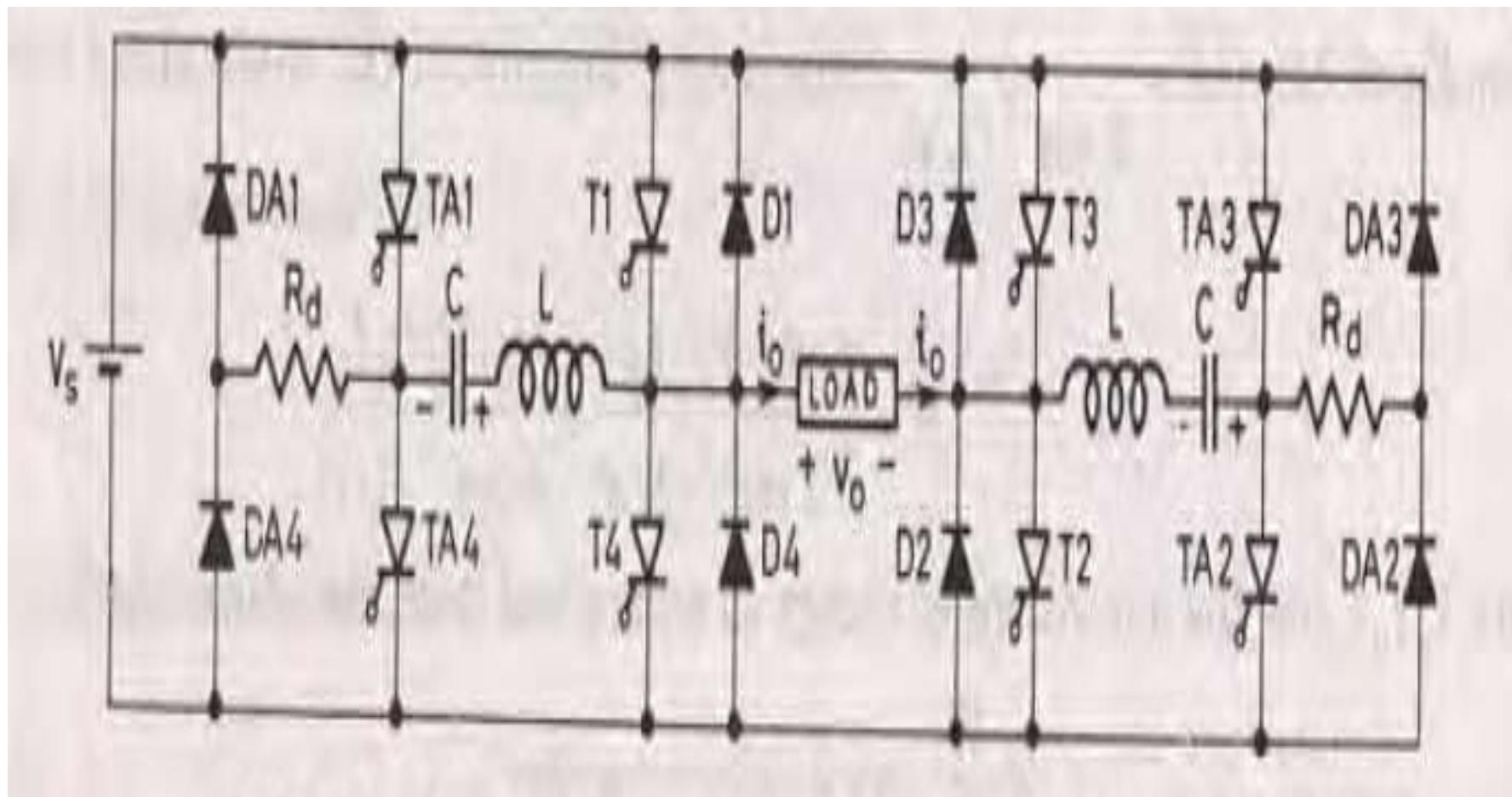
Single Phase modified McMurray Full Bridge Inverter



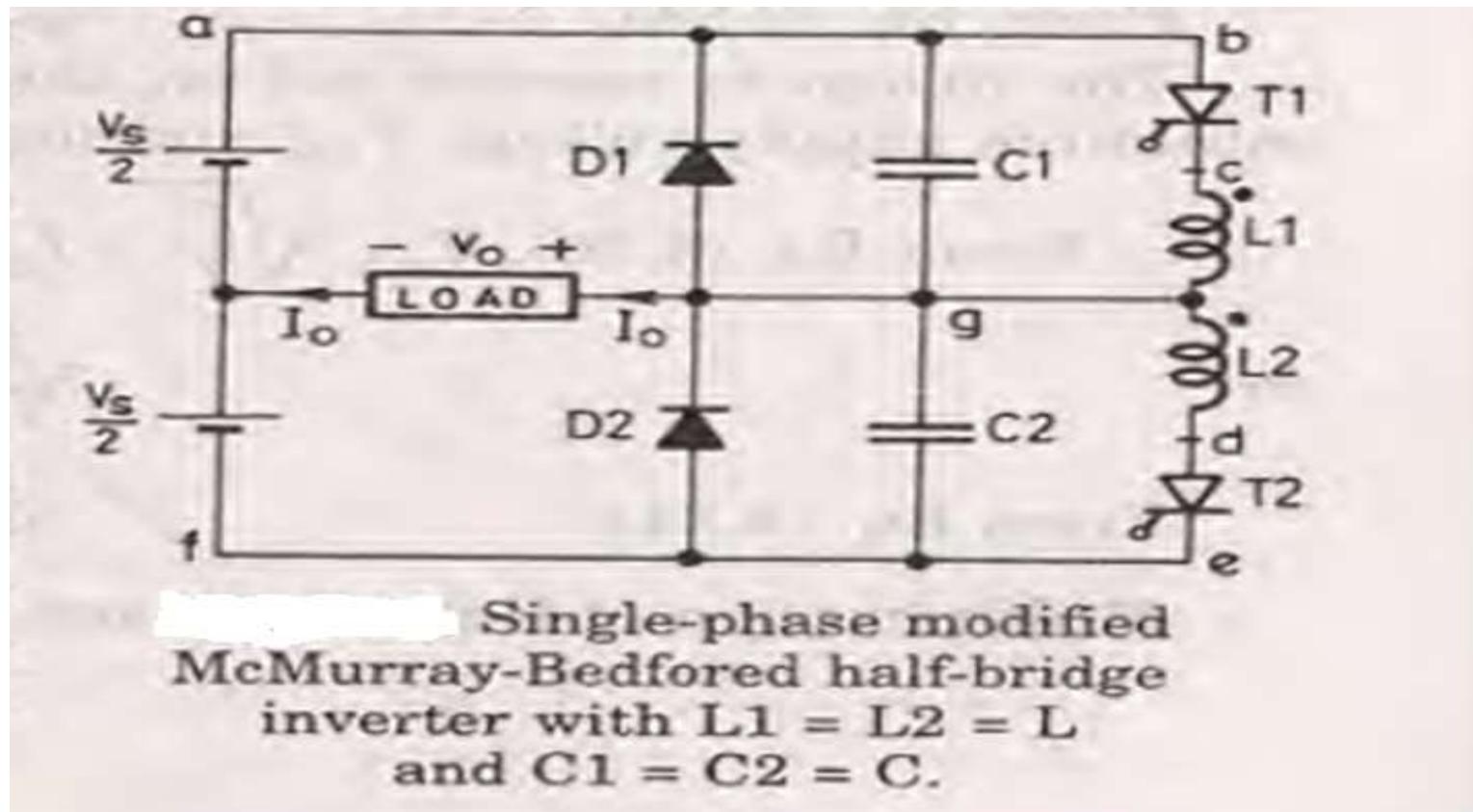
Single Phase modified McMurray Bedford Half Bridge Inverter




Understanding the concepts

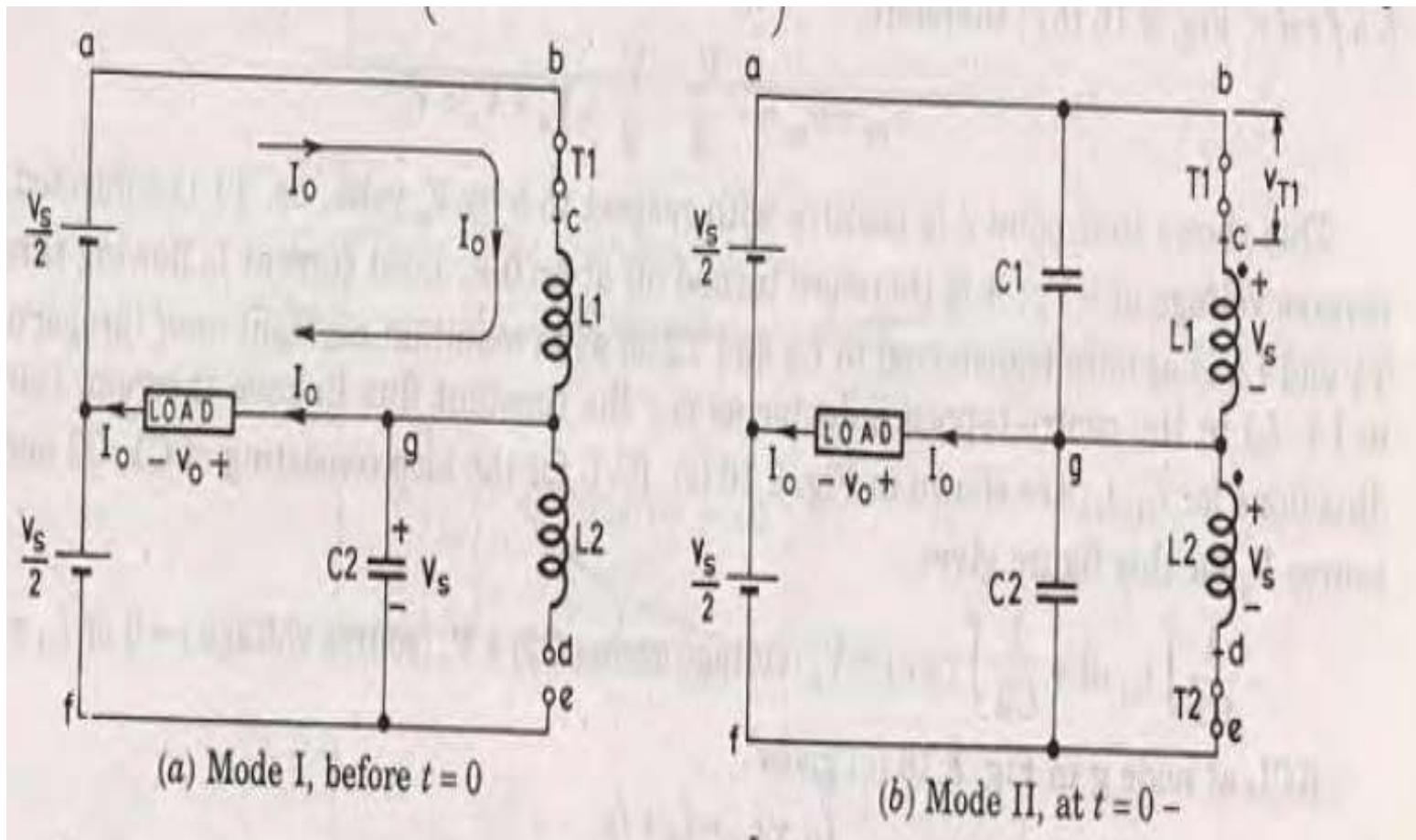


Understanding the Concepts

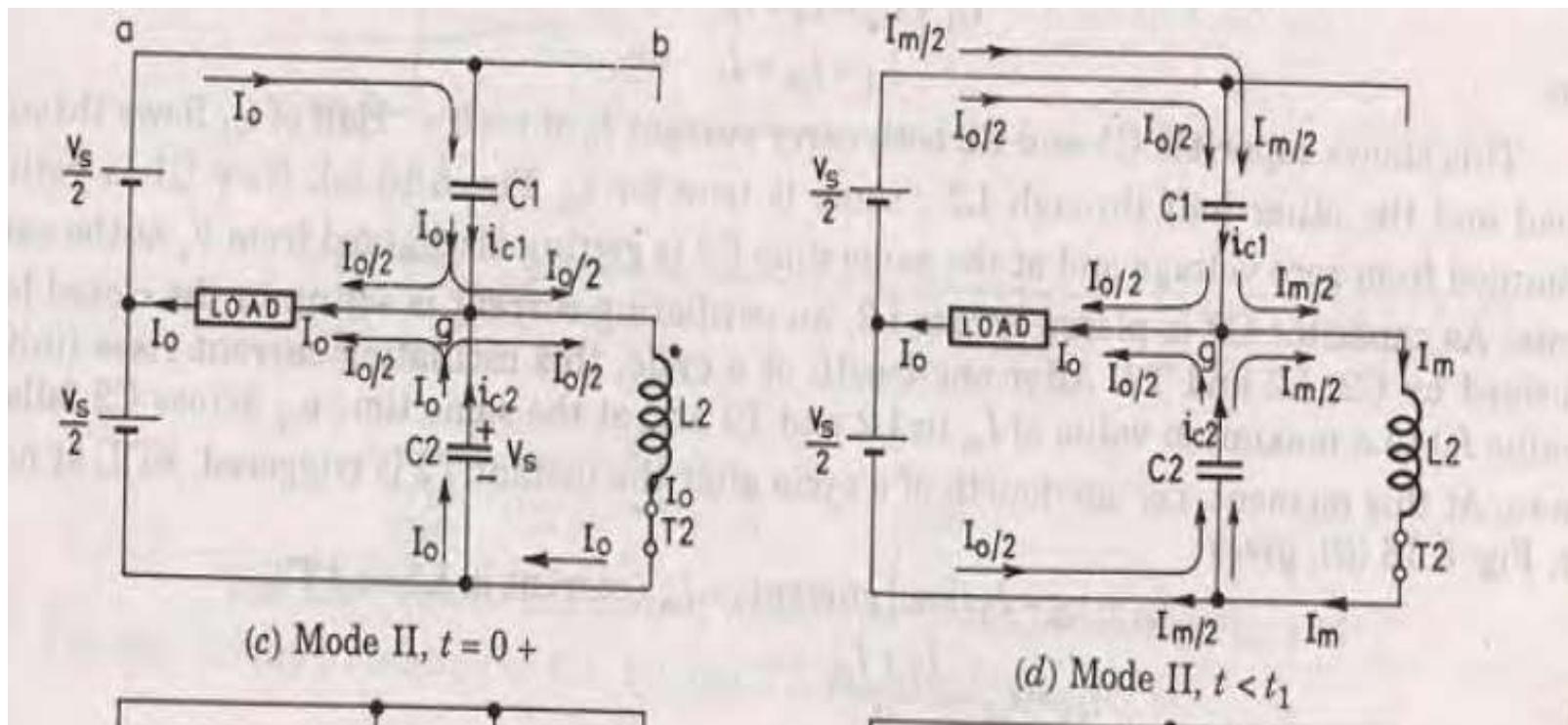

Understanding the Concepts

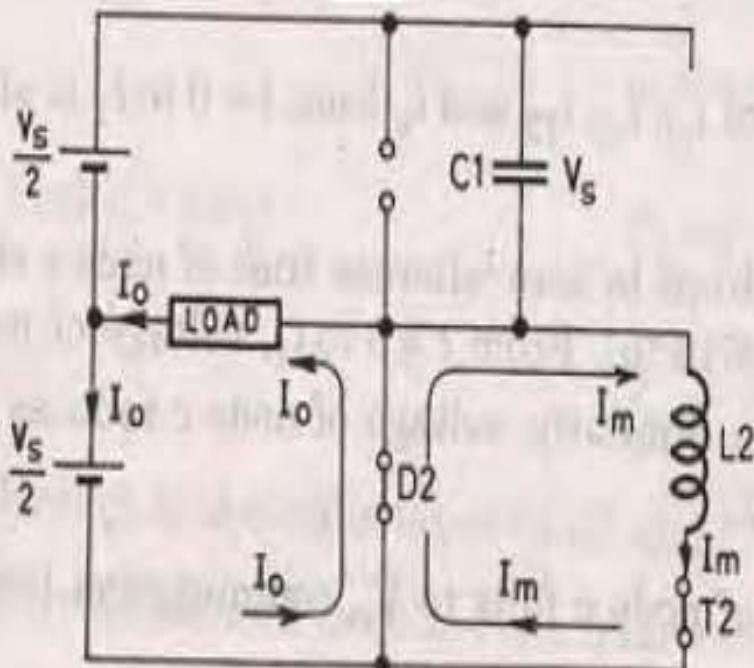

(e) Mode III, at t_1

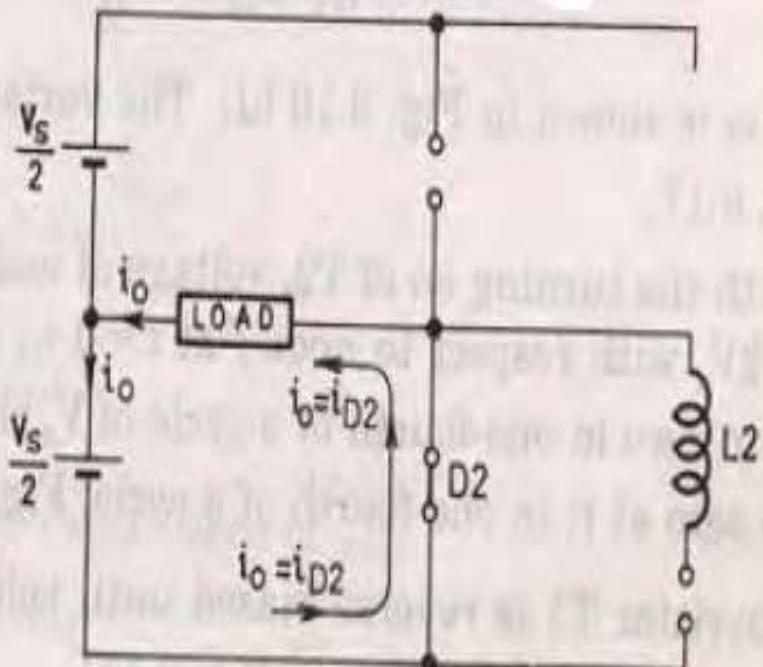

(f) Mode IV

Modified McMurray Bedford Full Bridge Inverter

