

TEMPERATURE COMPENSATION

Ref : BJT Biasing Circuit

Transistor Biasing

Facts reflected about Transistor Biasing

- <1> Basic Ground rules are followed to bias the BJT properly.
- <2> Identified Base Bias & Emitter Bias ckt. & corresponding transistor applications are mapped.
- <3> Transistor Switch is discussed and studied applications of it.
- <4> Emitter Bias ckt. is modified keeping in view to eliminate the effect of change β . Such that BJT can work as current source and amplifier effectively [By targeting fixed Q pt.]

Parameters affect Q point

The parameters which may affect the transistor operation in the active region -

$$I_{CQ} = I_{CQ} (\beta, V_{BE}, I_{CBO})$$

Change is very very small.

$$\Delta V_{BE} = -K \Delta T$$

$$2 \text{ mV}/^\circ\text{C}$$


[Taken care by temperature compensation circuit]

Taken suitable measure so as to get I_{CQ} & V_{CEQ} independent of β

Basic Concept

Temperature Compensation Circuit

The Basic idea

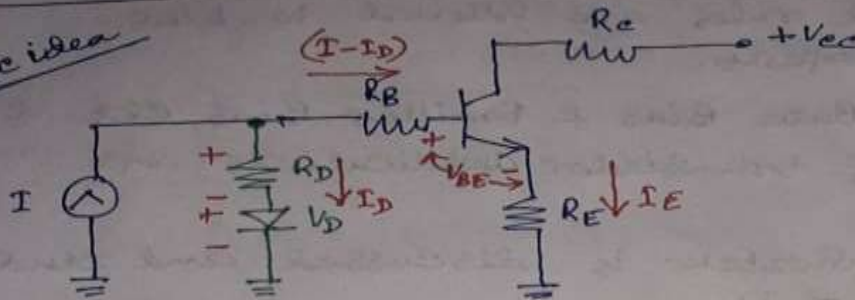

$$V_D + I_D R_D = (I - I_D) R_B + V_{BE} + I_E R_E$$

$$\therefore V_D + I_D R_D = I R_B - I_D R_B + V_{BE} + I_{CQ} R_E$$

$$\therefore I_{CQ} = \frac{(V_D - V_{BE}) + I_D (R_B + R_D) + I R_B}{R_E}$$

$$\therefore \frac{\Delta I_{CQ}}{\Delta T} = \frac{1}{R_E} \left[\frac{\Delta V_D}{\Delta T} - \frac{\Delta V_{BE}}{\Delta T} \right]$$

$$\text{As } \frac{\Delta V_D}{\Delta T} = \frac{\Delta V_{BE}}{\Delta T} = -K$$

$$\text{So } \frac{\Delta I_{CQ}}{\Delta T} = 0 \quad [\text{desired result is obtained}]$$

→ So the suggested circuit may act as TEMPERATURE COMPENSATION CIRCUIT.


Outcome

Analysis of the Result


- <1> The suggested Temp. Compensation Circuit has to be used in actual testing circuit & subsequently we have to check whether same result is obtained or not.
- <2> Temperature characteristics of the diode junction may not be same as the junction ch. of BJT. So it is recommended to use transistor instead and use it as a diode.

Temperature Compensation

1st attempt.

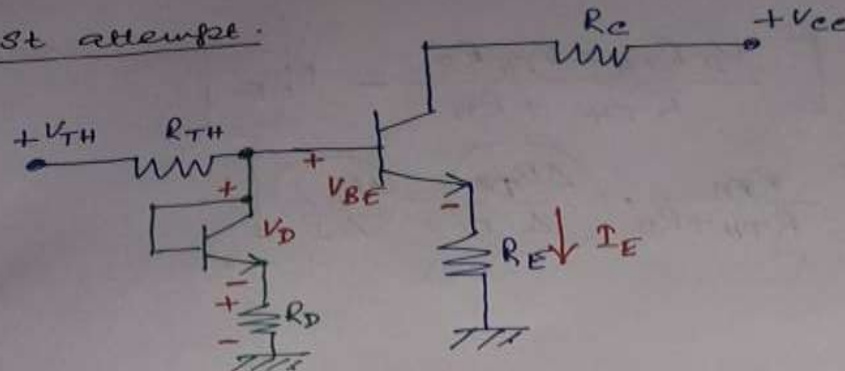

Simplification.

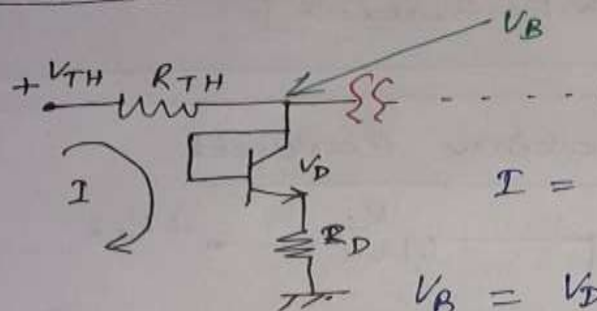


$$I = \frac{V_{TH} - V_D}{R_{TH} + R_D}$$

$$V_B = V_D + \frac{V_{TH} - V_D}{R_{TH} + R_D} \cdot R_D$$

$$V_B = \frac{V_D R_{TH} + V_D R_D + V_{TH} R_D - V_D R_D}{R_{TH} + R_D}$$

$$V_B = \frac{V_D R_{TH} + V_{TH} R_D}{R_{TH} + R_D}$$

Single Diode Compensation

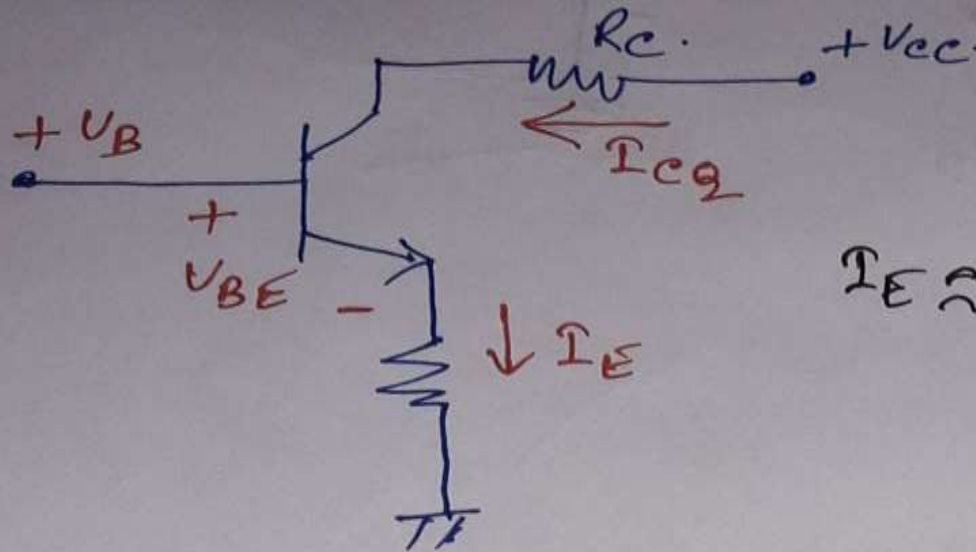

$$I_E \approx I_{CQ} = \frac{V_B - V_{BE}}{R_E}$$

Outcome

$$I_{CQ} = \frac{1}{R_E} \left[\frac{V_D R_{TH} + V_{TH} R_D}{R_{TH} + R_D} - V_{BE} \right]$$


$$\frac{\Delta I_{CQ}}{\Delta T} = \frac{1}{R_E} \left[\frac{R_{TH}}{R_{TH} + R_D} \cdot \underbrace{\left(\frac{\Delta V_D}{\Delta T} \right)}_{\approx -k} - \underbrace{\left(\frac{\Delta V_{BE}}{\Delta T} \right)}_{\approx -k} \right]$$

$$\neq 0$$

So this circuit failed as compensation ckt. [Single Diode Compensation]


Two Diode Compensation

Two Diode Compensation Circuit

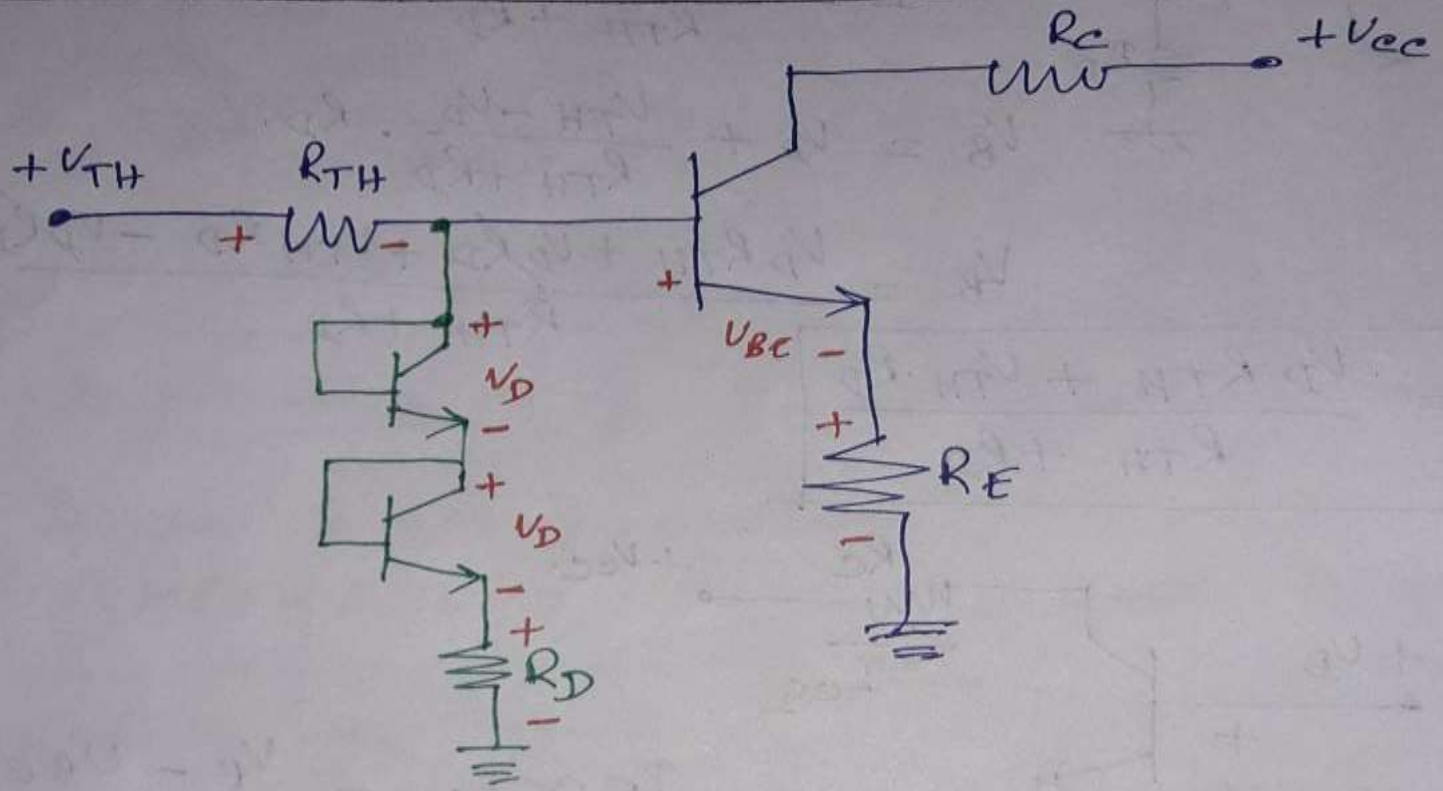

Two Diode Compensation

Simplification

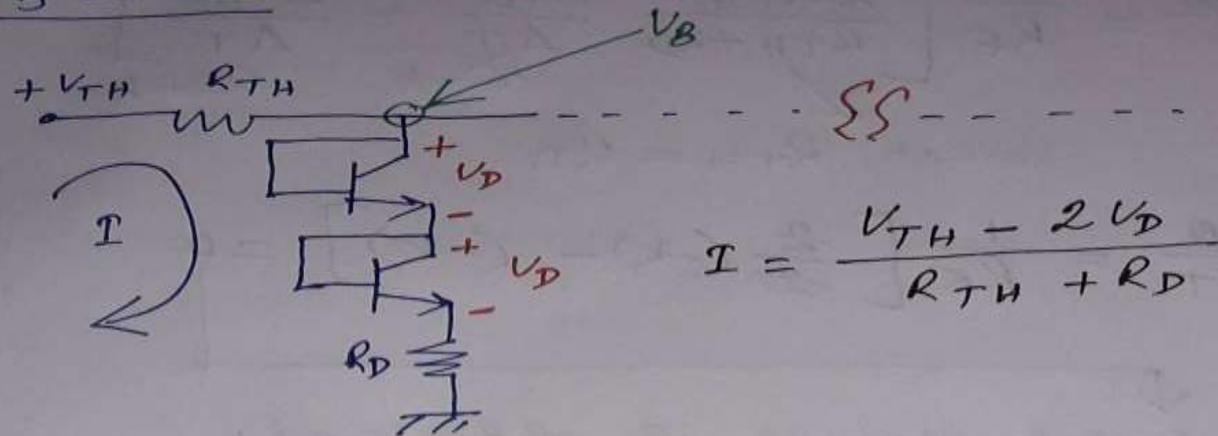


$$I = \frac{V_{TH} - 2V_D}{R_{TH} + R_D}$$

$$\begin{aligned} V_B &= 2V_D + I R_D \\ &= 2V_D + \frac{V_{TH} - 2V_D}{R_{TH} + R_D} \cdot R_D \\ &= \frac{2V_D R_{TH} + 2V_D R_D + V_{TH} R_D - 2V_D R_D}{R_{TH} + R_D} \end{aligned}$$

$$V_B = \frac{V_{TH} R_D + 2V_D R_{TH}}{R_{TH} + R_D}$$

Two Diode Compensation

Equivalent ckt.

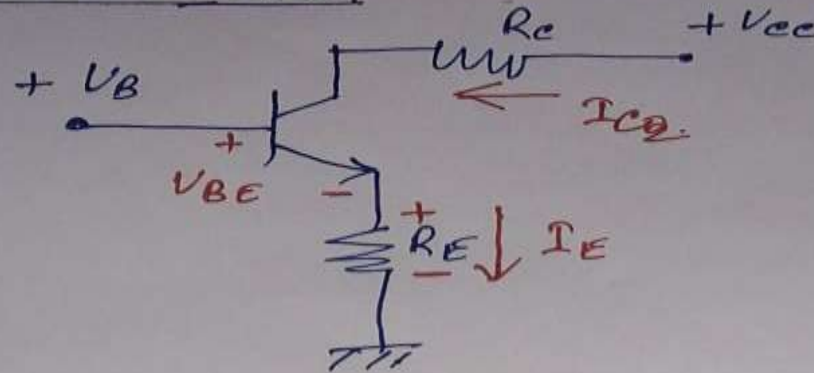

$$I_E \approx I_{CQ} = \frac{V_B - V_{BE}}{R_E}$$

$$= \frac{1}{R_E} \left[\frac{V_{TH} R_D + 2V_D R_{TH}}{R_{TH} + R_D} - V_{BE} \right]$$

Outcome

$$\frac{\Delta I_{CQ}}{\Delta T} = \frac{1}{R_E} \left[\underbrace{\frac{2R_{TH}}{R_{TH} + R_D}}_{\substack{\downarrow \\ \approx -k}} \frac{\Delta V_D}{\Delta T} - \frac{\Delta V_{BE}}{\Delta T} \right]_{\substack{\approx -k}}$$

Select $R_{TH} = R_D$.

$$\frac{\Delta I_{CQ}}{\Delta T} = \frac{1}{R_E} \left[\frac{2}{2} (-k) - (-k) \right] = 0$$

↓
So desired result is obtained.