

# Feedback Amplifier


# Background

## Feedback Amplifiers

open loop amplifiers has some typical limitations


- ① Gain is dependent on gain of the transistor
- So not controllable
- ② Gain is changing with temperature
- ③ Sometimes having nonlinear response.

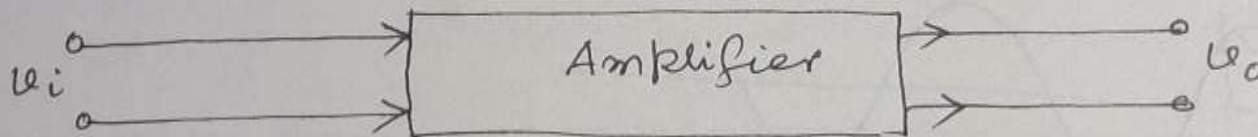So closed loop amplifiers are introduced in order to mitigate the limitations.



$$A = \text{Gain} = \frac{V_o}{V_i}$$

# Feedback Amplifiers

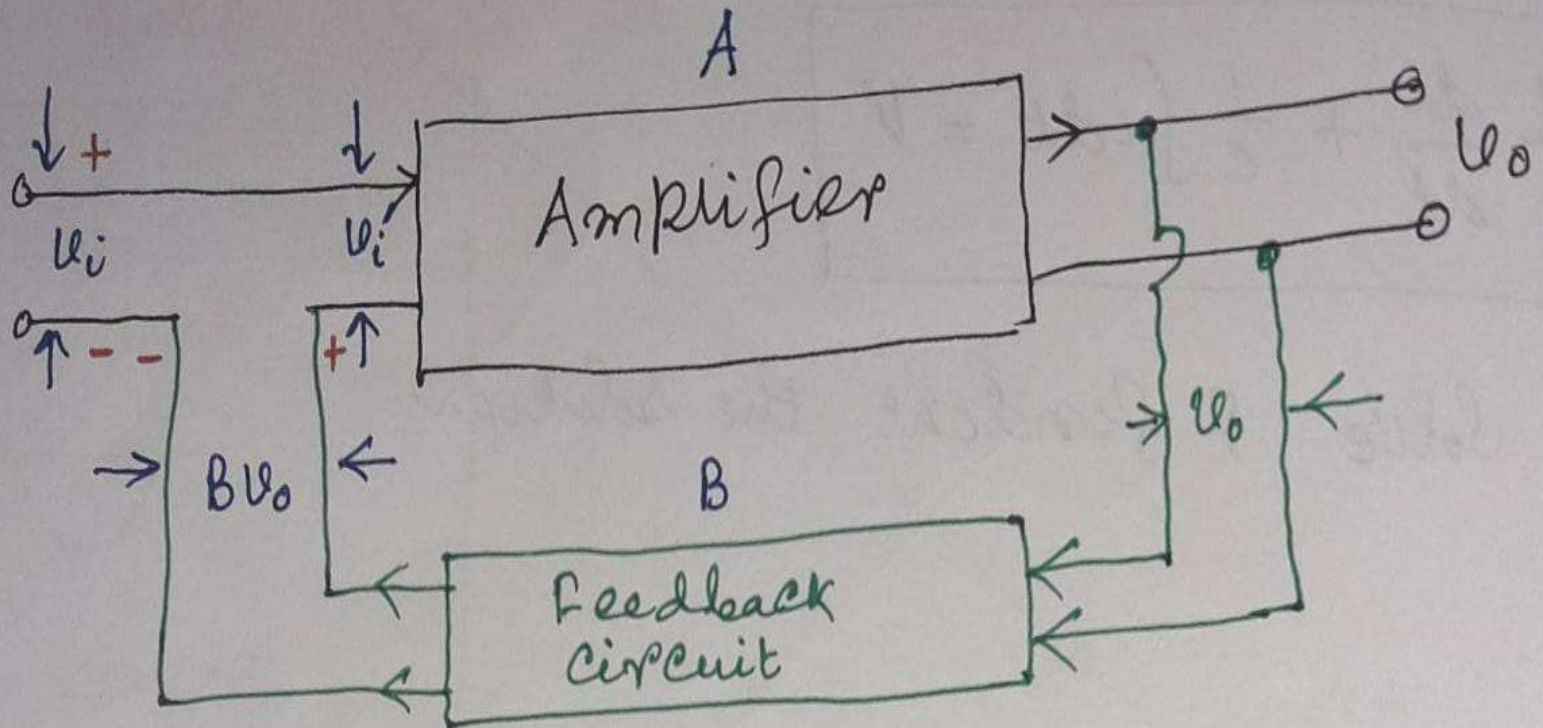

# Feedback Amplifiers

$$\begin{aligned}V_i' &= V_i - B V_o \\&= V_i - B (A V_i) \\&= V_i (1 - AB)\end{aligned}$$

$$A_f = \text{Closed loop Gain} = \frac{V_o}{V_i'} = \frac{A V_i}{V_i (1 - AB)}$$

$$A_f = \frac{A}{1 - AB}$$

$B$  = Gain of the feedback

# Feedback Amplifiers

Analysis of the result.

①  $(1-AB) < 1$ ,  $B \rightarrow +ve$ ,  $A_f > A$

Positive Feedback or Regenerative Feedback.  
Unstable

②  $(1-AB) > 1$ ,  $B \rightarrow -ve$ ,  $A_f < A$

Negative Feedback or Degenerative Feedback  
Stable

③  $1-AB = 0$ ,  $AB = 1$ ,  $A_f \rightarrow \infty$

No i/p, but o/p

OSCILLATOR


# Feedback Amplifiers

## Topologies of Feedback Amplifier


- (I) Voltage-Series feedback
- (II) Voltage-Shunt feedback
- (III) Current-Series feedback
- (IV) Current-Shunt feedback.



# Feedback Amplifiers

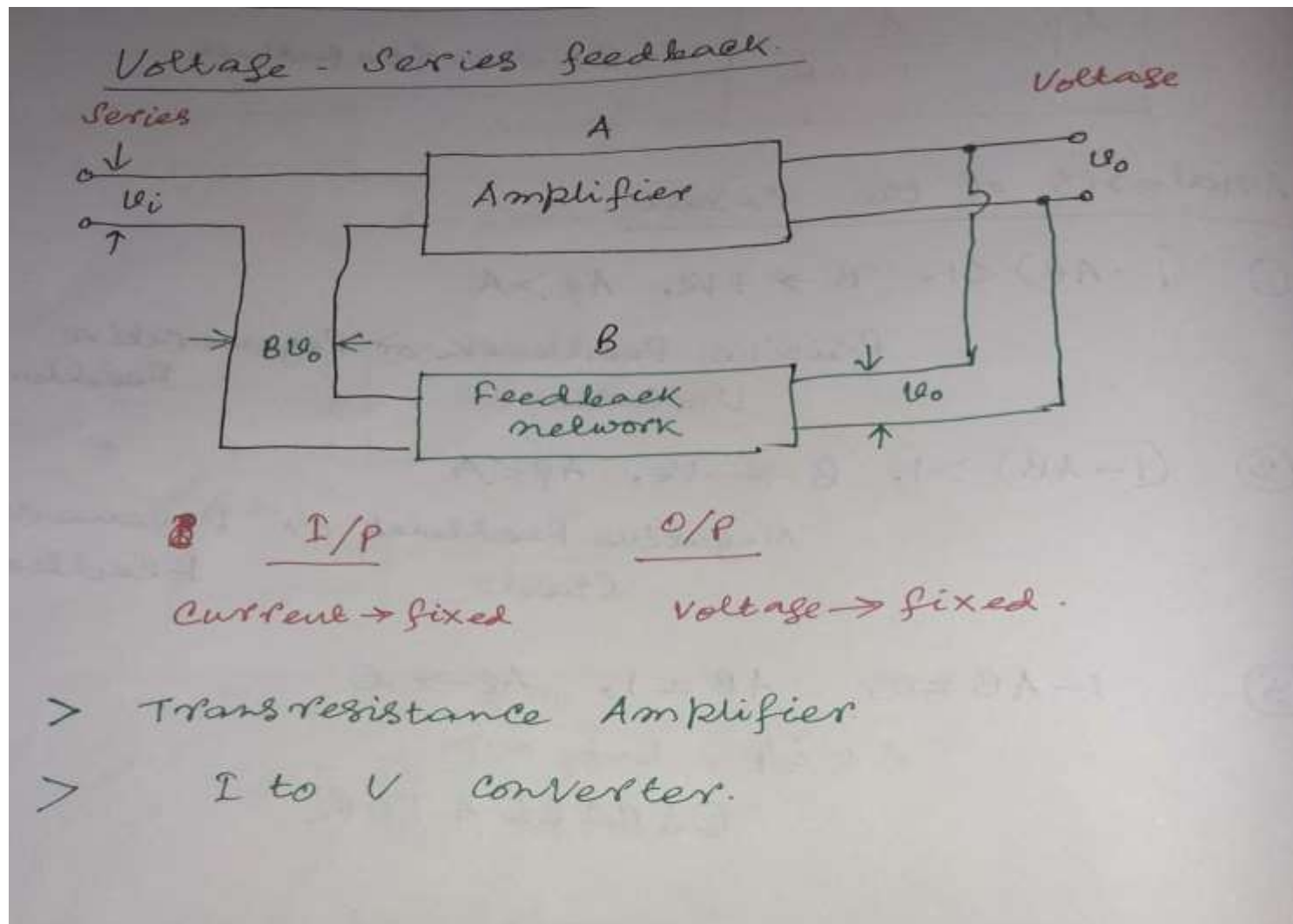


# Feedback Amplifiers

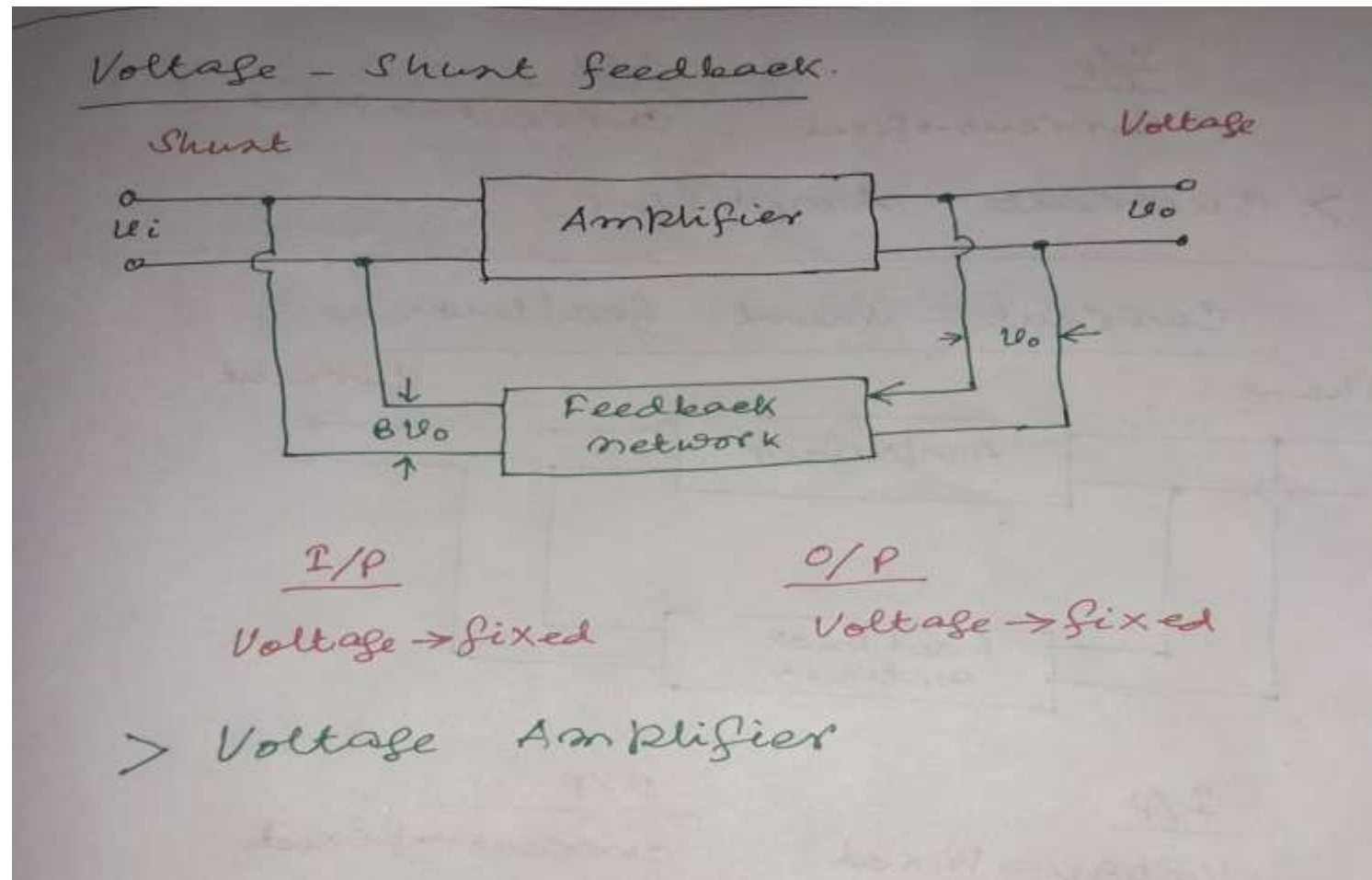




# Feedback Amplifiers

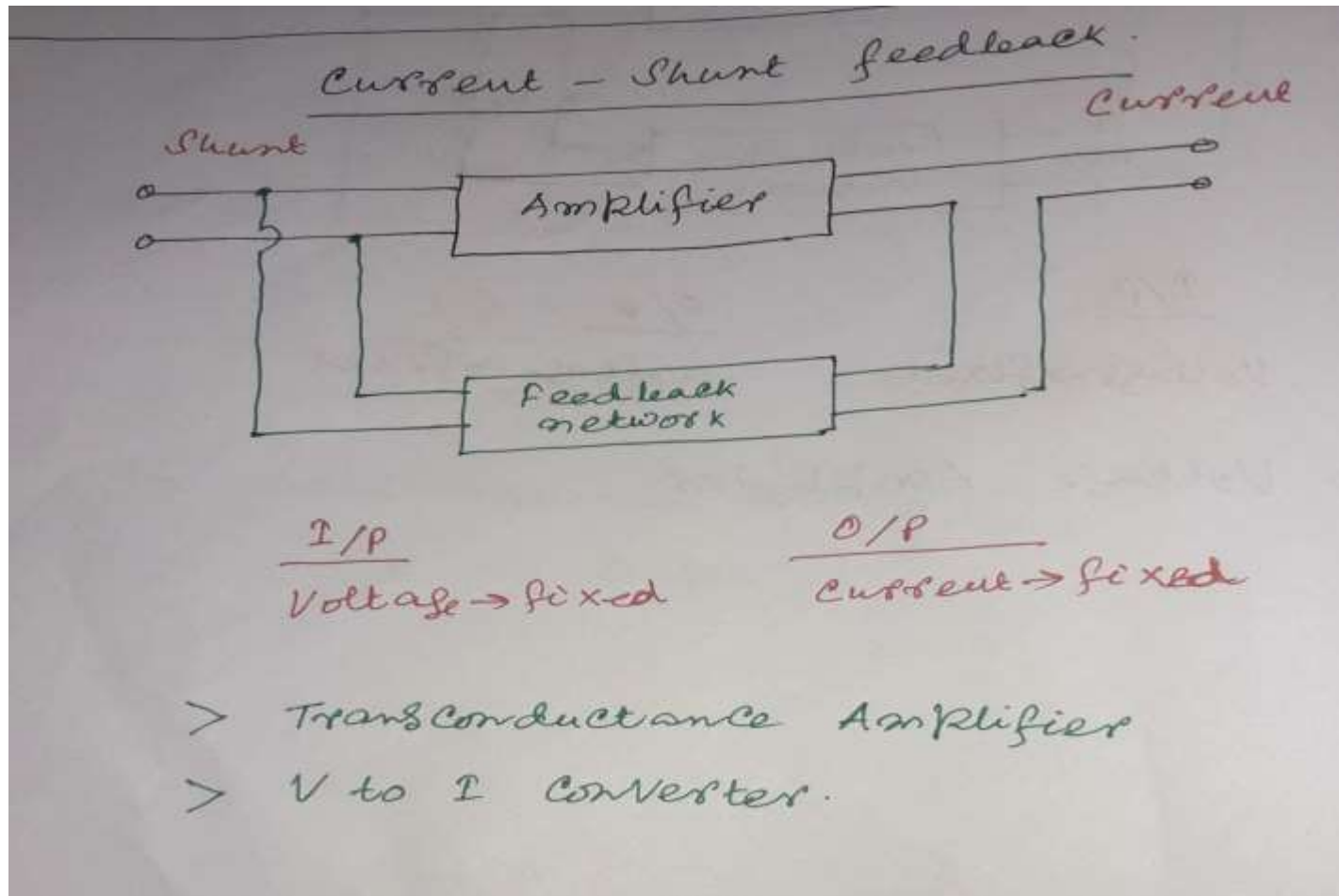

# Feedback Amplifiers

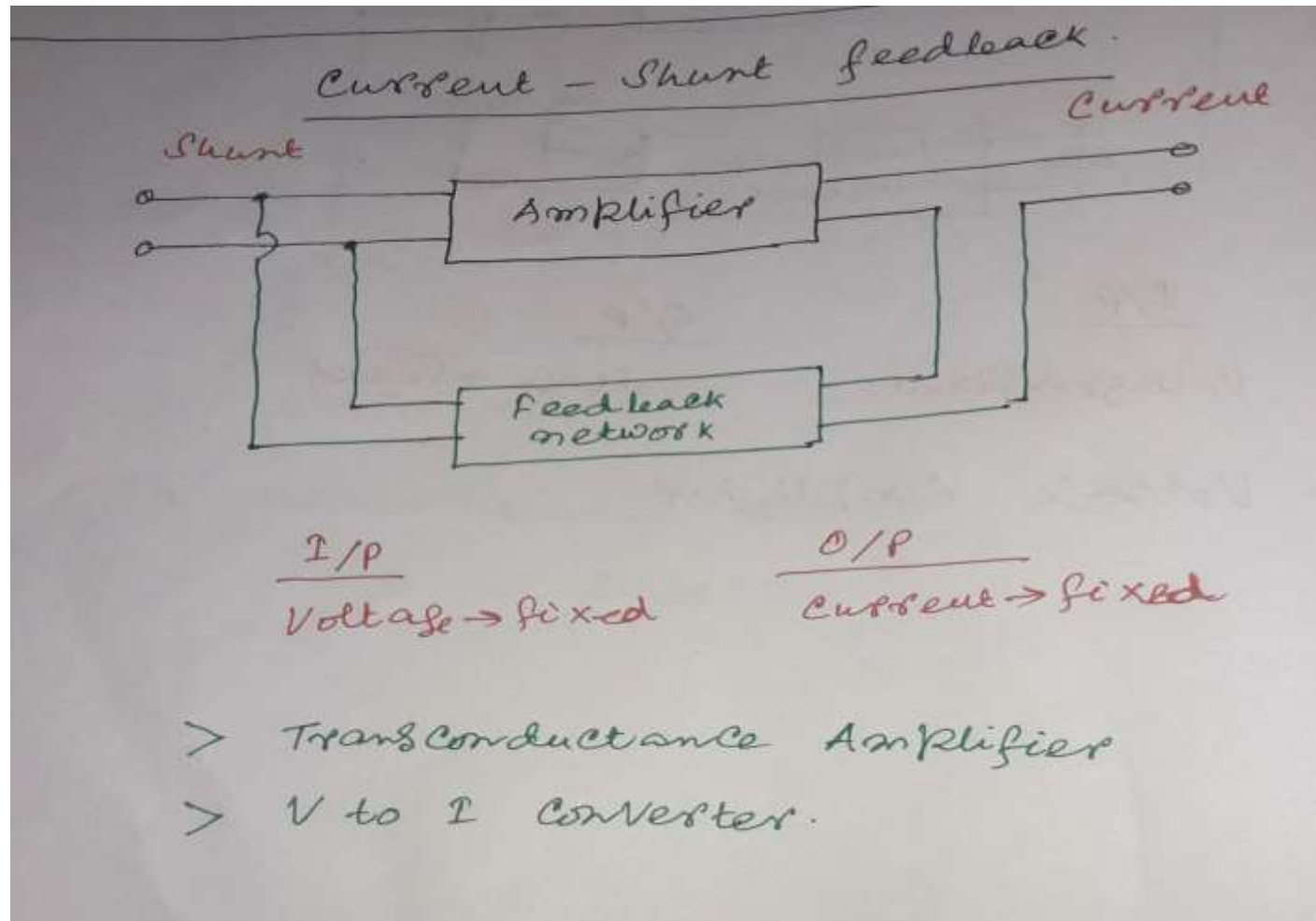

# Feedback Amplifiers

## Effects of negative feedback.

- (i) The stability of the amplifier is improved.
- (ii) Input impedance can be varied.
- (iii) Output impedance can be varied.
- (iv) Nonlinear distortion is reduced.
- (v) Noise is reduced.
- (vi) Bandwidth of the amplifier increases.

# Feedback Amplifiers

(i) Improvement of Stability

$$A_f = \frac{A}{1+AB}$$

$$\therefore (1+AB) > 1, \quad A_f < A$$

So ~~stability~~ stability is improved.

(ii) For negative feedback ... i/p impedance.

$$V_i' = V_i (1+AB)$$

$$\therefore Z_{if} = \frac{V_i'}{I_i} = \frac{V_i}{I_i} (1+AB) = Z_i (1+AB)$$

(iii) o/p impedance.

$$Z_{of} = \frac{V_o}{I_o}, \quad Z_o = \frac{V_o}{I_o'}$$

$$I_o = \frac{V_o - AV_i}{Z_o} = \frac{V_o + ABV_o}{Z_o} = \frac{V_o (1+AB)}{Z_o}$$

$$Z_{of} = \frac{V_o}{\frac{V_o (1+AB)}{Z_o}} = \frac{Z_o}{1+AB}$$

# Feedback Amplifiers

(i) Improvement of Stability

$$A_f = \frac{A}{1+AB}$$

$$\therefore (1+AB) > 1, \quad A_f < A$$

So ~~stability~~ stability is improved.

(ii) For negative feedback --- i/p impedance.

$$V_i' = V_i (1+AB)$$

$$\therefore Z_{if} = \frac{V_i'}{I_i} = \frac{V_i}{I_i} (1+AB) = Z_i (1+AB)$$

(iii) o/p impedance.

$$Z_{of} = \frac{V_o}{I_o}, \quad Z_o = \frac{V_o}{I_o'}$$

$$I_o = \frac{V_o - AV_i}{Z_o} = \frac{V_o + ABV_o}{Z_o} = \frac{V_o (1+AB)}{Z_o}$$

$$Z_{of} = \frac{V_o}{\frac{V_o (1+AB)}{Z_o}} = \frac{Z_o}{1+AB}$$

# Feedback Amplifiers

(iv) Reduction of noise.

$$\begin{array}{c} \downarrow \\ V_n \\ V_{of} = A_f \cdot V_n = \frac{A V_n}{1 + AB} = \frac{V_{on}}{1 + AB} \end{array}$$

$$(1 + AB) > 1, \quad V_{of} < V_{on}$$

(v) Enhancement of Bandwidth.

BW = Frequency range for which gain remains constant.

Frequency at which gain is one.

$$\text{Constant} = UGB = A f_0$$

$$\text{Constant} = UGB = A_f f_F$$

$$A f_0 = A_f f_F$$

$$\therefore f_F = \frac{A f_0}{A_f} = \frac{A f_0}{A / (1 + AB)}$$

$$\therefore \boxed{f_F = f_0 (1 + AB)}$$



# Feedback Amplifiers

Condition of Oscillation.

$$AB = 1$$

$|AB| = 1$  CRITERION I  
 $\angle AB = 0 \text{ or } 360^\circ$  CRITERION II

BARKHAUSEN CRITERIA



Oscillator